RADIO & TELEVISION NEWS

A ZIFF-DAVIS PUBLICATION

A good name to live by...

THIS COULD BE *YOUR* SHOP . . . and your good name on the Dealer Identification Plaque—for everyone to see.

And this could be a *new* customer at the door—confident that, in dealing with you, his set will be in good hands.

And, he would be right . . . because you've learned from experience that the superior quality of RCA receiving tubes and kinescopes is your best measure of protection against premature tube failures.

Helping to safeguard *your* good name is a vital, everyday service of RCA Tubes. And that protection is yours at no extra cost.

Learn from your *RCA Tube Distributor* how *two* good names can prosper together . . . how *you* can qualify for a Registered Dealer Plaque.

DYNAMIC NEW PROMOTION PLAN TO HELP YOU BUILD YOUR BUSINESS

Ask your RCA Tube Distributor for a copy of the colorful, 16-page booklet "A Magic Pass-Key to Customer Confidence." A brand-new campaign is outlined, illustrated, and described in full detail. Be sure to get your copy. It's free!

RCA
RCA Electron TUBES
WE USE RCA TUBES FOR BEST RESULTS IN SERVICING ALL MAKES AND MODELS OF TELEVISION AND RADIO RECEIVERS
Jones TV Service
LOCAL HEADQUARTERS

RCA RADIO CORPORATION of AMERICA
ELECTRON TUBES HARRISON, N. J.

I WILL TRAIN YOU AT HOME FOR GOOD PAY JOBS IN RADIO-TELEVISION

J. E. SMITH has trained more men for Radio-Television than any other man.

America's Fast Growing Industry Offers You

2 FREE BOOKS SHOW HOW MAIL COUPON

I TRAINED THESE MEN

LOST JOB, NOW HAS OWN SHOP
"Got laid off my machine shop job which I believe was best thing ever happened as I opened a full time Radio Shop. Business is picking up every week."—E. T. Slate, Corsicana, Texas.

GOOD JOB WITH STATION
"I am Broadcast Engineer at WLPM. Another technician and I have opened a Radio-TV service shop in our spare time. Big TV sales here . . . more work than we can handle." —J. H. Bangley, Suffolk, Va.

$10 TO $15 WEEK SPARE TIME
"Four months after enrolling for NRI course, was able to service Radios . . . averaged $10 to $15 a week spare time. Now have full time Radio and Television business." — William Weyde, Brooklyn, New York.

AVAILABLE TO VETERANS UNDER G.I. BILLS

WANT YOUR OWN BUSINESS?

Let me show you how you can be your own boss. Many NRI trained men start their own business with capital earned in spare time. Robert Dohmen, New Prague, Minn., whose store is shown at left, says, "Am now tied in with two Television outfits and do warranty work for dealers. Often fall back to NRI textbooks for information."

1. EXTRA MONEY IN SPARE TIME

Many students make $5, $10 a week and more EXTRA fixing neighbors' Radios in spare time while learning. The day you enroll I start sending you SPECIAL BOOKLETS that show you how. Tester you build with kits I send helps you make extra money servicing sets, gives practical experience on circuits common to Radio and Television. All equipment is yours to keep.

2. GOOD PAY JOB

NRI Courses lead to these and many other jobs: Radio and TV service, P.A., Auto Radio, Lab, Factory, and Electronic Controls Technicians, Radio and TV Broadcasting, Police, Ship and Airways Operators and Technicians. Opportunities are increasing. The United States has over 105 million Radios—over 2,900 Broadcasting Stations—more expansion is on the way.

3. BRIGHT FUTURE

Think of the opportunities in Television. Over 15,000,000 TV sets are now in use; 108 TV stations are operating and 1800 new TV stations have been authorized . . . many of them expected to be in operation in 1953. This means more jobs—good pay jobs with bright futures. More operators, installation service technicians will be needed. Now is the time to get ready for a successful future in TV! Find out what Radio and TV offer you.

You Learn Servicing or Communications by Practicing With Kits I Send

Television Is Today's Good Job Maker

TV now reaches from coast-to-coast. Qualify for a good job as a service technician or operator. My course includes many lessons on TV. You get practical experience . . . work on circuits common to both Radio and Television with my kits. Now is the time to get ready for success in Television!

Keep your job while training at home. Hundreds I've trained are successful RADIO-TELEVISION Technicians. Most had no previous experience; many no more than grammar school education. Learn Radio-Television principles from illustrated lessons. You also get PRACTICAL EXPERIENCE. Pictured at left are just a few of the pieces of equipment you build with kits of parts I send. You experiment with, learn circuits common to Radio and Television.

Mail Coupon—find out what RADIO-TELEVISION Can Do for You

Act Now! Send for my FREE DOUBLE OFFER. Coupon entitles you to actual Servicing Lesson; shows how you learn at home. You'll also receive my 64-page book, "How to Be a Success in Radio-Television." Send coupon in envelope or paste on postal. J. E. SMITH, Pres., Dept. 3EE, National Radio Institute, Washington 9, D. C. Our 39th Year.

Good for Both—FREE

MR. J. E. SMITH, President, Dept. 3EE
National Radio Institute, Washington 9, D. C.

Mail me Sample Lesson and 64-page Book, FREE. (No salesman will call. Please write plainly.)

Name ..... Age .....

Address .....

City ..... Zone ..... State .....

VETS write in date of discharge .....

RADIO & TELEVISION NEWS is published monthly by the Ziff-Davis Publishing Company at 185 N. Wabash Ave., Chicago 1, Ill. Entered as second-class matter July 21, 1948, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Authorized by Post Office Department, Ottawa, Canada, as second-class matter. SUBSCRIPTION RATES: Radio & Television News—one year, U. S. and Possessions, Pan-American countries, and Canada $4.00; all other foreign countries $5.00. Radio-Electronic Engineering Edition—one year, U. S. and Possessions, Pan-American countries, and Canada $6.00; all other foreign countries, $7.00. Postmaster—Please return undelivered copies under form 3589 to 64 E. Lake St., Chicago 1, Ill.

Editor and Asst. Publisher
OLIVER READ, B.Sc., W9YT

Managing Editor
WM. A. STOCKLIN, B.S.

Technical Editor
H. S. RENNE, M.S.

Service Editor
CHARLES TEPPER

Amateur Radio Editor
N. ROSA, W1NOA

Assistant Editors
P. B. HOEFER
M. C. MAGNA

Television Consultant
WALTER H. BUCHSBAUM

Short-Wave Editor
KENNETH R. BOORD

Staff Artist
FRANK SAYLES

Draftsmen
A. A. GANS, W2TSP
J. A. GOLANEK

Advertising Manager
I. L. OSTEN

Midwest Adv. Manager
JOHN A. RONAN, JR.

Western Adv. Manager
JOHN E. PAYNE

COVER PHOTO: Deciding on which audio equipment to buy is a fairly simple matter when a demonstration unit such as Asco's "Audiomat" is available to aid in the selection. (Ektachrome by Irving Greene)

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Secretary-Treasurer
G. E. CARNEY

Vice-Presidents
H. J. MORGANROTH
Production Director
LYNN PHILLIPS, JR.
Advertising Director
H. G. STRONG
Circulation Director

BRANCH OFFICES
CHICAGO (1)
64 E. Lake St., AN 3-5200
LOS ANGELES (14)
Statler Center, 900 Wilshire Blvd., Mich. 9836

First in radio-television-electronics
Average Paid Circulation over 200,000

RADIO & TELEVISION NEWS

Reg. U.S. Pat. Off.

Radio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U. S. Pat. Office.

CONTENTS — MAY, 1953

There's Cash Afloat ..... *Elbert Robberson* 35
The Diminutive Wire Recorder ..... *Harvey Sampson* 38
Audio Equalization ..... *Leon A. Wortman* 39
U.H.F. TV Test Equipment ..... *Walter H. Buchsbaum* 40
TV Parts Replacement Guide 42
Loudspeaker Enclosures ..... *Wm. A. Stocklin* 43
An Advanced Regenerative Circuit ..... *Irving Gottlieb, W6HDM* 48
A Transistor Sine-Wave Clipper ..... *Louis E. Garner, Jr.* 50
For Fringe Areas ..... *Jesse Dines* 52
Noise Immunity Circuits (Part 1) ..... *Milton S. Kiver* 54
Electro-Voice Baronet 57
The Asco "Audiomat" ..... *Irving Greene* 58
QRM-Cutting Selectivity for the Mobile Receiver ..... *George M. Brown, W2CVV* 60
U.H.F.-V.H.F. Antenna Coupler ..... *Edward Finkel & James C. Sarayiotes* 63
Transistor-Operated Photocell Relay ..... *Louis E. Garner, Jr.* 64
Mac's Radio Service Shop ..... *John T. Frye* 66
Know Your 1953 Du Mont "Telesets" ..... *Joseph Roche* 67
A Noise Limiter Deluxe ..... *J. J. Hoefer, WØIIJ* 76
Make Your Own U.H.F. Chokes ..... *E. J. Gauss, WØEOS* 83
New TV Stations on the Air 86
Specialize—For Profit ..... *Yvon O. Johnson* 90
Service Hints on Du Mont TV Sets 106
Radio-TV Service Industry News 142
New TV Grants Since Freeze Lift 148

DEPARTMENTS

For the Record ..... *The Editor* 8
Spot Radio News 14
Within the Industry 24
Parts Show Exhibitors 32
Short-Wave ..... *K. R. Boord* 74
What's New in Radio 100
Manufacturers' Literature 112
New TV Products 122
Technical Books 156

COPYRIGHT 1953
(All Rights Reserved)
ZIFF-DAVIS PUBLISHING COMPANY
Editorial and Executive Offices
366 Madison Ave., New York 17, N. Y.
VOLUME 49 • NUMBER 5

Member
Audit Bureau of Circulations

SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Subscribers should allow at least two weeks for change of address.

CONTRIBUTIONS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's, and contestant's rights, title, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material purchased.

NOW...from D.T.I.'s MILLION DOLLAR TRAINING CENTER

Learn to master TELEVISION

RADIO - ELECTRONICS

by getting EVERYTHING YOU NEED!

America's amazing multi-billion dollar Television field now offers you a chance of a lifetime to get started toward a grand job or your own business. With TV station limit now raised from over 100 to 2053, Television is headed for almost every community. Mail coupon today. See how you may prepare to cash in on the coming TV BOOM.

NOW— get training to suit your NEEDS

TAKE YOUR CHOICE

Come to D.T.I.'s great CHICAGO LABORATORIES

...one of the Nation's FINEST!

Now, in the heart of the nation's TV Center, you can get all of your preparation in D.T.I.'s big, modern, wonderfully equipped training laboratories. Loads of commercial equipment and ample, well qualified instructors help you get a thorough, practical preparation in the SHORTEST POSSIBLE TIME. Part time student Employment assistance can help you pay your way while in training.

EMPLOYMENT SERVICE

As soon as you complete either the Chicago Laboratory or Home Training, you'll find D.T.I.'s grand Employment Service ready to help you start earning real money. Get full facts. Mail coupon today.

Get ALL of your training AT HOME!...*including setting up your own HOME LABORATORY*

See how you may now get one of today's most complete, effective combinations of major home training aids—including (1) well illustrated lessons, (2) the wonderful aid of HOME TRAINING MOVIES and (3) 21 big shipments of electronic parts for setting up your own HOME LABORATORY. You work over 400 construction and test procedures to get the practical experience you need. This includes building and keeping a 5 INCH "SCOPE", jewel bearing MULTI-METER and a big 21 INCH TV SET. (D.T.I. offers another home training in Television-Radio-Electronics, but without the TV set.) Mail coupon today for exciting facts.

ABOVE: You build and keep this big 5 INCH commercial-type oscilloscope — one of the most useful test units used in TV today.

21 INCH
You build and keep this outstanding 21 INCH—sharp image—D.T.I. quality-engineered TV set. Can be readily converted to receive U.H.F.

Use 16 mm. MOVIES Only D.T.I. provides you with the loan of visual training movies at home to help you master important basic points faster . . . easier . . . better!

MILITARY SERVICE: If subject to military service, the training information we have for you should prove very helpful. Mail coupon today.

89 WAYS TO EARN MONEY IN TELEVISION RADIO ELECTRONICS

ACT NOW! MAIL COUPON TODAY
Get this publication FREE!

RN-5-J

DeFOREST'S TRAINING INC.
2533 N. ASHLAND AVE., CHICAGO 14, ILL.

I would like your Opportunity News Bulletin showing "89 Ways to Earn Money in Television-Radio-Electronics"; also, complete facts about the training opportunity made possible by your organization.

Name _____ Age _____

Address _____ Apt. _____

City _____ Zone _____ State _____

"ONE OF AMERICA'S FOREMOST TELEVISION TRAINING CENTERS"
— Established 1931 —

De FOREST'S TRAINING, INC.
AFFILIATED WITH
De VRY *Technical* INSTITUTE
CHICAGO 14 ILLINOIS

PICKERING

PROFESSIONAL AUDIO EQUIPMENT

BALANCED COMPONENTS / MAXIMIZE PLAYBACK PERFORMANCE

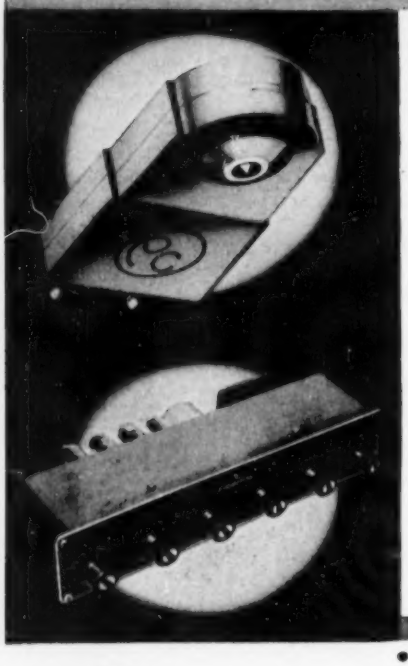

PICKERING CARTRIDGES . . .

are the choice of audio engineers throughout the world. They are universally acclaimed because of their high output, wide range performance and low distortion. They are used wherever a fine cartridge is required in radio stations, recording studios and for purposes of quality control by leading record manufacturers.

MODEL 410 AUDIO INPUT SYSTEM . . .

is designed to provide a complete audio control center. Model 410 may be used in any high quality playback system. Three input channels are provided—one for magnetic cartridges and 2 "flat" channels for other audio circuits. A 3-position equalizer network is built into the magnetic cartridge channel and provides accurate equalization for LP, AES and 78 rpm recording characteristics. Separate bass and treble controls are also provided. These are of the step-type and permit bass and treble adjustments in 2 db increments. The tone control circuits are intended to compensate for record characteristics and for listener-environment acoustical conditions. *They are not intended to compensate for amplifier and/or loudspeaker deficiencies.* Model 410 is intended for use with the highest quality professional type playback equipment. The output of the Model 410 is fed from a cathode-follower circuit and will work into any high quality audio or line amplifier having a high impedance input. It may also be used with a transformer for the purpose of feeding a 500 ohm line. Because of its flexibility, low noise and low distortion level, it is ideally suited for bridging and monitoring purposes and for critical listening applications.

THE MODEL 190 ARM . . .

is designed primarily for use with microgroove records. Its design has been recognized by leading audio engineers as that which incorporates all of the desirable tracking characteristics. Analysis has shown that for maximum performance with LP records the vertical mass of the moving arm element must be held to a minimum and further, that the arm must be counterbalanced about the vertical axis. This permits minimum stylus or tracking force and provides maximum record life. The Model 190 Arm embodies these all important features necessary for proper microgroove record playback.

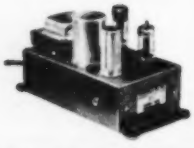

MODEL 230H EQUALIZER-PREAMPLIFIER . .

is unique in its accuracy of equalization and frequency response. The intermodulation distortion is .2 per cent at normal output level. It is intended for use with high quality amplifiers having gain and tone controls. When used with the Pickering Model 132E Record Compensator the 230H is ideal for radio station and recording studio use and for applications requiring accurate low noise and distortion free playback.

MODEL 132E RECORD COMPENSATOR . . .

is designed to be used in conjunction with a magnetic cartridge preamplifier such as the Pickering 230H or any preamplifier which provides 6 db per octave bass boost. Six playback positions are incorporated:

1—European 78 rpm Records
2—Victor 45 rpm and Decca 78 rpm Records
3—No high frequency roll-off, 500 cycle turnover
4—All Capitol Records, new Victor 33⅓, Audio Engineering Society Curve
5—Columbia, London and most LP Records
6—To remove the hiss from old noisy records

Precision elements are used in its construction to give accurate compensation. The 132E is inherently a low distortion R-C device.

PICKERING PROFESSIONAL AUDIO EQUIPMENT

"For those who can hear the difference"

...Demonstrated and sold by Leading Radio Parts Distributors everywhere. For the one nearest you and for detailed literature, write Dept. C-2

PICKERING ***and company incorporated • Oceanside, L. I., New York***

QRK?*

ALWAYS TOPS WITH A hallicrafters

You'll have the best QRK 100 watts can give with Hallicrafters HT20 transmitter—and you'll *listen* to more and hear it better on a Hallicrafters receiver. You be the judge—you hear the difference!

It's value like this—and more of it dollar-for-dollar in every price class—that has made Hallicrafters equipment the unchallenged first choice of the world's most critical expert, the American amateur radio operator, for 19 years.

Hallicrafters equipment is designed specifically for the ham operator—planned to meet his problems—planned to fit his pocketbook. The measure of Hallicrafters success is in the reputation this group of experts extends to this equipment. You can *hear* the answer every night of the year on the air—just listen!

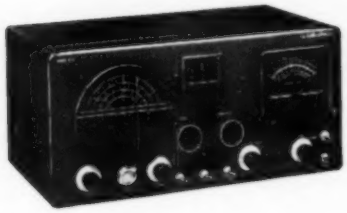

Top Selectivity—Low Price! Model S76—Dual Conversion Super with 50 kc amplifier for tops in selectivity, 500 C.P.S. at 6 db down—3.5 kc at 60 db down. Giant 4-in. "S" meter. 540-1580 kc, 1.72-32 Mc in 4 bands. 1 r-f, 2 conversion, 2 i-f stages. 5 pos. selectivity. Phono input jack. 3 watt output. **$179.50**

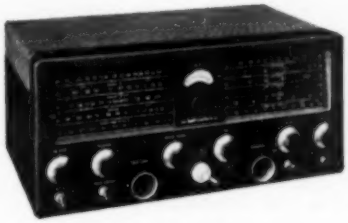

A Ham's Dream! Model SX71— Com. Rcvr. especially designed for top ham performance. Double conversion, built-in NBFM limiter stage. 538 kc to 35 Mc, 46-56 Mc in 5 bands. Temp. Comp., voltage reg. 1 r-f, 2 conversion, 3 i-f stages. Xtal. filter, 4-pos. selectivity, 18½" x 8⅞" x 12" deep. Ship. wt. 51 lbs. 115V, A.C. 11 tubes, reg., rect. **$224.50**

Model S-408— Covers Broadcast Band 540-1700 kc and three short-wave bands. 1.7-43 Mc. One r-f, two i-f stages. Electrical bandspread tuning. Switches for automatic noise limiter, code reception and three-position tone control. CW pitch control. Built-in PM speaker. 115V, A.C. Only **$119.95**

TVI Suppressed 100 Watter—Model HT20—Here's the transmitter you've been waiting for! Continuous coverage from 1.7 Mc to 30 Mc. Full band switching, no more plug-in coils; choice of 10 crystals. Shielded, filtered r-f compartment plus low-pass 52 ohm co-axial line output filter assures at least 90 db suppression of all harmonics above 40 Mc. Only **$449.50**

* QRK—International "Q" Signal for—"What is my readability?"

hallicrafters

Chicago 24, Illinois

World's Leading Manufacturer of Precision Radio and Television

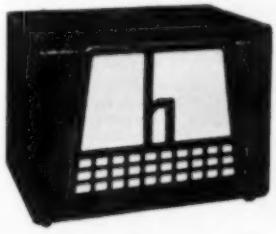

Matched Speaker, Model R46— The perfect speaker for SW. Includes transformer of 500/600-ohm input. Voice coil impedance 3.2 ohms. 10" cone. Black finish. 15" x 10⅞" x 10⅞" deep. Only **$19.95**

NEW SMALL VERSATILE
P.A. Lavalier
DYNAMIC MICROPHONE
For Chest, Desk or Hand Use

FIRST EVER IN SUCH SMALL SIZE FOR PUBLIC ADDRESS

Unlike any lapel microphone, the "647" offers full-range E-V dynamic microphone quality, ruggedness and performance characteristics for indoor and outdoor use. Response 60-13,000 cps, specially compensated for chest resonance. Output −57 db.

Only 4" x 1", the "647" can be worn around the neck, or used in the hand, on a desk or on a boom. When suspended from the neck, a unique clip provides secure support—frees the user's hands for gestures and demonstrations, permits him to move around.

Exclusive E-V Acoustalloy diaphragm is virtually indestructible. Acoustically-treated grille minimizes effects of wind and breath blasts. Supplied complete with combination neck cord and tie clip for microphone, belt clip for cable, rubber desk stand and 18 ft. cable. Available in Low or Hi-Z.

Model 647. List Price, **$80.00**
Net, **$48.00**

See your E-V Distributor or Send for Bulletin 201

Electro-Voice
410 CARROL ST. • BUCHANAN, MICHIGAN
Export: 13 E. 40th St., New York 16, U.S.A. Cables: Arlab

For the RECORD.

BY THE EDITOR

THE QUEST FOR REALISM

MAN strives continuously to give greater realism and depth to sight and sound. The physicist and the engineer continually are seeking better ways and means to give us "third dimensional" aural and visual transmission and reproduction.

The motion picture industry, faced with TV competition, has developed several systems including *Cinerama* and *Cinemascope*. The two are distinguished as three-dimension illusion *(Cinerama)* and wide-screen process *(Cinemascope)*. Both systems provide an "illusion" to both sight and sound and both have contributed a new concept of entertainment via film.

Of equal importance is the latest contribution to the broadcast industry announced recently by Columbia University—the perfection of a system of multiplex radio transmission.

It now appears, more than ever before, that FM will eventually replace AM for broadcast communications. It takes no crystal-gazer to foresee the far-reaching effects on the methods of transmitting intelligence of all kinds over multiplex FM systems.

To Dr. Edwin H. Armstrong (father of FM) and John H. Bose, must be given new recognition for this significant achievement and further development of the FM system. Basically, the new system doubles (perhaps more) the effective function of the FM transmitter. For example, an FM station can transmit a musical program on one channel and, at the same time, transmit another program simultaneously on a second channel.

Of particular interest to the serious listener of "hi-fidelity" is the system's ability to transmit a single program stereophonically on its two channels. This technique has been tested successfully at Dr. Armstrong's Alpine FM station at Alpine, N. J.

The transmission of multiple signals over a common carrier is not new. The Signal Corps has long used this technique. Telephone companies and other communicators are sending many simultaneous signals over single channels.

While multiplex operation of FM in the communications field has been in practical use for many years, its use in broadcasting presented many problems not of importance in the communications field. In pointing to his new development Dr. Armstrong stated, "Because of the extreme high fidelity requirements of the FM system, the problem of cross-modulation between the channels was not simple as the intrusion of one channel into the province of the other has to be kept below one part in a million."

The real significance of the new system, he added, is, "that the most 'Doubting Thomas' will now be obliged to recognize that FM will prevail as the final aural system. It would be completely impossible to multiplex on any AM system, either on the standard band or on a very high frequency band of the same frequency as the FM stations."

The cost of equipping a transmitter for multiplex operation is not high according to the inventor. Transmitters already using Serrasoid modulators which are employed in the new system are most readily susceptible to change, he said.

Receiver prices will doubtless follow the course they have always taken and sets will be produced at prices to fit everyone's purse. The audio enthusiasts, perhaps more than any other group, would provide a ready market for multiplex FM tuners for use with binaural audio systems.

Many of our readers have already heard binaural reproduction demonstrated at various Audio Fairs and shows. The program was transmitted simultaneously over an AM and an FM channel. The result (due to variations in equalization and other factors) left much to be desired for a true binaural facsimile of the program source. Multiplex FM broadcasting is certainly the most promising technique so far developed for providing binaural service to the music lover as well as to provide a stereo effect to mixed sound sources.

Engineers have become increasingly "binaural-conscious" in recent months—in the audio and film industries. The record industry recently became excited over binaural records (two separate sound tracks on one side). A new method will contain binaural sound in one groove on regular LP's. Many methods are being shown to and heard by the public. Some are good—others not so good. Some are complicated to the extreme—others use simpler means to create a stereo and binaural "effect." Dr. Armstrong's latest contribution will serve, when available, to give great impetus to the recording, transmission, and reproduction of wide range sound.

It becomes more and more apparent that the source of sound lies in the realm of physics, while the effect of sound is a physiological consideration. The engineering of sound consists of controlling the cause so as to produce the desired effect. . . . . O. R.

THE ONLY **COMPLETE** CATALOG FOR EVERYTHING IN TV, RADIO AND INDUSTRIAL ELECTRONICS

get your 1953 **FREE**

ALLIED

236-PAGE CATALOG

it's complete
it's value-packed

THE WORLD'S LARGEST STOCKS

- TV and Radio Parts
- Test Instruments
- Hi-Fi and P.A. Equipment
- Custom TV Chassis
- AM, FM Tuners & Radios
- Recorders and Supplies
- Amateur Station Gear
- Builders Supplies
- Equipment for Industry

QUICK
EXPERT
SERVICE

Send for it today!

Here's the *one* authoritative, complete Buying Guide to *Everything in Electronics*—packed with the world's largest selections of quality equipment at lowest money-saving prices. See the latest in TV custom chassis, TV antennas and accessories; AM and FM tuners and radios; High-Fidelity Custom Sound components; latest P.A. Systems and accessories; recorders; Amateur receivers, transmitters and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books—your choice of the world's *most complete stocks* of quality equipment.

ALLIED gives you every buying advantage; speedy delivery, expert personal help, lowest prices, liberal time payment terms, assured satisfaction. Get the latest 1953 ALLIED Catalog. Keep it handy—and save time and money. Send for your FREE copy today!

EVERYTHING IN ELECTRONICS

SEND TODAY FOR RADIO'S LEADING BUYING GUIDE

free

ALLIED RADIO

World's Largest Electronic Supply House

EASY-PAY TERMS

Take advantage of ALLIED's liberal Easy Payment Plan—Radio's best terms—only 10% down, 12 months to pay—no interest if you pay in 60 days. Available on Hi-Fi and P. A. units, recorders, TV chassis, test instruments, Amateur gear, etc.

TV & HI-FI SPECIALISTS

To keep up with developments in TV and High-Fidelity, look to ALLIED! Count on us for *all* the latest releases and largest stocks of equipment in these important fields. If it's *anything* in Television or High-Fidelity equipment—we have it in stock!

ALLIED RADIO CORP., Dept. 1-E-3
833 W. Jackson Blvd., Chicago 7, Illinois

☐ Send FREE 236-Page 1953 ALLIED Catalog.

Name .....

Address .....

City ..... *Zone* .... *State* .....

RADIART announces its 6300 series... an addition to the full line of

RADIART Seal-Vent RED SEAL VIBRATORS

Faster Starting

The exclusive RADIART design permits the briefest possible "Warm-up" period, thereby making the RADIART vibrators practically instantaneous starting. This added feature means greater performance.

Longer Life

There's more for your money in every RADIART vibrator-they last longer! Precision manufacture, using only the finest materials, assures long lasting, trouble-free performance.

Complete Replacement Line

RADIART has a CORRECT replacement vibrator for every original equipment vibrator. 12 Radiart vibrator types serve over 89% of all popular replacements. NOW...THE NEW 6300 SERIES IS READY FOR THE NEW '53 car MODELS with radios having 12 volt circuits.

Seal-Vented

Sealed at the factory to prevent the formation of an insulating film on the points while the vibrator is on the shelf...the sealed vent automatically opens when put in use to allow the vibrator to "breathe".

preferred by Servicemen Everywhere

SUBSIDIARY OF

THE RADIART CORPORATION CLEVELAND 13, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTORS • POWER SUPPLIES

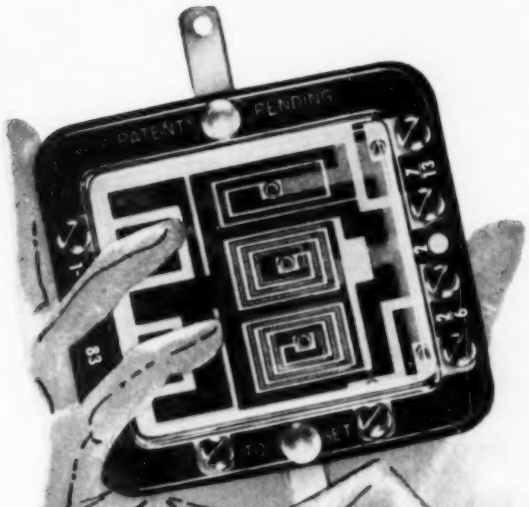

JETENNA • JET 283 and now . .

JFD introduces the revolutionary

JeTie Coupler, Q283

for VHF and UHF antennas

first of its kind!

- *joins one UHF and one VHF antenna*
- *joins two VHF antennas*
- *joins two VHF antennas and one UHF antenna*

. . . all with only ONE down-lead!

JFD Electronics

JFD gives you a direct line to profits with the amazing new JeTie coupler. Here's "single transmission line" reception on such disparate channels as 4 and 61—a miracle of engineering know-how that will pay off for you in countless sales. Made with a new silver printed circuit for ideal conductivity, the JeTie is hermetically sealed in a transparent moisture-resistant, dust-proof Butyrate case—the only one of its kind. Light weight, easy-to-attach, the JeTie coupler is the easy-to-sell answer to the new UHF and VHF stations in your territory.

LIST PRICE $5.30

For more information on the JFD JeTie, write to JFD Manufacturing Company, Inc.

Brooklyn 4, New York
Bensonhurst 6-9200
World's largest manufacturer of TV antennas and accessories

Barton Brasse advertising

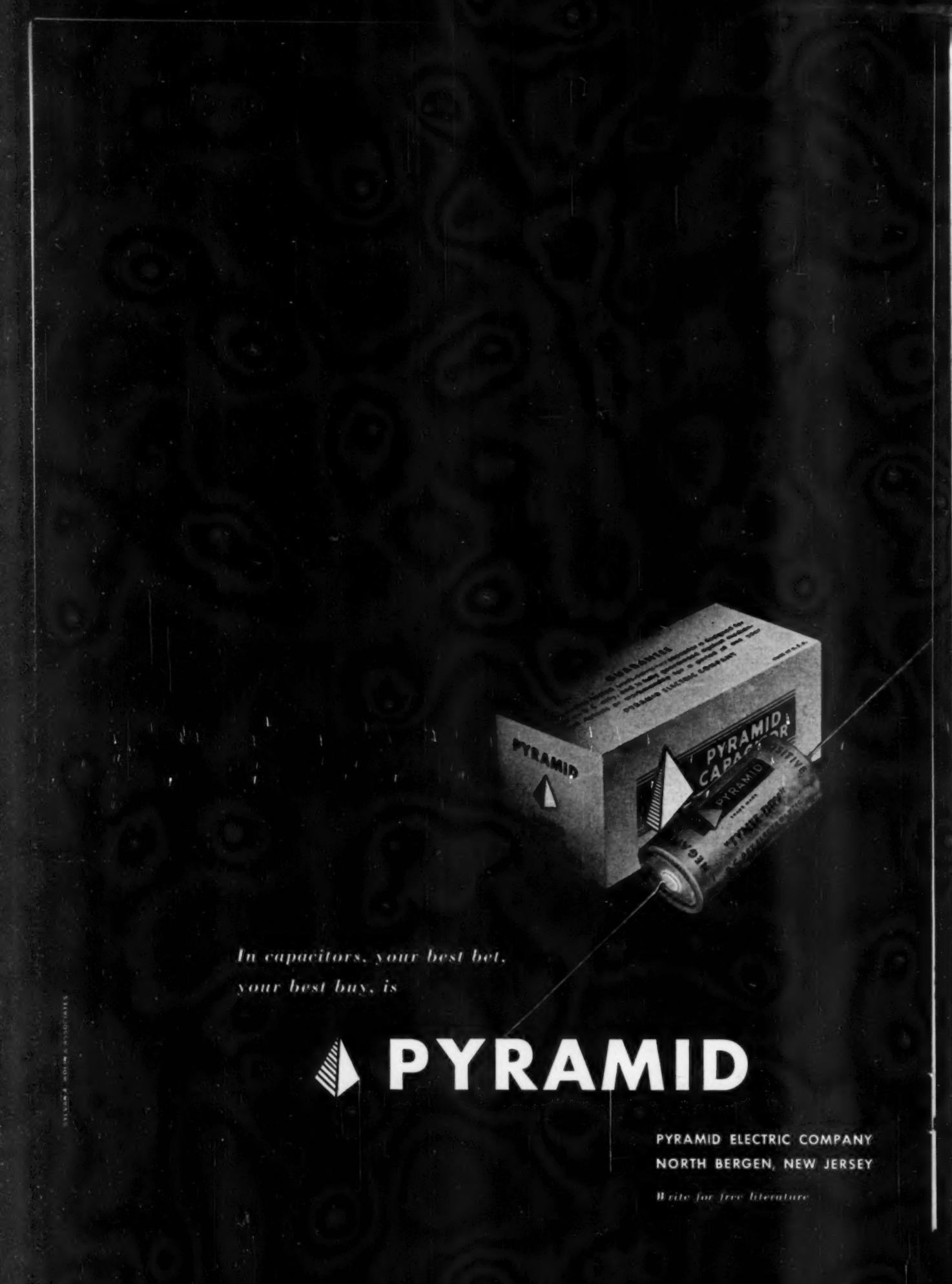

In capacitors, your best bet, your best buy, is

PYRAMID

PYRAMID ELECTRIC COMPANY
NORTH BERGEN, NEW JERSEY

Write for free literature

BUILD A BUSINESS and a REPUTATION!

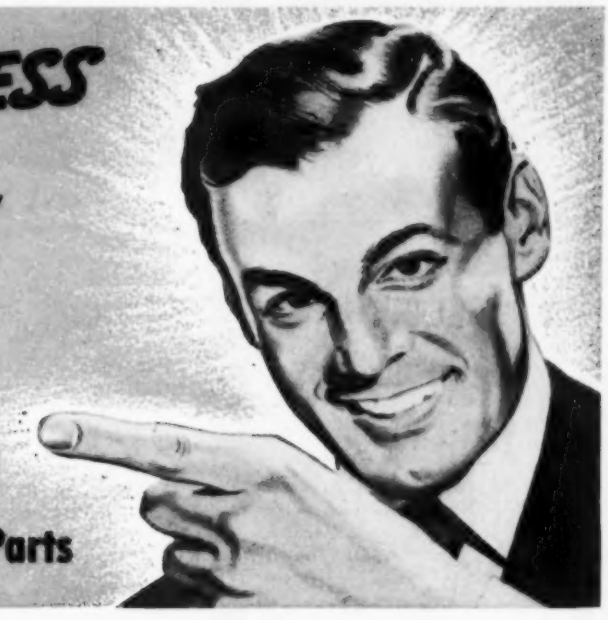

Replace with Genuine G-E Parts

In a business that's growing rapidly, an ever increasing number of expert servicemen carry the *complete* line of General Electric replacement parts. They realize the demand for these products and the opportunity G-E units offer to *increase sales...add to their reputations.*

G-E RECORD COMPENSATOR. "Hit of the New York Audio Fair." Here is a new G-E unit that is sure to build store traffic. Favorite old records sound like new. Modern recordings are interpreted more faithfully. Low cost is a plus feature for volume sales. Lends itself ideally to effective store demonstration.

G-E TONE ARMS. A line designed to bring users the full benefit of our famous variable reluctance cartridges. Stylus replacement requires only a few seconds. Skilled G-E workmanship and quality construction add up to customer satisfaction for many years.

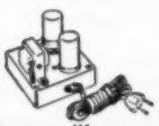

G-E PREAMPLIFIERS. New improved performance. Completely self-contained and ready to operate when connected to a power source. Ease of installation is a factor you'll appreciate. This product goes hand-in-hand with widely accepted General Electric Cartridges.

G-E CARTRIDGES. A complete line of single or dual units to meet every need for quality reproduction. Offers incomparable performance. Deliver smooth, wide range response; low tracking pressure. Available at prices your customers will really appreciate.

G-E WIDE-RANGE STYLI. General Electric manufactured the first wide-range diamond-sapphire* combination! Every stylus is designed to give unexcelled performance *up to 15,000 cycles.* Engineered to minimize record wear...add quality to the products you carry.

G-E SPEAKERS. 27 models in 8 sizes to choose from. G-E high fidelity speakers stand head and shoulders above the industry in providing peak performance at a modest price. Featuring aluminum base voice coils and Alnico 5 magnets, your customers are assured of a quality product for their listening pleasure.

**Some sapphires are synthetic*

● **Contact your G-E Distributor now for the new lucite Record Compensator counter displays, plus many other sales aids that do your selling job for you!**

1878 75 1953 YEARS OF ELECTRICAL PROGRESS

SEND FOR INFORMATION TODAY!

General Electric Company, Section 953,
Electronics Park, Syracuse, New York
Please send me information about G-E Parts.

NAME.....

ADDRESS.....

CITY..... STATE.....

GENERAL ELECTRIC

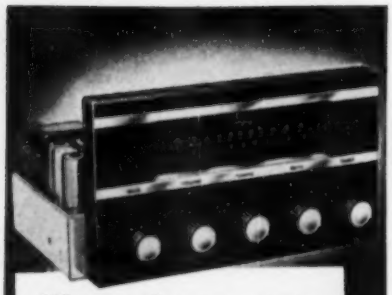

We rest our case on evidence you can hear

Words can't prove the performance of this superb High Fidelity Tuner. Neither can witnesses. When it's time for a decision, your judgement of the CRAFTSMEN 10 is based on one thing: evidence you hear *with your own ears*. Listen—and the conclusive evidence of incomparable sensitivity and flexibility will turn your trial into a lifetime of *distinctly* better listening.

the craftsmen® 10 high fidelity FM-AM tuner

- Two cathode followers furnish both audio output and detector output for remote installations.
- Built-in pre-amplifier, compensated for variable reluctance pick-ups.
- Automatic Frequency Control entirely eliminates drift, simplifies tuning.
- 5 microvolts sensitivity on both FM and AM.
- 10 kc filter on AM eliminates inter-station squeal.
- Bass and treble tone controls for boost, cut, or 20-20,000 cycle flat response.

JUDGE THE C-500 TOO! Williamson all-triode circuit—99.99% distortion-free!

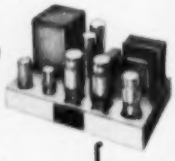

high fidelity by craftsmen means distinctly better listening

For information, write to:

The radio CRAFTSMEN, Inc.

Dept. R-5, 4401 N. Ravenswood Ave., Chicago 40, Ill.

Spot Radio News

*** Presenting latest information on the Radio Industry.**

By RADIO & TELEVISION NEWS' WASHINGTON EDITOR

THE MULTI-MILLION DOLLAR merger of *ABC*, operating 17 stations (6 AM, 6 FM, and 5 TV outlets) and a national network of nearly 300, with the *Paramount* picture-theater chain, which a number of experts felt certain would be delayed indefinitely after Senator Tobey's blast calling for an investigation in monopoly control, instead found itself officially blessed by the Commission shortly after the fiery Senator's demand.

In defending its action, the communication headmen said that it was no longer possible to delay a decision, and the approval was entirely in order now in the public interest.

The ruling, appearing in a 200-odd page brief, presented one of the most comprehensive reports ever issued on many vital phases of TV broadcasting, including the relationship of the motion-picture industry to TV, theater TV, properties of TV films, and operational costs.

In a discussion of the use of film, talent, and story rights on television, *Paramount* picture executives noted that they have no policy prohibiting the use of its motion picture film by telecasters, and are willing to release film when the TV industry can pay as much as picture theaters. At the present time, it was disclosed, TV can only pay a maximum of from 35- to 55-thousand dollars for the rights to televise films nationally, and national rights for the average film sell for from 10- to 20-thousand dollars. This is hardly enough to support features, it was said, for the average cost of production of about 30 feature films released by *Paramount* in the '51-'52 season was about $1,400,000 each, excluding the cost of distribution and advertising. Films which have been reissued for theater exhibition, it was said, have produced from $125,000 to $750,000 in revenue. When films are seen by the TV audience, without cost, their value to theaters is substantially reduced, the pix moguls added. Therefore, until the monetary return from the licensing of films for TV is comparable to that from theater exhibition, *Paramount* said it cannot afford to release its films for TV. The return will not be comparable, the brief disclosed, until there are more TV stations in operation. When that point has been reached, *Paramount* noted that it intends to make its library and new films, too, available for TV, unless they decide to make special TV pictures.

In addition to the difficulty arising from television's inability to pay as much for feature film as theaters, there are a number of legal and other problems which must be solved prior to releasing films for TV. *Paramount* said that it had many disputes over its rights to telecast its films with various guilds and musician unions, who have demanded additional compensation.

Commenting on theater TV, *Paramount* declared that it intends to apply on a nation-wide scale for authorization to transmit TV programs to theaters.

At the time of the hearing, there were sixty-nine theaters equipped with theater TV gear, of which ten were subsidiaries of the picture-theater chain. These installations were said to represent a total cost of over $200,000. *Paramount* theater execs revealed that the chain had experimented with over 100 theater TV events in its houses, and in each instance suffered a financial loss.

In a review of the financial plight of *ABC* and the need for additional capitalization, the brief disclosed that the network had found it necessary to borrow $2,000,000 during the '51-'52 period. It was also noted that at no time since the chairman of the net, Edward Noble, acquired the *ABC* system in '43, has a dividend been paid or has any salary been drawn, all the earnings having been plowed back into station improvements.

In contrast with other networks, with diversified and in many instances complementary resources, *ABC* said that it was dependent entirely on revenues from its radio and TV network operations, including its owned and operated stations. Because of the necessity for investing its limited funds in physical improvements, the network declared that it was without other funds needed for the development of a program service equal to that of its competitors. A few years ago, *ABC* was unable to hold some of its top entertainment stars on radio in competition with *CBS*, which was able to offer these leading lights capital-gains deals.

Under the merger, *ABC* and *Paramount* theater officers have testified

Concord Radio presents the world's most powerful TV antenna!

22 Db gain over tuned dipole!

motorless all-direction UHF-VHF-FM reception

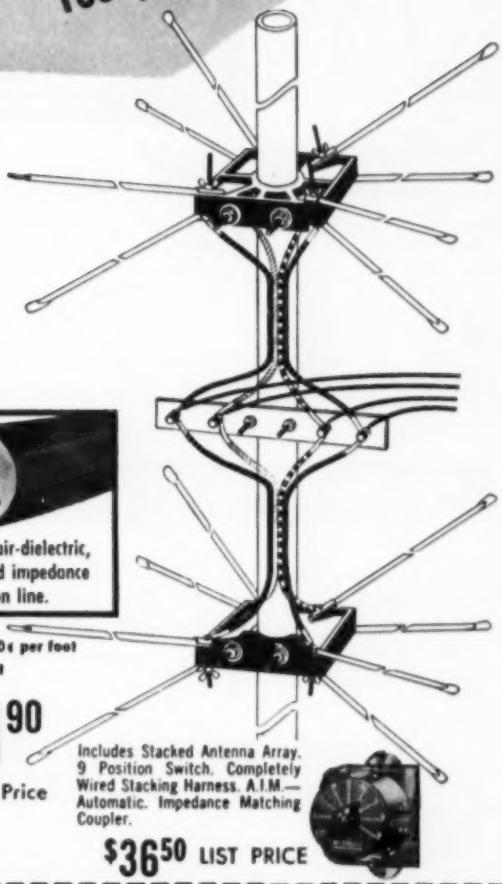

- Guaranteed 10 times more powerful than stacked 10 element Yagis.
- Receives channel 2-83 from all directions without a rotor.
- Broadband UHF-VHF and FM, motorless all direction reception.
- All aluminum flip-out assembly.

The only TV antenna that instantly beams the television set directly to the signal without a rotor. This antenna brings strong UHF & VHF signals from all directions to weak signal areas instantly... with a flick of the nine position switch located near the television set.

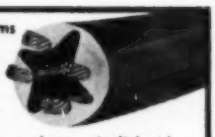

Four conductor air-dielectric, tubular, matched impedance transmission line.

4 Conductor Tubular Wire 10¢ per foot
$8.90 per hundred feet

$21.90 Dealer Price

Includes Stacked Antenna Array. 9 Position Switch. Completely Wired Stacking Harness. A.I.M.—Automatic. Impedance Matching Coupler.

$36.50 LIST PRICE

Mfg. solely by

ALL CHANNEL ANTENNA CORP.

Woodside, N.Y. under license Pat. No's 2,585,670. 2,609,503. 2,625,655. others pending.

MONEY BACK GUARANTEE To out-perform all other antennas (using rotor motors) on both UHF and VHF, including stacked ten element Yagis, stacked corner and bow-tie reflectors, four bay conicals, etc.

Concord Radio

53 Vesey Street, New York 7, N. Y. • Digby 9-1152

CONCORD RADIO 53 Vesey Street, New York 7, N. Y.

Please send me.....amount at $36.50 list price.

Please send me.....amount at $21.90 dealer net.

Dealers order on letterhead.

Please send me.....feet of 4 conductor tubular at 10¢ per foot.

Name.....

Address.....

City.....State.....

☐ Check Enclosed ☐ Money Order Enclosed

☐ C.O.D. enclosed please find 25% of total purchase price . . . check . . . Money Order.

☐ Please put my name on your "Special Bargain" mailing list.

( ) Enclosed find $.....in full. Send prepaid.

my Radio and T.V. REPAIR SECRET?

OHMITE®
DEPENDABLE REPLACEMENTS

Little Devil® COMPOSITION RESISTORS

Tiny, yes . . . but what dependability, ruggedness, and stability! And they provide an *extra* margin of safety—being rated at 70C rather than 40C. Completely sealed and insulated by molded plastic, they meet all JAN-R-11 requirements . . . are available in ½, 1, and 2-watt sizes in all RTMA values.

TYPE AB NOISE-FREE POTENTIOMETERS

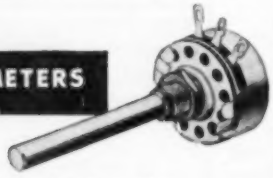

Because the resistance material in these units is solid-molded—not sprayed or painted on—continued use has practically no effect on the resistance. Often, the noise-level *decreases* with use . . . and they provide exceptionally long, trouble-free service. Rated at 2 watts, with a good safety factor.

BROWN DEVIL® AND DIVIDOHM® RESISTORS

BROWN DEVIL fixed resistors and DIVIDOHM adjustable resistors are favorite vitreous-enameled units! DIVIDOHM resistors are available in 10 to 200-watt sizes; BROWN DEVILS in 5, 10, and 20-watt sizes.

WRITE FOR STOCK CATALOG

OHMITE MFG. CO.
4885 Flournoy St.
Chicago 44, Ill.

Be Right With . . .
OHMITE
RHEOSTATS • RESISTORS • TAP SWITCHES

that there will be no joint buying of films for theater and television. While it is contemplated that *ABC* network programming will be 50% film, most of this film will not be motion-picture feature film, but film made especially for TV.

In a revealing analysis of the characteristics of motion picture and TV film, the brief declared that motion picture feature film represents only one type of programming on TV, and its use is subject to certain limitations and disadvantages. In the first place, it was noted, a small screen deprives the audience of background values, and certain lighting effects are unsuited for TV. Then, motion picture films are produced for a disciplined and concentrating audience free from the distractions that occur in many homes. In addition, the length of motion picture films and the unevenness of their lengths create problems, when they are fitted into the TV program structure. Finally, it was pointed out, the length of the feature films provides problems in securing sponsors, and in the case of networks, in securing clearances from stations. Advantages of films specially made for television are many, in contrast, it was brought out. They are not limited by the facilities for production as are live shows in the studio. The films can be used by stations at times when live programs cannot be cleared, and they can be used for rebroadcast or multiple showings. In addition, these films are technically designed for the TV receivers.

The brief noted that there was a view that the Commission's decision on the merger would eventually permit the motion picture industry to take over TV. This argument, it was said, ignores the fact that the operation of television stations is conducted pursuant to a statutory licensing plan. No transfer of a license may be made without Commission consent. And this consent is also required for a renewal of a license. Both require determinations as to the public interest. The fear of domination of television by motion picture interests, therefore, is unwarranted, it was emphasized, in view of the Commission's continuing supervision of the growth of television.

Madam Commissioner Frieda Hennock did not concur with her FCC colleagues and entered a seething dissent, which declared that the merger would not serve in the public interest, and the officers of the theater group were not qualified for the new assignment. According to Miss Hennock, the . . . "Commission has smashed . . . often beyond repair . . . precedents, procedures, and policies which have carefully been built up over the years of its regulatory process. In areas without established precedent, the Commission has taken an undue risk with the future of broadcasting by permitting the introduction therein of a new and potentially deleterious

(*Continued on page* 135)

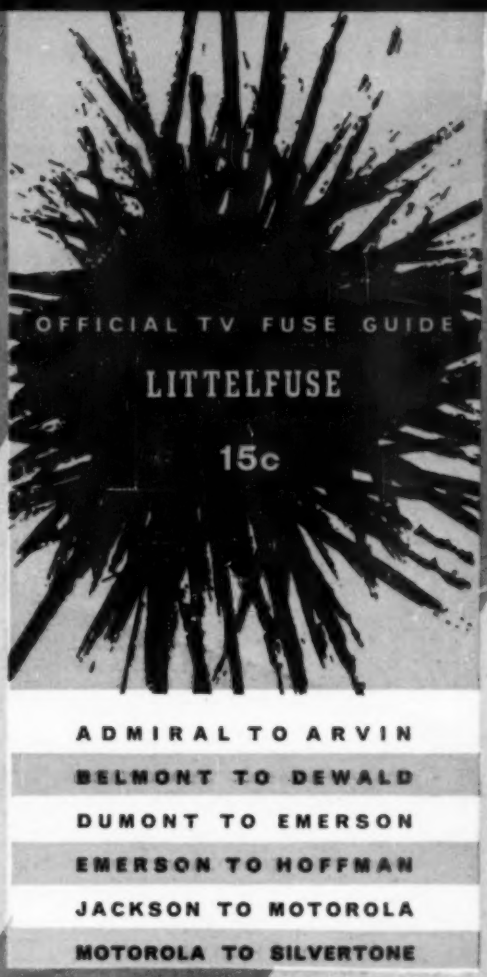

BOTH NEW – BOTH NEEDED

Littelfuse 1953 Official TV Fuse Guide tells you just what fuse to use—and when. 94 out of 100 times it's in the new Littelfuse One-Call Kit . . . brought up to the TV minute with a new fuse assortment. 45 TV fuses, 6 TV snap-on fuse mountings in a clear plastic hinged-cover bench box—custom-fitted to meet today's needs. Littelfuse Inc., Des Plaines, Ill.

WOULD YOU RISK 3¢ TO CREATE THE CUSTOMER CONFIDENCE THAT MEANS A MORE PROFITABLE FUTURE FOR YOU?

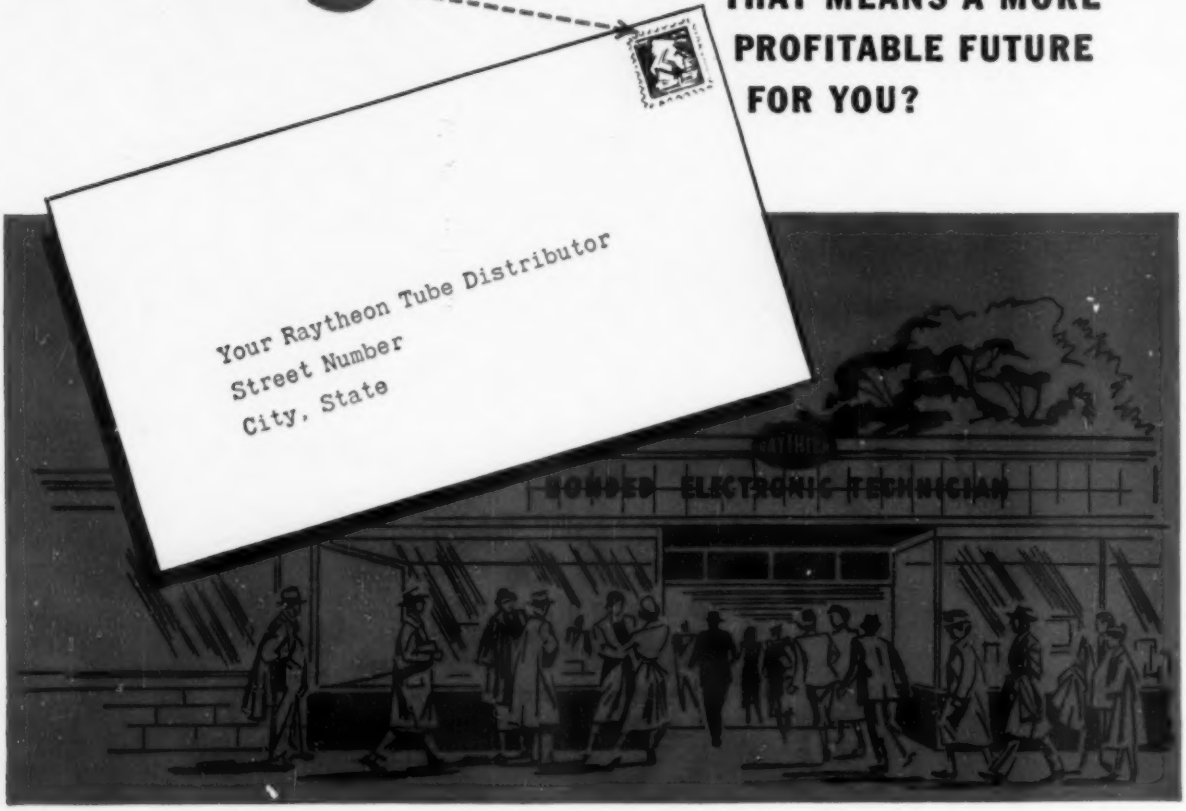

IF the answer is *yes,* write your Raytheon Tube Distributor right now. Ask him if you can qualify as a *Raytheon Bonded Electronic Technician.*

Here's why:

As a *Raytheon Bonded Electronic Technician* your repair work is guaranteed for 90 days — a guarantee cash-protected by a bond backed by Continental Casualty Company. You receive a registered Bond Certificate, Identification Cards, Decals, Creed Displays and other sales and shop helps, designed to build your business by creating customer confidence in you and your shop.

If you can qualify for this complete Raytheon Bonded program that is increasing volume and profit for thousands of service dealers from coast to coast *it costs you nothing.* It is Raytheon's investment in *your* future.

RIGHT . . . FOR SOUND AND SIGHT

RAYTHEON

RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division

Newton, Mass. Chicago, Ill. Atlanta, Ga. Los Angeles, Calif.

Excellence in Electronics

RAYTHEON MAKES ALL THESE

GET DEPENDABLE PERFORMANCE IN TV TEST EQUIPMENT!

Model ST-4A

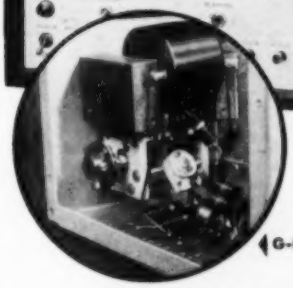

G-E VARIABLE PERMEABILITY SWEEP ELEMENT

All-Electronic Sweep

TROUBLE-FREE LIFE— NO MOVING PARTS!

Sweep Generator ST-4A. The problems of moving parts that wear or break and inaccurate measurements from jarred components so common with mechanical systems have been banished completely in the G-E Variable Permeability Sweep Generator. You get the adjustable wide-band linear sweep needed for TV work *plus* a total absence of moving parts! Good attenuation, extremely low leakage, and continuously variable center frequency. Covers all broadcast TV channels. Take the guesswork out of your test measurements. Use this sweep and your technicians can handle more work…handle it more efficiently…add to your profits and your reputation!

Model ST-5A

Marker Generator ST-5A. Marks all the critical frequencies on a pass band as well as having continuous coverage. Gives fast manipulation with crystal controlled accuracy for outstanding performance. Features separate crystal on each TV channel with simultaneous picture, audio and trap markers on both channel and intermediate frequencies.

Model ST-2A

Oscilloscope ST-2A. Reports from thousands indicate this scope does the job they need in TV circuit work. Used in conjunction with the G-E Sweep and Marker you have an unbeatable combination. Special features include wide frequency response plus DC amplifier to adapt the equipment to other applications.

Balanced Output Adaptor ST-8A. Converts single-ended Sweep Generator output to balanced output for 300 ohm television receiver work.

You can put your confidence in—

1878 75 1953 YEARS OF ELECTRICAL PROGRESS

GENERAL ELECTRIC

General Electric Company, Section 953
Electronics Park, Syracuse, N. Y.
Please send me complete specifications on G-E TV Test Equipment.

NAME.....
COMPANY.....
ADDRESS.....
CITY..... STATE.....

Depend on Mallory
for
Approved Precision Quality

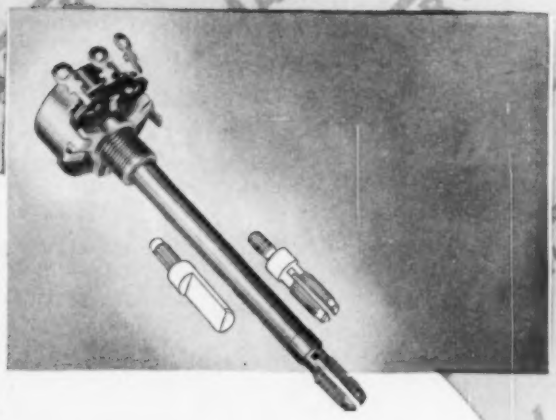

"WE'LL HAVE IT BACK TOMORROW"

Mallory Dual Control Kits

Three kits of controls and switches, selected to meet varying requirements in different parts of the country, will serve 50 different models of radio and television sets. You pay only for the controls and switches; attractive 3-drawer metal cabinet is free of extra cost. Get details from your Mallory Distributor.

Fast turnover . . . more jobs done per day . . . that's the answer to greater profits for any service shop. Every minute saved is time available for turning out more work.

That's why Mallory Midgetrols® were designed for fast, easy installation in any set . . . TV or radio.

***Round tubular shafts* can be cut accurately and quickly . . . fit split-knurl or flatted-type knobs.**

***AC switches* can be attached instantly without disassembling the control.**

***Unique design* simplifies inventory problems . . . makes them quickly available from your distributor.**

Midgetrols are engineered to match the electrical characteristics of the original equipment of any TV or radio set. They will give equal, and often better, performance and life than the original control.

For all your service work, use Mallory Midgetrols. They are the answer to fast installation . . . precision quality on every job.

This will save you time, too. Ask your Mallory Distributor for a copy of the Mallory Control Guide. It is a complete cross reference between set manufacturers' part numbers and the equivalent Mallory control.

MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

NO OTHER UHF ANTENNA COMBINES ALL 3

1 *Extra high gain*

2 *All channel reception*

3 *Sharp vertical and horizontal directivity*

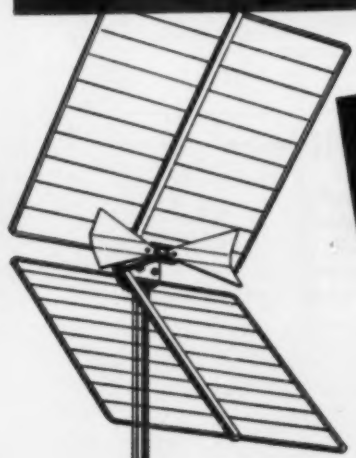

WALSCO

CORNER REFLECTOR

Model 4450 | **List $14.50**

Not 1... Not 2... but all 3 combined for amazing picture clarity

NOTHING . . . *absolutely nothing* compares with Walsco's Corner Reflector. It's the only UHF antenna that offers a 3-way *combination* that produces sharper, clearer TV pictures. Truly a masterpiece in precision electronic engineering.

COMPARISON CHART

	High Gain	All channel Performance	Sharp Directivity
WALSCO CORNER REFLECTOR	YES	YES	YES
ANTENNA B	NO	YES	NO
ANTENNA C	NO	YES	NO
ANTENNA D	YES	NO	YES

WALSCO *A Model to Fit Every Installation*

Walter L. Schott Co.
3225 Exposition Place
Los Angeles 18, California

Overseas Representative: Ad Auriema, Inc., 89 Broad St., New York 4, New York

New! another Channel Master development!

beats 'em all on UHF!

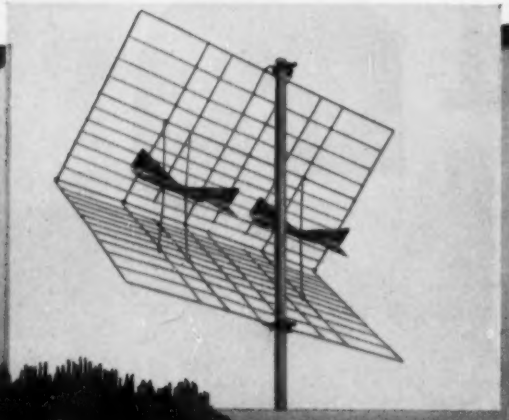

up to 16 db gain

CHANNEL MASTER'S TWIN CORNER REFLECTOR

Model No. 406

Gives the brilliant performance of 2 antennas!

THE MOST SENSITIVE UHF ANTENNA EVER DEVELOPED!

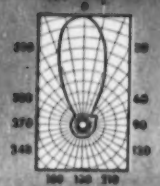

Twice the gain of the BEST standard UHF Corner Reflector

Extremely narrow forward lobe, with no side lobes and negligible rear lobe

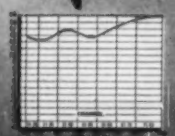

Excellent 300 ohm impedance match over the entire UHF range, provided by built-in, pre-cut matching harness

because Channel Master's Twin Corner Reflector really is 2 antennas . . .

stacked side by side into one simple structure

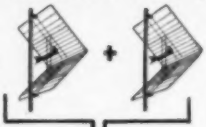

exclusive DUBL-DIPOLE design

- 2 antennas, electrically
- 1 antenna, mechanically
- One simple structure . . . one simple installation . . . highest gain, all-channel UHF coverage!

In any area you pick, the Twin Corner Reflector will out-perform any other antenna available today!

Ties together all 3 TV reception bands!

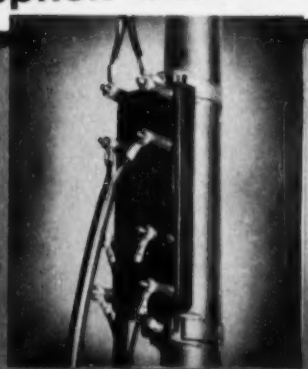

"Free spots" terminals. Impossible for dirt or rainwater to accumulate between the terminals, which can short out the picture. Assures you of brilliant, steady reception in ANY KIND OF WEATHER!

SINGLE LEAD • NO SWITCHING

ELIMINATES INTER-ACTION • NO SIGNAL LOSS ON VHF OR UHF

CHANNEL MASTER'S New!

TRIPLE-TIE model no. 9035

electronic inter-action filter

Combines up to 3 antennas with only 1 lead to the set.

1. Low Band VHF
2. High Band VHF
3. All UHF (Broad Band or Yagi)

Eliminates inter-action between all 3 antennas.

Designed to adapt all HI-LO VHF installations to UHF — quickly and economically

ULTRA FAN series — Complete VHF-UHF coverage

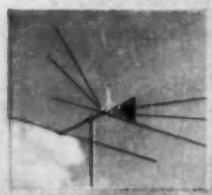

single bay — model no. 413

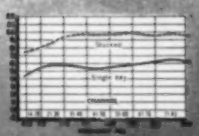

Today's most sensitive All-VU* antennas! The Ultra Fans actually operate on three separate electronic principles — automatically:

1. Low Band VHF (Channels 2-6) . . . Conical antenna with parasitic reflector
2. High Band VHF (Channels 7-13) . . . Large diameter V antenna
3. UHF (Channels 14-83) . . . Triangular dipole with sheet reflector

One set of All-VU* stacking rods provides highest VHF and UHF gain. Each Ultra Fan has its own 2-stage inter-action filter, so that only one transmission line to the set is required.

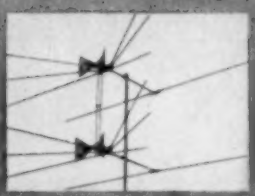

stacked — model no. 413-2

*All VHF, all UHF

ULTRA DAPTER
model no. 414

Instantly converts all Channel Master Super Fans into high gain, all-channel, VHF-UHF antennas. *Features a built-in inter-action filter.*

Your best bet for UHF!

CHANNEL MASTER Ultra-Tennas

America's most complete — most effective — UHF antenna line.

Channel Master's advanced engineering pays off again! While rain caused hundreds of UHF antennas to FAIL recently in Portland, *not one Channel Master antenna dimmed or shorted out a picture!* The facts speak for themselves: Rain or shine, Channel Master antennas outperform all others.

ULTRA BOW
model no. 401

The basic UHF antenna for primary signal areas, and the outstanding member of the bow-type antenna family.

Only Channel Master Antennas are designed to eliminate the "TWIN TERRORS" OF UHF RECEPTION:

- **Vibration, which causes picture flicker.**
  Eliminated by Channel Master's Ultra-Rigid construction and advanced mechanical design.
- **The accumulation of dirt or moisture around the antenna terminals, which dims and eventually shorts out the TV picture.**
  Eliminated by Channel Master's sensational "free-space" terminals which prevent the accumulation of foreign deposits at the feed points.

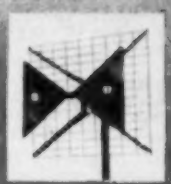

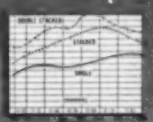

ULTRA BOW
with SCREEN REFLECTOR
model no. 403

Can be stacked in 2, 3, and 4 bays. High, all-channel UHF gain, excellent front-to-back ratio.

ULTRA VEE
model no. 404

- Good UHF gain
- Low VHF gain
- The most rigid UHF antenna of its type and size.

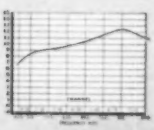

Gain: 11 DB, single
14 DB, stacked

DELTA WELD
Wide Band
10 Element
UHF Yagi

Custom-designed for full coverage of your specific area! Brilliant high gain performance across as many as *23 different channels.*

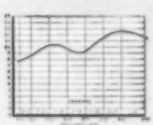

CORNER REFLECTOR
model no. 405

The outstanding all-channel UHF FRINGE antenna.

MEMBER
ANTENNA MANUFACTURERS ASSOCIATION

Sold through the nation's leading distributors

CHANNEL MASTER CORP.
ELLENVILLE, N. Y.

Write for complete technical literature

ULTRA-TIE model no. 9034
Electronic Inter-Action Filter

JOINS separate antennas into a single VHF-UHF antenna system, for use with a single transmission line.

SEPARATES VHF and UHF signals at the set or converter where separate inputs are provided.

The only filter with "free-space" terminals.

New Portable Battery-Operated Spring-Motor Tape Recorder

The Magnemite*

For all field recording without AC power! Smaller and lighter than a portable typewriter, the Magnemite* actually makes field recordings that can be played on *any* studio console equipment. Completely self-powered, the Magnemite* does away with bulky and cumbersome generators, storage batteries and rechargers.

Just check these unusual features:

- **Noiseless and vibrationless governor-controlled spring-motor assures constant tape speed.**
- **100 operating hours per set of inexpensive flashlight-type dry cell batteries.**
- **Earphone monitoring while recording, and earphone playback for immediate quality check.**
- **Operates in any position, and is unaffected by movement or vibration during operation.**
- **Warning indicator tells when to rewind, and shows when amplifier is on.**
- **Broadcast models weigh 15 pounds. Slow-speed models weigh only 10 pounds.**
- **Requires no more desk space than a letterhead, measuring only 11 x 8½ x 5½ inches.**

There's a choice of 5 different models for any recording need. High fidelity units, meeting primary and secondary NARTB standards, which record and play back frequencies up to 15,000 cycles, are available for broadcast stations, critical music lovers, and scientific research. For investigation, missionaries, reporters, and general dictation while traveling, there are units which play up to 2 hours per reel of tape.

AMPLIFIER CORP. of AMERICA
398 Broadway, N. Y. 13, N. Y

**Trade Mark Reg.*

Within the INDUSTRY

M. L. MYERS has been named assistant general sales manager of *Sparton Radio-Television* of Jackson, Michigan.

The post is a newly-created one designed to meet the needs of the company's augmented 1953 sales and advertising campaigns.

Mr. Myers, who has been on the company's sales staff for several months, served as division manager for the *Hercules Steel Company* and as sales manager for *Supermix, Inc.* before joining *Sparton*.

* * *

AMERICAN INSTITUTE OF MANAGEMENT has awarded certificates of management excellence to seven manufacturers in the radio and television field.

General Electric Co., Sylvania Electric Products Inc., and *Westinghouse Electric Co.* received awards for the third consecutive year. *Motorola Inc., Zenith Radio Corp., Philco Corporation,* and *RCA* were first-time winners.

In order to qualify for an award, the company must receive 7500 out of a possible 10,000 points. These credits are assigned for excellence in ten separate areas of management: economic function, corporate structure, health of earnings growth, fairness to stockholders, research and development, directorate analysis, fiscal policies, production efficiency, sales vigor, and executive evaluation.

* * *

EUGENE C. WHITE has been named to the newly-created post of industrial specialist for the tube department of the *General Electric Company*.

In his new position Mr. White will coordinate *G-E* policies for the sales of industrial tubes to manufacturers of electronic equipment.

For the past year he has been assistant to the sales manager of industrial and transmitting tubes. He is a Carnegie Institute graduate and has been with *G-E* since 1943.

* * *

TRIAD TRANSFORMER MANUFACTURING CO. has taken over the operations of **TETRAD CO., INC.,** manufacturers of miniaturized electronic components. Both firms are located in Venice, California. No change in personnel is contemplated . . . **DIVISION LEAD COMPANY** of Chicago has purchased **EAGLE-PICHER COMPANY'S** Metallic Products Division plant at Argo, Illinois. Equipment and personnel will be retained and absorbed into a combined operation . . . **ALLIED SOUND** of 115 W. 45th St., NYC, has changed its corporate name to **ASCO SOUND CORPORATION.** The management and activities of the firm are unchanged . . . **CLEVITE CORP.** of Cleveland has acquired the majority stock interest in **TRANSISTOR PRODUCTS, INC.** of Boston.

* * *

JOHN J. DOYLE, a 25-year-man with *Westinghouse,* has been named to the new post of manager of renewal sales for the company's tube division.

He was formerly manager of power tube sales and will now be responsible for planning and directing sales of all classes of tubes in the renewal tube market.

The company also announced the appointment of **JAMES L. BROWN,** as manager of equipment tube sales. He formerly headed cathode-ray and receiving tube sales.

These two new posts were created to enable the company to render more specialized service to distributors and service dealers as well as to equipment manufacturers.

* * *

HYTRON RADIO & ELECTRONICS CO. is constructing an ultra-modern television picture tube plant and warehouse in Kalamazoo, Michigan. It will be ready for occupancy during the summer of 1954 . . . **AMERICAN ELECTRONICS CO.** has moved to new and larger quarters at 1203-05 Bryant Ave., New York 59, N. Y. . . . A branch office at 2718 Linwood Blvd. in Kansas City has been opened by **L. F. WAELTERMAN CO.** of St. Louis. The firm acts as manufacturers representatives for a number of electronic firms. A. S. Engelman will be in charge of the new branch . . . **MORT'S RADIO SHACK, INC.** has moved to 1920-22 Milwaukee Ave. in Chicago. The new location offers ample parking facilities, a high-fidelity sound room, and housing for a complete line of radio and television components . . . **UNGAR ELECTRIC TOOLS, INC.** has moved to a new $200,000 plant near Venice, California. The new facilities include a one-story main office and factory building and a rear building to house a woodshop and machine shop . . . **ASTRON CORPORATION** has expanded its plant and manufacturing facilities at 255 Grant Ave. in East Newark, N. J. The additional space will permit the company to double its

AMAZING NEW TRAINING PLAN

Leonard C. Lane, U.S.M.A.
President of Radio-Television Training Association
Exec. Dir. of Pierce School of Radio and Television

NOW . . . YOU CAN BECOME A

LICENSED* TV TECHNICIAN

LICENSED TV MEN MAKE MORE MONEY

SET-UP YOUR OWN HOME LABORATORY WITH THE 15 BIG TELEVISION-RADIO KITS WE SEND YOU (At No Extra Cost)

AT NO EXTRA COST! YOU GET A ROUND TRIP TO NEW YORK CITY

FROM ANYWHERE IN THE U.S. OR CANADA—I pay your way to New York and return, PLUS 2 FREE weeks, 50 hours of advanced instruction and shop training at the PIERCE SCHOOL OF RADIO & TELEVISION. You use modern electronics equipment, including student-operated TV and Radio stations. You go behind the scenes of New York's big Radio-TV centers, to study first hand. And I give you all this AT NO EXTRA COST! (Applies to complete Radio-TV course only.)

Only RTTA makes this amazing offer.

YOU BUILD AND KEEP ALL THESE UNITS

—INCLUDING BIG SCREEN TV RECEIVER, plus Super-Het Radio Receiver, R.F. Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Receiver, AC-DC Power Supply. Everything Furnished Including All Tubes, and Big TV Tube

TAKES UP TO 21 in. PICTURE TUBE

EXTRA FEATURES THAT MEAN MORE MONEY FOR YOU!

Thousands of new job opportunities will be available for you right in your own state, now that the government has lifted restrictions on new TV stations. My simple, successful methods can PREPARE YOU NOW to take your place in America's booming TELEVISION and Electronics industries . . . help you get the success and happiness that you always wanted out of life. You learn the practical, easy way by using actual parts and equipment in the 15 big Radio-TV kits I send you, including a COMPLETE TV RECEIVER . . . yours to build and keep.

My Advanced Training Prepares You For Better Jobs

Then, after you finish your training for a position as a full-fledged TV Technician—where you can write your own ticket and choose from dozens of fascinating careers—*I don't stop there!* I continue to train you—AT NO EXTRA COST—to qualify for even better pay in the BETTER JOBS that demand FCC licenses, with my . . .

FREE FCC COACHING COURSE

PREPARES YOU AT HOME FOR YOUR FCC LICENSE

THE BEST JOBS IN TV AND RADIO REQUIRE AN FCC LICENSE

Given to every student at NO EXTRA COST after TV Theory and Practice is completed.

NOW! Advanced FM-TV Training For Men Who Know Radio

Prepares You For Higher Pay Jobs In A Few Months

COMPLETE theory and practical training course . . . complete with kits including large screen TV receiver.

FCC License Coaching Course Included FREE.

ATTENTION! VETERANS!

MY SCHOOLS FULLY APPROVED TO TRAIN VETERANS UNDER NEW G.I. BILL! If discharged after June 27, 1950—CHECK COUPON BELOW! Also approved for RESIDENT TRAINING in New York City . . . qualifies you for full subsistence allowance up to $160 per month.

I GET MY GRADUATES GOOD PAYING JOBS!

"As Merchant Ship Radio Officer, I receive $887. for 40-day trip. Your training helped me get this fine position."
— Stanley Nawrocki

I now hold a fine airlines position at La-Guardia Field, New York City, thanks to your excellent training."
— Joseph Rosenberg

"Your excellent instruction helped me get my present job as an airport radio mechanic for American Airlines."
—Eugene E. Basko

"Thanks to your training, I qualified for a good job as a Receiver Tester at Feceral Telephone and Radio."
—Paul Frank Seier

Many others working at NBC, RCA, CBS, Dumont, Philco, Emerson, Admiral and other leading firms.

RADIO-TELEVISION TRAINING ASSOCIATION

1629 Broadway, Radio City Station, New York City 19, N. Y.

Approved as a Correspondence School under the laws of the State of New York

BOTH FREE New Illustrated Book plus Sample Lesson

NO SALESMAN WILL CALL!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSN.
1629 Broadway, Radio City Station
New York 19, N. Y. Dept. T-5

Dear Mr. Lane:

Mail me your *NEW* FREE BOOK and SAMPLE LESSON that will show me how I can make BIG MONEY in TELEVISION. I understand I am under no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I am interested in: ☐ Radio-TV ☐ Advanced FM-TV
VETERANS: If qualified under new G.I. bill, check here ☐ Resident Study ☐

productive capacity for condensers . . . **MOULTHROP AND HUNTER,** manufacturers representatives, have moved to 160 Tenth Street in San Francisco . . . **KIMBLE GLASS CO.** is building a modern television bulb manufacturing center at Sayreville, N. J. Equipment to enable an output of approximately 150,000 television bulbs per month is now being installed . . . The offices and showrooms of **DALEO** and **MIDTOWN CABINET SALES INC.** have been moved to 160 E. 56th St. in New York. The company handles television and radio cabinets.

• • •

SYLVAN A. WOLIN, well-known in the electronic parts field for twenty years, has established his own advertising agency at 15 W. Palisade Ave. in Englewood, N. J.

Mr. Wolin recently resigned his position as vice-president in charge of sales of the *Pyramid Electric Company.* Prior to this association, he was with *Solar Manufacturing Corp.*

His firm will specialize in handling electronic accounts.

• • •

ROBERT C. SPRAGUE will return to *Sprague Electric Company* as chairman of the board of directors after an extended vacation. He withdrew his nomination as under-secretary of the Air Force when he decided against selling his stock in the firm he founded. The new officers of the firm, elected recently, will retain their posts . . . **PAUL EVANS** has joined *Heppner Mfg. Co.* as a design engineer. He was formerly a project engineer with *Sylvania* and on the engineering staff of *Westinghouse . . . General Instrument Corp.* has named **LEE BALLENGEE** as assistant sales manager and **B. V. K. FRENCH** as manager of the company's Chicago office . . . **DWIGHT W. BLOSER,** formerly chief engineer of the *Transicoil Corp.* of New York has been named vice-president of the firm. He will supervise the design, engineering, and production of the company's products . . . **GEORGE HALSTED** has been appointed to the newly-created position of field training manager for *Motorola Inc.* . . . The promotion of **HUGH F. COLVIN** to the post of vice-president and treasurer has been announced by *Consolidated Engineering Corp.* . . . **HERMAN N. LUBERT** is the new advertising and export manager for *Fada Radio & Electric Co., Inc.* . . . **MYRON T. SMITH** has been promoted to the post of sales manager for *General Radio Company.* **S. W. DeBLOIS** has been appointed export manager for the same firm . . . **JOHN H. CRAFT, JR.** is the new national service manager for the radio and television division of *Stromberg-Carlson Co.* . . . *Stewart-Warner Electric* has appointed **BURTON P. GALE** to the post of advertising manager . . . **NORMAN SKIER** is the new merchandise manager

(*Continued on page* 157)

UHF OR VHF television...

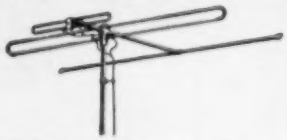

INLINE *Antenna for maximum broadband* VHF *gain over all channels.*

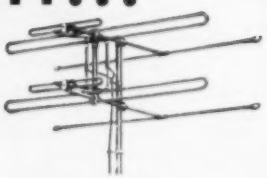

Stacked INLINE VHF *Antenna for fringe signal areas.*

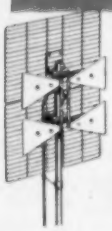

Two BO-TYs *stacked for increased gain and reduced vertical response.*

BO-TY *Antenna for all-channel* UHF *reception.*

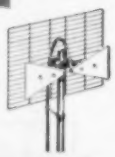

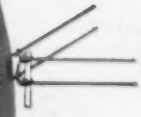

STACKED-V *for* VHF, UHF, *or* VHF-UHF *reception.*

CORNER REFLECTOR *for increased gain over* UHF *channels.*

RHOMBIC *for any* UHF *channels where narrow lobe and high gains are needed.*

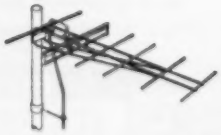

YAGI *for maximum gain over specific* UHF *channels.*

For the finest picture your set can produce use a Quality AMPHENOL Antenna best suited to the problems of your location. Consult your AMPHENOL Distributor or Dealer about the specific problems of your particular location.

AMPHENOL

AMERICAN PHENOLIC CORPORATION

Chicago 50, Illinois

ONLY THE PHILCO TUBE CHECKER

Tests 'Em All!

Mutual Conductance Dynamic Tube Checker Model 7052

Here's Philco's answer to your tube checking problems . . . a mutual conductance tube checker that tests 'em all from subminiature to acorn low power transmitting tubes . . . featuring the most sensational roll chart yet designed for efficiency and speed of operation. Its compact design, finished in beautiful grey leatherette with blue panel, makes it adaptable for both portable and counter top use. *Size—17" W x 18½" L x 10" D. Weight—21 lbs. (Shipping Wt. 24 lbs.). Operating Voltage—105-130 volts AC.*

- ✓ Most complete, easiest to use roll chart ever designed.
- ✓ Mutual conductance readings given directly in Microhms.
- ✓ Forecasts remaining tube life!
- ✓ Checks shorts and leaks between elements of tubes.
- ✓ Determines noise characteristics and gas content of tubes.

Now Yours on New SPECIAL PAYMENT PLAN

CATHODE RAY TUBE CHECKER

MODEL 7053. From Philco, the *only* emission CRT checker containing a built-in neon bulb calibrator for individual calibration of bulb sensitivity . . . for pin point accuracy and finest sensitivity each unit is individually calibrated . . . tests all picture tubes.

3-INCH OSCILLOSCOPE

MODEL 7020. The ultimate in portability . . . this Philco scope is 2½ times smaller than other 3" units . . . adaptable for bench use or field servicing . . . now, avoid guesswork with *pre-set* horizontal and vertical sweep rates. Provide measurements accurate to within 5%.

FILL OUT AND MAIL COUPON OR SEE YOUR PHILCO DISTRIBUTOR NOW

PHILCO CORPORATION, Accessory Division
Allegheny & "A" Sts., Philadelphia, Pa.

☐ I am interested in the Philco Test Equipment shown here. Please send me details of your SPECIAL PURCHASE PLAN for obtaining these units.

☐ Please send FREE copy of your new booklet on Philco Test Equipment.

NAME .....

ADDRESS .....

CITY ..... STATE .....

PHILCO Test Equipment

SPECIFICALLY DESIGNED FOR THE SERVICEMAN

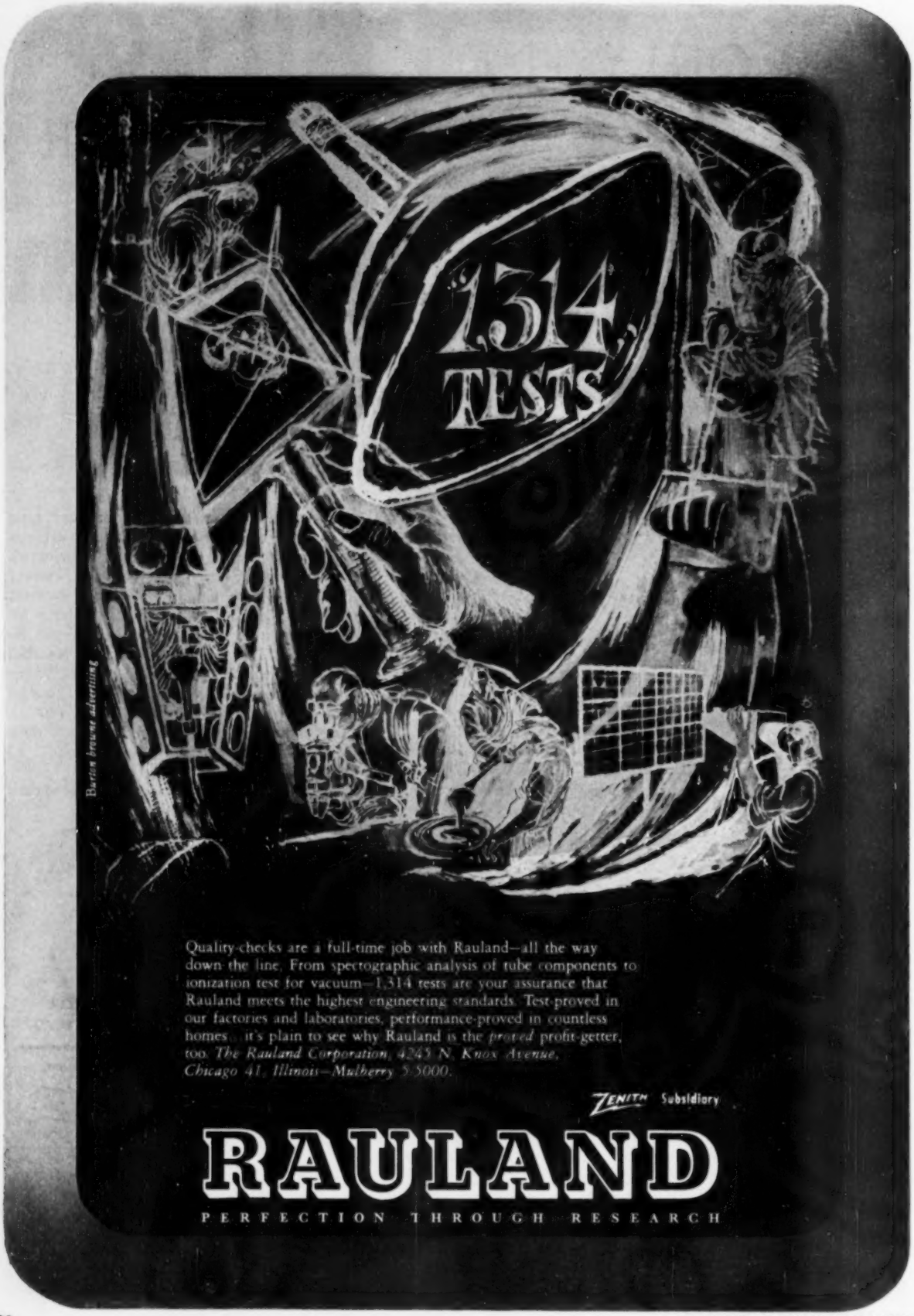

Quality-checks are a full-time job with Rauland—all the way down the line. From spectographic analysis of tube components to ionization test for vacuum—1,314 tests are your assurance that Rauland meets the highest engineering standards. Test-proved in our factories and laboratories, performance-proved in countless homes . . it's plain to see why Rauland is the *proved* profit-getter, too. *The Rauland Corporation, 4245 N. Knox Avenue, Chicago 41, Illinois—Mulberry 5-5000.*

ZENITH Subsidiary

RAULAND

PERFECTION THROUGH RESEARCH

Sweeping the Country!

BUY DIRECT AND SAVE

'PRE-FAB' **COLLINS** TUNERS and RECEIVERS

AUDIO PRODUCTS CO.

Collins Audio Products Co. is in no way affiliated with Collins Radio Co.

Two ALL NEW Complete Kits for Every High-Fidelity Need

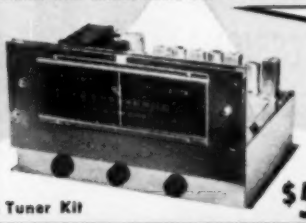

FM Tuner Kit **$55**

The FM-11 tuner is available in kit form with the IF Amplifier mounted in the chassis, wired and tested by us. You mount the completed RF Tuning Unit and power supply, then after some simple wiring, it's all set to operate. 11 tubes: 6J6 RF amp, 6AG5 converter, 6C4 oscillator, 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF, (2) 6AU6 limiters, 6AL5 discriminator, 6AL7-GT double tuning eye, 5Y3-GT rectifier. Sensitivity 6 to 10 microvolts, less than ½ of 1% distortion, 20 to 20,000 cycle response with 2DB variation. Chassis dimensions: 12½" wide, 8" deep, 7" high. Illustrated manual supplied. Shipping weight 14 lbs.

Each Collins Tuner Kit is complete with punched chassis, tubes, power transformer, power supply components, hardware, dial assembly, tuning eye, knobs, wire, etc., as well as the **completed** sub-assemblies: FM tuning units, AM tuning units, IF amplifiers, etc., where applicable. Since all these sub-assemblies are wired, tested and aligned at the factory, Collins Pre-Fab Kits are easily assembled even without technical knowledge. The end result is a fine, high quality, high fidelity instrument at often **less than half the cost** — because you helped make it and bought it direct from the factory. Bring your present reproducing system up to date with a new Collins Tuner.

FM/AM Tuner Kit **$77.50**

The original 15 tube deluxe FM AM pre-fab kit redesigned on a smaller chassis. The tuner now measures 14" wide by 12" deep by 7½" high. This attractive new front and dial assembly opens up new applications where space is at a premium. Kit includes everything necessary to put it into operation—punched chassis, tubes, wired and aligned components, power supply, hardware, etc. Kit comprises FMF-3 tuning unit, IF-6 amplifier, AM-4 AM tuning unit, magic eye assembly and complete instructions. All tubes included. Shipping weight 19 lbs.

Selected Basic Components For Special Applications

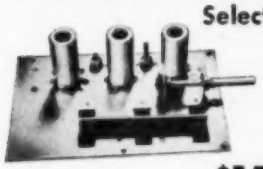

FMF-3 Tuning Unit **$15.25**

The best for FM. The most sensitive and most selective type of "front end" on the market. 6 to 10 microvolts sensitivity. Image ratio 500 to 1. 6J6 tuned RF stage, 6AG5 converter, 6C4 oscillator. Permeability tuned, stable and drift-free. Chassis plate measures 6½"x4½". In combination with the IF-6 amplifier, the highest order of sensitivity on FM can be attained. Tubes included as well as schematic and instructions. Draws 30 ma. Shipping weight FMF-3: 2½ lbs. Dial available @ $3.85

IF-6 Amplifier **$19.75**

A remarkable value! 6 tubes are used in the IF amplifier: 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF's, (2) 6AU6 limiters and 6AL5 discriminator. High gain, wide-band response (200 KC) for highest fidelity. 20 to 20,000 cycles. Distortion less than ½ of 1%. Draws 40 ma @ 220 volts. Chassis plate dimensions: 11-5/16"x2½" Shipping weight: 3 lbs.

AM-4 Tuning Unit **$24.50**

Tops in AM superhet performance! A 3-gang tuning condenser gives 3 tuned stages with high sensitivity and selectivity. Assembly is completely wired, tested and aligned ready for immediate use. Frequency coverage 540 KC to 1650 KC at a sensitivity of 5 microvolts. Tubes 6BA6 RF amplifier; 6BE6 converter; 6BA6 IF amplifier and 6AT6 detector. Draws 30 ma @ 220 volts. Mounts on a chassis plate measuring 4"x7⅜", Shipping weight 2½ lbs. Dial available at $3.85.

RD-1C Tuner & Dial **$28.50**

The COLLINS RD-1C FM tuner chassis is unique in the field. A whole, compact FM tuner and dial that fits in the palm of your hand. Convert AM sets to FM/AM receivers for only a few dollars! Unlimited applications where space is at a premium. Use in conjunction with your phonograph amplifier. Full frequency response to 20,000 cycles. Sensitivity 20 microvolts, permeability tuned. Tuning unit and IF amplifier on the same chassis plate. Draws 40 ma @ 100 volts. Tubes: 6AG5 converter, 6C4 oscillator, (2) 6AU6 IF amplifiers, 6AL5 in new ratio detector circuit. Shipping weight tuner and dial 5 lbs.

MAIL COUPON TODAY

To: Collins Audio Products Co. Inc.
P.O. Box 368, Westfield, N. J.
Tel. WEstfield 2-4390

☐ FM Tuner Kit ☐ FM/AM Tuner Kit ☐ Slide Rule Dial Assembly
☐ FMF-3 Tuning Unit ☐ IF-6 Amplifier ☐ RD-1C Tuner and Dial
☐ AM-4 Tuning Unit

NAME .....

ADDRESS .....

CITY ..... STATE .....

Amount for Kit $..... See weights, add shipping cost $.....

Total amount enclosed $..... Check ☐ Money Order ☐

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS

G.E. AGAIN TELLS AMERICA THE

● **These ads, and those run in Life and Collier's last fall, are all part of the public relations program General Electric is sponsoring in the interests of the TV Service industry.**

50,000 MEN LIKE "DUSTY" RHODES MAKE TV SERVICE A "PROFESSION"

"DUSTY" RHODES, owner of Rhodes Radio and Television, Paterson, N. J.

HE GIVES PATERSON, N.J., A PROFESSIONAL TEAM OF ACE SERVICE MEN

Across the country, TV service has become accepted as a new "profession." One of the reasons is this new industry's high calibre of men. Take "Dusty" Rhodes of Paterson, N. J. He's on the Chamber of Commerce's Board of Directors. He's president of the Radio and Television Service Men of N. J. He's active on the Community Chest. In other words, he's a credit to his calling and his community.

J. PALMER MURPHY, manager, Greater Paterson Chamber of Commerce, says: "'Dusty' Rhodes is the kind of man any community would be happy to have—a definite asset."

RICHARD E. KINN, salesman, says: "I've sent innumerable people to him—that shows how much I think of his service." Kinn's wife says: "His men are polite and efficient."

MRS. ROSE ZARROW, housewife, says. "Rhodes' service is wonderful. As soon as you call them they're here—no petty excuses—just like the minute-men."

BEN MERKER, Rhodes' service manager, is a graduate of DeForrest Training School and like all Rhodes' service men he regularly attends technical seminars and courses.

One of a series of informative advertisements on TV service.
Tube Department, General Electric Company, Schenectady 5, N.Y.

GENERAL ELECTRIC

TRUE STORY OF TV SERVICING

- **Four powerful, informative ads in Look Magazine**
- **Reaching 13,187,140 readers**
- **Reporting the *facts* on typical TV Service Dealers**
- **Convince present and future set owners of the know-how and integrity of TV Service Dealers**

THIS BOOKLET FOR SET OWNERS...

outlining the intricate requirements of TV servicing —was also made available to service dealers. And, through G-E tube distributors and tube dealers, hundreds of thousands of copies are finding their way into the homes of America.

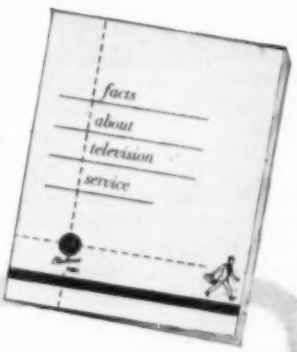

What are <u>you</u> doing to follow through on this effort in your own locality?

HERE'S WHAT YOU <u>CAN</u> DO:

1. You can build customer goodwill through full explanation of service charges.
2. You can endorse sound business practices in your own service associations.
3. You can actively "sell" service, to increase your income and prestige in your community.
4. You can support distributors and programs which advance the interests of the Service Dealer.

TUBE DEPARTMENT, SCHENECTADY, N. Y.

GENERAL ELECTRIC

161-1A3

for every audio need

CANNON PLUGS

you can hear the difference

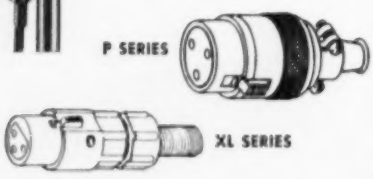

In addition to the lines illustrated, the 45E Test Point Jacks and connectors in the GB, U, and M1-4 series are available through the 130 selected franchised distributors for Cannon Electric. Other electronic-electric distributors also sell certain items in the Cannon line, including XL, M1-4, and GB series connectors, and a variety of Cannon Specialty Lights. Write for the RJC and Audio Connector Bulletins.

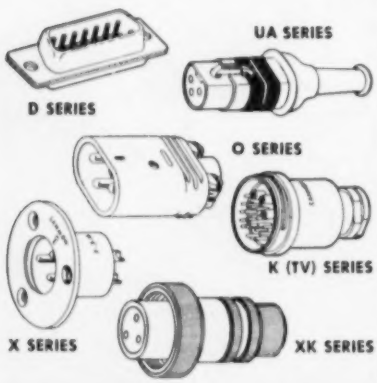

CANNON ELECTRIC

Since 1915

FACTORIES IN LOS ANGELES, TORONTO, NEW HAVEN

Representatives in principal cities. Address inquiries to Cannon Electric Co., Dept. E-145, Los Angeles 31, California.

PARTS SHOW EXHIBITORS

May 18-21, Conrad Hilton Hotel, Chicago, Illinois

Aerovox Corporation
Akro-Mils, Inc.
Alliance Manufacturing Co.
Allied Electric Products, Inc.
Alpha Metals, Inc.
Alpha Wire Corporation
Alprodco, Inc.
Altec Lansing Corporation
American Microphone Co.
American Phenolic Corporation
American Radio Hardware Co.
American Television & Radio Co.
Amperite Corporation, Inc.
Anchor Radio Corporation
Approved Electronic Instrument Corp.
Argos Products Co., Inc.
Astatic Corporation
Astron Corporation
Atlantic Wire & Cable Co.
Atlas Sound Corporation
Audak Company, Inc.
Audio Devices, Inc.
A-V Tape Libraries

Baker Manufacturing Co.
Barker & Williamson, Inc.
Belden Manufacturing Co.
Bell Sound Systems, Inc.
Blonder-Tongue Labs., Inc.
David Bogen Co., Inc.
Brach Manufacturing Corporation
British Industries Corporation
Brush Development Co.
Bud Radio, Inc.
Burgess Battery Co.
Burlington Instrument Co.
Bussmann Manufacturing Co.

*Caldwell-Clements, Inc.
Camburn, Inc.
Centralab
Channel Master Corporation
Chicago Transformer Division
Clarostat Manufacturing Co., Inc.
Clear Beam TV Antenna Co.
Cleveland Electronics, Inc.
Columbia Wire & Supply Co.
Condenser Products Co.
Consolidated Wire & Associated Companies
Continental Carbon, Inc.
Copperweld Steel Company
Cornish Wire Company, Inc.
*Cowan Publishing Corp.
Crescent Industries, Inc.
Crest Laboratories, Inc.
Crest Transformer Corporation
Crestwood Recorder Division

Davis Electronics
Drake Electric Works, Inc.
Dukane Corporation
Allen B. DuMont Labs., Inc.
Duotone Company, Inc.

Hugh H. Eby, Inc. (Eby Sales Co.)
Elcor, Inc.
Elco Corp.
Eldico of New York, Inc.
Electronic Instrument Co., Inc.
Electronic Measurements Corporation
Electronic Publishing Co., Inc.
Electro Products Laboratories, Inc.
Electro-Voice, Inc.
Electrovox Company, Inc.
Ellar Woodcraft Corporation
Equipto Division
Erie Resistor Corporation

Federal Telephone & Radio Co.
Finney Company
Fisher Radio Corporation
Freed Transformer Co., Inc.
Fretco, Inc.

Gee-Lar Manufacturing Co.
General Cement Manufacturing Co.
General Electric Co.
General Fuse Co.
General Industries Co.
General Instrument Corporation
Gonset Co.
Grayburne Corporation
Grayhill
Great Eastern Mfg. Co.
Guardian Electric Manufacturing Co.

Halldorson Transformer Co.
Hallicrafters Co.
Hammarlund Manufacturing Co., Inc.
Hardwick, Hindle, Inc.
Haydon Products Corporation
Hickok Electrical Instrument Co.
Hi-Lo TV Antenna Corporation
Hytron

IE Manufacturing
Illinois Condenser Co.
Illinois Transformer Co.
Imperial Radar & Wire Co.
Indiana Steel Products Co.
Industrial Development Engineering Associates, Inc. (I.D.E.A.)
Industrial Television, Inc.
Insuline Corporation of America
International Resistance Co.

Jackson Electrical Instrument Co.
James Vibrapowr Co.
J-B-T Instruments, Inc.
Jensen Industries, Inc.
Jensen Manufacturing Co.
Jerrold Electronics Corporation
Jersey Specialty Co., Inc.
JFD Manufacturing Co., Inc.
E. F. Johnson Co.
Jontz Manufacturing Co.
*Jobber News

Kester Solder Co.
Kleer-Vue Mfg.

La Pointe Electronics, Inc.
Lenz Electric Manufacturing Co.
Littelfuse, Inc.
Lowell Manufacturing Co.

P. R. Mallory & Co., Inc.
Markel Electric Products, Inc.
Don McGohan, Inc.
Merit Coil & Transformer Corporation
James Millen Manufacturing Co., Inc.
J. W. Miller Co.
M. A. Miller Manufacturing Co.
Model Engineering & Mfg., Inc.
Modern-Aire Manufacturing Corporation
Mosley Electronics

National Carbon Co.
National Co.
National Electric Products Corporation
National Union Radio Corporation
National Video Corp.
Newcomb Audio Products Co.

Ohmite Manufacturing Co.
Oxford Electric Corporation

Par-Metal Products Corporation
*Parts Jobber

(*Continued on page 166*)

NOW! ULTRA-HI "CONICAL-V-BEAMS" ©

by telrex

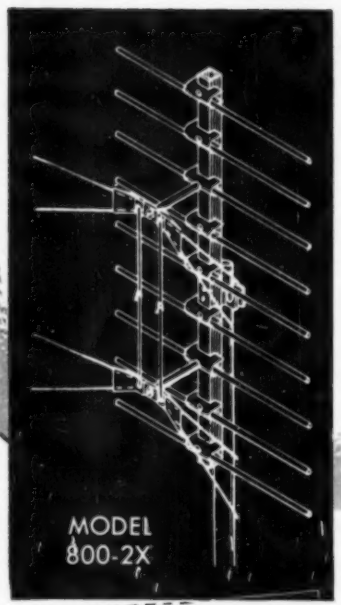

Outstanding Broadband UHF Antennas featuring—

● **STACKED HI-GAIN "CONICAL-V-BEAM" DIPOLES** — Ultra sensitive stacked array with excellent directivity for clean, snow-free, ghost-free long distance reception.

● **BROADBAND**—Stacked "CONICAL-V-BEAM" dipoles insure flat hi-gain response with full video and tone fidelity on any UHF channel, plus freedom from flicker or flutter!

● **HURRICANE DESIGN — FACTORY ASSEMBLED** — Light weight, ruggedized construction of the finest, most durable materials available today. Easily installed in a minimum of time.

NEW!

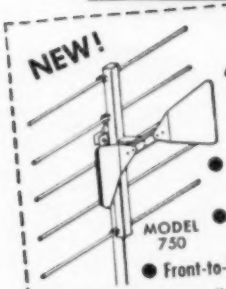

ULTRA "BOW-TIE" SERIES

- Peak efficiency — no "dead" spots
- Gain over 13db (stacked)
- Front-to-back ratio over 25db
- Simplicity of installation
- Rugged, all aluminum "Hurricane" construction
- Sectionalized design — basic units interchangeable for single bay, stacked or parabolic assembly

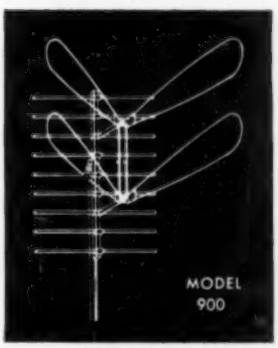

VISIT BOOTH 131
ELECTRONICS PARTS SHOW
HOTEL CONRAD HILTON
May 18th to 21st

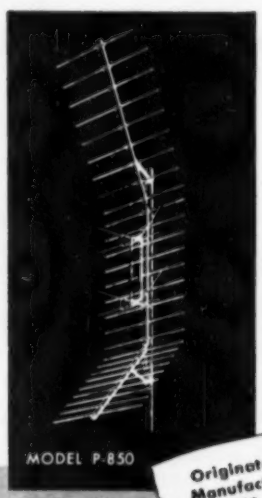

TELREX — TESTED, TRIED AND PROVEN FOR EVERY RECEPTION AREA, NEAR OR FAR!

"CONICAL-V-BEAMS" are produced under Re-issue Patent Number 23,346.

telrex INC.
CONICAL-V-BEAMS

AMERICA'S OUTSTANDING TELEVISION BEAM

Originators and Manufacturers of "CONICAL-V-BEAMS" — insist on the Original!

ASBURY PARK 7, N. J.

320K SIG. GEN.
KIT $19.95 WIRED $29.95

145K SIG. TRACER
KIT $19.95 WIRED $38.95

950K R-C BRIDGE & R-C-L COMP. KIT $19.95 WIRED $29.95

360K SWEEP GEN.
KIT $34.95 WIRED $49.95

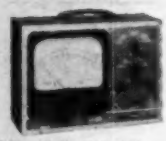

New 214K VTVM KIT
$34.95 WIRED $54.95

OVER 1/4 MILLION

EICO INSTRUMENTS

in use the world over!

New 377K SINE & SQUARE WAVE AUDIO GEN. KIT $31.95 WIRED $49.95

New 536K MULTIMETER
KIT $12.90 WIRED $14.90
1,000Ω/v; 31 ranges

1040K BATTERY ELIM.
KIT $25.95 WIRED $34.95

EICO new modern facilities for research, development and production—your greater assurance of . . .

LABORATORY PRECISION AT LOWEST COST

1171K RES. DECADE BOX
KIT $19.95 WIRED $24.95

625K TUBE TESTER
KIT $34.95 WIRED $49.95

CRA PIX TUBE ADAPTOR
for Tube Tester $4.50

New 565K MULTIMETER
KIT $24.95 WIRED $29.95
20,000 Ω/v; 31 ranges

315K DELUXE SIG. GEN.
KIT $39.95 WIRED $59.95

NEW 7" Push-Pull OSCILLOSCOPE

- Boosted vert. sensitivity: 10 mv rms/in.
- Extended flat freq. response: 10 cps—1 MC (±2 db).
- 3-step freq.-compensated attenuator; cathode follower input.
- Internal voltage calibrator; dir.-cal. screen.
- Extended sweep range: 15 cps—100 kc.
- Int. pos. or neg., ext. & line sync.
- On front panel: sawtooth, 60 cps outputs; intensity mod. & ext. sync inputs.
- Var. phasing of int. 60 cps sweep.
- Direct connection to CRT plates.

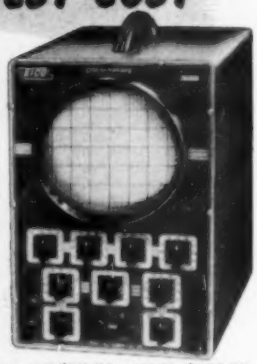

470K KIT $79.95 WIRED $129.50

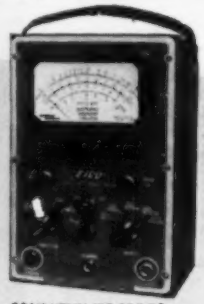

221K VTVM KIT $25.95
WIRED $49.95

HIGH VOLTAGE
PROBE $6.95

425K 5" PUSH-PULL SCOPE
KIT $44.95 WIRED $79.95

You Build EICO Kits in One Evening, but . . . They last a Lifetime! and You SAVE OVER 50%

YOU be the judge. See the famous EICO line TODAY — in stock at your local jobber — and SAVE!

Write NOW for FREE newest Catalog 5-R.

America's greatest instrument values bear the name—

EICO Reg. U.S. Pat. Off.

See EICO's Exhibit at The May Trade Show, Hotel Stevens, Chicago, May 18-21, Booth 202.

ELECTRONIC INSTRUMENT CO., Inc., 84 Withers Street, Brooklyn 11, N. Y.

© 1953

Prices 5% higher on West Coast. Specifications and prices subject to change without notice.

THERE'S CASH AFLOAT

By ALBERT ROBERSON

At left, the author checks a ty... local marine radiotelephone w... a simple dummy load. ... The "telephone" has a four-tub... receiver and small transmitt... on one chassis. Above is pa... has two-way radio and many ... have radio direction finders and ... ultrasonic depth indicator units.

A big new field of servicing is growing up and has hardly been touched. Marine radio all over the country offers the small service shop or the amateur a bright new opportunity.

I JUST built a two-story concrete building with money earned selling and servicing small boat radio equipment.

"Not for me," you might say—"there's no water for a hundred miles around."

But, just a minute! U. S. Coast Guard registration of motor boats has been showing a rise of about 10,000 craft yearly, with almost a half a million now afloat—and a large percentage of these boats have home ports well inland. For example, boat and engine sales agencies are springing up in states that at one time were the driest in the Union, in the wake of Federal reclamation, power, and conservation projects throughout the mid-continent.

It has gotten to the point that salt water is no longer necessary for marine business; places like Las Vegas and Sioux City are blossoming with marine activity, and wherever a boat sales agency can prosper, so can a marine radio business: from California to Rhode Island, and from Montana to Mexico.

Unlike the television service "boat," which many missed because they waited to see how far it would go before making the jump, and which just kept right on sailing until it was out of sight, this boat is just getting ready to "shove off." The man who equips himself and jumps right now can be in on the maiden voyage. From all signs it appears that this boat is heading into smooth waters for the would-be small businessman who, because of the well-established competition, is having rough going in the older fields.

There are a few personal qualifications to satisfy, and a few other technical ones, but nothing "out of this world" is needed either in the way of qualifications or equipment. Anyone who is capable of making a success in any other branch of the radio business can do it here, and the rewards are gratifying. Not only financially, but in the knowledge that in being expert in this highly important specialty, your radio training is being put to its best possible use: insuring the safety and welfare of a large segment of the public.

First of all, you must have at least a Second Class FCC ticket, phone or telegraph. The next most important requisite is the ability to get along with different kinds of people. You will possibly, as a matter of everyday work, stand face-to-face with every conceivable kind of person from opera stars to men covered with the mud they dredge for a living; and you must be able to show them that you know what you are doing. This is guaranteed to take practice and the exercise of a great deal of practical psychology, but the mental and facial calisthenics will pay well. It is notable that the people who own boats also own a modicum of cash. Serve them well, and you can latch onto a reasonable piece of it yourself.

Many people shy like frightened horses at the mention of getting any kind of FCC license, or taking a government examination. Assuming, however, that the technician who may want to enter this field is a competent one, as he should be, it would cost him little effort to master the material on transmitters required for Second Class licenses and to familiarize himself with the regulations that would apply to him. The Second Class examination material is hardly more difficult than that for the old amateur Advanced Class exam, though there is more of it. An established shop that has an active amateur among its technicians could probably depend on him to sail through the commercial test.

It should not be necessary to state that anyone hopeful of success in this field should be a good workman, as well as a sound theorist. But it is necessary to stress the great difference between the kind of work that can get by in the corner phono-television emporium, and the genuine first class craftsmanship that is absolutely required in the marine field. If the television set you have just worked on quits in the middle of "Uncle Milty," there is no earth-shaking loss. But if the radiotelephone a man needs to call the Coast Guard in an emergency stops putting out, it can cost some-

one's life. Hence a greater-than-normal sense of responsibility is needed.

To be successful within a reasonable period of time, the worker must not only bring some knowledge of his own to the job, but must continue to dig up more along the way. It is not enough to try to get by on just what is learned accidentally—ferreting out information must become second nature. Perhaps in no other field is there more scorn for the inept than in boating. So learn as much about boats as you can. Let no one say: "Oh, that guy. He doesn't know the blunt end from the sharp end." Remember that the blunt end is the stern, and carry the ball from there.

The instruments used in ordinary receiver servicing must be augmented by a few more to enable you to make measurements on transmitters. So, in addition to the sensitive volt-ohmmeter and the signal generator that represent the absolute minimum for any kind of work, at least the following instruments are required:

1. A frequency meter. This can be of the BC-221 family, or any commercial instrument covering the frequency range from 2 to 3 megacycles.

2. A dummy antenna, capable of indicating transmitter power output from 2 watts to 100.

3. A portable field strength meter.

4. An AM modulation meter. (This may be combined with the field strength meter.)

The instruments should be of good quality, remembering that not only do lives possibly depend upon their accuracy but also that your work on transmitters will fall under Federal Communications Commission surveillance—and it is very difficult to cook up satisfactory answers when they ask such rude questions as why a certain transmitter was over-modulating or radiating harmonics, and what, Old Man, do you intend doing about it?

In addition to the instruments, it will be necessary to have in the shop a husky d.c. power supply giving 6 volts up to 50 amperes; 12 volts up to 25 amperes, and 32 volts up to 10 amperes. Occasionally, you will encounter sets operating from 117 volts d.c., but I have found it possible on boats large enough to have 117 volts to service the equipment right on board, without removing it to the shop.

Of course, the cleanest source of all this d.c. power would be a nice heavy transformer and rectifier bank, such as those put out by *Mallory* and others. However, the man starting in business will find it possible to get by very well for a time with five fairly husky automobile batteries hooked in series, with a charger that will put about 6 amperes into them. When charged, or with the charger running, output will be a good 32 volts.

The only batteries that really need to be first class are the ones which you will use for 6 or 12-volt equipment. The ones making up the rest of the 32 volts can be junked batteries, as long as the cells are not absolutely shorted or open. The 32-volt equipment draws very little current, by comparison with the lower voltage gear, so the charger can be used to supply the actual running current for your 32-volt bench work, and the "dead" batteries will suffice very well as a filter to fill in current between peaks of the rectifier output.

These items are enough to start with, and it is better to wait until experience has filled out your list before gathering together a large and expensive layout.

The kind of sets you may expect to sell and service will depend upon your locality. In some places the most important item of service may be radar, loran, or sounding instruments. In others, the loop direction finder may have the greatest play; but almost everywhere will be found a market

Schematic of a typical marine radiotelephone. The receiver is a straightforward four-tube superhet, with nothing unusual except the added fixed-frequency channels. The extremely simple transmitter should hold no terrors for anyone. Servicing requires a few items of special equipment and a d.c. source. This unit is a Hudson American Corp. "Corsair II."

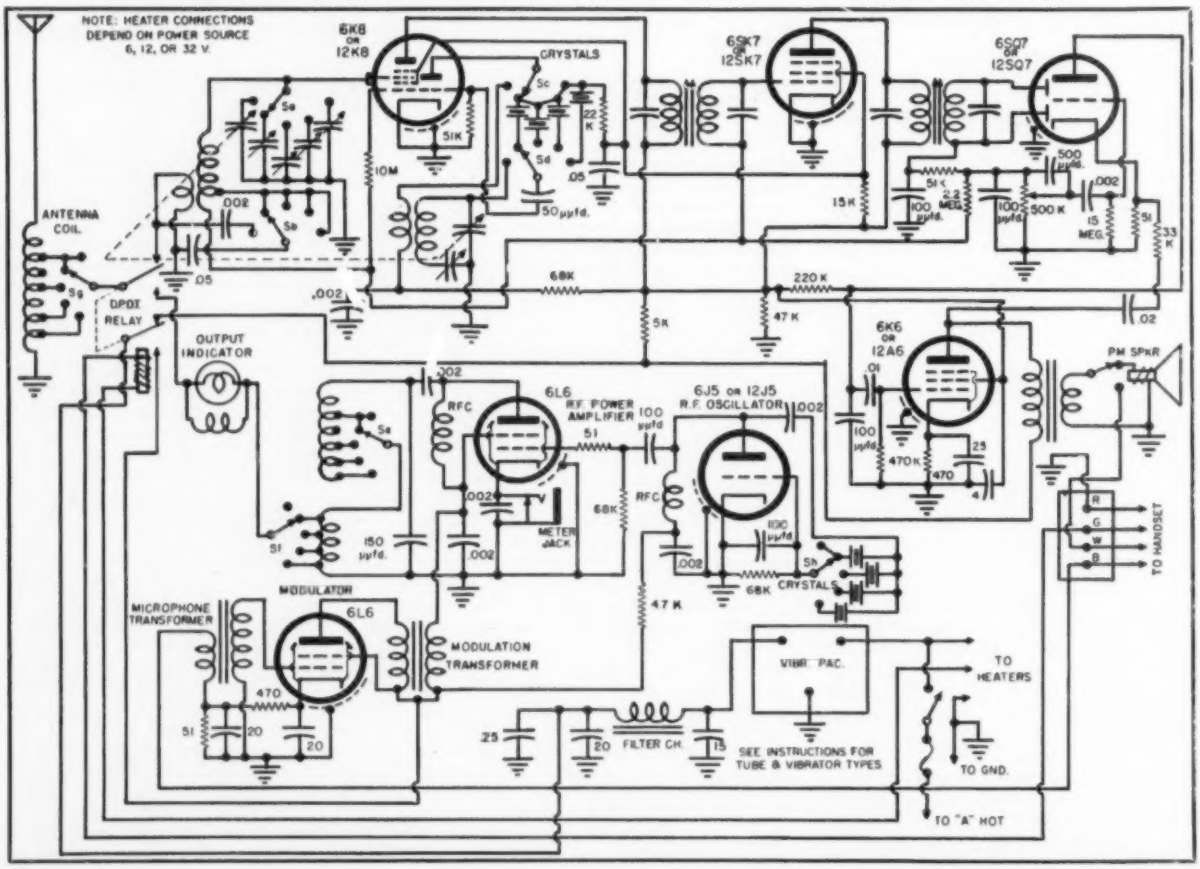

for marine type broadcast receivers and two-way radiotelephones.

Radio receivers for this market stem basically from old-time battery models, such as were used on farms. Nowadays, however, they use a d.c. input vibrator power supply which will operate directly from the boat battery, so they are built for 6, 12, or 32 volts. The main advance in their design over older sets will be slightly more rugged and moisture-proof construction, and the inclusion in the tuning range of the marine radiotelephone frequencies—from 2 to 3 megacycles. An assortment of 6, 12, and 32-volt vibrators, both synchronous and the simple interrupter types, glass fuses, and 0Z4 and 6X5 tubes added to a normal receiver-tube stock will permit service of most marine receivers.

Radiotelephones for marine use have all been designed to fulfill the absolute minimum requirements for communication, to keep size, weight, power drain, and expense all at a reasonable level. For example, none but the largest and most expensive of them have a speech amplifier. Instead, a telephone carbon mike which peaks sharply on voice frequencies feeds through a transformer into the modulator grid. Common practice is to modulate a 6L6 r.f. amplifier with another 6L6; an 807 with another 807, etc.

Transmitter circuits all follow the pattern of a Pierce or other untuned crystal-controlled oscillator, capacity-coupled to a beam-pentode power amplifier. Those installed in coastal waters cover 2 to 3 megacycles; lake and river sets cover from 2 to as high as 9 megacycles. The r.f. output circuits are designed for a Marconi antenna of from 12-foot length on up to one quarter wavelength. Tuning is accomplished in transmitter circuits by placing clips on the tuning coils or by movable slugs. There is one adjustment for each frequency, with all channels pre-tuned by the installer. Once tuned, the transmitter is closed, so the operator (who may be a shrimp fisherman or a used car salesman) will not be able to tamper with the circuits.

"Telephones" of about 10-watts output are powered by a 35-watt vibrator power supply, the output of which is fed either to the receiver plates or the transmitter, as the telephone is "keyed." The receivers are 4-tube jobs, with the antenna coupled directly into the mixer, and input circuits are slug-tuned. The better sets have the receiver oscillators crystal-controlled and all adjustments pre-made, as in the case of the transmitter.

A push-to-talk button on the handset actuates the antenna and power supply changeover relays. The circuit of one of the most popular radiotelephones of the past decade is shown on page 36 as an example of the circuitry to be expected.

Dynamotors power telephones larger than the 10-watters. It is well to locate a source of odd sizes of carbon brushes for servicing these dynamotors. Sometimes it is even necessary to saw and file larger brushes to fit these machines.

Among the best sales and service prospects are tugs and workboats. Elimination of revenue losses due to wasted time has, in many cases, paid for an installation like this in only one day's operation. Receiver at left monitors the ship-to-ship channel while the radiotelephone at right is busy on the ship-to-shore frequency. Pleasure-craft owners are also increasing use of radio, for safety and convenience.

Direction finders closely resemble the marine receivers in make-up, with the addition of a low frequency band to tune in marine radio beacons from 286 to 314 kilocycles. A shielded loop turned by a handle on top of the receiver cabinet is the means for finding the null-line or bearing of beacons or other stations; and a compass "rose" calibrated in degrees as well as the cardinal and inter-cardinal points is incorporated for transferring bearing lines onto a chart. After installation, direction finders are usually "calibrated" by the installer, which is to say that he determines the amount of radio field distortion around the vessel by comparing radio with visual bearings.

One other marine application of the electronic art the beginner can work with is the depth finder. This is the grand-daddy of radar. A high frequency sound wave is shot out of the bottom of the boat and an electro-mechanical timer measures the interval until its return, with the dial indication in feet or fathoms (6 feet).

(*Continued on page* 161)

Barge crews used to depend on uncertain whistle signals to convey instructions and reports. This radiotelephone, shown in the bunkhouse of an oil barge, makes communication quick, precise, and certain. It can protect lives and property if the engineless barge gets into trouble. This 12-watt unit has a 100-mile range. The typical compact construction makes installation and servicing relatively easy.

A DIMINUTIVE WIRE RECORDER

By
HARVEY SAMPSON
Pres., Harvey Radio Company, Inc.

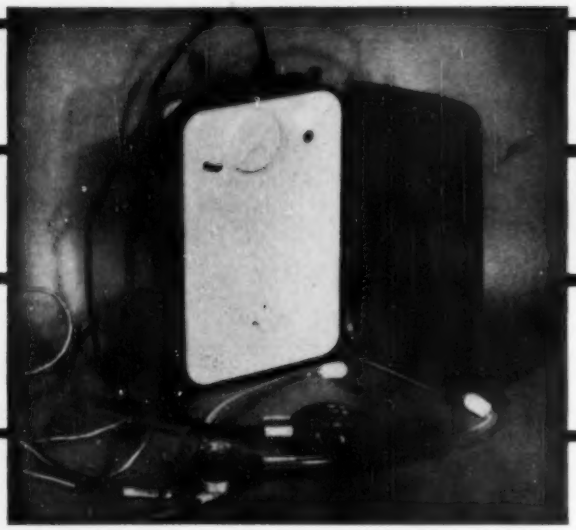

Fig. 1. The "Minifon" measures but 4⅛" x 7" x 2" when contained in its soft leather zipper case. Crystal diaphragm microphone and stethoscope-type earphones come with each recorder.

Technical details on a commercial pocket recorder-reproducer which measures a mere 6⅝ x 4¾ x 1⅜ inches over-all.

EVER since the advent of magnetic recording there has been a steady demand for an ultra-compact device meeting the requirements for a highly portable instrument, entirely self-operated and capable of continuous recording over long periods of time. In the past a few attempts have been made to produce pocket devices but these were not perfected to the point where it was practical to produce them commercially.

The German-made *"Minifon,"* however, does possess almost unlimited possibilities in varied fields of communications, commerce, medicine, and intelligence. Because of its diminutive size, it is ideally suited for street interviews, dictation out in the field, and for gathering realistic sound effects.

The wire used with the *"Minifon"* measures .05 mm or .002" in diameter. The wire speed is approximately 30 cm or 11.8 inches-per-second, which is approximately half the speed employed by the American-made machines. This extremely fine wire is level-wound to slightly more than ¼" on the spool. Up to 2½ hours of material may be recorded on a single *"Minifon"* spool.

Diagram of the German-made "Minifon." Special jacks provide "Rec.-Play" transfer.

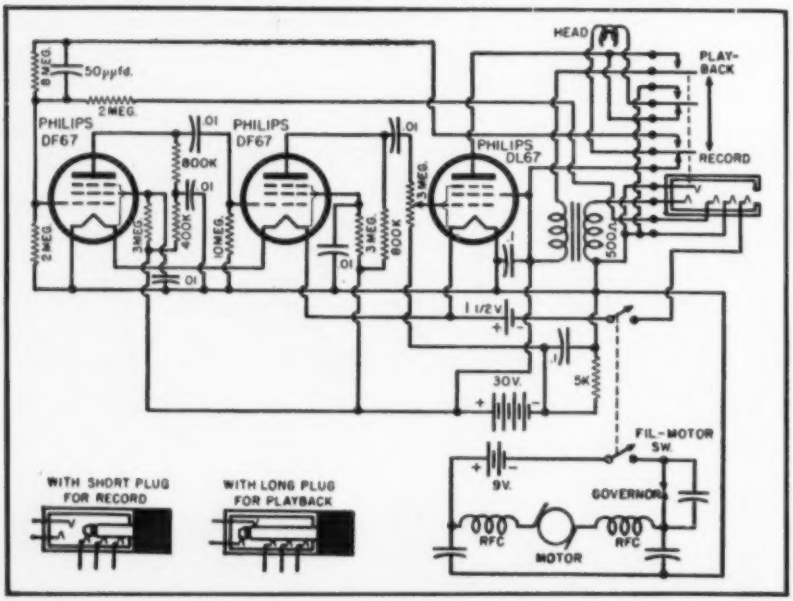

The take-up spool is dynamically balanced so that it may also serve as a flywheel in the forward direction. Because the *"Minifon"* may be operated in any position, a locking hub screw is provided on the supply spool, together with a guide pin to prevent slippage.

The "record-playback" head has the same diameter as a fifty-cent piece. Level-wind is provided by a heart-shaped cam located beneath the sub-assembly. A permanent magnet type erase head pivots to come into direct contact with the wire for erasure. The remaining components include the miniature permanent magnet d.c. motor and its helically-wound spring drive belt. Physically, the motor is about the diameter of an average individual's thumb, with an over-all length of less than 2½" including the shaft and governor.

An ingenious jack switch has been devised for the *"Minifon"* which serves to transfer the amplifier circuits from "record" to "playback" when miniature phone plugs of different length are inserted. A tiny gain control, approximately ¾" in diameter, is located next to the output transformer.

The *"Minifon"* amplifier employs two *Philips* Type DF67 high-gain pentodes and a DL67 output pentode in a conventional resistance-coupled amplifier. These tubes are similar to the *Raytheon* CK series. Fixed bias is applied to the output tube grid through the return leg of the volume control to "B—." A 5000 ohm resistor to the negative ground circuit provides the necessary voltage drop. The single 30 volt hearing-aid type B battery and a 1½ volt penlight cell furnish complete power to the amplifier. Contact bias is used on the DF-67's.

As mentioned previously, there is a unique jack system (which could more properly be referred to as a series

(*Continued on page* 158)

AUDIO EQUALIZATION

By LEON A. WORTMAN

Why do identical audio systems sound different in different locations and why do records vary from disc to disc?

The author has been an audio amplifier design engineer and audio facilities engineer for several broadcast stations, chief engineer of KRUX, chief of the technical data division of Fairchild Recording, and director of advertising and sales promotion of Audio & Video Products Corp. and its three subsidiaries. His articles on audio have appeared in most of the technical publications.

PRIOR to the advent of the modern and low output level cartridges such as the *Audax, G-E, Pickering,* and other reluctance and magnetic types, playback preamplifiers were unnecessary in the home entertainment field and were associated almost exclusively with microphones. These new cartridges made the general public acutely aware of the role of the playback preamp as an important link in the chain of a sound reproduction system. For one thing, it became aware of the necessity for *compensation* in the preamplifier to make up for inherent characteristics of the pickups at certain portions of the audio spectrum. As these new pickups became more readily obtainable, the general public availed itself of them and heard recordings in its own home in a way which gave a new aesthetic excitement to the listener. Thus the audio industry found roots in a new activity, the high-fidelity enthusiast.

Then came new awareness, such as an observation of the vast differences in sound quality among the record labels, even among the top five: *Capitol, Columbia, Decca, Mercury,* and *RCA Victor.* This started a new movement—playback equalization for everybody. The now familiar equalizer-preamplifier was evolved, a thought- and discussion-provoking device, if ever there was one!

All of us have been reading numerous articles and expositions about phonograph record playback systems. However, our fears have been growing as we witness the increasing complexity of the preamplifier-equalizer units being suggested. A lot of the pleasure of turning on a record player and settling back to enjoy the "finest in audio" is being sacrificed to the scientific purist's ideas without regard for the human and psychological elements involved. The trend is toward a handsomely styled *mass* of toggles, rotaries, turnovers, boosts, attenuators, and calibrations. We now anticipate the ultimate in developments, a "calendar" switch which would select, from its 21 x 10^5 positions, the year in which each of the five major companies issued the particular recording the listener would like to manipulate into playback position.

We are becoming aware of two additional phases in audio evolution. *One,* we have been impressed with the fact that the five great labels have different sounds, but, now, we realize that records made by the *same* company differ considerably. *Two,* we discover that what sounds grand in my living room and on my equipment may sound better, or maybe not so good, in yours and *vice versa.*

To consider the first of these two "new phases," the differences among the records in the catalogue of one given company, let's relate it to your own experiences. Do you have a favorite concert hall in which you find a symphony orchestra delightful to hear? Probably, like most of us who enjoy sophisticated pleasure, you also have a favorite section or seat in that hall. Why do we have these favorites? Why do we feel that the New York Philharmonic, for example, sounds better in Carnegie Hall than it might in the equally large Ziegfield Theatre? It's the room acoustics, the characteristics of the hall. And, when we say "characteristics of the hall," as we all do say, aren't we perhaps talking about equalization. Therefore, don't we find that the differences in the sound impinging on our ears in one section of the hall as it varies in moving to another section of the same hall much like the adjusting or tuning of a filter or an equalizer? When we have found the seat which enables us to hear the sound which gives us the effect we seek on concert eve, we have actually manipulated a mechanical tone balance control.

This bears on recording and audio equalization in a pure sense, the sense that equalization, because of the characteristics of the chamber in which the original recording occurs, is automatically introduced at the very moment the original recording is being made! Further, the microphone has its inherent characteristics. The usual lengthy connecting cables and their characteristics may also contribute to this *pre-equalization.* Now, let's depart from this for a moment, but, hold the train of thought as we consider the second related "new phase" of our audio evolution—the differences between sounds in your home and mine.

Assume you and I are using the very same equipment setup, from turntable through to the loudspeaker and its enclosure. Yet the two setups sound different, very noticeably different, even when we use the same records for comparison. We try a simple experiment, moving the baffle to various spots in the living room, seeking the best spot for sound. (We did it in the concert hall, trying to find the best seat for hearing. Why not the reverse in positioning the baffle?) Sure enough, we find a spot that seems best. The sound is more pleasing and requires less treble attenuation, less bass boost. Now, we do the same with my baffle and we find an optimum location in the room. We find, strangely, that, although I can almost duplicate your sound, I must use different bass-treble control settings. What has happened then? The living room's inherent characteristics (not necessarily resonance) have contributed equalization between the loudspeaker and the ear. The living rooms are the only different element in our two electrically alike systems. Isn't this all relative to the symphony orchestra performing in different halls, and obtaining very different sounds?

Now, quickly back to the first "new phase" given some paragraphs ago. The engineer is monitoring and mixing the original sounds being picked up by the microphones and is putting them on magnetic tape for later mastering. Of course, he's using a monitor amplifier and loudspeaker. The amplifier is flat, no electrical equalization. The loudspeaker is an excellent one, enclosed according to the manufacturer's recommendations. *Please be fully aware that,* in accordance with what was heard in the monitor speaker, the microphones were moved about and finally placed to the auditory satisfaction of the conductor, the recording director, and the engineer. Also, different conductors and directors have their own ideas of what is tone "balance." Actually, what was done? The best spot in the hall was found for the microphones, to suit the accepted spot in the unidentifiable monitoring-recording room — with its inherent characteristic, or equalization. And, since each record company does its original

(*Continued on page* 120)

U.H.F. TV TEST EQUIPMENT

By
WALTER H. BUCHSBAUM
Television Consultant
RADIO & TELEVISION NEWS

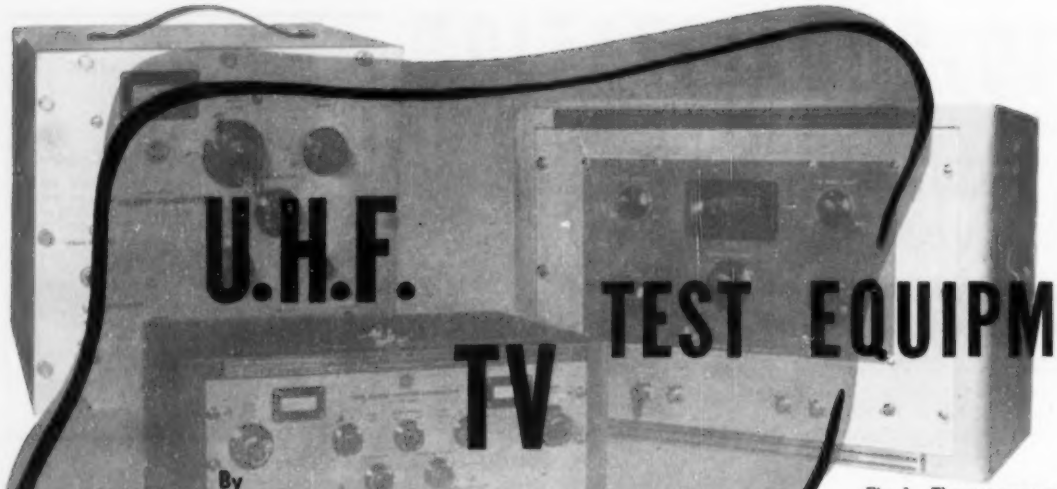

Fig. 1. Three sweep generators for the u.h.f. TV band. Left, the RCA model WR-41A, center, the RCA model WR-40A, and right, the Polytechnic Research and Development Co. type 907.

Survey of available u.h.f. test equipment and timely data on using v.h.f. instruments for servicing u.h.f. tuners.

THE rapid growth of u.h.f. television has removed this topic from the theoretical plane and dropped its problems right into the lap of the service technician. As with v.h.f., correct alignment and troubleshooting without instruments is not feasible and the first step in preparing for u.h.f. is the procurement of suitable test equipment. In some instances service technicians may prefer to send an inoperative u.h.f. tuner back to the manufacturer. However, the long waiting time, shipping charges, and uncertainty of this procedure is a nuisance to the customer as well as the service technician. Eventually, tuners will be out of warranty and require repairs which the technician should be able to do himself. In the long run, u.h.f. test equipment will certainly find its way to every test bench, just as v.h.f. equipment has done.

The purpose of this article is to discuss the types of equipment required, describe currently available items, and those planned for immediate release, and give pointers on utilizing v.h.f. equipment for some u.h.f. chores.

The only portion of the TV receiver where u.h.f. requires new circuits and new equipment is in the tuner. At the present time u.h.f. reception is accomplished either by special u.h.f. strips in the v.h.f. tuner, external u.h.f. converters, or by a combination v.h.f.-u.h.f. tuner. In either system only the u.h.f. portion is different from previous circuits used in v.h.f. sets. The u.h.f. section usually consists of an r.f. network tuned to the u.h.f. channels and a separate oscillator beating with the incoming signal to produce either a v.h.f. signal or else a 40 mc. i.f. signal for the receiver. In some u.h.f. tuners and in all strip-type systems the v.h.f. local oscillator harmonics are used instead of a separate u.h.f. oscillator. The mixer in all instances is a crystal diode, frequently a 1N82 silicon type. From this information we can see that test equipment will be needed to align the u.h.f. r.f.-bandpass networks and to check the u.h.f. oscillator frequency.

EDITOR'S NOTE: Although a method for using v.h.f. test equipment to service u.h.f. circuits is given in this article, rapid and efficient servicing of these circuits will require the use of u.h.f. test equipment. All of the u.h.f. sweep generators available and described herein are laboratory type, and not designed specifically for TV service. However, they may be used for service and in their general circuitry, characteristics, and method of application they are the forerunners of commercial service units.

Types of Equipment

For aligning v.h.f. networks the sweep generator-oscilloscope method, as shown in Fig. 2, has proven most efficient and reliable. It permits visual presentation of the actual frequency response curve of the network under test and the effect of every adjustment is visible at once. Since most r.f. networks in the v.h.f. TV system are designed for about 6 mc. bandwidth, a sweep width of 10 to 15 mc. is sufficient to show both slopes of the response curve. For accurate frequency measurement crystal markers are often used.

Basically, the same type of sweep generator-oscilloscope setup is desirable for u.h.f. alignment. In u.h.f. tuners, however, the r.f. bandwidth is much greater than for v.h.f., ranging from 15 mc. up to 60 mc. for some types of tuners. This means that a suitable sweep generator should have up to 70 mc. sweep width. Another difference from v.h.f. lies in the fact that most present u.h.f. tuners do not use an r.f. amplifier. This means that the output signal of the sweep generator must be sufficiently strong to give a good scope picture even if it is directly connected through a detector. Because standing waves become quite important at u.h.f. it is important that the diode detector be properly loaded which, in turn, means some attenuation and still more loss of signal. These factors all mean that a sensitive scope will be needed as well as a sweep generator with a fairly high signal output. In order to determine actual frequencies a marker signal must be added to the sweep generator. The accuracy of this marker can be less than that required at v.h.f. because the r.f. bandpass is much broader than the 6 mc. required for a single channel and the local u.h.f. oscillator can be tuned accurately on a station signal. The percentage accuracy, however, must still be high because a 1% error, for example, at 500 mc. means a 5 mc. error.

The oscilloscope required may be the same as that used for v.h.f. since the scope, for most adjustments, will be connected to the second detector load resistor as in v.h.f. This will give the bandpass characteristics of the tuner and i.f. circuits for the frequencies in which we are interested. Also, if the signal generator is furnishing the input signal by way of high order

harmonics (as will be explained later) the input signal will probably be very low and amplification will be necessary before a usable signal can be fed to the scope. If it is desired to investigate any of the tuner circuits directly a rectifier probe may be used with the scope, but it should be borne in mind that the input signal must be relatively large to be usable so far forward in the circuit.

So far as other test instruments are concerned, the same v.t.v.m.'s, multimeters, and similar equipment that were found useful on v.h.f. can be used for u.h.f. since after the mixer crystal in the converter the signal is a v.h.f. one and is handled in the regular way as before. Signal generators will be usable if they are capable of generating high enough harmonics of sufficient strength so as to fall into the u.h.f. range for oscillator adjustments, marker signals, etc. The problem of harmonics will be discussed with sweep generators in following paragraphs and is also applicable to signal generators. Most u.h.f. signal generators available are of laboratory or professional type and not specifically designed for service work. Since the sweep generator-oscilloscope method of TV alignment and adjustment has been found to be the most efficient, and since in many instances an r.f. signal output is available from the sweep generator, we will not concern ourselves with signal generators any further in this article.

The problem of u.h.f. test equipment resolves itself, therefore, to the choice of a sweep generator. For u.h.f. alignment the most desirable instrument is undoubtedly a u.h.f. sweep generator, preferably with accurate markers included. At the present time, however, most of the manufacturers of such instruments have not yet brought out such a sweep generator for the service technician. All of them, however, have indicated that they are working on these instruments and hope to produce them sometime in 1953. Until u.h.f. sweep generators, retailing for $200 to $300 become available, the service technician is faced with a difficult choice. There are some good u.h.f. generators on the market, but their prices range from about $600 to $1000 and over. For most average service shops such an investment is hardly warranted, especially if the near future will bring a lower priced instrument on the market. Some service shops, such as those located in active u.h.f. areas, will find the more expensive sweep generator a good investment since it permits them to do better and faster work and it gives them a definite edge over their competition. Before discussing these u.h.f. sweep generators we will present a method of aligning u.h.f. circuits using only v.h.f. equipment.

V.H.F. Gear for U.H.F. Work

The principle which makes it possible to use v.h.f. equipment for u.h.f. networks is a familiar one, namely harmonic generation. The second, third, and fourth harmonics of v.h.f. generators will cover the u.h.f. TV band when used in correct combinations.

The use of a particular v.h.f. sweep generator depends, however, on its upper fundamental frequency limit. This is so because the higher the harmonic used, the smaller will be the signal output available. If your sweep generator has an upper frequency limit of 240 mc. on fundamentals, for example, it will be necessary to use the fourth harmonic to cover Channel 83 (884 to 890 mc.). If your generator, on the other hand, has an upper fundamental frequency limit of about 100 mc. the ninth harmonic will have to be used to sweep Channel 83, with a resultant reduction in the signal available. Exactly how much signal is available depends on the instrument. Of course, the minimum signal that can be used depends on the tuner and receiver sensitivity. Tests with the instrument you now have will quickly tell you whether or not it can be used for u.h.f. alignment and testing.

The method described below applies to any v.h.f. sweep generator with an upper center frequency limit of about 240 mc. Generators which do not go so high may be used for this method utilizing higher harmonics than indicated here.

1. Align the picture and sound i.f. stages and v.h.f. tuner extremely carefully with the v.h.f. sweep generator and marker generator.

2. Connect the vertical scope terminals to the second detector at the video i.f. section.

3. Set the u.h.f. tuner to Channel 14 (470 mc.). If double conversion is used, tune the v.h.f. tuner to the correct channel.

4. Connect the sweep and marker generators to the tuner using maximum sweep output.

5. Tune the generator to 235 mc.

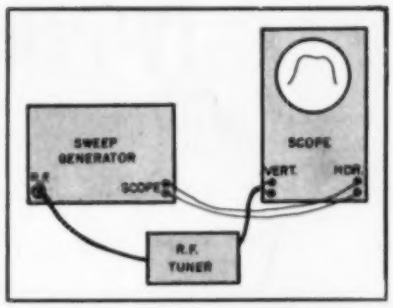

Fig. 2. Test setup for visual alignment.

The second harmonic is now exactly 470 mc. To check actual frequencies, tune the marker generator from 235 to 238 mc. and observe how the marker travels over the entire response curve. The marker signal should appear at the i.f. video carrier point when the second harmonic is 471.25 mc., or the marker dial reads 235.6 mc. Increasing the marker frequency to 237.8 mc. will place the second harmonic marker signal at the u.h.f. sound carrier (475.75 mc.) and on the scope the marker will dip into the sound i.f. carrier spot. If the sweep generator output is reduced and the marker modulated with 400 cps, horizontal bars should appear on the picture tube. Once the frequencies are set, the sweep and marker are adjusted again for a good i.f. response curve on the scope. Then u.h.f. adjustments are made to increase the amplitude of the response curve without affecting its over-all shape.

This process is repeated at each channel in the area. For higher frequency channels third and fourth harmonics must be used. For example, in order to align Channel 23 a signal from 524 to 530 mc. is required. The third harmonic of 174.7 to 176.7 or the fourth harmonic of 131 to 132.5 mc.

(*Continued on page* 138)

Fig. 3. Oscillator assembly of the Polytechnic u.h.f. sweep generator.

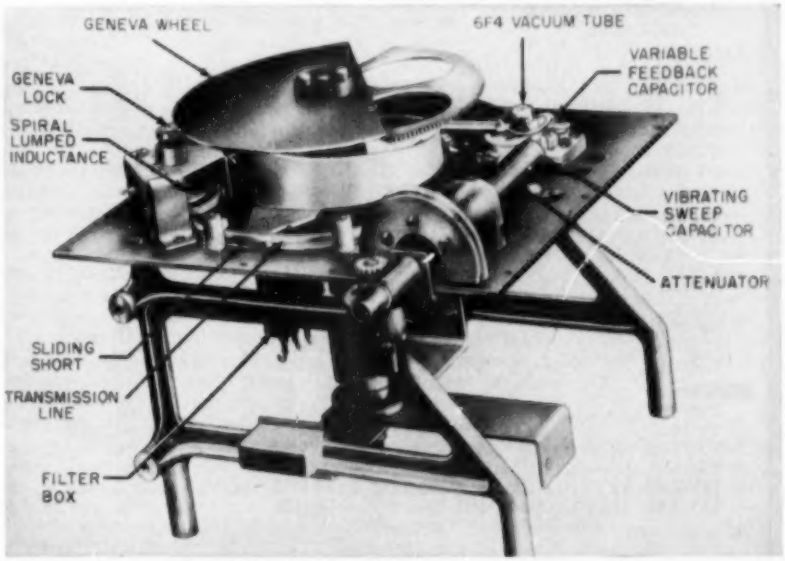

TV PARTS REPLACEMENT GUIDE

Use this guide to order from your parts distributor the correct replacement for a defective TV part. Tables in succeeding issues will cover transformers for other leading TV receiver brands as well as other replacement parts.

TV POWER TRANSFORMERS

RECEIVER MFG. PART NO.	CHICAGO PART NO.	HALLDORSON PART NO.	MERIT PART NO.	STANCOR PART NO.	TRIAD PART NO.	THORDARSON PART NO.
ADMIRAL						
80B1	PH-70	P9205	P-3052	PM8408*	R-8B	
80B7			P-3165	P-8154**	R-33A	T-26R00
80B11	TP-400	P9707	P-3059	P-8154	R-35BC	T-26R00
80B12	TP-210	P9701	P-2952†	P-8155	R-12B	T-26R00
80B13	PV-120†		P-3052†	P-6012	R-12A	
80B15	TP-400	P9707	P-3059	P-8154	R-35BC	T-26R00
80B16	TP-210	P9209	P-2952†	PM8410*	R-12B	T-26R00
80B17	TP-375	P9717	P-3067	P-8160	R-35	T-26R00
80B19	TP-380	P9705	P-3069	P-8171	R-20B†	T-26R23
80B23-1	PH-120	P9207	P-3052	PM8404†	R-12B	
80B24-1		P9735	P-3067*	P-8165	R-35BC	T-26R00
80B32			P-3098		F-25X	
80C26-1	TP-225	P9733	P-3077	P-8164	R-39BC	T-26R00
80C26-2	TP-225	P9733	P-3077	P-8164	R-20B	T-26R00
AIR KING						
M-94157-1, 201T6	TP-365	P9721	P-3061	P-8156†	R-31BC	T-26R00
RC1098		P9725	P-3067	P-8156	R-40BC	T-26R00
A 10109			P-3069	P-8171	R-35BC†	T-26R00
PC 10109				P-8171	R-39BC†	T-26R00
Model A-1016	TP-365	P9721	P-3061	P-8156	R-31BC	
Model 2017R	TP-375	P9717	P-3067*	P-8160	R-35BC	
AIRLINE						
22E27				P-8158		
22E56		P9731	P-3067,3074	P-6165	R-33BC & F52X	T-26R00
52-170	TP-410	P9713	P-3169†	P-8159	R-35A	T-26R00
53X286	PH-120B	P9713	P-2954	P-6014†	R-11B	T-26R04
53X290	PH-70*				R-10B	
53X297	TP-355	P9713	P-3063	P-8159	R-35BC	T-26R00
53X298	TP-355	P9713	P-3078	P-8159	R-38BC	T-26R00
53X302	TP-360	P9713	P-3059		R-37BC	T-26R00
53X308		P9713		P-8159	R-33BC	
53X313	TP-392	P9713	P-3067	P-8159†	R-33BC	T-26R00
53X318	TP-360	P9713	P-3059	P-8169	R-35BC	T-26R00
C12A-18839	TP-360	P9713	P-3059	P-8159	R-35BC	T-26R00
Model 05GCB-3019A, 94GCB-3023		P9731	P-3078	P-8154*†	R-38B	
ANDREA						
ST-3019		P9728	P-3174		R-40A	
ST-3022	PV-200*†	P9318	P-3165*†	PC8413	R-39A	T-26R00
ST-3023	PV-200*†	P9708	P-3169*	PC8413*	R-34A	T-24R94
ST-3033			P-3169†		R-33A	T-26R00
ST-3035			P-3169†		R-50A	
ST-3041	TP-355†	P9711	P-3169	P-8170	R-35A	T-26R00
ARVIN						
Model 4162	TP-356*		P-3078*			
E22571	TP-410	P9713	P-3059	P-8169		
E22807	TP-405	P9711	P-3067‡	P-8156†	R-37BC	T-26R00
E23086						
E23397	TP-225	P9733	P-3077	P-8164	R-39BC	T-26R00
E23837			P-3078		R-39BC†	T-26R00
E23840		F5515			F-18X	
E24654	TP-356*	P9707	P-3078*		R-39BC&F-51X	T-26R00
BENDIX						
TP0Y00			P-3169		R-39BC&F-16X	T-26R00
TP0Y01	TP-392		P-2955,3074		R-33BC	T-26R00
TP0Y02	TP-370†	P9702	P-3070†	P-8160*†	R-42BC	T-26R00
TP0Y03	TP-360	P9303	P-3070		R-35BC	T-26R00
TP0R00	TP-355*†	P9713	P-3070	P-8159	R-42BC	T-26R00
TP0H03	PH-70	P9305	P-2951	PM8407	R-5B	

* ADD SERIES RESISTOR TO REDUCE "B+" VOLTAGE. † DRILL NEW MOUNTING HOLES. ‡ REWIRE FILAMENTS.
** USE UNIVERSAL MOUNTING BRACKETS.

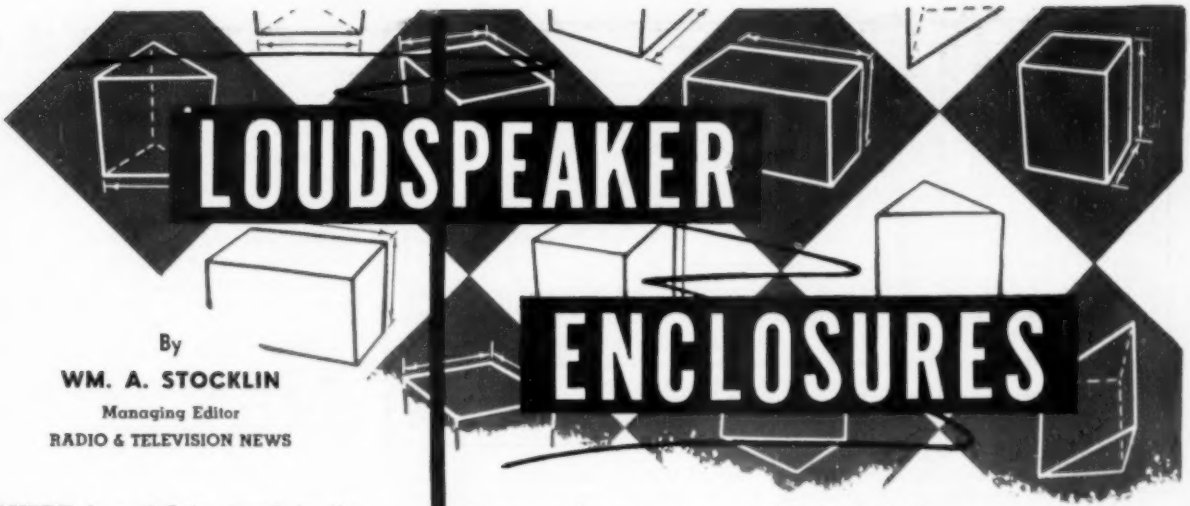

LOUDSPEAKER ENCLOSURES

By

WM. A. STOCKLIN

Managing Editor

RADIO & TELEVISION NEWS

By popular request—a detailed laboratory report on actual—not theoretical—performance of small cabinet "Helmholtz" resonator-type loudspeaker enclosures.

In view of the many requests we have received for performance data on small speaker enclosures, RADIO & TELEVISION NEWS is bringing you an unbiased report on laboratory tests made under our direct supervision. Although only one "Helmholtz" resonator was used in the comparisons, we believe that the results apply equally well to other types. Although the various small speaker enclosures on the market today differ in design, they are, basically, "Helmholtz" resonators.

THERE is a definite trend in the acoustic and audio field to explore the possibilities of the small enclosure for sound reproduction. This is a logical step in the development of the acoustic field, because it follows so closely the miniaturization program of the electronics field as a whole.

It seems to be the trend these days that the electronic field does the pioneer work, and then the audio field jumps on the bandwagon. Perhaps this is a logical sequence of events because, in the last analysis, we cannot have faithful acoustic reproduction unless the electronic signal fed to the loudspeaker is good.

It is not detrimental nor derogatory to the acoustic engineer's point of view to consider miniaturization or even subminiaturization. The fact that in the electronic field we now have amplifiers, transmitters, and receivers small enough to fit into our pockets or even onto our wrists, is really an admirable state of affairs. Great developments are in store for us in miniaturization. However, miniaturization does have its limitations, be it in electronics, or mechanics, or acoustics. Certainly, at the present stage, at least, we cannot expect a pocket-sized transmitter to radiate kilowatts of power. Such a thing today is somewhat unthinkable. Yet, because of this we would hardly say that miniaturization is bad. Nor will we say that miniaturization in the acoustic field is good or bad simply because it is in miniature form.

We have to analyze the situation from the point of view of its application. There are times when miniaturization may be perfectly suitable to an environment, and likewise times when miniaturization is not desirable. What we shall be primarily concerned with in this discussion will be the general form which the miniaturization takes, and then the performance of such miniature systems as compared to what we call the more conventional systems of today. Perhaps at this stage we should stop calling them miniature systems. We termed them such up to now only to highlight certain aspects of development. A box which measures only about from 1 to 1½ cubic feet certainly is small compared to a box which measures 10 or 12 cubic feet and which, up to now, we have been told provided the ultimate in reproduction. So when we hear of an enclosure that is only 1¼ or 1½ cubic feet in volume, it, in a sense, is miniature. We will discuss this problem, not of miniaturization *per se*, but with a view of the *adaptability and the performance* of a small enclosure *versus* a large enclosure.

First, let us say that no matter how good or how bad a system may be, there are always circumstances under which a system may be unusable. Certainly, the dweller in a small apartment which is a combined living room, bedroom, and dining area, all wrapped into one, is limited in the choice of non-essential pieces of equipment he can put into his room.

The word "non-essential" is used in a broad sense, of course. The author knows of a newly-married couple who found that the most necessary piece of furniture for their new 1½ room apartment was a large corner type of enclosure for the gentleman's loudspeaker. Well, it so happens that these people are in the music instruction field and at the same time are audiophiles. They started out married life with a corner cabinet as their first piece of furniture. That is an extreme, for we wouldn't expect to find this in the usual "efficiency" home or to expect it from the usual user of audio equipment. First the consumer must fit his enclosure into his living space or into the area where he intends to use that enclosure. If he has only a couple of cubic feet into which to squeeze an enclosure, then the small enclosure does and will do a good job for him. Parenthetically, we will say at this stage, that this statement does not limit the scope of the small enclosure. We merely take note that in these circumstances the small enclosure does do a good job.

However, there is no question in anyone's mind that if we were to try to fill a reception room 30 x 50 feet in area, that a small enclosure of this sort would not be entirely suitable, and that it might be advantageous to go into large enclosures which could accommodate large speakers or perhaps many speakers of considerable size so that adequate coverage of the area could be obtained with optimum quality. Let us bridge this introduction to the heart of the subject with a simple statement that all enclosures have a usefulness depending upon the circumstances under which they are going to be used.

Baffle Types

It is not commonly realized that no matter what its type, *an enclosure* is a resonant device. Open baffles and horns are anti-resonant devices. To speak of a given type enclosure as a "Helmholtz" resonator does not put it

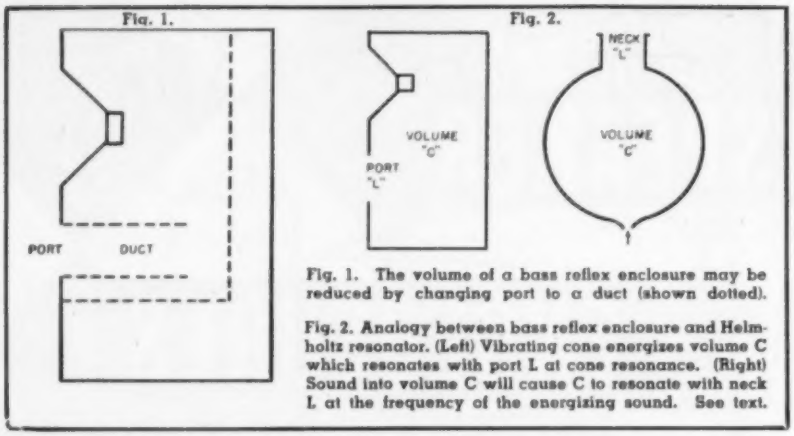

Fig. 1. The volume of a bass reflex enclosure may be reduced by changing port to a duct (shown dotted).

Fig. 2. Analogy between bass reflex enclosure and Helmholtz resonator. (Left) Vibrating cone energizes volume C which resonates with port L at cone resonance. (Right) Sound into volume C will cause C to resonate with neck L at the frequency of the energizing sound. See text.

in a class by itself. The fact is, all reflex baffles are Helmholtz resonators. The formulas for the design calculations of a bass reflex speaker are built around the Helmholtz resonator. Fig. 2 gives a simple analogy of the situation. The back capacitive volume (C) of the cabinet is the capacitive volume (C) in the cavity of the Helmholtz resonator; the inductive area of the vent (L) in the reflex cabinet is equivalent to the inductive area (L) of the neck of a Helmholtz resonator, and the speaker resonance itself energizes the cavity enclosure volume just as the sound directed into the cavity of the Helmholtz resonator energizes the Helmholtz cavity. So we must realize from the start, that to speak of an item as working on the Helmholtz resonator principle does not necessarily remove it from the general class of baffles. If we keep this classification in mind we will have a clearer picture and a better basis of comparison for the type of enclosures to be discussed.

Now, what is the function of an enclosure? Generally, it is to provide loading on the speaker so that its radiation is optimum. We are familiar with speakers mounted in simple flat baffles, open at the back end, a type of baffle from which we have, fortunately, grown away.

The enclosure which quickly followed the use of the flat baffle was the infinite baffle. The infinite baffle is a closed device without any exhaust into the air. This completely isolates the sound field into which the speaker operates from the rear wave of the speaker; and in this manner we obtain a wave front with no cancellation from the rear wave at all. For a while, the infinite baffle was the best type of baffle available for home use. It served as a piece of furniture and, acoustically, it had merit. It did serve to damp out the large self resonance of the speaker considerably. At the same time, however, it had two deleterious effects. The resonance, although somewhat damped out, moved up in frequency and therefore the low frequency response tapered off somewhat, and secondly, the acoustic output of the speaker was considerably reduced because its back wave was completely absorbed within the cabinet.

To make use of this back wave of the speaker, there was developed the reflex type of loudspeaker or, as commonly known by the more technically-minded, the phase inversion type of enclosure.

The phase inverter is simply a box in which the loudspeaker is mounted with the front side of the speaker facing forward and the rear of the speaker facing the inside of the cabinet. In this enclosure the port acts in conjunction with the enclosure volume to take the rear wave from the speaker and to operate on it so that when it comes out of the port of the enclosure it is in-phase with the radiation from the front side of the speaker. This is instantly equivalent to doubling the power output of the speaker at the low frequencies.

One might say "Well, that's as good as having two loudspeakers," and actually on the low frequencies that is exactly the case. If well utilized, the bass reflex speaker does make use of the rear and front wave of the speaker to give an acoustic output near optimum.

This type of reflex enclosure is the simpler version. A more rigorous type of bass reflex speaker is one where the port is actually the end of a duct, which duct leads into the cavity within the cabinet as shown in Fig. 1. Now the use of such a duct, which for some unaccountable reason, has not been employed extensively, tends to reduce the volume of the enclosure tremendously.

It may be shown that an enclosure which has a volume of 5½ cubic feet may be reduced to 3 cubic feet by the use of a duct coupling the enclosure volume to the port. The bass reflex speaker has suddenly shrunk because of its method of port escapement, but it is still a bass reflex speaker, nonetheless—or more properly—a Helmholtz resonator.

Now we come to the anti-resonant baffles, the horn "enclosures" which have mushroomed so rapidly into prominence. A good horn is characterized by *no* resonances. Its transmission characteristics are such that it gives smooth output from its cut-off frequency at the low frequency end to whatever higher frequency the driving speaker will function. This characteristic of anti-resonance is brought about by the fact that a horn

Fig. 3. Six types of enclosures used in making the tests discussed in article. (A) 1¼ cubic foot Helmholtz resonator. (B) 1¼ cubic foot bass reflex. (C) 3 cubic foot bass reflex. (D) 4½ cubic foot horn enclosure with corner not part of horn. (E) 4½ cubic foot horn enclosure where corner is part of horn. (F) 4½ cubic foot bass reflex partly horn-loaded.

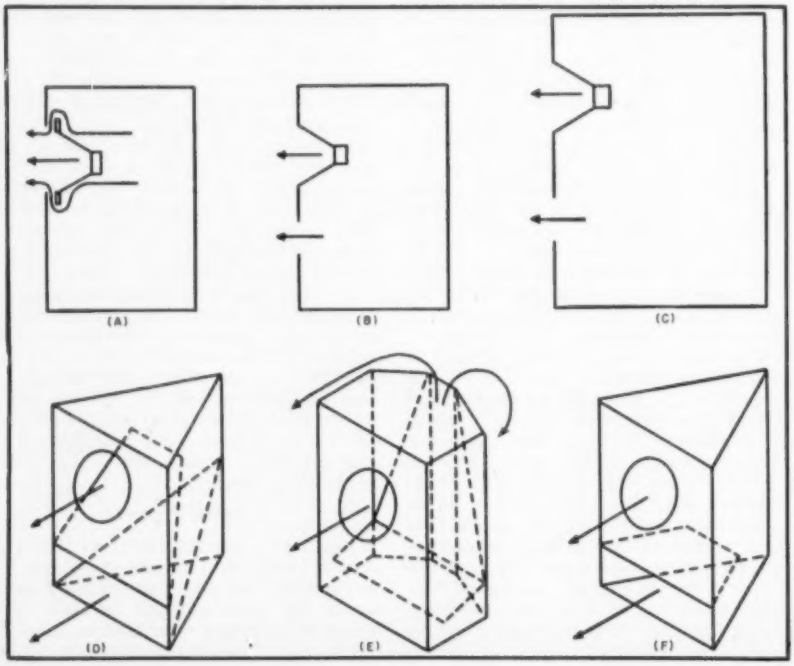

is a pure transmission line terminating at one end in the speaker impedance and at the other end into the characteristic acoustic impedance of open "space." If properly designed, such a transmission line acts as an untuned device, or "anti-resonant." In addition to being anti-resonant in themselves, horns serve to damp out speaker resonances by loading the speaker with an acoustic column of air before its radiation hits free space. An increase in low frequency efficiency is the usual result.

This then, in brief, is a general outline of baffle theory to help us analyze objectively their various properties and peculiarities, be the enclosures small, large, "Helmholtz," "reflex," or "horn."

Measurement Objectives

Now what form shall this objective analysis take? Perhaps the first consideration is the frequency response of the enclosure, especially on the low frequencies. The second consideration would be the cleanliness of the response at these low frequencies.

On this basis, then, it was decided to make just such an objective analysis, employing a single speaker, such as recommended with a given small enclosure of the Helmholtz type and to then compare various other types of enclosures using the same speaker as the driver unit.

It is worthwhile to digress here for a moment to point out that loudspeakers must be matched to the cabinets in which they are to operate. This was stressed in a rather indirect way in the early part of this discussion. It was pointed out that for proper operation of the enclosure, the size of the enclosure and the port vent of the bass reflex had to be properly proportioned to the resonant frequency of the speaker and the diaphragm area of that speaker. We cannot, in general, say that in all instances a speaker or an enclosure will operate better or best in another enclosure, unless we specify the loudspeaker with which that particular enclosure is to work.

There is a wide area of divergence at this point, which we will logically have to avoid on the basis that this is not a discussion of what type of loudspeaker is best suited for a given job, but what type of enclosure is best suited for a specific speaker. On this basis, keep in mind that whatever results are obtained or divulged in this discussion may be radically changed for the better or for the worse if the analysis of one type of enclosure is made with one speaker and the analysis for another type of enclosure is made with a different speaker. On an objective basis, however, merely to classify or categorically compare types of enclosures, it is necessary to stick to one type of loudspeaker. As previously mentioned, the speaker used in this analysis is the one that is recommended for the typical Helmholtz resonator which we are to evaluate against the general field of loudspeaker enclosures comparable in size, and otherwise.

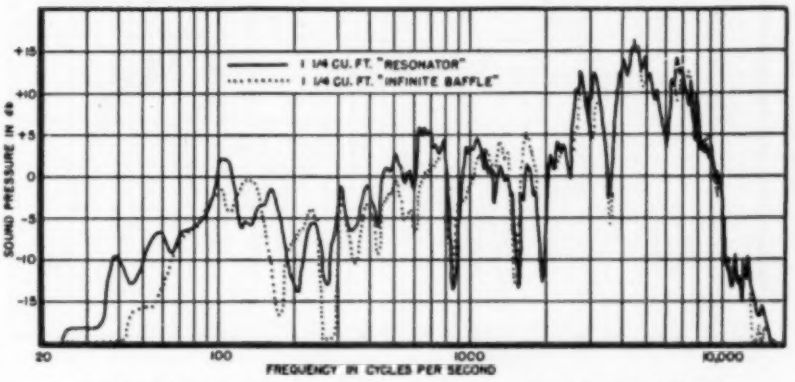

Fig. 4. Relative response of the Helmholtz resonator and an infinite baffle type.

Having thus logically limited ourselves to the one reference speaker, what enclosures are we going to study? Since the reference system consists of a 1¼ cubic foot enclosure of the Helmholtz resonator type, it would be advantageous to make a comparison between this reference enclosure and another enclosure of the same volume, but of the more conventional bass reflex type. This test will thus evaluate the two "basic" types of operation for enclosures of the same size, as shown in Figs. 3A and 3B. We must analyze the effect of increasing the volume of the enclosure by utilizing a bass reflex enclosure of approximately 3 cubic feet (Fig. 3C). Then in the 4½ cubic foot class we shall compare corner type of enclosures, Figs. 3D, 3E, and 3F. Parenthetically, the last three differ in their basic concepts. Fig. 3D represents a horn type of enclosure with front and rear radiation, which utilizes the corner of the room merely to sit in. Fig. 3E represents a horn type enclosure again utilizing front and rear radiation, but where the walls of the room corner form part of the horn system. Finally Fig. 3F represents the more conventional bass reflex enclosure whose port is actually the mouth of a short horn loading the rear cavity.

Now the problem of how to measure the performance of these various enclosures becomes important. If we are going to measure a cabinet such as that shown in Fig. 3E, which requires the corner of a room, are we not penalizing the other cabinets if we do not measure them likewise? The answer is "yes." We would penalize the cabinets if they were not measured in the same corner that the actual corner-employing type of enclosure used. Locating an enclosure in a live acoustical corner of a room tends to reinforce the low frequencies through the reflected mutual impedance of the diaphragm image onto itself from the walls. In any instance, irrespective of the cabinet used, whether it be a corner-employing type or simply a corner-convenience type, we would obtain a different measured effect from a corner of a room than from the midsection of the room. Therefore, in all the measurements to be discussed from here on, we must bear in mind that the speakers were all placed in the same panelled corner. This panelled corner was, in turn, located in an anechoic chamber of considerable size.

Measurement Results

Of immediate interest is the operation of the 1¼ cubic foot Helmholtz resonator type of enclosure as compared with the same volume of enclosure using the same speaker but with no auxiliary acoustic devices built into this alternate enclosure. The alternate enclosure was then simply

Fig. 5. Corresponding impedance curves of systems compared in the graph of Fig. 4.

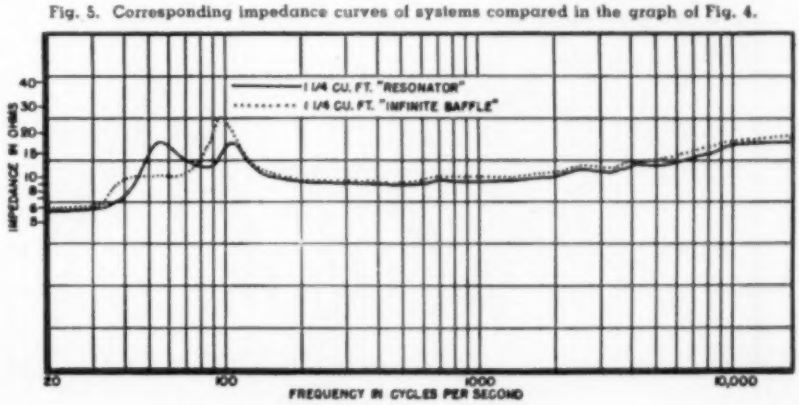

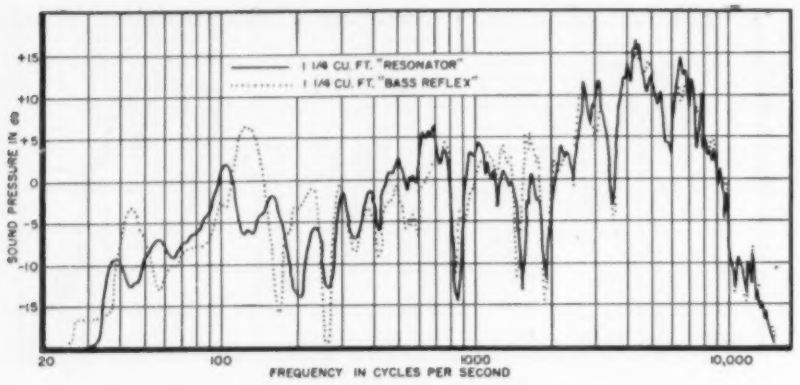

Fig. 6. Relative response of a 1¼ cubic foot resonator and bass reflex of same size.

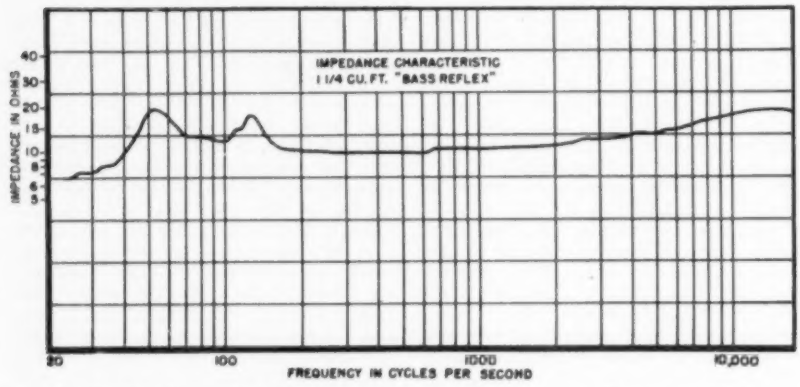

Fig. 7. Impedance characteristic of the 1¼ cubic foot bass reflex type cabinet.

an enclosed box, sealed tight, with the opening for the speaker located in identically the same section of the cabinet as was the case for the Helmholtz resonator. The acoustic performance of these two enclosures is given in Fig. 4, where the full line curve represents the "resonator" and the broken curve represents the alternate similar volume. It will be observed that the "resonator" enclosure has a response which extends into the low frequency by approximately one octave lower than does the uncompensated cabinet of the same size. The corresponding impedance curves of these systems are given in Fig. 5, and it will be noted that where in the Helmholtz resonator type of cabinet there are two equally-spaced impedance peaks, one at 58 cps and the other at 110 cps, that in the uncompensated cabinet there is simply one resonant point at about 100 cycles. This is the evidence we have been looking for concerning cabinet damping. In the Helmholtz resonator there is a nice balance of cabinetry against speaker resonance. Whereas the original free air resonance of the speaker tested was 84 cps, the "resonator" converted the impedance characteristic into two peaks, one at 58 cps and the other at 110 cps. This same speaker when put into the 1¼ cubic foot enclosure without compensation produces a system resonance of 100 cps, which is considerably higher than the free air resonance of the speaker. The general effect of the infinite type of baffle with no acoustic compensation is to tighten up the speaker in a limited frequency range.

Suppose we now convert this alternate 1¼ cubic foot enclosure into a bass reflex enclosure. Applying the necessary phase inversion formulas for the evaluation of cabinet volume, port area, and speaker resonance, we arrive at a port area of approximately seven square inches. Such a port was cut into the enclosure close to the speaker and a second comparison was made. This comparison is shown in Fig. 6. Suddenly things have happened. By simply adding this seven square inches of port to the infinite baffle we have immediately increased the performance of the system over considerable areas of the low frequency end. This type of enclosure now gives more acoustic output than does the Helmholtz resonator between 40 and 50 cycles, an area where, previously, the infinite baffle was completely deficient. From 50 to 150 cps there is an interplay of energy which balances the two systems very closely.

To those interested in the theory of coupled circuits, as it applies to acoustics, the impedance curve of Fig. 7 should prove of value. It will be observed that whereas we had a single peak at 100 cps for the closed volume, we now find two peaks for this same volume converted into a bass reflex unit; one peak at 51 cps and the other at 120 cps. It is a beautiful illustration of the acoustic compensation possible for any type of enclosure if the compensations are properly made. It is worthy of note that whereas the bass reflex enclosure gives more response in these resonant areas with a consequent dip between these two high output areas, the Helmholtz resonator gives lower output in these resonant areas but relatively higher output between these peaked areas.

This is typical of a situation where there are closely coupled circuits. There are high resonant peaks of output with a large trough between them, or closely spaced resonant peaks with a minimum trough between them. We should point out here that volume for volume the bass reflex enclosure and "Helmholtz" enclosure are pretty well balanced. *The former has higher output, in general, in the low frequency area. The latter has smoother response in the low frequency area.*

Now we come to the problem of "How does an increase in cabinet size affect performance?". For this test a three-cubic-foot cabinet was made up without any acoustic compensation, namely an infinite baffle. The results of this comparison are shown in Fig. 8. It will be noticed that the low frequencies are practically identical with those of the 1¼ cu. ft. Helmholtz resonator, with minor variations in the small ups and downs between the two curves. The 3 cu. ft. cabinet gives a nice smooth response as does

Fig. 8. Relative response of 1¼ cu. ft. resonator and a 3 cu. ft. infinite baffle.

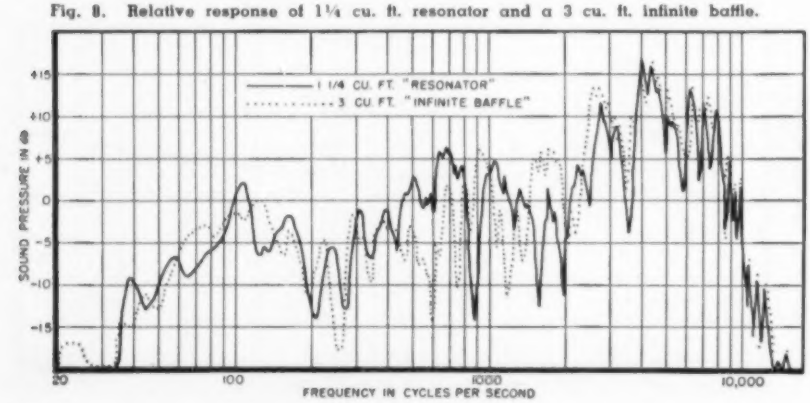

the Helmholtz resonator type of ⅛ its dimensions. We might ask how is it that we get so little output in this three cubic foot baffle? Again this is an infinite type baffle without any port relief or acoustic compensation of any kind and so the prime function of the baffle is simply to subdue the back wave.

If, however, we put a port of 35 square inches in this cabinet, far different results would be obtained, as shown in Fig. 9. It will be seen that the frequency response for the three cubic foot cabinet is now far in excess of what it was without the port. Now there is a world of difference between the original reference enclosure of the Helmholtz resonator type and the three-cubic-foot bass reflex enclosure. It should be reiterated at this point that we are not trying to justify the use of a large cabinet. We are attempting to analyze, study, and digest the characteristics of cabinets. The fact that one shows more output than the other simply means that where there is space available, that space may be used to advantage.

Of final interest from point of view of response is the next set of curves shown in Figs. 10, 11, and 12 in which are compared the Helmholtz resonator and the corner enclosures of 3D, 3E, and 3F respectively. The great improvement in the low frequency response is readily evident. An examination of all these frequency response comparisons, as a function of enclosure volume, leads to the general conclusion that with judicious use of larger volumes, optimum results may be expected from a given speaker. As much as four times the power output is available at the lower frequencies for a given speaker, for a fixed input when checked in an enclosure such as in Fig. 3F, as against the original enclosure with which we started. (The difference of six db on the output curve represents four times in output power.) Now certainly four times the output power is a considerable gain if we can obtain it. Simply because an enclosure is small is no reason for its use when and if a larger enclosure is possible.

Frequency response is not the sole criterion of an acoustic system. The cleanliness of the reproduction is equally important. Now here is a very involved problem. It is not as easy to dispose of this problem as it was of frequency response. How should distortion be measured? There is a school of thought that says we should be interested in the degree of distortion from the systems when these systems are *fed with equal inputs*. Then there is the school of thought that says we are interested in the distortion we get out of the two systems when the systems are *developing equal outputs*. The former method disre-

(*Continued on page* 149)

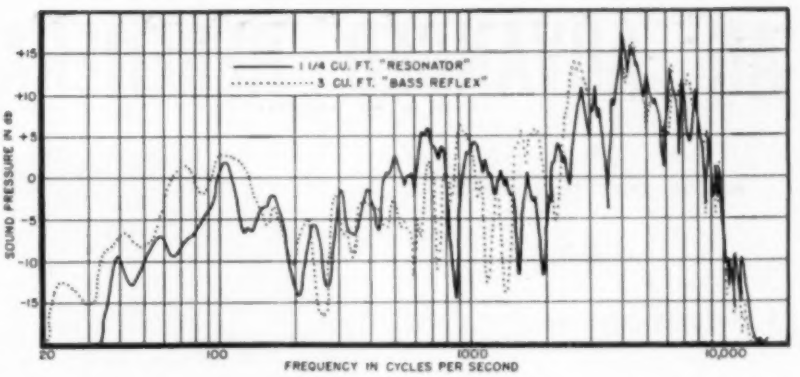

Fig. 9. Relative response of a 1¼ cu. ft. resonator and a 3 cu. ft. bass reflex.

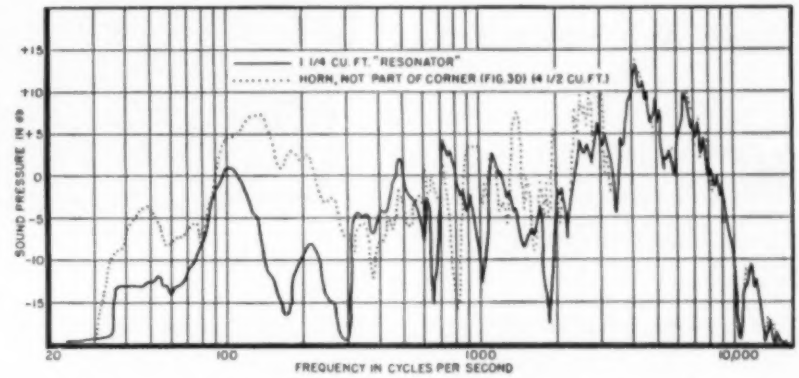

Fig. 10. Relative response of a 1¼ cu. ft. resonator and a 4½ cu. ft. horn which is not part of the corner. See the test set-up shown in (D) of Fig. 3.

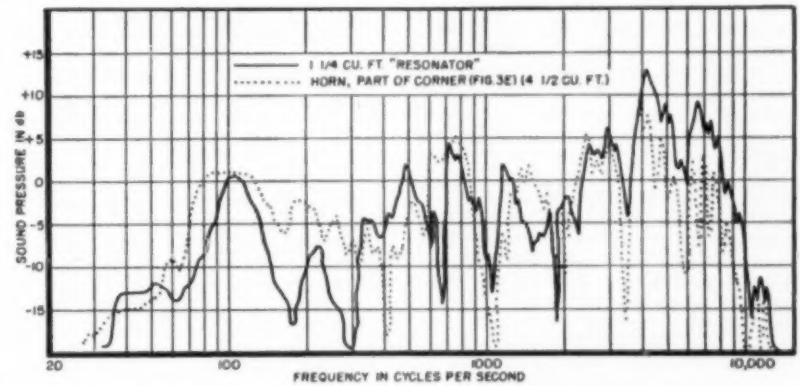

Fig. 11. Relative response of the 1¼ cu. ft. resonator and a 4½ cu. ft. horn which is a part of the corner of the test room. Refer to Fig. 3E for details.

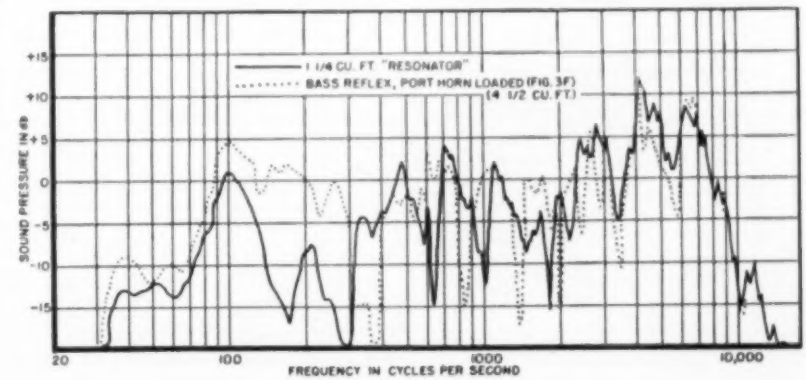

Fig. 12. Relative response of the 1¼ cu. ft. resonator and a 4½ cu. ft. bass reflex with the port horn loaded as illustrated in the diagram of Fig. 3F.

AN ADVANCED REGENERATIVE CIRCUIT

By
IRVING GOTTLIEB, W6HDM

A cathode follower in a novel application overcomes the old defects of a popular circuit.

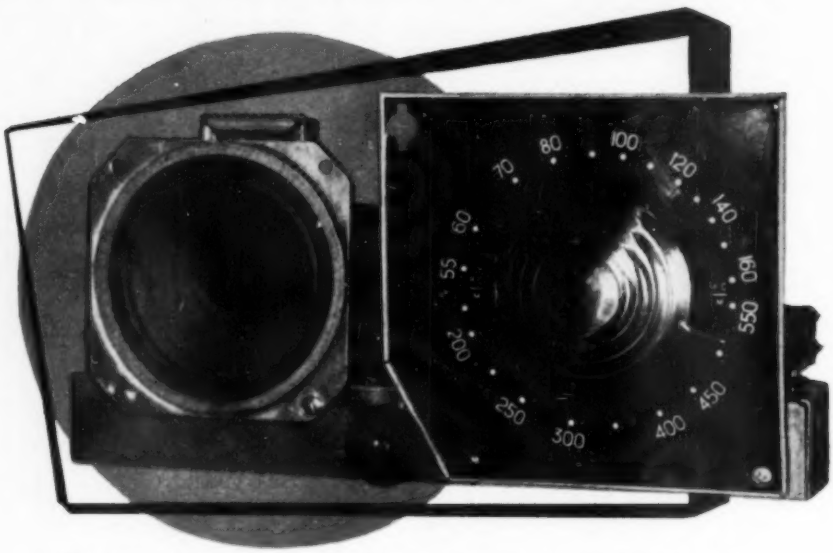

The advanced regenerative receiver is built on a broadcast receiver type chassis.

MANY an amateur or short-wave enthusiast has cut his eyeteeth on the regenerative receiver, thereafter maturing along a course of technical evolution marked by the construction of more complex superheterodynes.

Very little progress has been made since the early days of radio in improving the performance of the regenerative detector. This is surprising considering that the gain afforded by this circuit is sufficient to render audible the thermal noise of the input circuit components. Certainly, any attempt to eliminate the shortcomings which have thus far attended reception with the regenerative detector is a worthwhile effort. It is the intent of this article to describe a modified version of the regenerative receiver which provides a measure of performance not hitherto obtainable with the ordinary regenerative circuit.

One of the drawbacks of the conventional regenerative detector is that much of the inherent sensitivity of this demodulation technique cannot be utilized for phone reception. If the regeneration control is advanced too far, the oscillatory state of the detector will fluctuate with the modulation envelope, thereby destroying the intelligibility of the signal. Closely associated with this defect is the fact that selectivity is poor for phone signals. These, and other undesirable features, such as critical regeneration control and detuning effect of regeneration adjustment can be attributed primarily to one cause. This will be brought out in the ensuing discussion on the operating characteristics of the conventional regenerative detector.

The regenerative detector is, in essence, a reflex circuit, *i.e.*, the tube performs more than one function at a time. Actual demodulation, or "detection," takes place in the grid-cathode circuit. The grid is impressed with both audio and radio frequencies and these are amplified in the plate circuit. The radio frequency component of the signal is fed back to the input of the tube, therein reenforcing the original signal. The audio frequency component is passed on to subsequent audio amplifiers. Now, the demodulation process in the grid circuit involves the flow of current on alternate positive cycles of the radio frequency carrier which exists across the resonant circuit. In other words, the grid-cathode circuit acts as a diode rectifier and constitutes a load to the *LC* tuned circuit. This, of course, degrades the "*Q*" of the tuned circuit and, as a consequence, the amplitude of the signal energy existing across its terminals diminishes. As a corollary to this statement, it is also true that the selectivity of the tuned circuit is decreased by the grid-cathode loading effect. Not only is this effect inherent in such a diode circuit, but the actual amount of resonant-circuit loading will be determined by the strength of the signal.

The strength of a phone signal is continuously varying by virtue of modulation. Therefore, the "*Q*" of the tuned circuit changes at an audio frequency rate. We have now touched upon the basic weakness of the ordinary regenerative detector circuit. The loading of the resonant circuit by a diode detector is bad enough but it is particularly objectionable in the regenerative detector.

Let us examine the reason: the magnitude of the feedback e.m.f. induced in the grid-cathode resonant circuit is, among other things, determined by its "*Q*". However, as we have seen, the "*Q*" of the resonant circuit varies with the amount of loading imposed by the grid. In turn, the grid loading effect increases with the strength of the impressed signal. As a consequence of these relationships, the feedback is not just a constant determined by the setting of the regeneration control. Instead, it varies with the modulation of the signal because modulation constitutes a continuous change in instantaneous signal strength. This causes the detector to become unstable with less regeneration than would be the case if the "*Q*" of the resonant circuit were independent of signal level and grid loading effect. We could, under such circumstances, expect non-critical approach to the threshold of oscil-

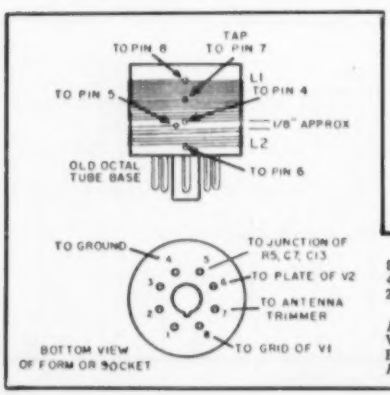

Mechanical details and winding data on coils L_1 and L_2 for the regenerator.

	L_1	L_2	Ant. Tap
80 m.	26 t.	7 t.	C.T.
40 m.	14 t.	5 t.	C.T.
20 m.	6 t.	3 t.	3rd t. from gnd. end

All coils closewound on octal base forms. Windings are of 5/40 Litz wire or #26 en. or Formvar. Approx. spacing of L_1 and L_2, 1/8". Adjust for optimum performance.

lation by the regeneration control. The receiver would operate with more positive feedback and, paradoxically in terms of the ordinary regenerative detector, with greater stability. Selectivity would also be better, inasmuch as positive feedback supplies the dissipative losses of a resonant circuit, thereby increasing the effective "*Q*".

Another improvement which could be anticipated from the foregoing discussion, if we could successfully isolate the resonant circuit from the grid loading effect, involves the elimination of the detuning influence of the regeneration control. This is so by virtue of the fact that the resonant frequency of an *LC* circuit is affected by resistance as well as inductance and capacitance, although to a lesser degree. Since the loading imposed by the flow of grid current is equivalent to that of a resistance which varies with signal strength, the conventional regenerative detector is bound to suffer in some degree from this undesirable feature.

The Solution

Now that the somewhat obscure and elusive shortcomings of the regenerative detector have been in large measure attributed to tuned circuit loading, the solution to the problem obviously entails the isolation of the resonant circuit from the current demands of the grid. This was accomplished by the author by the insertion of a cathode follower between the resonant circuit and the detector grid-cathode circuit. The feedback coil was then coupled to the input of the cathode follower rather than to the detector itself. The manner in which this is done is depicted in the schematic diagram. Control of regeneration is obtained by varying the plate voltage of the cathode follower. The smoothness of this control would, in itself, justify the circuit.

Since the resonant circuit is not loaded, it is well to wind the coils to display a high "*Q*". This results in the receiver showing good selectivity for strong phone signals when little regeneration is used. Therefore, it is advisable to use Litz wire in the construction of the coils. Any expedient which decreases the losses of the resonant circuit will pay much better dividends in this circuit than in conventional regenerative receivers.

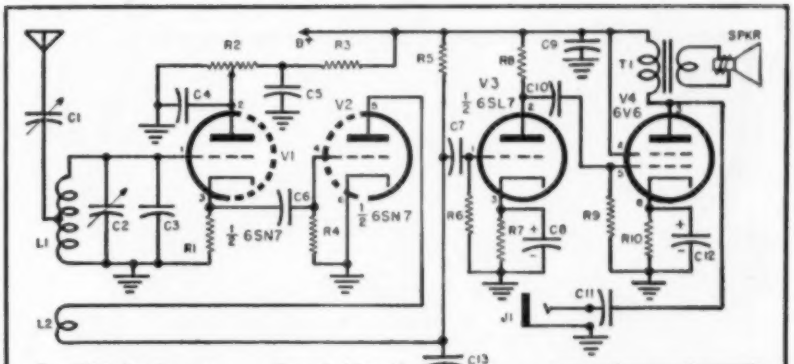

R_1—4700 ohm, 1 w. res.
R_2—200,000 ohm pot.
R_3—150,000 ohm, 1 w. res.
R_4—1.5 megohm, 1 w. res.
R_5, R_6—470,000 ohm, 1 w. res.
R_7—1000 ohm, 1 w. res.
R_8—220,000 ohm, 1 w. res.
R_9—330,000 ohm, 1 w. res.
R_{10}—620 ohm, 1 w. res.
C_1—35 μμfd. ceramic or air trimmer
C_2—170 μμfd. section of dual b.c. cond. or 140 μμfd. midget cond.
C_3—22 μμfd. ceramic or mica cond.
C_4—.1 μfd., 600 v. cond.
C_5—.5 μfd., 600 v. cond. (paper or "bathtub")
C_6—250 μμfd. ceramic or mica cond.

Ground either side of the 6.3 volt filament winding.

C_7, C_{10}, C_{11}—.01 μfd., 600 v. cond.
C_8, C_{12}—4-20 μfd., 50 v. elec. cond. (Observe polarity)
C_9—8 μfd., 450 v. elec. cond. (Observe polarity)
C_{13}—100 μμfd. ceramic or mica cond.
L_1, L_2—See coil table
T_1—Output trans. 3000 ohms to 4 ohm v.c.
Spkr.—3" PM speaker with 4 ohm v.c.
V_1, V_2—½ 6SN7 tube
V_3—½ 6SL7 tube
V_4—6V6 tube
B+—approx. 200 v. d.c., well filtered

Circuit diagram and parts list of the cathode-follower regenerative receiver.

The constructor should experiment with the spacing of the feedback coils in order to achieve optimum results. This adjustment is much easier than in the ordinary regenerative set. Superregeneration and fringe howl can result only from a gross departure from the specified parameters. Tighter antenna coupling and, likewise, closer coupling between the feedback coil and the resonant circuit are permissible in this system. In the conventional regenerative detector circuit, there is coupling from grid to plate as well as in the reverse direction. This only serves to make the threshold adjustment of the regeneration control more critical. In our modified receiver, the cathode follower stage makes the feedback path unidirectional, i.e., energy can be returned from output to input of the detector tube, but not in the reverse direction.

The builder will find that the combination of feedback coil spacing and antenna coupling which allows the threshold of regeneration to occur approximately between the first 20 and 60 degrees of rotation of R_2 will provide good results.

The fixed condenser, C_5, is included in order to make the "*Q*" of the resonant circuit more uniform over the tuning range. This helps to reduce the effect of tuning on the setting of the regeneration control. This effect is negligible over a frequency spectrum as wide as that used by the amateur bands. As a result, once the regeneration control is set, the set has the "feel" of a superhet when it is tuned.

Although many signals will be heard with a short piece of wire strung up around the room, it is highly desirable that a reasonably good outdoor antenna be used. This receiver definitely overcomes several of the shortcomings of the ordinary regenerative set. In common with small receivers however, the antenna system plays a major role in governing the quality of performance.

The receiver was constructed around a broadcast radio chassis. The 170 μμfd. section of the original dual variable condenser was used for tun-

(*Continued on page 98*)

Under-chassis view. Good use is made of the sockets and holes of the original broadcast receiver. Wiring is rather simple.

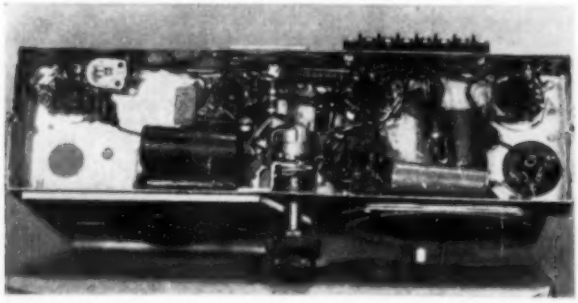

Rear view. The tuning condenser, dial, and speaker are from the old broadcast set, but new parts and chassis may be used.

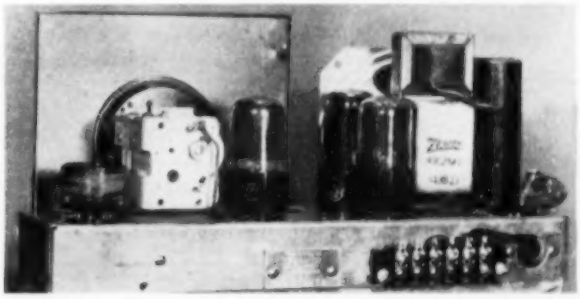

A TRANSISTOR SINE-WAVE CLIPPER

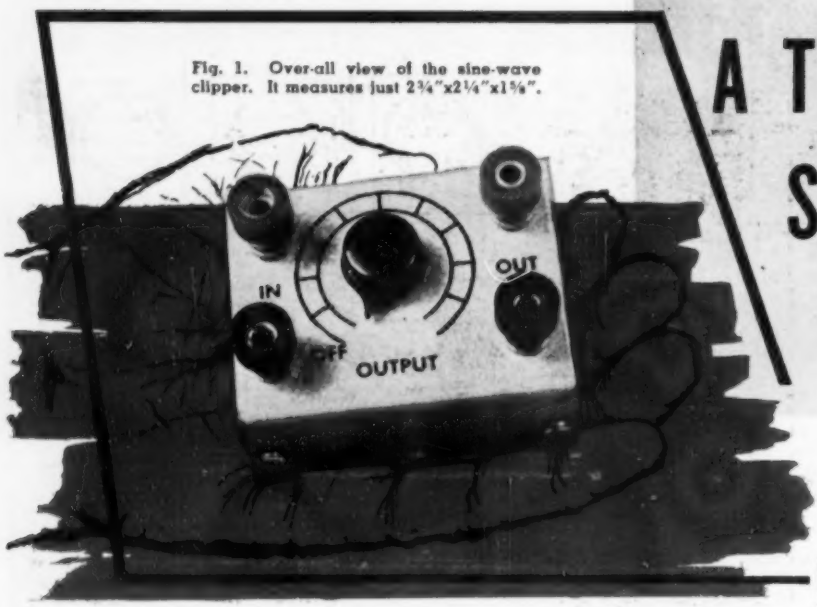

Fig. 1. Over-all view of the sine-wave clipper. It measures just 2¾"x2¼"x1⅝".

By
LOUIS E. GARNER, JR.

This useful test accessory can be used alone or built into an existing audio oscillator. It is compact and reliable.

THE instrument shown in Fig. 1, although small enough to be held comfortably in the palm of the hand, is, nonetheless, capable of producing good quality rectangular waves when driven by a sine-wave signal of moderate amplitude. A further feature of the instrument is that the level of the output signal can be easily controlled, *from zero to an amplitude several times greater than the input signal.* The instrument is completely self-contained! No external power source or batteries are required for its operation.

These features have been made possible in the compact instrument shown by utilizing the new *Raytheon* CK722 junction ("*p-n-p*") transistor in a clipper circuit requiring a minimum of additional components. This is apparent from the interior view, Fig. 5, and from the schematic diagram, Fig. 2.

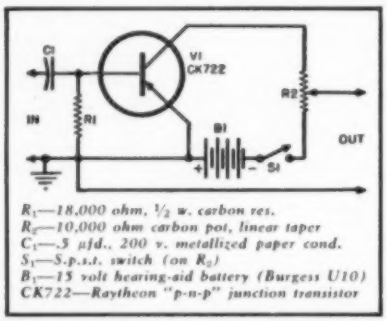

R_1—18,000 ohm, ½ w. carbon res.
R_2—10,000 ohm carbon pot, linear taper
C_1—.5 µfd., 200 v. metallized paper cond.
S_1—S.p.s.t. switch (on R_2)
B_1—15 volt hearing-aid battery (Burgess U10)
CK722—Raytheon "p-n-p" junction transistor

Fig. 2. Complete schematic of the sine-wave clipper. CK722 "p-n-p" transistors are used.

Circuit Description

Referring to the schematic diagram of Fig. 2, the CK722 transistor has been connected in a conventional grounded emitter amplifier circuit, *but without "bias" voltage between the base and emitter.* C_1 serves as the input d.c. blocking condenser, R_1 as the input resistor, R_2 as the load resistor, and battery B_1 as the power source.

When a transistor amplifier is operated without "bias," and a sine wave is applied to its input, the output consists of a series of fairly narrow rounded pulses. This effect has been noted previously (see "The Transistor in Simple Circuits" by W. H. Minor. December, 1952, *Radio-Electronic Engineering* Edition of RADIO & TELEVISION NEWS). The appearance of the output signal when a 10 kc. sine-wave signal of low amplitude is applied to the input of the circuit is shown in Fig. 4D.

As the amplitude of the input signal is increased, the top of the pulse is clipped, and a rectangular waveform is obtained, as shown in Figs. 4A, B, and C. The frequency of the sine-wave signals used to obtain these patterns are, respectively, 45 cps, 5 kc., and 25 kc.

Peak clipping occurs because the peak collector current reaches the maximum possible with the load resistor and voltage source used and, therefore, no further increase in current flow is possible. This was demonstrated in the circuit shown by measuring the peak-to-peak signal across load resistor R_2. The measured value was approximately 15 volts, or equal to the supply voltage.

With the circuit shown, clipping occurs when the input signal is between three and five volts. A good output waveform is obtained over the entire audio range from 30 cps to 30 kc. as long as the input signal level is maintained. In addition, the output waveform remains of constant amplitude regardless of minor variations in input as long as sufficient signal is supplied to maintain the clipping action.

The output waveform is also relatively unaffected by the setting of the output control, R_2, except as far as amplitude is concerned, due to the low value of this potentiometer. An output "blocking condenser" has not been included in the model.

In order to prevent even a minute current flow when the unit is not in use, a switch has been provided in the collector circuit (S_1) and is mounted on control R_2. When in use, the current drain averages only a fraction of a milliampere (the *peak* is about 1.5 ma. drain) and, therefore, the battery life

Fig. 3. Basic instrument set-up for making gain measurements with test unit.

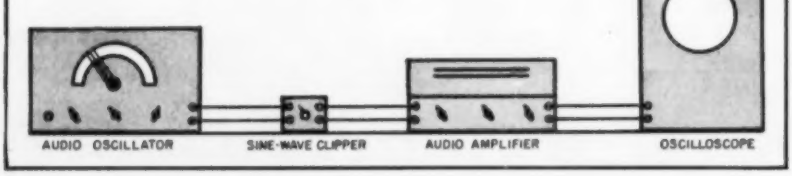

should approach the normal "shelf life."

Construction Hints

The entire circuit is easily assembled in the smallest of the *Bud* "Miniboxes" (CU-3000, 2¾"x2¼"x1⅝") if reasonable care is taken and the components specified in the parts list are used. The use of a *metallized* tubular paper condenser in the input is particularly important as it is virtually impossible to fit a conventional paper condenser of large capacity (.5 μfd.) into a box of this size and still have room for the remaining components.

Leads should be kept reasonably short and direct to avoid stray capacities to ground with resulting deterioration of the output waveform. This should not prove too difficult as short leads are almost naturally used in a circuit wired as compactly as is shown in the photographs (Figs. 1 and 5).

The arrangement of parts used by the author is apparent from the illustrations, but the reader need not follow this layout exactly. As long as excessively long leads are avoided, the layout is non-critical.

For best results, it is essential that a *carbon* potentiometer be used for R_2, although a linear taper is not absolutely necessary. If a wirewound pot is used, however, deterioration of the signal waveform at high frequencies (due to residual inductance) is likely.

In the model shown, connections to the battery have been made by soldering leads directly to the battery terminals and wrapping with *Scotch* electrical tape to prevent accidental shorts. The battery is held in place by a simple bracket found in a commercial "hardware assortment."

The "panel" of the instrument has been labeled by using standard black decals and then spraying with clear plastic to provide additional protection.

The transistor has been wired directly into the circuit by its tinned leads. Although there are special sockets available for the CK722, the author feels that their use would only be justified in equipment designed for continuous 24-hour-per-day operation, due to the inherent long life of transistors.

Circuit Modification

The 15 volt hearing aid battery, B_1, may be replaced by batteries of lower voltage without affecting signal waveform or the action of the circuit—the only difference will be in the amplitude of the output signal. The lower the supply voltage, the lower the maximum output signal. Voltages as low as 3 volts have been tried experimentally without deterioration of output waveform quality.

If a fixed output signal level is preferred to an adjustable output, R_2 may be a fixed carbon resistor, the ½ watt size is satisfactory for use here.

An output d.c. blocking condenser, similar to C_1, but connected between the circuit output and the output terminal or binding post, may be used if desired, and will make it unnecessary to check for a blocking condenser in the circuit to which the clipper is connected for test purposes (or to use an external blocking condenser).

The switch on the output control may be replaced by any suitable s.p.s.t. switch—a toggle, lever, rotary, or slide switch may be used.

If both input and output blocking condensers are used, and a battery of larger size than the one given in the parts list used, it may be necessary to assemble the unit in a larger container. The next largest size *Bud* "Minibox" should be suitable unless regular paper condensers and an extremely large battery are employed.

Where preferred, the circuit may be assembled as part of an existing audio oscillator rather than as a separate accessory. If this alternative is adopted, a switch should be provided so that a choice of either "Sine" or "Rectangular" waves may be made by the operator, or separate output terminals should be provided so that both sine and rectangular waves are available on the front panel simultaneously.

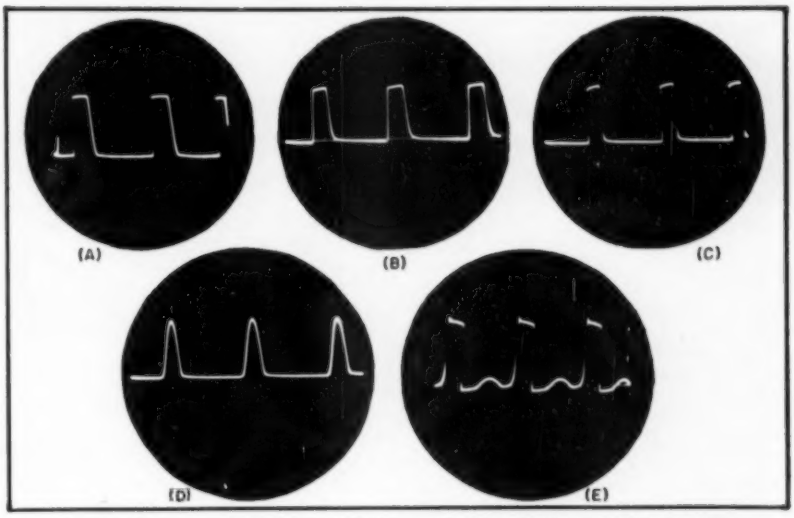

Fig. 4. Waveforms from clipper. (A) 45 cps. (B) 5 kc. (C) 25 kc. (D) Output when 10 kc. sine-wave signal of low amplitude is applied. (E) Overdriven unit.

Fig. 5. Internal view of clipper. All hookup leads should be kept as short as possible.

Operation: Once the wiring is completed, the builder should become familiar with the basic operation of the clipper before attempting to use it in practical test and experimental work. The best way to do this is to connect the output terminals of the clipper to the "Vertical Input" terminals of an oscilloscope. An audio sine-

(*Continued on page* 163)

Fig. 6. Sine-wave clipper used in conjunction with audio generator and scope. See text.

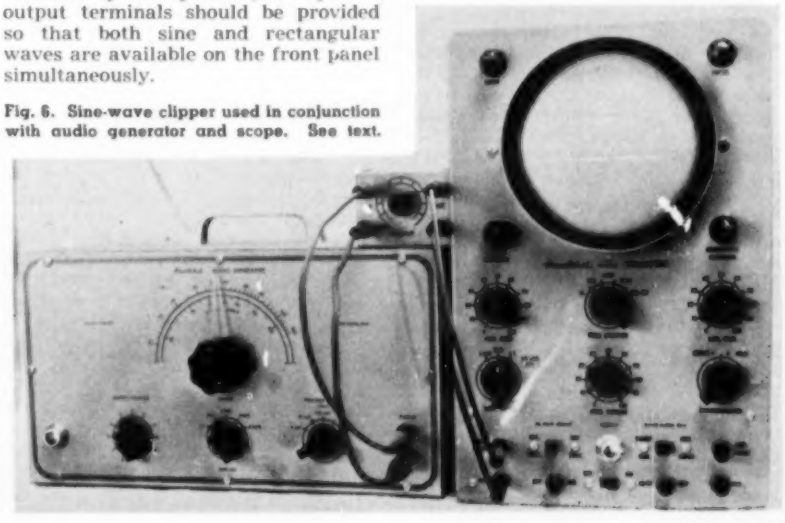

FOR FRINGE AREAS

By
JESSE DINES

Special circuits used in a popular fringe area receiver may be duplicated for better picture and sync stability.

THE art of television design has reached the stage where any standard receiver on the market today can be expected to do a creditable job under normal conditions. New competitive designs must make their appeal to the public by offering something extra. With the national growth of television consciousness this medium has ceased to be a strange metropolitan phenomenon. The frontiers are rolling back beyond the fringe. This is the direction in which new design is moving.

Many manufacturers found that the highly regarded *RCA*-designed 630 circuit was an excellent starting point for a super-powered fringe area receiver. To this circuit they have added many improvements based upon the advances in receiver circuitry since the 630 was introduced. To understand what improvements were required, it would be advisable first to consider to what troubles fringe area receivers are subject.

The fringe area generally produces four major receiver complaints:

1. Weak picture, characterized by inability to obtain good contrast and the presence of snow.
2. Weak or garbled sound.
3. Poor sync control resulting in tearing and/or rolling.
4. Excessive susceptibility to interference caused by poor rejection and a relatively low signal-to-noise ratio.

The remainder of this article will discuss some circuits that may be used to reduce these complaints and provide good reception. These circuits have been used successfully by the *Airex Radio Corporation* in their fringe-area TV receiver model 630FA.

Front End: The most important thing to do to improve a fringe area receiver is to increase its signal-to-noise ratio; or, in other words, to provide the receiver with more *usable* gain. In this way, clearer picture and sound, as well as increased sync stability due to the relatively larger sync voltages result. To increase the gain the 630FA and most fringe area receivers use the latest type cascode tuner with a 6BK7 as the r.f. amplifier and a 6J6 as the oscillator-mixer. The 6BK7 is a miniature twin triode with an internal shield giving the high gain of a pentode and the low noise of a triode. There is a marked improvement in signal-to-noise ratio. There is also less local oscillator radiation and, consequently, less interference to other sets.

Sync Amplifiers: As mentioned previously, receiver susceptibility to interference increases in a fringe area. Because of this, spurious signals, such as bursts of noise, tend to upset the sync system by triggering the vertical and horizontal oscillators. The result is picture tearing and/or rolling. To combat this, the 630FA uses a circuit consisting of two 6J5 sync clippers in parallel, as shown in Fig. 1A. The sync take-off point at the plate of the 1st video amplifier simultaneously feeds both clipper grids by means of direct coupling. The high-frequency sync clipper incorporates a cathode network (R_1-C_1) with a relatively short time constant; the low-frequency sync clipper employs a cathode network (R_2-C_2) with a relatively long time constant. The grids are normally from 6 to 8 volts negative with respect to the cathodes. The circuit operates in the following manner:

Suppose high-frequency transients, such as bursts of noise, attempt to enter the sync amplifier circuit. The relatively short time constant of the high-frequency clipper causes them to be grounded through C_1. This effectively puts the cathode at ground potential and degeneration is removed from the high-frequency clipper. This, in turn, causes the stage to amplify to a much greater extent (since the grid is directly coupled its voltage will be highly positive), an increased clipping action results, and the high-frequency transients are prevented from entering the 2nd sync amplifier stage. By the same token, low-frequency transients are prevented from entering the sync system by removing degeneration from the low-frequency clipper.

Vertical Circuit: When the brightness control is advanced in fringe area receivers, or when the picture tube has aged, the blanking effect of the relatively weak sync pulses is overcome, and annoying white streaks appear in the picture. The reason is that most receivers use a simple arrangement to extinguish the electron beam of the picture tube during vertical retrace time; more specifically, the sync pulses, fed to the picture tube along with the rest of the video signal, are used for this purpose. The circuit employed in the 630FA for improved blanking is shown in Fig. 1B. Here the peaked portion of the greatly amplified vertical-output pulse is used as the principal blanking pulse. It goes from the secondary of the vertical output transformer, through R_2 and C_1, to the picture tube cathode. The *RC* combination reshapes the pulse for optimum use. Note the change in waveforms before and after the *RC* network.

Horizontal Sync Circuit: When a set ages, there is an increasing tendency for horizontal jitter or tearing to mar the top of the picture. The usual cause is an increasing susceptibility to change in cathode voltage on the horizontal sync discriminator due to transients. This effect is even more noticeable when the set is in a fringe area. To minimize the effect of a reduction in the 2-volt bias, a 1N34 germanium crystal is used as a negative clamper diode as shown in Fig. 1C. With its associated network, R_1-C_1, it provides excellent regulation of the desired negative voltage by eliminating transients quickly while maintaining a fixed voltage across the discriminator load resistors.

Video I.F. Strip: In fringe areas, it is always necessary to get as much audio and video gain as possible. Four 6CB6's are used for the i.f. amplifiers which give greater amplification. The cumulative effect over the entire strip is a substantial increase in gain. As in the standard 630, the split-sound design is used, but greater audio gain is obtained by advancing the audio i.f. take-off point an extra stage. Instead of coming directly from the tuner, the sound i.f. is taken from a sound trap at the output of the 1st video i.f.

The intermediate-frequency band on which the set operates has also been shifted somewhat from that used in the old 630. The new band of i.f. operation places the sound carrier at 21.9 mc. instead of 21.25 mc. Keeping in mind the susceptibility of fringe-area receivers to interference, this minimizes self-generated interference

on the picture or sound of certain channels. It also lifts the receiver out of danger as far as the new 15-meter amateur band is concerned.

Contrast Control: In many receivers the contrast control is a bias-level adjustment applied to the video i.f. stages. Its manipulation, of course, varies the amplitude of the entire composite video signal, including the sync pulse portion. Since sync circuit take-off is accomplished later on in the video amplifier, sync sensitivity is directly affected by contrast adjustments. Switching from one channel to another or reduction of contrast often tends to unsync the receiver. This becomes increasingly annoying in fringe areas where the sync level is very low. The contrast control in the 630FA appears as a single-stage adjustment in the cathode of the 2nd video amplifier (see Fig. 2). Sync pulse amplitude at the take-off point, the 1st video amplifier, is unaffected.

Width Control: A frequently recurring and constantly irritating servicing problem is that of obtaining adequate control over width. A weak driving signal to the horizontal output stage grid in fringe areas, as well as accumulated differences in the values of components, within tolerance on an individual basis, will often affect circuit operation to a great extent. The width control frequently lacks sufficient range to make up for these differences, even in new sets. The problem becomes particularly painful as sets age. As shown in Fig. 3A, the width coil, normally a winding of relatively high impedance shunted across a portion of the high-voltage transformer secondary, is a low-impedance winding placed directly in series with the horizontal winding of the deflection yoke. In this manner, its ability to affect sweep voltage fed to the yoke is greatly increased. In fact, the variation in width thus obtained is one-third the total horizontal sweep. The 600-ohm resistor shunted across half the width coil serves to damp out any ringing that may develop.

Audio Circuit: Increased audio gain is obtained through the use of a 12AX7 dual triode as the 1st audio amplifier and phase inverter. The push-pull output stage uses a pair of 6AQ5's. Maximum output is thus increased from the usual 3 watts to about 8. Push-pull operation also furnishes reduced distortion.

A.G.C. Circuit: Automatic gain control presents a major problem in fringe areas. Most of the time manufacturers will recommend removing a.g.c. altogether in these areas. This is done to keep the input signal level as high as possible where picture or sound fading is sacrificed for gain.

This receiver uses an a.g.c. circuit which is adaptable for both strong and weak signal areas as shown in Fig. 3B. The circuit features the usual a.g.c. secondary winding on the flyback transformer, which connects the output of the a.g.c. keying tube (6AU6) to the a.g.c. line. As ordinarily driven, this tube tends to develop heater-to-cathode shorting, resulting in loss of picture. This occurs when potentials in excess of 100 volts are applied to the cathode. In the circuit of Fig. 3B a 45-volt drop across R_1 keeps the cathode voltage down to 90 volts, reducing the possibility of failure in this stage.

Also, an externally adjustable threshold control, R_2, is inserted between the a.g.c. line and ground. The proper amount of a.g.c. action may thus be chosen for any particular installation. For fringe-area operation, a.g.c. action may be completely eliminated by rotation to one extreme of the control; at the other extreme, full operation may be obtained to prevent signal overload in strong-signal areas. The advantage for areas where signal strength varies greatly is obvious: the threshold control may be reset from channel to channel.

For prolonged, trouble-free operation, all parts used in the fringe area receiver should be of superior quality, high rating, and close tolerance. Molded plastic condensers, for example, should be used throughout in preference to paper tubulars. They are less subject to breakdown or to change in value with changes in temperature or humidity.

The integrator network used in this chassis is a printed circuit, installed and replaced as a unit. It has proven to be more compact, easier to service, and less subject to breakdown than separate-component circuits.

An interesting feature of the 630FA is the provision for prolonging tube life. A time-delay relay tube is used in series with the output from the low-voltage rectifier. The tube consists of a heater and two heat-sensitive switch contacts. When the tube is cold the contacts are open. As the heater, which is connected in parallel with the other tube heaters of the chassis, warms up the two contacts, they expand and close, completing the low-voltage power supply circuit. By the time this has happened all tube heaters are warm. This results in efficient, long-life operation of the tubes, including the CRT. —30—

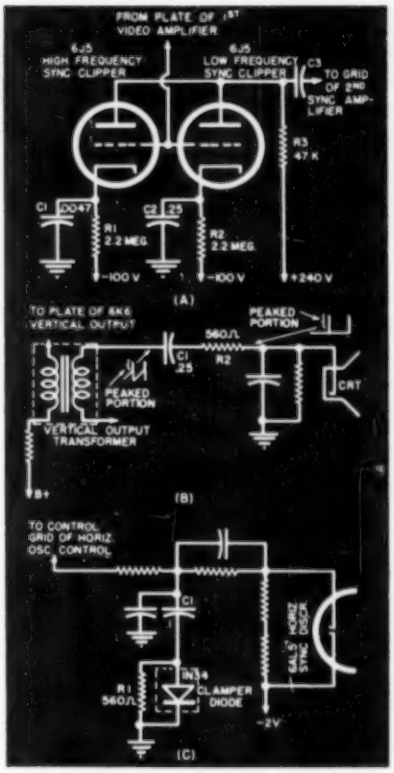

Fig. 1. Circuits used for improving noise immunity, retrace blanking, and automatic frequency control in fringe area receivers.

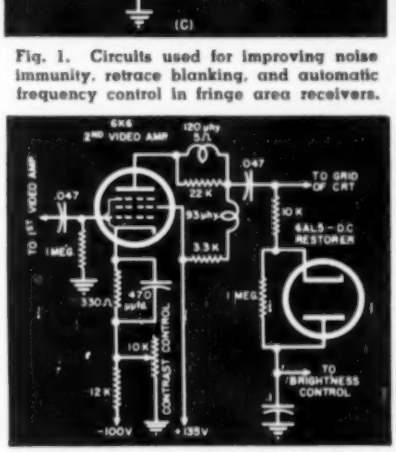

Fig. 2. Contrast control circuit which leaves sync pulse unaffected during adjustment.

Fig. 3. (A) Circuit for increasing the range of the horizontal width control. (B) Keyed a.g.c. circuit with threshold control for weak and strong signals.

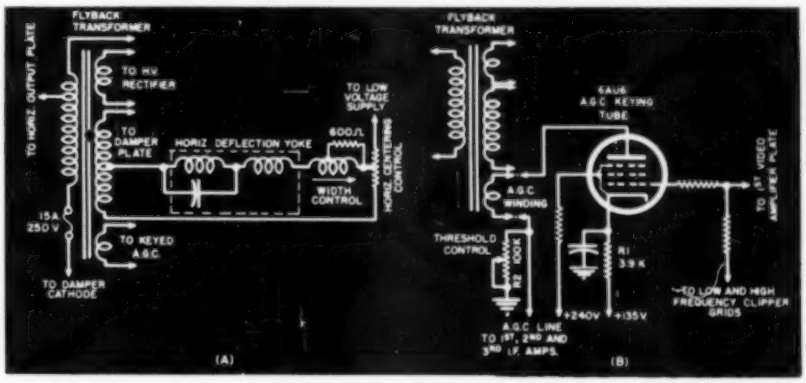

NOISE IMMUNITY CIRCUITS

By MILTON S. KIVER
Pres., Television Communications Institute

Part 1. Know your TV receiver noise rejection and sync stability circuits for more efficient, faster servicing.

ONE of the factors which strongly influences the design and servicing of a television receiver is the fact that the eye is a more sensitive organ than the ear. Because of this, a considerable effort is made to protect television receiver circuits from external interference, especially the impulse type of noise. While such pulses may have only a momentary disturbing effect on the picture elements, they can be particularly destructive to the smooth functioning of the receiver's horizontal and vertical sweep systems. A strong pulse can cause the picture to roll (indicating loss of vertical synchronization) or it can break the image up into a series of diagonal slices (indicating loss of horizontal synchronization). Neither effect is desirable and special precautions are taken to avoid them.

One of the simplest circuits used to minimize the effects of noise is shown in Fig. 1. The video signal coming into the first video amplifier (V_{115}) from the preceding video second detector has the sync pulses negative. Any impulse noise voltages that may be present and which could disturb the sweep oscillators would also extend in the same direction. (Noise pulses extending in the opposite direction would not possess the proper polarity to disturb the sweep oscillator.) At the first video amplifier stage, the grid, plate, and screen voltages are so chosen that with a normal signal input level at the grid, the tube is working over most of its operating range. See Fig. 4. Any large noise pulse that may come along would then drive the grid into cut-off, and effectively suppress much of the noise voltage. In effect this serves to improve the signal-to-noise ratio of the receiver.

An extension of the foregoing method is employed in the circuit shown in Fig. 2. It was found that the peak-to-peak video signal at the grid of the first video amplifier varied over a 2 to 1 range. This meant that if the sync pulse tips were near tube cut-off on strong signals, they would not be near cut-off on weak signals. Hence, noise pulses received with weak signals would be in a better position to disrupt sweep circuit operation than they would be when strong signals were being received.

To get around this situation, the plate voltage of the first video amplifier is made to vary with signal strength. When a weak signal is received, the plate voltage on this tube drops and hence less voltage is now required to drive the tube into cut-off. On the other hand, when a strong signal is reaching the receiver, the video amplifier plate voltage rises, accommodating the tube to this situation.

The variation in video amplifier plate voltage is accomplished in the following manner (see Fig. 2). The plate leads of the first and third video i.f. amplifiers are returned to "B+" through resistors R_{210} and R_{211}. These same resistors also supply the plate voltage for the first video amplifier. In other words, the plate currents of all three tubes flow through the two resistors. Now, when a weak signal is being received, the a.g.c. bias voltage on the first and third video amplifiers is low, permitting these tubes to draw a larger plate current. This, in turn, means a greater voltage drop across R_{210} and R_{211}. Since the plate of the first video amplifier receives its voltage through these resistors, its voltage will decrease.

By the same line of reasoning, when a strong signal is being received, the a.g.c. bias increases and the video i.f. tubes draw less current. This decreases the voltage drop across R_{210} and R_{211}, enabling the video amplifier to receive more plate voltage. Thus, the plate voltage of the video amplifier is raised and lowered in accordance with variations in signal strength, thereby leading to a better signal-to-noise ratio.

Fig. 1. Simple noise immunity circuit. The first video amplifier (V_{115}) is so biased that noise pulses drive the grid to cut-off minimizing their effect.

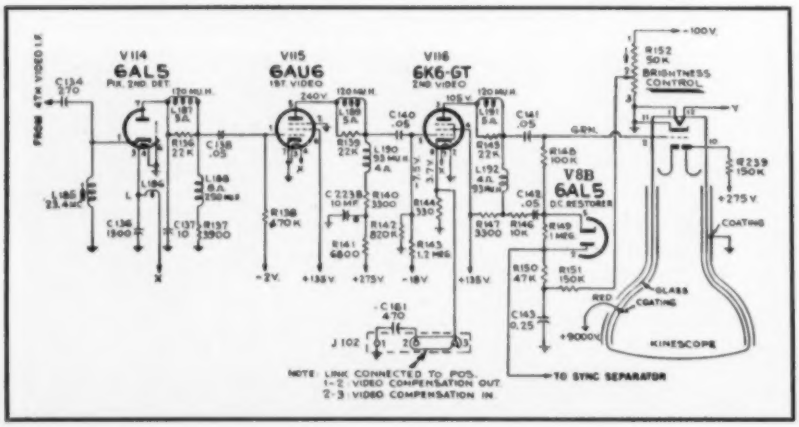

6BN6 Noise Immunity Circuit

Noise immunity circuits have been placed in the video amplifier stages (as above) and in the sync separator section. In the latter circuits, one approach has been through the use of special purpose tubes, such as the 6BN6. To fully appreciate the unusualness of this tube, consider its physical structure. This is shown in Fig. 5 and is seen to differ quite markedly from conventional tube design.

Electrons emitted by the cathode are formed into a thin concentrated beam by the action of the focus electrode and the first accelerator slot and projected onto grid #1. Beyond grid #1 a further focusing takes place, this time caused by the curved screen grid and the grounded second accelerator lens slot and aided by the curvature of grid #1. This group of elements projects the refocused beam onto grid #2 and from here is passed on to the plate.

Now, the concentrated beam of electrons approaching grid #1 can be stopped completely if the grid is only slightly negative, possibly no more than −1.5 to −2 volts. When the grid potential rises above the cut-off voltage, current flow starts up and increases rapidly until current saturation takes place at a slightly positive grid voltage. Raising the grid potential above this value does not provide more current. Thus, within the range of a few volts, the tube can be driven from cut-off to saturation.

Grid #2 can also cut-off the beam

current, but only if it is strongly negative. If it is made zero or positive, it will permit electrons to pass without altering their number. In other words it functions as an open gate, while grid #1 determines the extent of the tube current flow.

The structural diagram of the 6BN6 (Fig. 5) is seldom used. Instead, the schematic representation of Fig. 3 is used. Grid #1 of Fig. 5 is shown at pin 2 of Fig. 3. The accelerator is available at pin 5. Grid #2 is shown at pin 6. The plate is pin 7 and the cathode, focus electrode, lens, and shield are all tied together at pin 1. Pins 3 and 4 attach to the heater elements.

One application of the 6BN6 as a sync separator is presented in Fig. 6. The output of a 1N64 video second detector is fed to a 6AB4 amplifier. The sync pulses are negative at the detector output but the 6AB4 amplifies and inverts these before transferring them to the 6BN6 sync separator. The amplification increases the size of the pulses so that they have more than sufficient amplitude to run the 6BN6 from saturation at one end to cut-off on the other.

The signal coming into the 6BN6 from the 6AB4 is coupled to grid #1 of the 6BN6 tube. The grid bias on the tube is initially zero, but when the positive sync pulses arrive, the tube draws a small amount of grid current which, after a number of cycles, charges C_1 to a negative voltage. Between sync pulses, C_1 discharges slightly through R_1, but the positive tip of each arriving pulse produces sufficient grid current flow to recharge C_1 to its previous level. At this positive tip, then, current flows through the 6BN6 and onto the sweep circuits that follow. All other sections of the incoming video signal are more negative than the sync pulses and since only −1.5 volts are required to cut the tube off, it can be seen that the rest of the signal is effectively suppressed. If there are any strong noise pulses present which extend in the same direction as the sync pulses, they are flattened due to tube saturation.

The grid-leak method of biasing the 6BN6 enables it to accommodate itself to weak signals as well as to strong signals. In other words, the sync separator bias is self regulating.

RCA Noise Suicide Circuit

Noise suppression or noise immunity circuits are designed principally to protect the sweep oscillators of the receiver. Of the two, it is the vertical oscillator that requires the greater amount of protection since the horizontal system is, in nearly all instances, protected by an automatic frequency control network. In recognition of this fact, *RCA* employs the following noise inverting (or, as they called it, "noise suicide") circuit. See Fig. 9.

When a strong noise pulse reaches the receiver, it is sufficiently powerful at the grid of the 4th video i.f. amplifier to cause the grid to go positive. The sudden surge of current through the tube causes the screen grid voltage to drop sharply and this decrease, in the form of a negative pulse, is coupled to the grid of the sync separator stage. C_1 and R_1 serve as the coupling circuit between the screen grid of the 4th video i.f. amplifier and the control grids of the sync separators.

The noise pulse is detected along with the normal video signal by the video second detector and then amplified by the video amplifier. The noise pulse now has a positive polarity. It is then applied to the grids of the sync separators, this being the normal path by which sync pulses are transferred into the deflection systems. At the grids of the sync separators, the negative noise pulse obtained from the plate of the 4th video i.f. amplifier and the positive noise pulse (from the video amplifier) cancel each other. As a result, only the normal sync pulses remain to control the sweep oscillators.

It should be noted that normal signals passing through the video i.f. system do not drive the grid of the 4th i.f. amplifier positive and hence do not send any pulses through C_1 and R_1 to the grids of the sync separators. Thus, when the normal sync pulses reach the sync separators, they are not cancelled out.

Minimizing the effect of strong noise impulses is uniquely carried out in the circuit shown in Fig. 7. A triode tube

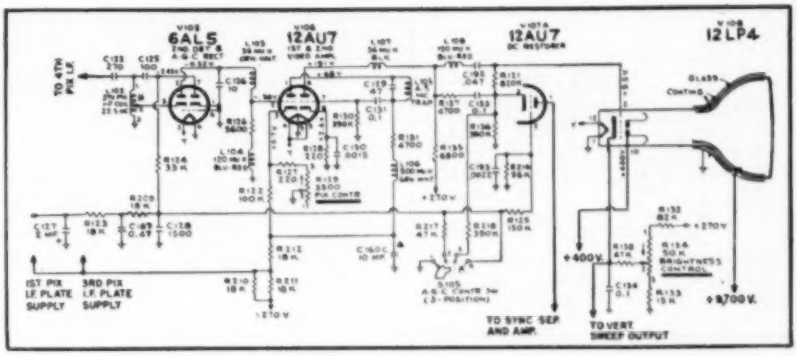

Fig. 2. Improved version of noise suppression circuit shown in Fig. 1.

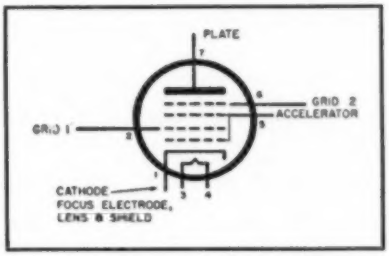

Fig. 3. Schematic symbol of the 6BN6 tube.

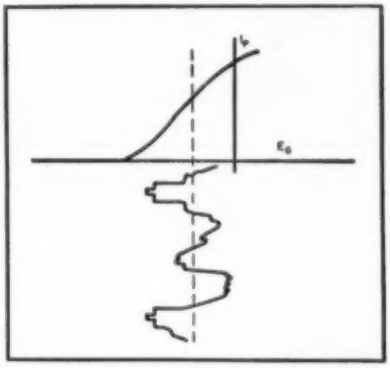

Fig. 4. The first video amplifier of Fig. 1. is operating over most of its range with normal signals; negative noise pulses are cut off.

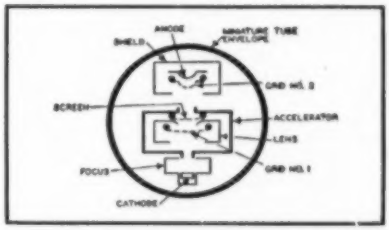

Fig. 5. Internal construction of the 6BN6.

Fig. 6. Application of the beam-gated 6BN6 tube as a sync separator.

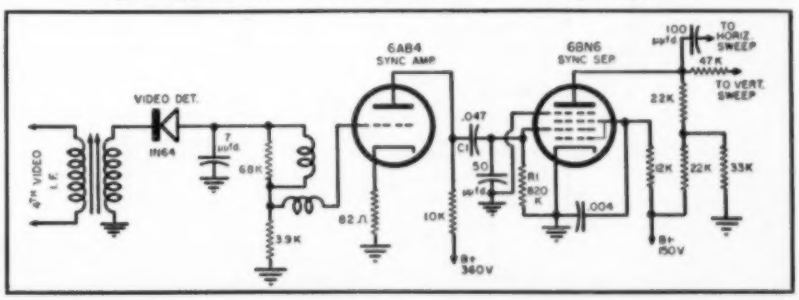

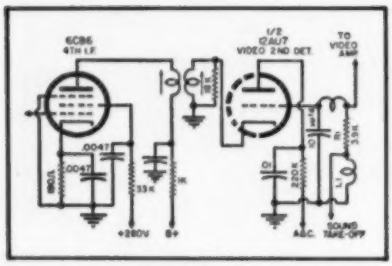

Fig. 7. A noise suppression circuit used by RCA. See text for operational details.

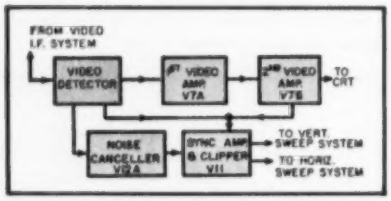

Fig. 8. Block diagram of G-E noise canceller.

is employed in the video second detector stage although, as far as the detection action is concerned, only the cathode and control grid provide the detection. (The control grid serves as a diode plate). Whatever video signal is produced appears across R_1 and L_1 for application to the following video amplifier.

The plate of the triode is tied into the a.g.c. line and is normally negative. Therefore, no current flows through the plate circuit. However, when a strong pulse appears, the cathode is driven more negative than the plate, and current flows rather strongly in the plate circuit. This causes the plate and cathode to appear as a low impedance diode across the output of the final video i.f. amplifier, effectively loading down this circuit and reducing the amplitude of the noise pulse.

Note, then, that the triode functions as essentially two diodes. One diode, formed by the cathode and control grid, is the detector. The other diode, formed by the cathode and plate, is normally nonconductive. However, when a noise pulse causes it to conduct, it acts as a relatively low impedance across the output of the final video i.f. amplifier, loading this circuit down.

G-E Noise Canceller Circuit

A circuit which contains a special noise canceller tube is employed in some *General Electric* television receivers. To better understand the operation of this circuit, it will be best to consider first the block diagram of this set. This is shown in Fig. 8. The box labeled "Noise Canceller" receives its signal from the output of the video second detector. This voltage is amplified, inverted, and then fed to the "Sync Amplifier and Clipper" box. This latter stage also receives a portion of the video signal from the video second detector. (A line is drawn from the final video amplifier to the sync amplifier indicating that some voltage is fed back from this point, too. However, for the purpose of explaining the operation of the noise canceller circuit, this latter feedback may be disregarded.)

A schematic diagram of the noise canceller circuit is shown in Fig. 10A. The grid of the sync amplifier, V_{11A}, is fed the composite signal with the sync pulses pointing in the negative direction. This signal is amplified, inverted, and developed across the plate load resistor, R_{102}. At the same time, the composite video signal is applied to the cathode of the noise canceller tube, V_{12A} through condenser C_{105}. This tube is controlled by two bias controls. An automatic bias is provided by the a.g.c. voltage fed to the grid (not shown in Fig. 10A), and a manual bias is provided by the picture stabilizer potentiometer, R_{101}, connected to the cathode. The noise canceller tube is biased so that it starts to conduct only when noise signals extending above the sync level occur. This tube is shunted across the sync amplifier tube V_{11A} and when it starts to conduct, it virtually short circuits the sync amplifier output, thereby preventing the noise pulse from travelling on to the following clipper tube and the horizontal and vertical sweep systems. If the noise pulse extends over several lines, it may wipe out the associated sync pulses and when the noise pulse itself is removed, there is no sync information left for the sweep system. Generally only a few sync pulses are involved and no loss of synchronization occurs because of the flywheel effect of the sweep oscillators and their tendency to continue operating at the same frequency if left temporarily untriggered.

The a.g.c. voltage does not suffice to bias correctly the noise canceller tube over a wide range of input signals. However, by adding the picture stabilizer potentiometer, bias adjustment over a wide range can be achieved.

Instructions for adjusting this control are as follows:

1. If noise is experienced, turn the control clockwise until the noise disappears. Picture distortion may occur if advanced too far.

2. If two stations of different signal strength are to be received, turn the control until interference is at a minimum when receiving the weak station. Adjust the control to avoid picture distortion on the strong station and minimum interference on the weak station.

Before we leave this circuit, a word about the two signal paths leading to the sync amplifier, V_{11A}. One path comes from the video detector, the other from the output of the final video amplifier. Considering path 1, from the video detector, we see from Fig. 10B that even the strongest incoming signal will still preserve the sync pulses. Also, on the strongest signal, the noise pulses would be clipped off and for such signals the noise canceller circuit would not be required. The noise pulses of medium and weak signals, however, would get through.

Now let us look at the video signal coming in along path 2. This has been amplified and is so strong that the sync amplifier stage will show a compressed sync pulse on a strong station. See Fig. 10C. Any noise pulses coming in with strong or medium video signals now will be cut off and therefore only a weak station would require the noise canceller circuit.

Thus, if the sync amplifier, V_{11A}, were to receive only the signal from

(*Continued on page* 128)

Fig. 9. Simplified diagram of RCA noise suicide circuit used in their KCS66 chassis. The d.c. voltages of the sync separators are controlled by a.g.c. potentiometer R_2.

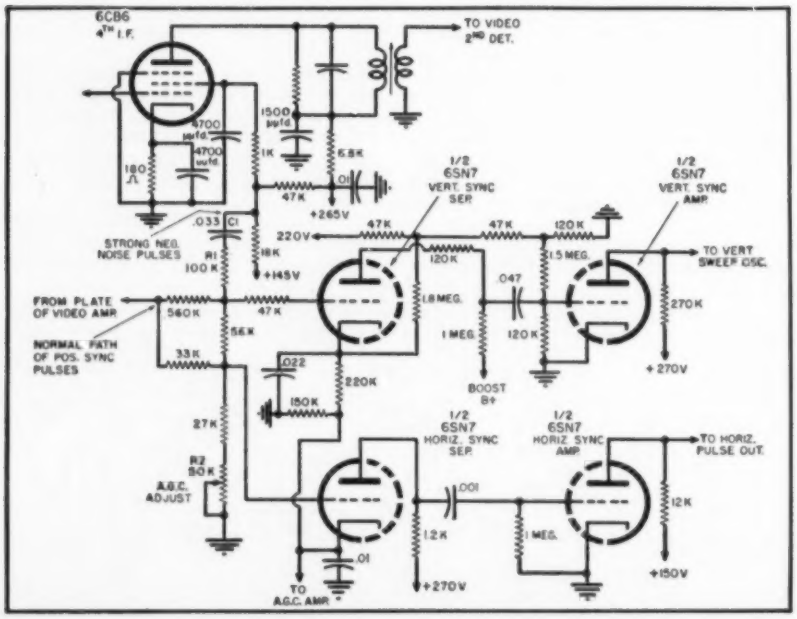

ELECTRO-VOICE

Baronet

Construction details on a commercially available folded horn cabinet. For ultimate performance an Electro-Voice SP-8-B speaker should be used.

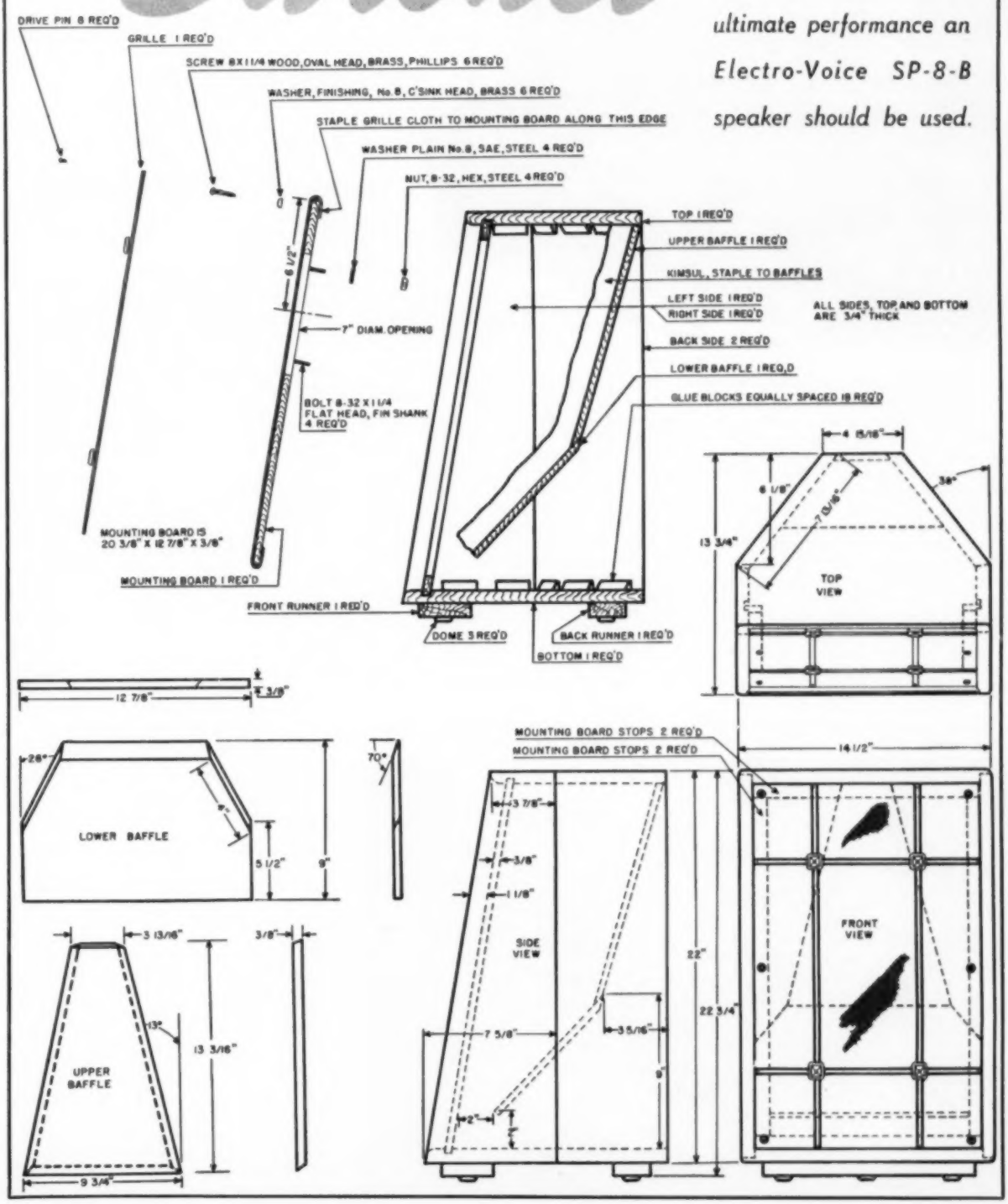

THE ASCO "AUDIOMAT"

By **IRVING GREENE**
Vice-President, Asco Sound Corp.

Music lovers can compare audio equipment under ideal conditions before making their selections.

Test control center for selecting over 9000 combinations of hi-fi audio components.

THE "Audiomat" was designed to provide the maximum flexibility in order to meet the demands of the present as well as future trends in high fidelity equipment. It is capable of providing *split second* switching between any one of ten radio tuners, ten record players, twenty amplifiers, two tape recorders, or twenty speakers. It permits playback of tape from the two recorders through any one of the twenty amplifiers thence through any one of the twenty speakers. Any program from any one of the ten radio tuners or ten record players can be recorded on tape by merely pushing a button. Many steps from the control panel to the equipment racks are saved by the remote control of a.c. power to the equipment. The units are always ready for immediate operation and by the simple flick of a switch any component in the two racks is ready for instant comparison.

The various units of equipment are mounted into specially designed racks which provide two advantages in addition to "listenability." These rack-type cabinets simulate the type of housings in which the equipment will be mounted in the home and give the prospective buyer an idea of the amount of space required for his installation.

A loudspeaker "wall" has been set up to demonstrate speakers in an "A-B test" under ideal conditions. The 14 speakers are mounted in a common "infinite baffle" so that they can be compared on their own merits under identical conditions. This eliminates the problems which arise when one speaker is housed in, say, a *Jensen* bass reflex enclosure and another in an *Aristocrat* folded corner horn for the test and then ultimately installed in an *R-J* enclosure in the customer's home.

The other six speakers used in the demonstration unit are actually two- and three-way systems installed in cabinets or enclosures designed specifically for the speaker system by the manufacturer. In the center of the speaker wall, mounted from the ceiling at an angle, is an indicating panel which contains 20 plastic nameplates that are illuminated when the speaker under test is in the circuit. Thus the listener is always aware of which speaker is under test.

A second demonstration room is very similar to the main salon except that it more nearly duplicates the physical layout of the average home. A miniature "Audiomat" is set up in this "den" to enable customers to select equipment under "home" conditions.

A block diagram of the "Audiomat" demonstration system is shown in Fig. 1. The heart of the entire system is the "Audiomat A-B Test Control Center." Here 67 push-buttons, actuating leaf contacts tipped with silver, control d.c. voltages that energize the coils of more than 80 relays. The relays, designed to switch a unit into the circuit within a fraction of a second, are of the plug-in type (simplifies replacement in the event of a breakdown). The contacts in the relays are gold plated for minimum noise and long life. The relays are hermetically sealed and shielded for minimum hum pickup. As shown in the diagram, only d.c. cables are run from the control panel to each of the two racks. Hence, all of the signal wires are kept to a minimum length thus avoiding diffi-

One of the two equipment racks used in the "Audiomat" demonstration system. Note the pull-out drawers in which the various audio components are compactly mounted.

culties resulting from long leads. The relays plug into specially-wired chassis that are mounted behind the equipment racks. Access to the chassis and relays is easily accomplished through regulation wire panel doors mounted on the wall. The chassis are mounted "rack style" into the openings in the wall behind the back of the equipment rack. All wiring is shielded and all grounds terminate at *one point*, thus eliminating ground loops. The indicating lights for each unit mounted in the rack are energized by the voltage fed across the relay coils. In this manner the relay and the light indicating the unit under test are energized simultaneously at the push of a button. Selection of inputs to any amplifier is automatically accomplished. When a record player is to be switched into the circuit, the listener need only place his record on the turntable, set his player in motion, and switch the selector knob on the amplifier to "phono." Equalization for each of the different type pickups is accomplished by a "correcting resistor" installed across the cartridge terminals to permit the proper "terminating impedance."

Direct current for the relays and indicating lights is supplied by two regulated 6 volt d.c. power supplies. All 6 volt lines are fed to the racks through a special duct installed in the floor. One power supply is for the relays (with the exception of the relays used to select the amplifier inputs) and the indicating lights. The other is used to feed the amplifier input selector relays. These relays are thrown into the circuit with a specially designed master relay.

Another duct installed into the floor carries the 20-speaker transmission lines. Each line is wired with an L pad so that the efficiencies of different speakers can be balanced if the customer wishes to compare them under equal loudness levels. Normally, all pads are out of the circuit and are used only at the request of a listener.

The FM tuners and television units are fed from an antenna line by means of a *Blonder-Tongue* transmission system. A double-array yagi mounted on a 30-foot tower is installed on the roof of a 12-story building. This system feeds an antenna line to 10 radio tuners and 6 television units.

The value of such a demonstration unit becomes clear when one considers the wide range of all types of audio equipment now available.

It is only a few years ago that the audio enthusiast could make his selection of equipment unhesitatingly—he could choose the products of Company A or Company B—they being the only manufacturers in the field.

Today literally hundreds of companies are producing quality equipment for the lush new "audio market" and the selection of equipment has become a bewildering procedure. Only by trying out a representative group of amplifiers, speakers, pickups, phono turntables, record changers, etc. can the customer find the equipment which appeals to his ear and his pocketbook.

A unit such as the "Audiomat" enables the customer to make a true comparison under parallel conditions. Customers are secure in the knowledge they have selected their equipment thoroughly and well.

This unique and practical unit has elicited enthusiastic response from the many music lovers who have been able to select their own "custom" equipment from the wide variety of audio components available. —30—

Fig. 1. Block diagram of the "Audiomat" demonstration system. See text for explanation of the function of the various circuits.

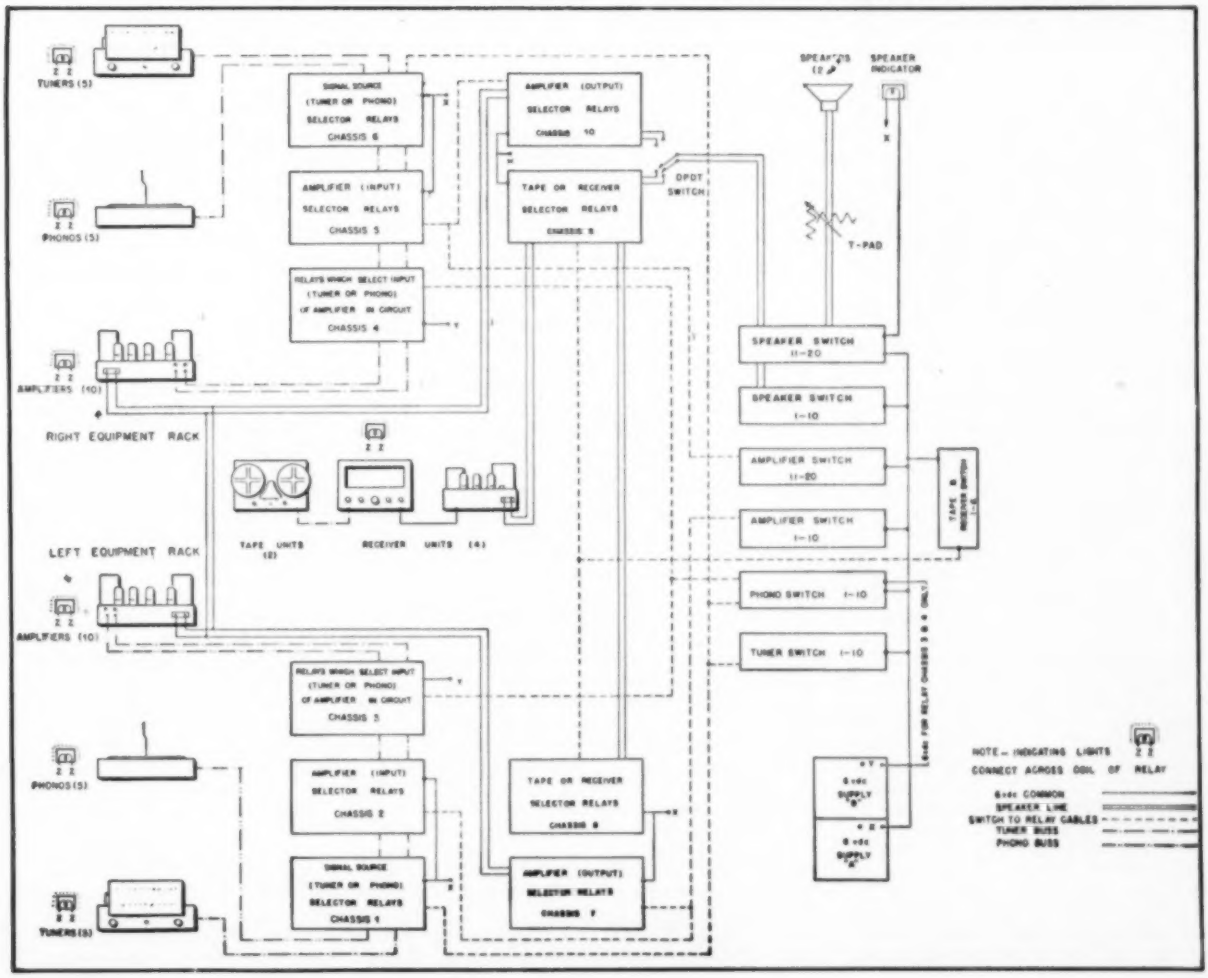
TUNERS (5)
PHONOS (5)
AMPLIFIERS (10)
RIGHT EQUIPMENT RACK
LEFT EQUIPMENT RACK
AMPLIFIERS (10)
PHONOS (5)
TUNERS (5)
SIGNAL SOURCE (TUNER OR PHONO) SELECTOR RELAYS CHASSIS 6
AMPLIFIER (INPUT) SELECTOR RELAYS CHASSIS 5
RELAYS WHICH SELECT INPUT (TUNER OR PHONO) OF AMPLIFIER IN CIRCUIT CHASSIS 4
AMPLIFIER (OUTPUT) SELECTOR RELAYS CHASSIS 10
TAPE OR RECEIVER SELECTOR RELAYS CHASSIS 9
DPDT SWITCH
SPEAKERS (20)
SPEAKER INDICATOR
T-PAD
SPEAKER SWITCH 11-20
SPEAKER SWITCH 1-10
AMPLIFIER SWITCH 11-20
AMPLIFIER SWITCH 1-10
TAPE OR RECEIVER SWITCH 1-8
PHONO SWITCH 1-10
TUNER SWITCH 1-10
TAPE UNITS (2)
RECEIVER UNITS (4)
RELAYS WHICH SELECT INPUT (TUNER OR PHONO) OF AMPLIFIER IN CIRCUIT CHASSIS 3
AMPLIFIER (INPUT) SELECTOR RELAYS CHASSIS 2
SIGNAL SOURCE (TUNER OR PHONO) SELECTOR RELAYS CHASSIS 1
TAPE OR RECEIVER SELECTOR RELAYS CHASSIS 8
AMPLIFIER (OUTPUT) SELECTOR RELAYS CHASSIS 7
6 VDC SUPPLY B
6 VDC SUPPLY A
NOTE — INDICATING LIGHTS CONNECT ACROSS COIL OF RELAY
6 VDC COMMON
SPEAKER LINE
SWITCH TO RELAY CABLES
TUNER BUSS
PHONO BUSS

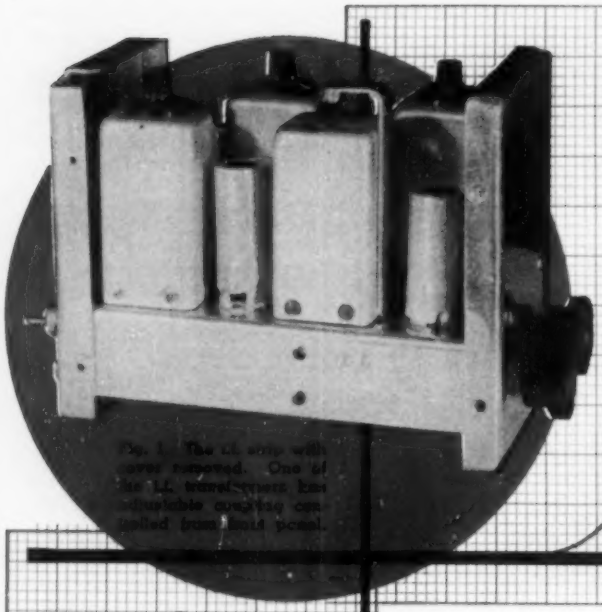

QRM-CUTTING SELECTIVITY FOR THE MOBILE RECEIVER

By
GEORGE M. BROWN
W2CVY

Fed directly by the amateur-band converter, this i.f. strip provides adjustable selectivity for mobile reception, which is often sorely missed in the average mobile installation.

IT HAS only been in very recent years, and after the ubiquitous BC-453 "Q5-er" showed how much room for selectivity improvement there was even in some of the best and most expensive communications receivers, that manufacturers have been building into them the kind of selectivity required for coping with the QRM in the really crowded amateur phone bands such as 75 and 20. Little has been done, however, to provide similar performance in mobile receivers, where selectivity is often as important as at the home station. The usual practice is to buy or build a converter, and to use the standard automobile broadcast receiver, usually working at 1500 kc., as the remainder of the receiving system. The lack of a noise clipper can be corrected by adding one to the BC receiver. This, however, requires digging into somewhat critical portions of the circuit, and has been known to result in seriously impaired performance on the broadcast band. The consequent strain on family amity is roughly equal to that produced by the first hole drilled in the body of the car for the whip antenna mount. An S-meter circuit too can be provided, by tapping onto the cathode of an r.f. or i.f. stage, but the auxiliary circuitry must be designed for the particular receiver.

The lack of selectivity presents an even tougher problem. After all, we can hardly expect the automobile BC receiver manufacturers to worry much about our plight. Their receivers are built for a different job, and they really don't do so badly. Adding a BC-453 "Q5-er" will work, if the receiver i.f. is in its band, but its size is against it, and a plate power supply must be provided, since it is probably too much additional load for the BC receiver vibrator to handle. In addition, when the time comes to turn the car in on a new one with a different arrangement of tail lights or three propeller spinners instead of an inadequate one or two, the whole process must be repeated. Through some lamentable oversight (I'm sure that must be the reason) last year's radio just won't fit in this year's dash.

After considering these facts of life, and having quite a few 75-meter QSO's broken up when a perfectly readable S-7 or 8 signal was completely blanketed by a stronger one, ten or fifteen kc. off the frequency, it was decided to see if the whole problem couldn't be solved by a single unit. It seemed logical to retain the power supply of the broadcast receiver, and its audio system from gain control to speaker, but to draw the dividing line between the broadcast equipment and the ham equipment at the input to the gain control rather than at the BC antenna input. In addition to permitting whatever selectivity was desired to be built in, this approach permitted designing effective noise-clipping into the demodulator, and also incorporating the necessary circuitry for an S-meter, all in a single small unit.

The "i.f. strip" that resulted turned out to be a straightforward job, with no bad habits and no ticklish tendencies. As shown in the schematic, Fig. 2, it takes the 1500 kc. output of the converter, converts it to 85 kc., and then really goes to work on the selectivity. It includes a built-in peak-clipper, variable selectivity, and a jack for an S-meter—all in a box small enough to strap to the converter, or mount under the dash, and still leave knee room.

Input Circuit

The input transformer, T_1, was made from a 1415 kc. i.f. transformer from a 3 to 6 mc. SCR-274/N receiver. In order to avoid tapping the primary coil, a tapped-condenser type of line-to-grid matching was used, by adding the 2000 $\mu\mu$fd. condenser C_3 in series with the ground side of C_2, the original 180 $\mu\mu$fd. ceramic button. The only other change required was to remove two turns from the primary and three from the secondary, to permit tuning to 1500 instead of 1415 kc. These two tuned circuits, together with the usual single-tuned 1500 kc. output transformer in the converter, provide enough selectivity to attenuate the image of the 85 kc. i.f. by over 60 db, even though it is only 170 kc. away.

There is nothing sacred about the type of input transformer used. If the SCR-274/N type is not available, any permeability-tuned 1500 kc. interstage i.f. transformer such as a *J. W. Miller Co.* 912-W2 would be equally satisfactory, with no modification except to add C_3. C_3 should be made approximately ten times the capacity

of C_2. Also, non-surplus 50-kc. transformers may be used in the i.f. stages, as will be discussed below.

I.F. Amplifier

In order to obtain the high degree of adjacent-channel selectivity that was desired, two stages of i.f., using the three 85 kc. i.f. transformers from a beaten-up BC-453 were used. After removing the little mounting plates that are found on them the transformers were mounted directly to the chassis, using the same four screws each that held them to the plates. There seems to be no particular advantage in retaining the original plug-in mounting, and direct mounting provides a more solid and compact assembly, as well as eliminating the difficulty of trying to salvage the spun-in mounting bases from the original chassis. The external leads were soldered directly into the transformer terminals.

The same method, of course, was used in mounting the 1500 kc. input transformer, since it is identical mechanically to the 85 kc. units.

The plates and screens of all tubes are all fed from the same 100- to 125-volt source, with suitable decoupling circuits. This method of operation permits a single bypass condenser for each tube for both plate and screen, not only saving condensers and screen dropping resistors, but also simplifying wiring. The mutual conductance of the tubes used with plate and screen voltage equal is almost identical to that obtained with higher voltage on the plates, and the power-handling capacity is entirely adequate. Further to save space and for ease of mounting, six of the .05 μfd. bypass condensers were salvaged from the same BC-453 that contributed the i.f. transformers, in the form of two triple units.

Note that all of the i.f. transformers except one have taps on both coils, one for the plate and one for the grid. This feature is intended to increase the "Q" of the circuits, and hence the selectivity, by reducing the grid and plate loading. All originally were so tapped, but it was found desirable to use the full secondary of T_2 in order to obtain a few db more gain that seemed to be needed. The increase in gain was marked, and the decrease in selectivity was negligible.

The BC-453 transformers are built with adjustable coupling, permitting them to be tuned in the uncoupled position and then coupled up to or slightly beyond critical. This feature permits a considerable degree of control over the passband of the amplifier and the temptation to bring one of these controls out to the front panel, for an operating selectivity control, was too great to resist. The Rube Goldberg mechanism shown in the photographs, Figs. 3 and 4, did the job. Note that the selectivity control knob on the panel operates a crank pin, which is coupled by a connecting rod to a bell crank, mounted on the opposite side of the chassis. This bell crank, in turn, operates a push rod, which goes up through the chassis and is secured to the adjusting rod at the top of the transformer by means of a bushing and set screw. It is necessary to remove the threaded bushing at the top of the transformer, normally used to hold the protecting cover, in order to get enough room to make a secure connection to the adjusting rod. In order to prevent vibration from changing the adjustment, and to obtain a snug fit for the shaft that

Fig. 2. Circuit diagram of the selective mobile i.f. system. The input is fed by an amateur-band converter; power and audio are supplied by the car broadcast receiver (connections in Fig. 6). The system has its own noise clipper and a.v.c.

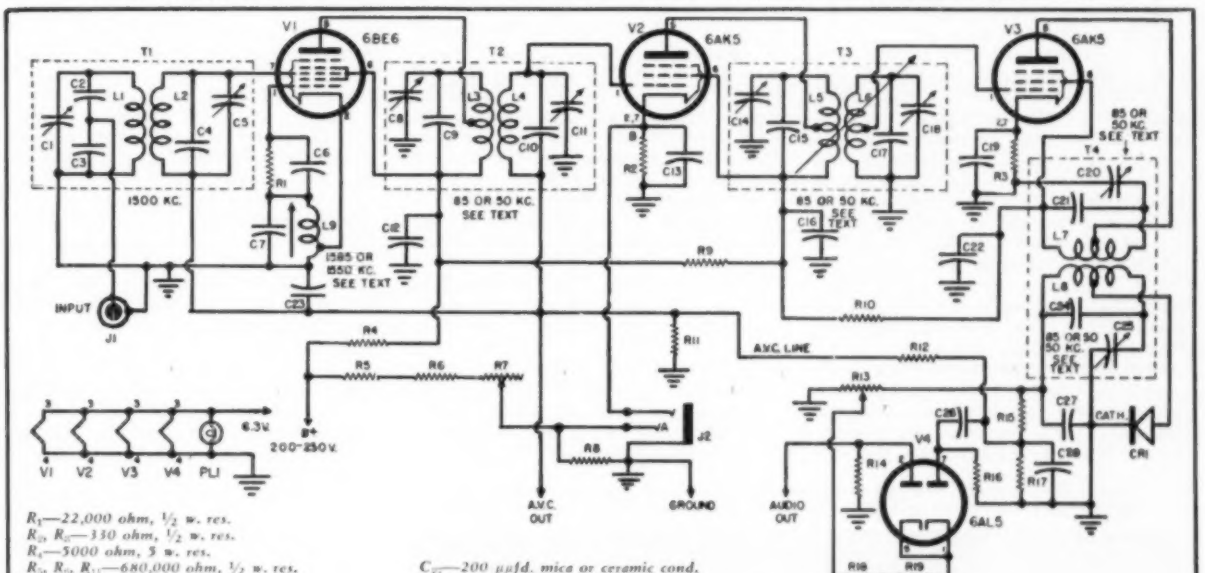

R_1—22,000 ohm, ½ w. res.
R_2, R_{12}—330 ohm, ½ w. res.
R_4—5000 ohm, 5 w. res.
R_5, R_6, R_{11}—680,000 ohm, ½ w. res.
R_7—500,000 ohm pot.
R_8—15,000 ohm, ½ w. res.
R_9, R_{10}—1500 ohm, ½ w. res.
R_{13}—1 megohm, ½ w. res.
R_{14}—100,000 ohm pot.
R_{15}—470,000 ohm, ½ w. res.
R_{16}—100,000 ohm, ½ w. res.
R_{17}, R_{18}, R_{19}, R_{20}—220,000 ohm, ½ w. res.
C_1, C_3, C_4, C_{11}, C_{14}, C_{15}, C_{20}, C_{21}—12 μμfd. trimmer cond.
C_2, C_5, C_9, C_{10}, C_{13}, C_{17}, C_{23}, C_{24}—180 μμfd. ceramic cond.
C_6—2000 μμfd. mica or ceramic cond. added to T_1
C_8—250 μμfd. mica or ceramic cond. (Osc. grid coupling)
C_7—250 μμfd. silver mica or zero-coefficient ceramic cond.
C_{12}, C_{18}, C_{19}, C_{22}, C_{26}, C_{27}—.05 μfd., 600 v. cond.
C_{22}—.05 μfd., 400 v. cond.
C_{25}—.1 μfd., 600 v. cond.
C_{27}—200 μμfd. mica or ceramic cond.
C_{28}—100 μμfd. mica or ceramic cond.
Note: C_{14}, C_{15}, C_{16} and C_{17} are part of T_3. C_{19}, C_{20}, C_{21} and C_{22} are part of T_4. C_{19}, C_{20}, C_{21} and C_{22}, C_{20} are two 3-section condensers used in BC-453 and similar receivers.
PL_1—12 volt, 150 ma. pilot light
CR_1—1N34 crystal diode
J_1—Coaxial connector
J_2—Three-circuit jack
L_1—Part of T_1, modified by removing 2 t. (Not necessary with non-surplus part)
L_2—Part of T_1, modified by removing 3 t. (Not necessary with non-surplus part)
L_3—Part of T_2
L_4—Part of T_2 modified by using entire coil for output instead of tap
L_5, L_6—Part of T_3
L_7, L_8—Part of T_4
L_9—Osc. coil, 75 t. #32 en. wound on Millen #69046 form, cathode tap 6 t. from gnd. end
T_1—Input trans, 1500 kc. i.f. trans., (from SCR-274/N 3-6 mc. receiver modified by addition of C_3 and removal of two turns from L_1 and three from L_2 or J. W. Miller Co. #912-W2 unmodified except for addition of C_3)
T_2—85 kc. trans. from BC-453 (modified by using entire secondary for output instead of tapping down. See text. Or Millen #64051)
T_3—85 kc. trans. from BC-453 (modified to permit coupling adjustment from front of panel. See text. Or Millen #64051 unmodified)
T_4—85 kc. trans. from BC-453 or Millen #64051
V_1—6BE6 tube
V_2, V_3—6AK5 tube
V_4—6AL5 tube

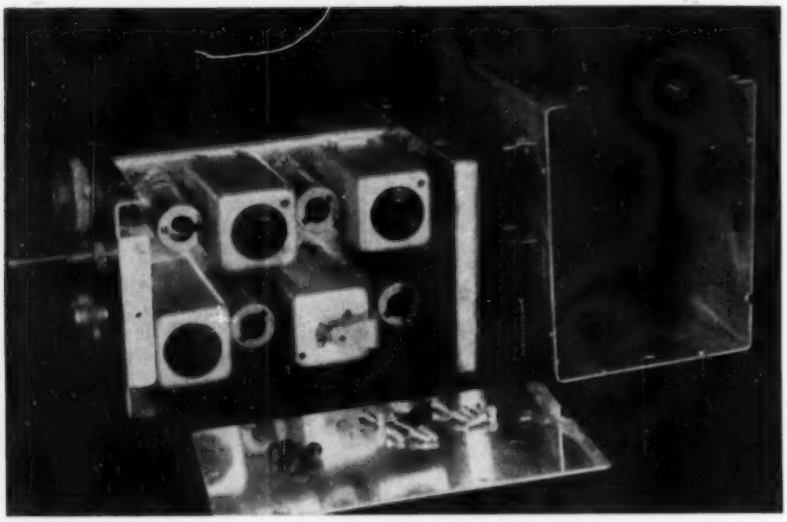

Fig. 3. Top view, showing tube and transformer layout and sheet-metal covers. The method of adjusting the coupling of T_1 (lower right) is explained in the text.

comes through the panel, a *Millen* #10061 dial lock was used as a nut on the inside end of the shaft bushing. Adjustment of the tapered nut of this excellent device permits just the desired frictional drag on the control, and zero slop in the bearing. Its use for this and similar applications is highly recommended.

This may all seem like a lot of trouble to obtain a little front-panel control of selectivity but it has turned out to be well worth the effort expended. With the control set for maximum selectivity, the bandwidth is 3 kc. at 6 db down, and 12 kc. at 60 db down, enough to do a lot of QRM-cutting on a band as crowded as 75, but rather sharp and difficult to tune on 10. At minimum selectivity, it is 7 kc. wide at 6 db down, and about 18 at 60, about right for ten, and also useful on 75 when few stations are on and the added highs provided by the wider passband can be received without QRM. And it is always fun when showing off your mobile rig to be able to amaze the converter-BC receiver addict with the way you can clip sidebands and cut through the QRM just by turning the selectivity knob.

BC-453's, and even their 85 kc. i.f. transformers separately, are still available, but they are beginning to get scarce and more expensive on the surplus market. The best commercial substitute presently available appears to be the *James Millen Co.* #64051. If such a unit is used, it will be necessary to increase the size of the chassis and case slightly to accommodate these transformers, and to eliminate the front-panel selectivity control. The *Millen* transformers are designed for 50 kc., rather than 85 kc. as the ones from the BC-453 are, but all that is necessary to accommodate the different i.f. is to adjust the oscillator frequency to 1450 or 1550 kc., instead of 1415 or 1585. The range of the tuning slug will be found adequate.

Detector-Clipper

A 1N34 crystal is used for the demodulator, working directly into the 6AL5 double series-gated noise clipper. R_{13} was provided as a front-panel adjustment of clipping level, but there is considerable question as to whether or not it is needed. In practice, it was found that the optimum adjustment was for minimum clipping, at which position there was no noticeable distortion from the clipping, and it seemed to do almost as good a job on ignition noise as with heavier clipping and more distortion. It is easy to include, however, and occasionally does some good.

The a.v.c. voltage is obtained from the same germanium diode, and applied to the mixer and first i.f. It is also brought out for use in the converter, where it is most helpful in combating overloading from nearby stations. No a.v.c. is used on the last i.f. stage. This tube has a hard job assigned to it, since it has to supply a considerable amount of power to the diode demodulator and it can't do it properly if it is throttled back by a.v.c. Reduction of the power-handling capabilities of the last i.f. tube by a.v.c. with consequent overloading is the unsuspected cause of much distortion in some receivers. It should seldom be used, and then with great caution.

Fig. 4. Bottom view. Note the crank pin, connecting rod, and bell crank at right for operating the selectivity control push rod, which goes up through the chassis.

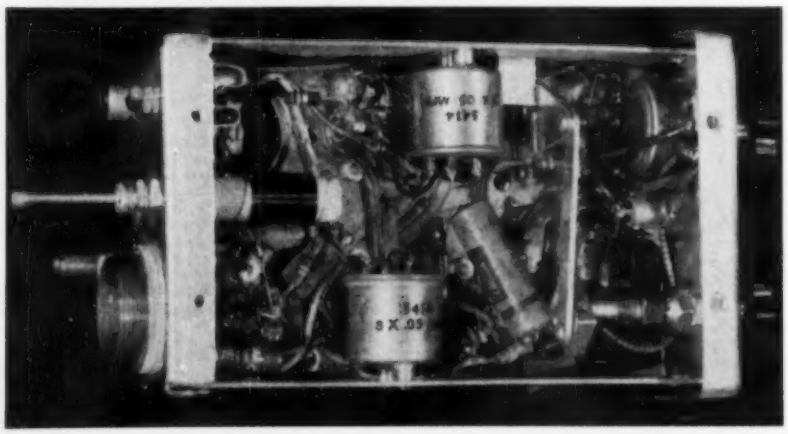

S-Meter Circuit

The S-meter circuit shown is designed to produce zero current on the associated meter with zero signal, and increasing current with signal, in contrast to a simple meter in the cathode of a tube controlled by a.v.c. (which reads backward) indicating maximum with no signal and less with increasing signals. This circuit is also not seriously affected by plate voltage changes, particularly in the weak signal and noise level range, where a simple cathode meter may change two or three "S" units depending upon battery condition.

The circuit operates on the bridge principle, with R_7 being adjusted for zero current on the meter with the antenna grounded. Under this condition, a.v.c. voltage is zero, and cathode current of V_2 is maximum, producing a maximum voltage at point "B" (cathode of V_2, Fig. 2). The zero-current adjustment of R_7 produces the same voltage at point "A" (in J_2, Fig. 2). When a signal is received, a.v.c. causes the cathode current of V_2, and hence the voltage at "B" to drop, and current flows from "A" to "B."

The values shown for the resistors are intended for a 150-microampere meter. If a meter of less sensitivity is used, the total resistance of the R_7-R_8-R_9 combination and R_6 will need to be decreased accordingly. A higher sensitivity meter can be used by inserting a resistor in series with it to keep it on scale with the strongest signal. R_5 and R_6 may be replaced by a single resistor of suitable value if desired.

Construction

The entire unit was built on an aluminum chassis 3⅝" by 6⅛" (about 4⅛" by 6⅝" with *Millen* i.f. transformers), bent up from sheet stock.

(*Continued on page* 116)

U.H.F.-V.H.F. ANTENNA COUPLER

By

EDWARD FINKEL and JAMES C. SARAYIOTES

JFD Manufacturing Co., Inc.

Single lead-in from separate v.h.f. and u.h.f. antennas is possible when using a coupler of the type described here.

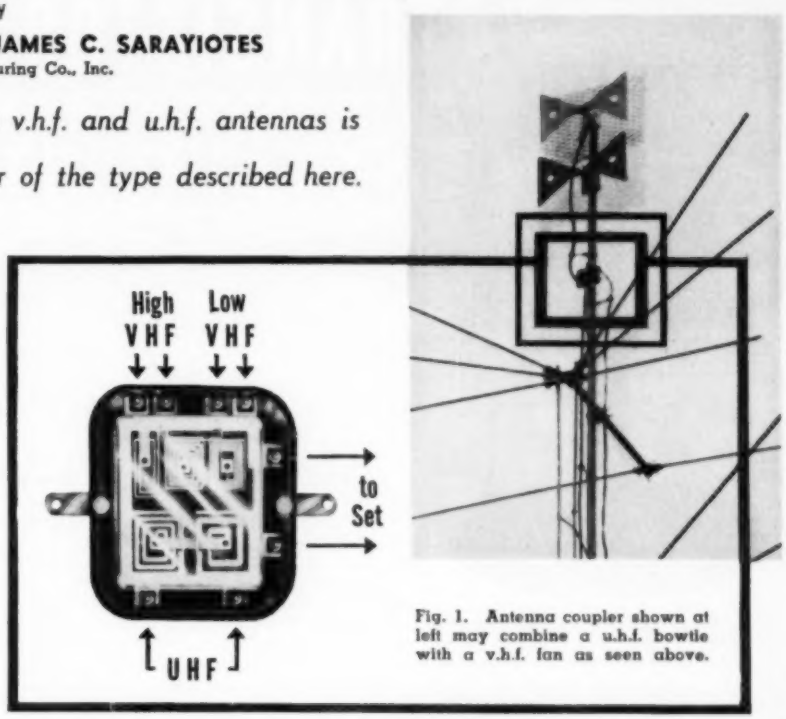

Fig. 1. Antenna coupler shown at left may combine a u.h.f. bowtie with a v.h.f. fan as seen above.

IN AREAS now receiving u.h.f. service in addition to v.h.f. transmissions, the service technician will often encounter the home owner's reluctance to add yet another antenna to his private skyline and his additional reluctance to invest in a second complete antenna installation to provide u.h.f. signals. Among the new TV products introduced recently is the *JFD* "JeTie," a printed circuit coupling device which combines separate low v.h.f., high v.h.f., and u.h.f. antennas on a single mast with a single downlead. It thus solves the "skyline" problem and minimizes the expense of the u.h.f. antenna installation when added to the existing v.h.f. antenna.

Interestingly enough, the major number of v.h.f. installations, converted to receive u.h.f., require a coupler for quite another reason. TV sets adapted to receive u.h.f. by strip conversion (and most new continuous tuning v.h.f. and u.h.f. sets also) provide only one pair of input terminals. It is not possible to bring separate v.h.f. and u.h.f. downleads to these receivers. A coupling device which will permit the antennas to be terminated in a single downlead is, therefore, a necessity.

For installations using separate u.h.f. translators or converters, providing a pair of terminals for u.h.f. and a separate pair for v.h.f., a coupler at the antennas, a single downlead, and a second coupler at the receiver provide for a completely matched 300-ohm system, a faster, less expensive installation, and a less complicated skyline.

The "JeTie" is a passive broadband network, designed to match the popular 300-ohm balanced input system.

Fig. 2 is a simplified schematic representation of the coupler. The TV downleads are always connected to terminals A and H, and the leads from the u.h.f. antenna (470-890 mc.) are always connected to F and G. When a broadband v.h.f. antenna (54-216 mc.) is used, it is connected across B and E. When separate antennas are used for the high and low v.h.f. bands, the low-band antenna is connected to B and C and the high-band antenna is connected to D and E.

Operation of the *JFD* "JeTie" depends on the properties of the parallel-resonant circuit. Reference to the simplified schematic, Fig. 2, shows that it consists of five parallel-resonant networks. The circuit parameters are such that over the low v.h.f. frequency range, a very high impedance is presented across terminals B, C and a short circuit is presented across terminal pairs D, E and F, G. For the high v.h.f. band, short circuits are presented across terminal pairs B, C and F, G; and a very high impedance is presented across D, E. For signals in the u.h.f. band, shorts are presented across B, C; and D, E and a very high impedance is presented across terminals F, G.

The reason the circuit works in this fashion is that the impedance of a parallel inductance-capacitance network is purely resistive at resonance. Away from the resonant frequency the impedance is inductive or capacitive, depending upon the frequency. The magnitude of the impedance away from resonance depends on the "*Q*" of the circuit; it will be low if the "*Q*" is high and *vice versa*.

It can, therefore, be seen that with the appropriate choice of "*Q*" and *L/C* ratio for each network, it is possible to connect the v.h.f. and u.h.f. antennas simultaneously to a single pair of downleads, and have each properly terminated in the 300-ohm receiver input (over its appropriate frequency range) with a minimum insertion loss and voltage standing wave ratio.

Fig. 2. Equivalent circuit of the coupler showing the antenna connecting points.

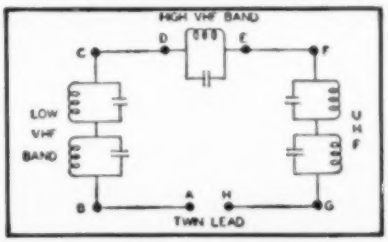

The fact that coupling devices of this type are always exposed to rain, heat, cold, snow, and humidity poses very exacting problems, for the accumulation of dirt and rain water threaten to create capacitive effects which can seriously change the electrical characteristics. The "JeTie" is, therefore, hermetically sealed and, as a result, is free from this serious danger.

The housing of the "JeTie" has been deliberately designed to provide maximum separation of the printed circuit from the shell of the enclosure. Five eighths of an inch separates the printed circuit from the shell of the enclosure, thereby minimizing the possibility of developing unwanted capacitive effects between what dirt may accumulate on the shell and the printed circuit itself. In addition, the smooth, convex enclosure surface minimizes the possibility of dirt accumulation. The surface of the coupler, which will face the sun, is clear and silvered, effecting a rejection of heat. The surface which faces away from the sun is black effecting an efficient conduction of heat away from the coupler. —30—

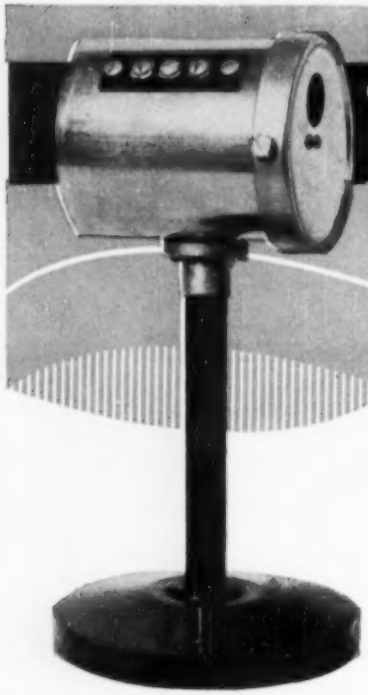

TRANSISTOR-OPERATED PHOTOCELL RELAY

By

LOUIS E. GARNER, JR.

Construction details on a simple unit which has many uses in the home or shop. Power requirements are low and cheap.

Fig. 1. Over-all view of author's unit. A discarded exposure meter cell was used.

WHILE battery-operated, self-contained photocell relays are certainly not new (see "A Photoelectric Headlight Dimmer" by P. J. Vogelgesang, RADIO & TELEVISION NEWS, January, 1953), the unit shown in Fig. 1 does possess several unique features. First, no resistors, coils, transformers, condensers, or vacuum tubes are used in its construction. Secondly, a single inexpensive, comparatively low voltage battery is all that is required for its operation and this is contained within the small housing shown. The battery life is fairly long, due to the low current drain.

All these features are made possible by the use of a self-generating photocell, together with a direct current *transistor* amplifier. Only a few parts are required for the device, as can be seen in the schematic diagram (Fig. 2), and the interior view given, Fig. 6.

Circuit Description

The operation of the circuit may be easily followed by reference to the schematic diagram of Fig. 2. The *Raytheon* CK721 transistor ("*p-n-p*" type) is the "heart" of the device, and is connected as a direct-coupled grounded emitter amplifier. This serves to amplify the weak current obtained from the photocell sufficiently to operate the relay, RL_1.

As long as no light falls on the photocell, the base current of the transistor is essentially zero, and negligible collector current flows through RL_1, which remains open. When light is allowed to fall on the photocell, a small base current starts to flow, permitting a corresponding increase in the flow of collector current through the relay. The collector current is several times greater than the base current, with a current amplification of ten comparatively easy to achieve.

As the light intensity increases, base current and collector current also increase, until the current through the relay is sufficient to close it.

If the light intensity falls off, a corresponding decrease in base and collector current is obtained. However, the relay does not open until the light level drops appreciably, since less current is required to hold the relay closed than is needed to close it. Under normal conditions, the base current does not exceed a few hundred microamperes, while the collector current does not exceed a few milliamperes.

Collector voltage is supplied by battery B_1, with switch S_1 provided to open the collector circuit when operation of the unit is not desired.

Thus, *only five electrical components* are used in the entire device—a photocell, a transistor, a relay, a switch, and a battery.

Construction Hints

With the single exception of the photocell, all the parts used in building the device are easily obtained from radio-electronic wholesale parts distributors. A "self-generating" photocell may or may not be available at a particular distributor, depending on local demand. Although this item is commercially manufactured, not all supply houses have sufficient demand for the item to warrant stocking it.

The photocell used by the author in building the model shown is a selenium cell salvaged from a defective exposure meter of the type used in amateur photographic work. These meters consist of the basic photocell together with a microammeter. Since the meter movement is more susceptible to mechanical damage than is the photocell, it is sometimes possible to pick up a "defective" unit in which only the meter movement is damaged—the photocell is virtually in perfect condition. In most cases, the cost is negligible.

Even where it is necessary to purchase an exposure meter in "operating" condition, the price of a used unit is likely to be quite low. A used but operating unit offers the further advantage of supplying the experimenter with a sensitive microammeter for other work.

A certain amount of ingenuity may have to be exercised by the builder in mounting the photocell, depending upon its actual shape and size—some are round, others square, and still others rectangular. The one used by the author is shown in Fig. 5.

In mounting the photocell proper, it is best not to attempt to solder leads to it. Use spring contacts made from phosphor bronze or similar material. If a commercial unit is used, it will generally have leads or terminals provided.

No special precautions are necessary when assembling and wiring the circuit, and the builder may follow his own inclinations as far as layout is concerned. The unit shown in the photographs was housed in an old shield can, but almost any type of housing may be used—a plastic or wooden box, a small metal utility box, or even a small chassis, with a bottom plate used as a "cover."

A hole must be provided in the housing, of course, to permit light to

strike the photocell. Generally, no lens will be required unless the builder wishes to increase the over-all sensitivity somewhat by concentrating light from a large area on the cell, using a good sized lens.

The effect of light striking the unit from an angle can be reduced either by using a lens ahead of the photocell or by mounting a closed tube in front of the cell, as shown in Fig. 3. The interior of the tube should be finished in dull black to reduce interior reflections. The tube has not been used in the model shown in the photographs.

Parts Substitutions: A toggle, lever, rotary, or almost any type of switch may be used in place of the slide switch employed in the model. A lock switch is particularly good for this application, as it permits only the owner to turn the unit "on" or "off."

Other relays may be used in place of the one specified in the parts list. When choosing a substitute relay, pick one having good sensitivity. The relay should have a reasonably high coil resistance and should close on *less* than 5 ma. However, the so-called "plate" relays are not suitable for use here due to their high coil resistance, requiring much higher supply voltages for proper operation. Best results will be obtained with sensitive relays having a coil resistance of 3000 ohms or less.

In general, the more sensitive the relay, the more sensitive will be the complete device (requiring less light for operation).

If other relays are used, it may be found possible to use a supply voltage of less than 15 volts.

In any case, the choice of a battery should depend on the intended operation of the unit. A hearing aid type battery (*Burgess* U10) was used in the model and is given in the parts list. This particular battery was chosen because of its low cost, ready availability, and reasonable life under the low current drain required by the device.

Where the unit is to be used in an application requiring extreme battery life, a larger battery might well be employed.

Adjustment and Operation

Once the wiring has been completed, a milliammeter should be connected in series with the relay and the unit turned "on." Light should then be permitted to fall on the photocell. A marked increase in collector current flow should occur, as indicated by the milliammeter reading. If this current increase does not occur, reverse the connections to the photocell —base current must have the correct polarity.

Next, the relay's sensitivity must be adjusted so that the relay closes when light is falling on the photocell and opens when the light source is interrupted. Use a focused light source supplying the same amount of light as will later be used in the intended application. The relay's sensitivity can be changed by tightening or weakening the tension on the armature spring and by adjusting the armature's position relative to the core piece.

Be sure sufficient light is employed, the sensitivity of the completed unit may vary considerably, depending on the photocell used, the relay used, the adjustment of the relay, and other factors.

In the model built by the author, the light obtained from a 3-cell flashlight held two to three feet away from the opening in the housing was sufficient to operate the relay. This light fell through a ¾" diameter round hole in the housing to strike the photocell. Because of this, only about half the photocell's area was used. Greater sensitivity could have been obtained by using all of the photocell's active area. The set-up employed in this test is shown in Fig. 4.

Applications

The applications of the photocell relay described in this article parallel the applications of photoelectric relay units in general, although there is somewhat greater versatility because operation is possible anywhere (special power is not required) and because of the small size possible in assembling a complete unit. However, a review of possible applications might be of interest to the reader, and may aid him in selecting or devising special applications of his own.

In considering applications for the photocell relay, the device can be considered as a switch that performs any one of the following functions, depending on how the connections to the relay contacts are made:

1. To open a circuit when light strikes the photocell.
2. To open a circuit when light striking the photocell is interrupted.
3. To close a circuit when light strikes the photocell.
4. To close a circuit when light striking the photocell is interrupted.

Irrespective of the connections chosen, it is best to supply power to operate the external device from a separate power source, rather than to attempt to use the small battery in the photocell relay circuit proper.

A few possible applications follow, but these should, by no means, be considered a complete list.

Burglar Alarm: The light source and photocell relay may be arranged so that anyone entering a protected area causes an alarm bell to sound.

Doorway Annunciator: A light

(*Continued on page* 165)

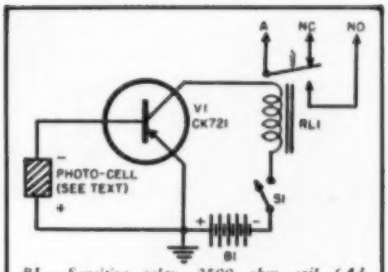

RL_1—Sensitive relay, 2500 ohm coil (Advance Type 850 or equiv.)
S_1—S.p.s.t. slide switch
B_1—15 volt hearing-aid type battery (Burgess Type U10)
V_1—CK721 "p-n-p" transistor (Raytheon)
Photocell—Selenium photocell (salvaged from exposure meter)

Fig. 2. Complete circuit diagram of photocell relay. Only five components are used.

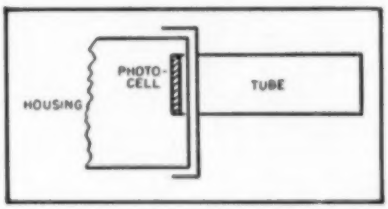

Fig. 3. A shield in front of cell cuts off light which might strike cell from an angle. Suitable for door-opener application.

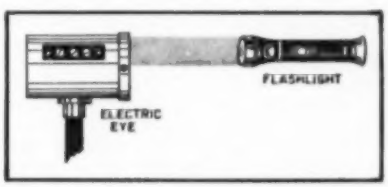

Fig. 4. Test set-up for photocell relay.

Fig. 5. Photocell used by author. Other sizes and shapes may be used. See text.

Fig. 6. Interior view of photocell relay.

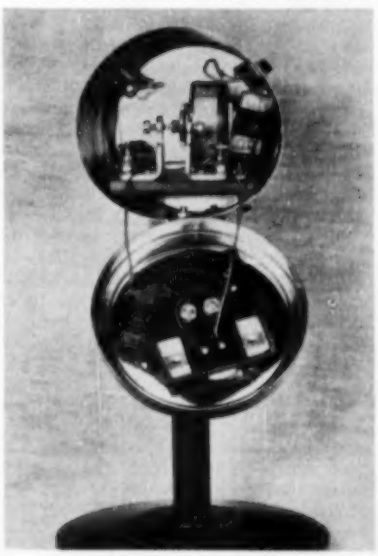

MAC'S RADIO SERVICE SHOP

By JOHN T. FRYE

A LITTLE LIGHT ON FM

"MAC," Barney suddenly blurted, "I've got a problem."

"So what. I'm not going to play Dorothy Dix to your Romeo," Mac warned his assistant; "and if you want advice about your love life you can just—"

"I *never* have any trouble with my women," Barney interrupted; "and if I did I'd certainly not ask you for help. Taking such a trouble to an ancient flint-hearted Scotsman would be like asking an Eskimo about cactus. My problem," he concluded witheringly, "has to do with the one subject you know something about: radio."

Mac smothered a grin at this sharp thrust. "It's nice of you to admit I know something about something," he said with suspicious mildness.

"Last night," Barney said, "a friend of mine by the name of Mr. Smith was over at the house, and we got to talking about frequency modulation. He has always been interested in radio and had read a lot about it, but one thing he has never been able to get clear in his mind is how changing the frequency of the carrier can modulate that carrier. He simply cannot see how swinging the carrier farther and farther each side of the center frequency can produce louder and louder tones in the receiver. I tried to explain it to him with no luck at all. To tell you the truth, by the time I finished 'explaining' to him how FM works I was not sure about it myself."

"You should have used an analogy," Mac observed. "The only way you can explain details of an unfamiliar subject to a person is in terms of something that he does understand."

"Okay," Barney challenged, "let's see you dig me up a good analogy I can spring on Mr. Smith tonight."

"Since we are trying to cast some light on the subject of FM and since we are talking now to a very light intellect, suppose we use a light analogy," Mac began. "Assume we have a direct-current lighted neon lamp shining on a photoelectric cell. As we know, the output of the cell depends upon the amount of light falling on its sensitized plate. While steady direct current is lighting our lamp, its light output will be constant and the output of the cell will maintain a fixed value with no variations.

"Next, let us place an alternating current generator in series with the d.c. source lighting our neon lamp. Let's assume the output of the generator is correct to double the brilliance of the lamp when the two voltages aid each other and that the lamp output is reduced to zero when the a.c. voltage and the d.c. voltage oppose one another. Since the neon lamp responds instantly to the voltage across it, its light output will vary smoothly in step with the frequency of our a.c. generator. If that generator puts out 400 cycles-per-second, our light will be going up and down 400 times a second. The photocell responds to the light reaching it, so its output will also be rising and falling 400 times each second.

"The whole system is similar to an amplitude-modulated radio transmitting-receiving system. The lamp is the carrier generator. The a.c. generator is the modulator. The amplitude-modulated light beam is the amplitude-modulated carrier. The cell that faithfully reproduces in its output circuit the variations in the light intensity falling upon it is the AM detector. Note carefully that swinging our d.c. lighted lamp back and forth in a small arc in front of the photocell does not materially change the amount of light falling on that cell and so produces no change in its output."

"I'm with you so far," Barney encouraged.

"Good. Suppose now we replace our single photocell with two carefully matched cells mounted as close together as possible and with their sensitive areas facing the lamp. Furthermore, let us place a mask between the lamp and those cells with a small opening in the mask so proportioned that the light from the lamp just covers the inside half of each cell's sensitive area. The outside halves are in darkness.

"The output of this new light-detector is measured *across* the two photocell outputs; in other words, the only time we will get a reading is when there is a *difference* in the outputs. That means that now if we connect our a.c. generator in series with the d.c. source and make our light brighten and dim as we did before, there will be no equivalent variation in the output of our twin photocell detector. While the output of each cell will be rising and falling in accordance with the variation in light falling on a portion of its sensitized plate, the two outputs will be rising and falling exactly in step with each other; so there will never, at any time, be a difference in voltage measured from one output to the other."

"It's getting a little thicker, but I'm still following—I think," Barney muttered.

"Now let's see what happens when we move our lamp sideways," Mac continued. "As soon as the lamp starts to move, the light shining through the hole in the mask begins to move *off* one of the photocell plates and *on* to the other. The output of the cell whose sensitized area is receiving more light begins to increase; the output of the cell from which the light is leaving begins to decrease. The combination output—measured across these opposite-going individual outputs—begins to rise, and it continues to do so until the lamp has been moved far enough away from its original position so that one of the photocell plates is receiving all the light and the other is in complete darkness. Continuing to move the lamp in the same direction causes the light to move off the plate on which it is shining, and then this cell's output starts to fall toward the zero output of the other cell still in darkness.

"On the other hand if we return the lamp slowly to its original position the voltage difference between the two photocell outputs returns to its original balanced zero condition; but if the lamp is moved on past this point so the cell that formerly lost the light now gains it and the other cell slides into darkness, our combination output again approaches a peak value equal to that attained before, but this time the polarity is reversed.

(*Continued on page* 159)

KNOW YOUR 1953 DU MONT "TELESETS"

By **JOSEPH ROCHE**
Allen B. Du Mont Laboratories, Inc.

Circuit operation and servicing procedures for efficient handling of the new Du Mont RA-166/167, 170/171 chassis.

THE 1953 *Du Mont* "Telesets" have many new features designed to provide optimum response both in primary and fringe signal areas. In order to efficiently service these new chassis, the service technician should understand the operation of the various circuits and, further, should be appraised of the correct procedure for testing and aligning. This article will attempt to convey this information to the reader. Only those circuits which are new or unusual will be explained in detail. The information contained in this article applies to the *Du Mont* RA-166/167 and 170/171 chassis.

All of these chassis are equipped with 13-position turret v.h.f. tuners of similar design. The tuner r.f. amplifier is a 6BK7 in a low-noise cascode circuit. A 6J6 dual triode serves as the oscillator and mixer.

The RA-171 is equipped with separate u.h.f. and v.h.f. tuners. When the v.h.f. tuner turret is placed in the thirteenth position the output of the u.h.f. tuner is connected to the input of the v.h.f. tuner. In addition, the v.h.f. oscillator is disabled and the necessary components in the u.h.f. tuner are switched to permit the v.h.f. tuner to operate as a 41 mc. i.f. amplifier.

The u.h.f. tuner is of the continuous-tuning type. The tuner circuits consist of a double-tuned preselector, a crystal diode mixer and a u.h.f. oscillator, as shown in Fig. 1. Capacitively-tuned shorted coaxial lines are used in the preselector circuits. The coaxial lines are less than a quarter wavelength long and are, therefore, predominately inductive. The lines are tuned to the desired frequency by the addition of capacitance (C_1 and C_2) across their unshorted ends. In this way the tuned lines become parallel resonant circuits. C_1 and C_2 are variable and tune the preselector circuits through the entire u.h.f. band.

The input impedance of the tuner is 300 ohms, balanced to ground. The transmission line is coupled to the first preselector circuit by two half-turn loops located between the inner and outer conductors of the line. Coupling between the first and second preselector circuits is provided by two loops, L_{102} and L_{103}. The loops function in the same manner as conventional link coupling. Two loops are used to provide more uniform coupling over the tuning range. The output of the preselector is applied to a crystal mixer, CR_{102}, by means of a tap on the inner conductor of the second tuned line. The tapped line is analogous to a tapped coil in a lower frequency circuit.

A push-pull, tuned-plate, tuned-grid circuit is used in the u.h.f. oscillator. To permit the use of an existing tube type of known reliability and availability the oscillator is operated at one-half the desired frequency. Operation at a lower frequency also results in improved stability and uniformity in manufacture. The oscillator tube is a 6J6.

The oscillator plate coil is a flat half turn, stamped from heavy sheet metal to provide maximum uniformity and rigidity. The plate circuit is tuned by means of a split stator condenser, C_4. The rotor of C_4 is ganged with the preselector and harmonic selector tuning condensers. L_{105} in the oscillator grid is self resonant at the lower end of the oscillator tuning range. It maintains the oscillator output at the lower frequencies where it would normally fall off.

The oscillator output signal is applied to a crystal harmonic generator, CR_{101}. Coupling between the oscillator and the harmonic generator is provided by coupling loop L_{104}. The harmonic generator distorts the oscillator signal, increasing its harmonic content. The proper oscillator harmonic signal is selected by means of a third tuned coaxial line. By means of a tap on the center conductor of the harmonic-selector coax line, the oscillator 2nd harmonic signal is applied to the mixer, CR_{102}.

The i.f. signal appears across L_{103}. From this point the signal is link coupled (L_{106}) through a 72-ohm coax line to the input of the v.h.f. tuner. The v.h.f. channel selector actuates S_{101}, applying "B+" to the u.h.f. tuner, when it is switched to the thirteenth or u.h.f. position.

The output frequency of the u.h.f. tuner is 41 mc. and the v.h.f. tuner operates as a 41 mc. i.f. amplifier when receiving u.h.f. stations.

I.F. and Detector Circuits

Four 41 mc. stagger-tuned intercarrier i.f. stages, employing 6CB6's, are provided. The grid circuit of the first video i.f. stage is double tuned. All of the other coupling circuits are

Fig. 1. The u.h.f. tuner used in the Du Mont RA-171 chassis. The output of this circuit is a 41 mc. i.f. signal which is fed to the cascode v.h.f. tuner of the set.

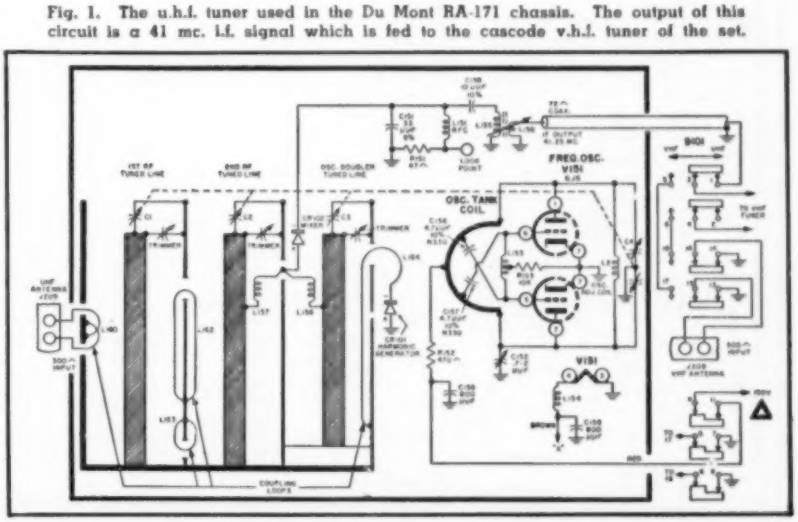

Fig. 2. Complete schematic diagram of the Du Mont RA-166/167, 170/171 chassis.

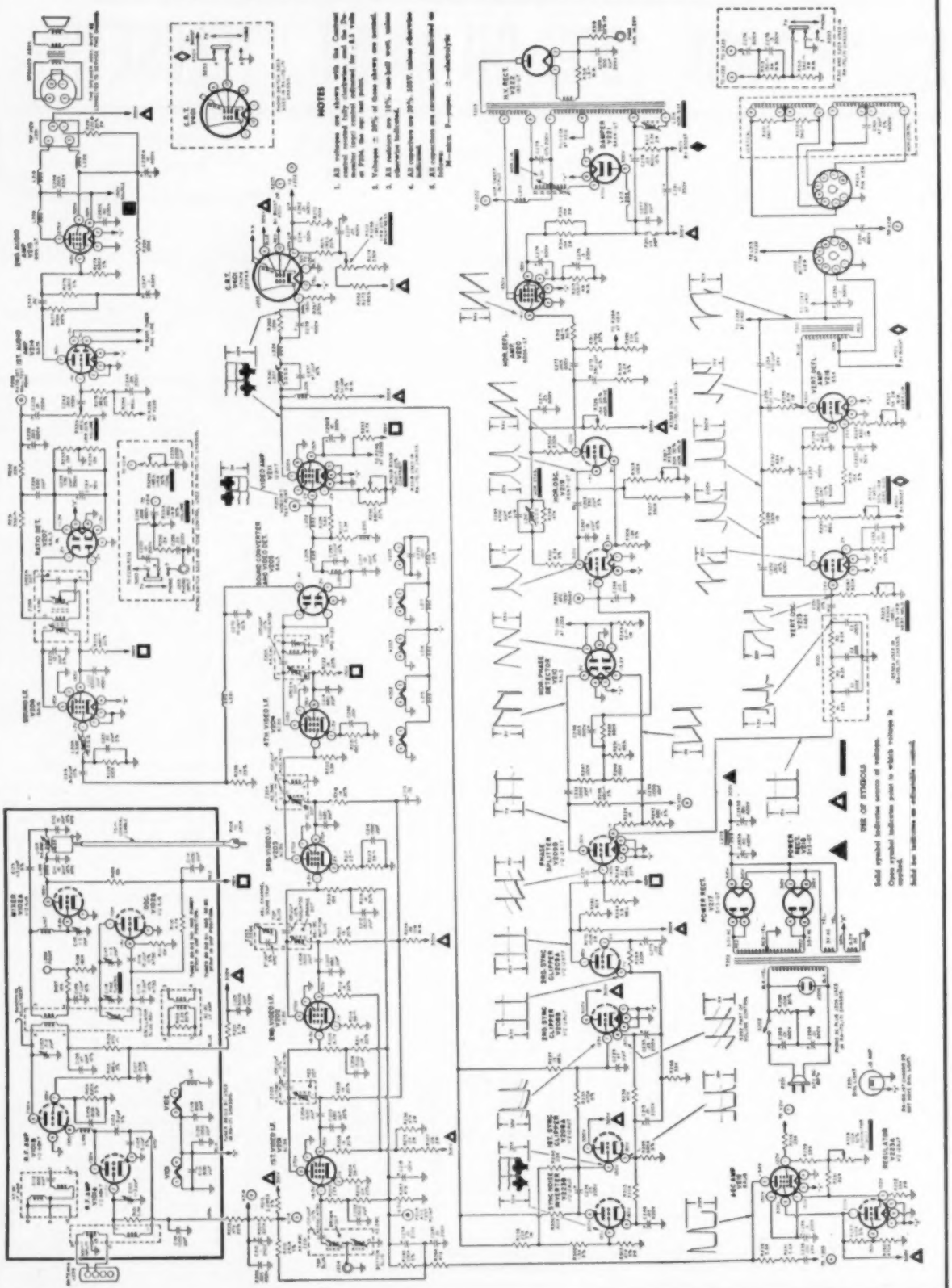

single tuned. A 47.25 mc. absorption type, adjacent-channel sound trap is provided in the plate circuit of the second i.f. stage.

Separate video detector and sound i.f. converter diodes are provided in place of the usual single diode. The use of separate diodes makes possible an increase in the amplitude of the sound i.f. signal at the output of the sound converter.

Direct coupling is employed between the video detector and the video amplifier as well as between the video amplifier and the CRT. A single high gain 12BY7 video amplifier stage is used. A single 4.5 mc. sound i.f. stage is employed followed by a ratio detector and two audio amplifier stages.

A.G.C. Circuits

A keyed a.g.c. system with provisions for delaying application of a.g.c. voltage to the v.h.f. tuner is used in these chassis. Delaying the application of a.g.c. voltage to the tuner greatly improves fringe performance by permitting the r.f. amplifier to operate at full gain on weak signals. It also permits the choice of a.g.c. circuit component values which allow the a.g.c. voltage to rise rapidly on strong signals, providing maximum performance over a wider range of input signal levels for a given setting of the a.g.c. control.

The a.g.c. circuit is shown in Fig. 4. The a.g.c. voltage at the plate of the amplifier, V_{212}, is applied to the delay circuit shown within the dotted lines. The delay network is shown in Fig. 3 with the diodes and condensers removed. The negative a.g.c. voltage appears at point A, causing a current to flow through R_{245} and R_{261} in the direction indicated by the dotted arrows. If we assume that this current is 225 microamps, point A will be approximately −55 volts with respect to ground. A bucking voltage of +270 volts is applied to R_{210}, producing a current through the circuit as indicated by the solid arrows. The total resistance of R_{261}, R_{245}, R_{210}, and R_{215} is 2,667,000 ohms, therefore, the current due to the +270 volts is approximately 100 microamps.

Since the direction of the current due to the bucking voltage is opposite that due to V_{212}, the currents subtract and the resultant current through R_{261} and R_{245} is 125 microamps, flowing from point A to ground. As a result, point A becomes approximately 31 volts negative. The a.g.c. voltage for the i.f. stages is taken off at the junction of R_{245} and R_{261}. The voltage at point A divides across these resistors producing a potential of approximately −5.9 volts at the i.f. a.g.c. take-off.

Since point A is 31 volts negative and point C is 270 volts positive, the total drop across R_{210} and R_{215} is 301 volts. This voltage divides across the resistors producing a drop across R_{210} of approximately 27 volts, making point B 27 volts positive with respect to A, or 4 volts negative with respect to ground. The tuner a.g.c. voltage is taken off at point B and applied to the tuner r.f. amplifier through resistor R_{205}.

Fig. 3. Partial schematic of the a.g.c. delay circuit showing the currents produced by the a.g.c. amplifier and the bucking voltage from the power supply. →

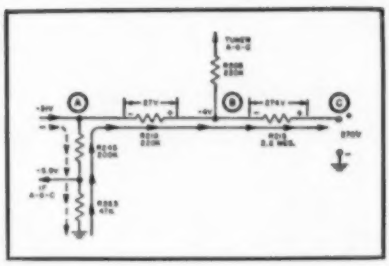

The delay action of the circuit is described with reference to Fig. 5. Assuming that the same conditions exist as in Fig. 3, point A is −31 volts and point B is −4 volts. Now assume that the voltage at point A is gradually made less negative. This will cause the voltage at point B to gradually become less negative. When the voltage at point A is reduced to approximately −27 volts, the voltage at point B will be zero. A further reduction in the voltage at point A will cause the voltage at point B to become positive. V_{214} keeps this from occurring.

When the voltage at point A is sufficiently negative to produce a negative voltage at point B the plate of the diode is negative and it does not conduct. Therefore, it has no effect on the circuit. When point B tends to become positive, the diode begins to conduct, acting as a very low resistance to ground (practically a short circuit) and maintaining point B at zero potential.

Now let's see what occurs as the signal level at the input of the receiver changes. When the signal is very weak the a.g.c. voltage at point A is not very negative and point B tends to become positive, but the action of the diode keeps it at zero potential. As the signal strength rises, the voltage at point A becomes more negative. However, point B remains at zero until the signal level is great enough to produce approximately −27 volts at point A. The diode now ceases

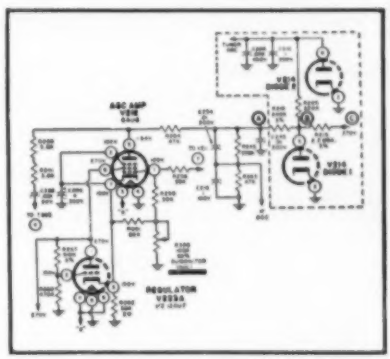

Fig. 4. The delayed a.g.c. circuit.

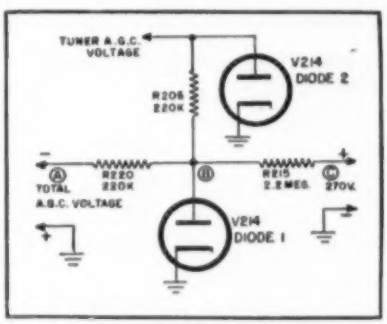

Fig. 5. Diode 1 of V214 produces the delay action of the a.g.c. circuit of Fig. 4.

Table 1. Normal resistance readings to ground at the pins of all tubes in Fig. 2.

		1	2	3	4	5	6	7	8	9
V201	6BC6	80K	56	.1	0	30K	30K	0		
V202	6CB6	50K	56	.1	0	30K	30K	0		
V203	6CB6	50K	61	.1	0	30K	30K	0		
V204	6CB6	3	100	.1	0	25M	25M	0		
V205	6AL5	3	3	.1	0	1K	0	3.3K		
V206	6AU6	100K	0	0	.1	25M	25M	0		
V207	6AL5	INF	INF	.1	0	15K	0	15K		
V208	12AU7	25K	60K	680K	.1	.1	25K	520K	720K	0
V209	12AT7	50K	220K	3.9K	.1	.1	25M	3.9M	1.6K	
V210	6AL5	12	12	.1	0	4.8M	0	4.8M		
V211	12BY7	0-350	3.3K	0	0	0	.1	25K	25M	0
V212	6AU6	30K-40K	27K-30K	.1	0	280K	25K	27K-30K		
V213	6AB4	INF		.1	0		820K-1.8M	1K		
V214	6AT6	2M	0	0	.1	400K	600K	500K		
V215	6W6GT		.1	25K	25K	270K		0	25M	
V216	6S4		820-5.8K		0	.1	2.2M			INF
V217	5Y3GT		25K		18		18		25K	
V218	5Y3GT		25K		18		18		25K	
V219	6SN7GT	5.3M	30K-50K	1.8K	80K-110K	250K-265K	1.8K	0	.1	
V220	6BQ6GT		0	500K	32K	500K		.1	150	Cap INF
V221	6AX4GT			INF		25K		0	.1	
V222	1B3GT		INF		INF		INF	INF		CAP INF
V223	12AU7	25K	300K	30K	.1	.1	150K	30K	1M	0
V401*	CRT	0	1M-1.5M				25K			

	*10	11	12
	INF	100K	.1

The above resistance readings were taken with an RCA Model WV97A v.t.v.m. All readings are in ohms, K = 1000, M = million. When the reading is affected by a control two readings are given. These readings indicate the variation produced by the control.

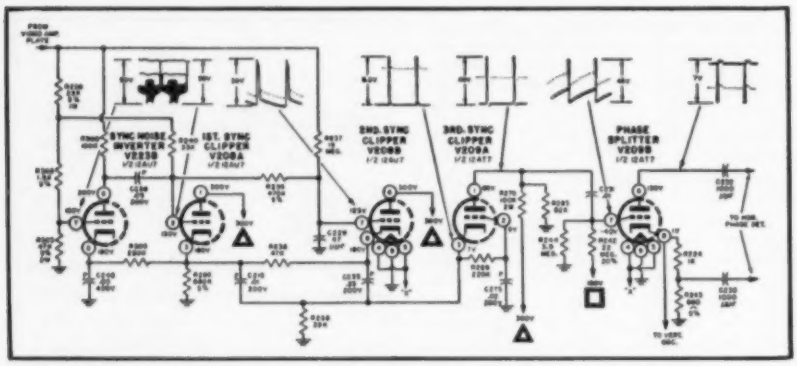

Fig. 6. Schematic diagram of the vertical and horizontal sync circuits.

to conduct and as the input signal level continues to increase, making point A more negative, point B also becomes negative and a.g.c. voltage is applied to the tuner r.f. amplifier.

To keep the plate current of the r.f. amplifier from exceeding the maximum tube ratings, a minimum grid bias of −.5 volt must be maintained on the tube. This bias is obtained from the plate of diode 2 in Fig. 5. When the voltage at point B is zero the plate of diode 2 assumes a potential of −.5 volt, due to contact potential. This contact potential is produced by random electrons which strike the plate of the diode and create current flow in R_{208}.

As shown in Fig. 4, a voltage regulator tube, V_{221A} is provided to stabilize the cathode voltage on the a.g.c. amplifier. This tube prevents line voltage or power supply load fluctuations from affecting the a.g.c. voltage.

Sync Circuits

The sync circuits are shown in Fig. 6. The composite video signal at the plate of the video amplifier is applied to the upper end of R_{228}. That portion of the signal which appears across R_{263} is applied to the grid of the noise inverter, V_{221B}. V_{221B} is biased beyond cut-off and under normal operating conditions there is no signal at the plate of the stage.

When a noise pulse that is greater than the sync pulse comes through, it drives the tube into conduction and a pulse appears in its output. The output of the noise inverter is coupled to the grid of the first sync clipper, V_{220A}. The composite video signal is also applied to the grid of the first sync clipper. The noise cancellation

(*Continued on page* 153)

Table 2. Alignment procedure for the video and sound i.f. circuits of the Du Mont RA-166/167, 170/171 chassis.

STEP	SIGNAL GENERATOR FREQUENCY	SIGNAL GENERATOR CONNECT TO	OUTPUT INDICATOR	CONNECT TO	ADJUST	REMARKS
VIDEO I.F. ALIGNMENT						
1	44.5 mc. no sweep	Pin 5 V101	V.T.V.M.	Pin 2, V211	Z205 for maximum reading	Set signal generator output to maintain reading on lowest range of V.T.V.M.
2	42.5 mc. no sweep	Same	V.T.V.M.	Same	Z204 for maximum reading	Same
3	46.1 mc. no sweep	Same	V.T.V.M.	Same	Z203 (bottom) for maximum reading	Same
4	43.75 mc. no sweep	Same	V.T.V.M.	Same	Z202 for maximum reading	Same
5	47.25 mc.	Same	V.T.V.M.	Same	Z203 (top) for minimum reading	Increase signal generator output to obtain reading on V.T.V.M.
6	43.5 mc. center freq. 10 mc. deviation (min.)	Same	Oscilloscope through crystal probe	Pin 5 V201	Mixer plate coil (L109) and Z201 (top) for 44.8 mc. marker on one peak. Z201 (bottom) for 42.5 mc. marker on other peak	Adjust for waveform below
7	4.5 mc. 400 cps AM	Pin 2 V211	Oscilloscope through crystal probe	Junction R266, R267, and C239	L207 for minimum reading	
SOUND I.F. ALIGNMENT						
8	4.5 mc. Approx. 1 mc. sweep	Pin 5 V205B	Oscilloscope through crystal probe	Pin 7 V207	L204 and Z206 (bottom)	Adjust for waveform below
9	As above	As above	Oscilloscope direct	Junction R232, C228	Z206	Adjust for waveform below

TRAIN *FASTER* — TRAIN *BETTER* — TRAIN *EASIER*
IN 10 MONTHS — OR LESS — FOR
RADIO-TELEVISION

Our 21st Year Training Men for Greater Incomes and Security in Radio-Television

I SEND YOU 18 BIG KITS

of Radio Television parts and equipment. Much of your training will be actual construction and experimentation . . . the kind of truly PRACTICAL instruction that prepares you for your Radio-Television career.

Frank L. Sprayberry
President
Sprayberry Academy of Radio

YOU BUILD the Television set and the powerful superhet radio receiver shown above. IN ADDITION to the other test units shown here (many are not shown because of lack of space). All equipment I send you is YOURS TO KEEP.

NEW! NO OBLIGATION PLAN

You Have No Monthly Payment Contract to Sign
Pay For Your Training as You Earn and Learn

You can get into Radio-Television, today's fastest growing big money opportunity field, in *months* instead of years! My completely new "package unit" training plan prepares you in as little as 10 months or even less! *No monthly payment contract to sign—thus NO RISK to you!* This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. Start your own profitable Radio-Television shop . . . or accept a good paying job. I have trained hundreds of successful Radio-Television technicians during the past 21 years—and stand ready to train you, even if you have no previous experience! Mail coupon and get all the facts—FREE!

Valuable Equipment Included With Training

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. You perform over 300 demonstrations, experiments and construction projects. You build a powerful 6-tube 2-band radio set, multi-range test meter, signal generator, signal tracer, many other projects. All equipment and lessons are *yours to keep* . . . you have practically everything you need to set up your own profitable Radio-Television service shop.

Earn Extra Money While You Learn!

All your 10 months of training is IN YOUR HOME in spare hours. Keep on with your present job and income while learning. With each training "package" unit, you receive extra plans and "Business Builder" ideas for spare time Radio-Television jobs. New television stations everywhere, open vast new opportunities for trained Radio-Television Technicians—and those in training. If you expect to be in the armed forces later, there is no better preparation than practical Sprayberry Radio-Television training.

SPRAYBERRY ACADEMY OF RADIO

111 NORTH CANAL ST.
Dept. 25-W, Chicago 6, Ill.

MAIL COUPON TODAY! NO OBLIGATION

I invite you to get all the facts—

FREE TO YOU 3 BIG RADIO-TELEVISION BOOKS

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training —without cost! Rush coupon for my three big Radio-Television books: "How to Make Money in Radio-Television," PLUS my new illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—ALL FREE. No obligation and no salesman will call. Mail coupon NOW!

SPRAYBERRY ACADEMY OF RADIO, Dept. 25-W
111 North Canal St., Chicago 6, Ill.

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Be sure to include 3 books FREE.

Name..... Age.....

Address.....

City..... Zone..... State.....

THE NEPCO LINE

New Standard

UHF

NEPCO announces a complete line of Ultra High Frequency antennas. These antennas meet the most rigid specifications of mechanical design. Vibration—the most critical factor to be considered in UHF antennas—is held to a minimum through advanced design features, thus producing the clearest picture possible.

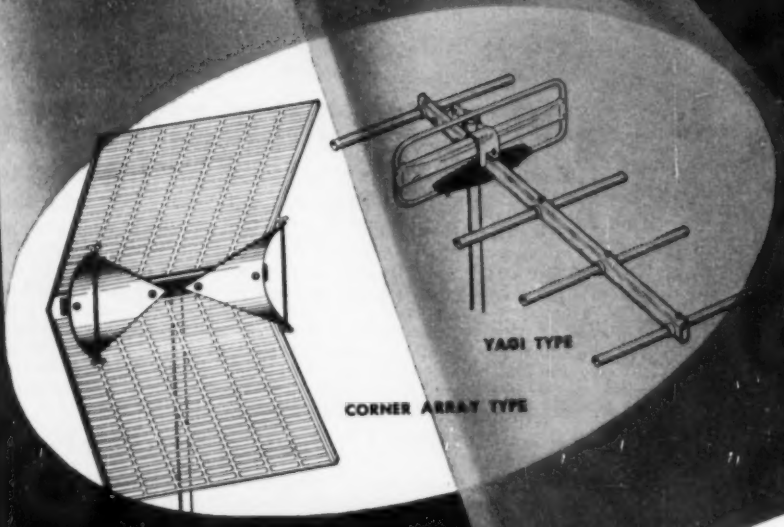

VHF

The NEPCO Line of antennas is designed to give optimum results for full band width. The superior mechanical features maintain the electrical effectiveness and performance CONSTANTLY, regardless of weather conditions.

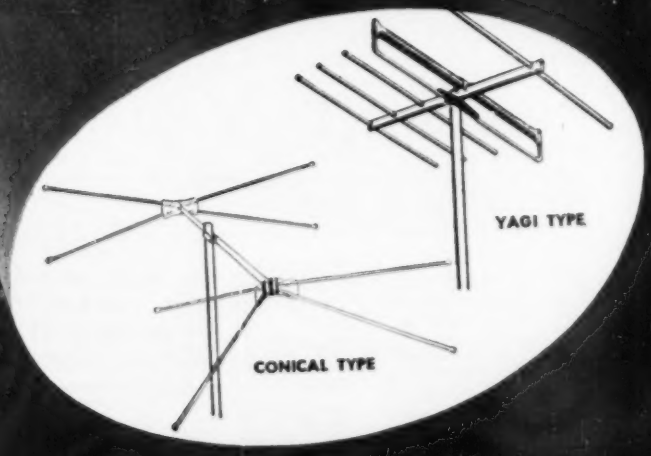

ANTENNAS

of Quality

All NEPCO-Yagi antennas incorporate full channel coverage. They have maximum front-to-back ratio with maximum admittance—all possible because there are no wing-nuts, flutes or slots to destroy inherent impedance and induce corrosion, the bane of all antennas operating at high frequencies.

The NEPCO-Conical antenna features the same mechanical strength design needed to guarantee top performance. Aluminum elements are permanently secured with patented "Vibration-proof" imbedding screws. Erection is speeded due to fewer bolts and mechanical parts to assemble and tighten.

New "Glastic" antenna insulator

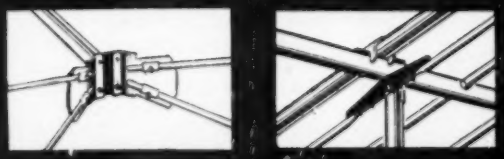

- Withstands very high mechanical stress.
- Best possible electrical characteristics.
- Lightweight.
- Stronger, more rigid, more weather resistant than materials 3 times its thickness.

The NEPCO *Line includes:*

Yagi Antennas • Conical Antennas
UHF Antennas • Masting • Eave mounts
Wall Brackets • Vent Mounts • Guy Rings
Chimney Banding • Chimney Mounts • TV Wire
Banding & Mast Clamps • Add-a-Tower Plates

National Electric Products

RADIO & TELEVISION DEPARTMENT, PITTSBURGH, PA.

NEPCO *Telescoping Masts*

- Heavily electro-galvanized with baked enamel finish.
- Swedged for accuracy and close fit.
- ⅜" bolts to assure rigidity.
- Full 16 gauge metal.
- Complete with full rotating guy rings.
- Installation up to 40 feet.
- Lightweight, easily erected by two men.
- Packed in individual cartons.

NEPCO *"Zee" Line*

- Low-loss UHF TV receiving wire, mechanically perfect for maximum signal.
- Constant impedance under all conditions.
- Comes in strong, flat cartons.
- Easy to stock, easy to handle, easy to pull out for cutting to any desired length.

UHF *Antenna Mast Adaptor Bracket*

- Quick, adjustable method for installing UHF antennas on *existing* masts.
- Same rugged features as Nepco Mounts.
- Electro-galvanized plus baked enamel finish.

Master of the Elements

THE NEPCO LINE

International SHORT-WAVE

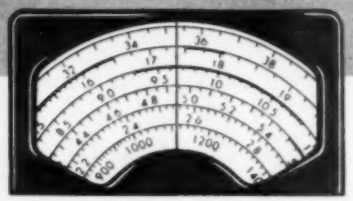

Compiled by KENNETH R. BOORD

BEGINNING with this issue, due to space limitations, the *ISW DEPARTMENT* will, of necessity, be confined largely to items about *new* stations and *changes* in calls, powers, frequencies, and schedules. Please continue to send your *top-flight* DX items to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, USA. Thanks!

* * *

Around the World

(*NOTE:* When this was compiled, some stations had not yet gone on *summer* schedules; hence, in some instances schedules may now be *one hour earlier* than listed herein.—K. R. B.)

Afghanistan—Kabul Radio, 9.975, more recently has been on the air most days 1100-1115A, but some days (such as Sun.) continues with request session to 1135A. (Pearce, England)

Albania—Tirana, 7.850, has *English* now 1600. (Pearce, England) The 6.55A channel carries *separate* program, closes 1605. (Ridgeway, South Africa)

Anglo-Egyptian Sudan—Radio Omdurman has *dropped* its 31-m. outlet, is more recently on 7.664 and 6.438. (Ridgeway, South Africa)

Angola—CR6RO, *Radio Clube de Bie*, Silvo Porta, has *returned* to 7.584 from 7.214; heard 0115-0230, 1200-1545. (Ridgeway, South Africa) CR6RG, *Radio Diamang*, Dundo, 9.340, verified via airmail; listed schedule for all-Portuguese sessions as 1300-1430 and 0600-0730 Sun., holidays. (Hardwick, N. Z.; Kary, Pa.)

Argentina—LRA, 17.72, noted with *English* to North America 1700-1930. (Klein, Va.)

Austria—Radio Wien, Vienna, noted 0915 with recordings parallel on 7.245, 9.664. (Pearce, England)

Azores—By now, Ponta Delgada, 11.090, should be on *summer* schedule 1400-1500. Noted by Saylor, Va., others, 1600-1900 on 4.865.

Balearic Islands—Radio Menorca was spotted recently on 7.410, rather good strength 1400. (Mercier, France)

Bechuanaland—ZNB, 8.233A, Mafeking, relays SABC news 1200, weak, heavy CWQRM. (Hardwick, N. Z.)

Belgian Congo—OTH, 9.210, Leopoldville, relays VOA in Russian 1615-1645, 2215-2245. (Brown, N. Y.) OQ2AB, 11.900, Elizabethville, heard in Sweden 0930-1000 sign-off. (DX-Radio, Sweden)

Belgium—From May 1, *Radio National Belge*, Brussels, will be scheduled 0500-0600, ORU3, 17.860; 0600-0700, ORU3, 17.860, ORU4, 15.335; 0700-0800, ORU3, 17.860, ORU4, 15.335, ORU5, 11.850; 1200-1245, ORU3, 9.745; ORU5, 15.335, ORU5, 11.850; 1245-1300, ORU3, 9.745; 1300-1600, ORU3, 9.745, ORU4, 15.335; 1300-1600, ORU5, 6.000; 1600-1615, ORU3, 9.745; 1615-1800, ORU3, 9.745, ORU4, 11.85; 1815-2200, ORU3, 9.767, ORU4, 9.144, ORU5, 9.705, with relay by OTC, 9.655, Leopoldville, Belgian Congo. (Lindholm, Sweden)

Bolivia—CP38, 9.496A, La Paz, heard signing on 0557 with "Onward, Christian Soldiers." (Niblack, Ind.)

Brazil—By now, Sao Paulo should have *two new* 50 kw. stations on the air—*Radio Emissora de Piratininga*, 6.025, 9.635, 11.745, and *Radio Exelsior*, 6.125, 9.585, 15.265. (ISWC, London) PRL7, 9.720, Rio de Janeiro, good level around 2000. (Norman, Ga.) Noted closing 2100. (Morrison, R. I.) ZYZ20, 4.905, Rio de Janeiro, heard 2020 with music. (URDXC)

British Guiana—ZFY, *Radio Demerara*, Georgetown, listed schedule on 5.981, 2 kw., as 0515-1145 (from 0545 Sun.), 1445-2045. (Scheiner, N. J.)

British Honduras—Radio Belize, 4.951, is reported with *English* 1315-1400, 2000-2100. (ISWC, London)

British New Guinea—Port Moresby sent this schedule—VLT7, 7.280, 1545-1745, 0315-0745; VLT9, 9.520, 2100-2245, 0100-0300; all-*English* except has native 0130-0300 weekdays. (Scheiner, N. J.)

Bulgaria—Radio Sofia has *English* for Europe 1345-1400, 1600-1630 on 7.671, 6.070; for North America 2000-2030, 2300-2315 on 9.700. (Pearce, England, others)

Canary Islands—EA8AB, Santa Cruz de Tenerife, is now heard near 7.305 to 1800 closedown (1830 Sat.) (Radio Amateur, London)

Cape Verde Islands—CR4AA, 7.130, noted 1600-1700 in Portuguese. (French, Mass.)

Ceylon—Radio Ceylon noted closing on 15.120 at 0230. (Pearce, England) Heard by Cushen, N.Z., on 4.870 lately to 1145 sign-off, excellent strength; noted by Reeder, Pa., on 11.975 at good level 1100 with religious broadcast, and by Washington, N. J., closing 1145 (some days runs later).

Chile—CE1174, 11.740A, Santiago, signs off 2400. (Niblack, Ind.)

China—Radio Peking, 6.100, and other channels, now has POW messages Tue. and Fri. (perhaps other days) in English session 0400. (Gay,

(*Continued on page* 129)

(Note: Unless otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until noon are shown as 0000 to 1200 while from 1 p.m. to midnight are shown as 1300 to 2400.) The symbol "V" following a listed frequency indicates "varying." The station may operate either above or below the frequency given. "A" means frequency is approximate.

Radio Tetuan, listed 6.067, broadcasts daily from these attractive studios at 0800-1000, 1400-1800 EST in Spanish and 1000-1200 EST in Arabic. Location is Sp. Morocco.

For opportunities within your reach

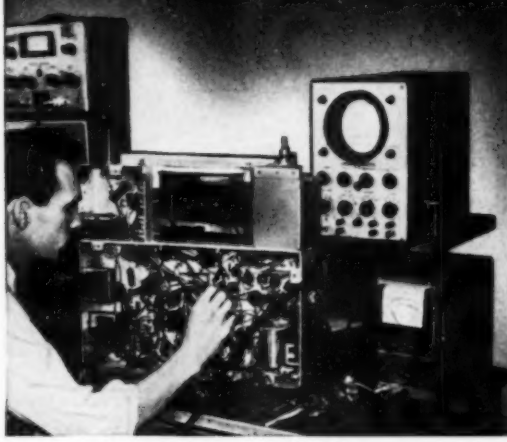

See what the RCA TV Servicing Course offers you

Good-pay jobs. A business of your own.

OPPORTUNITIES FOR GOOD-PAY JOBS in Television are within your reach when you study TV Servicing by the RCA Institutes Home Study Method. Or perhaps you would like to start a TV Service business of your own.

If you are not satisfied with the way your future now stacks up, see how easily you can change the course of your career. RCA Institutes Home Study Course in TV Servicing is helping thousands of other people to better jobs. It can help you. Right now thousands of opportunities are going begging. There is a critical shortage of trained TV servicemen. This is *your* big opportunity.

Easy-to-understand, illustrated lessons

The entire course is divided into ten units of several individual lessons. You study them at home in your spare time. Lesson-by-lesson you learn the theory and step-by-step procedures of installing TV antennas, of servicing and trouble-shooting TV receivers. Hundreds of pictures and diagrams help you understand the how-it-works information and the how-to-do-it techniques. You will be amazed how easily you absorb the knowledge of each lesson, how quickly you train yourself to become an experienced technician.

Experienced engineers and faculty prepared the course, grade your lessons

The RCA Institutes course was written and planned by instructors with years of specialized experience in training men by home-study and resident-school methods. The course embodies RCA's background of television experience plus knowledge gained in training several thousand technicians. A study of the course parallels an apprentice's training. Your lessons are carefully examined and accurately graded by friendly teachers who are interested in helping you to succeed.

One of the leading and oldest Radio-Television training schools

Founded in 1909, RCA Institutes, Inc. has been in continuous operation for the past 44 years. Its wide experience and extensive educational facilities give students, just like you, unsurpassed technical training in the highly specialized field of radio-television-electronics.

RCA Institutes is licensed by the University of the State of New York . . . an affiliate member of the American Society for Engineering Education . . . approved by the Veterans Administration . . . approved by leading Radio-Television Service Organizations.

It costs so little to gain so much

RCA Institutes makes it easy for you to take advantage of the big opportunities in TV Servicing. The cost of the TV Servicing Home Study Course has been cut to a minimum. You pay for the course on a pay-as-you-learn unit lesson basis. No other home study course in TV Servicing offers so much for so little cost to you.

RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. *Write for free catalog on resident courses.*

SEND FOR FREE BOOKLET—Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.

MAIL COUPON NOW!

RCA INSTITUTES, INC., Home Study Dept. RN553
350 West Fourth Street, New York 14, N.Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)

Name _____
(please print)

Address _____

City _____ Zone _____ State _____

RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION of AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

TRANSFORMER SPECIAL #188

FOR AMPLIFIERS, TRANSMITTERS, EXCITERS, ETC. RATINGS: PRIMARY 115V, 50-60 CYCLES. SECONDARY DELIVERS 350 VDC (FROM F. W. RECT.) AT 250 MA. FILAMENTS: 6V @ 3A, 6.3V @ 2A AND 6.3V @ 6A. ELECTROSTATIC SHIELD BET. PRIMARY & SECONDARY. A GREAT BUY AT ONLY **$5.75**

SPARE PARTS FOR APN-9

	EACH
POWER TRANS., PT. NO. 352-7395-2	$4.95
COUNTER TRANS., T111, T112, T117, PT. NO. 352-7251-2	2.50
COUNTER TRANS., T113, T114, T115, T116, T118, T119, T120, PT. NO. 352-7250-2	2.50
I. F. TRANS., T107-T110, PT. NO. 352-15545	1.00
RESISTOR: R150, R157, R162—54,000 OHMS	.50
RESISTOR: R130—220,000 OHMS	.50
RESISTOR: R159—120,000 OHMS	.50
RESISTOR: R152, R164—17,000 OHMS	.35
RESISTOR: R142—4300 OHMS	.35

W. E. PRECISION RESISTORS

1% TOL. 1 WATT

D-164886A	2.69 OHMS	D-162707CY	2500 OHMS
D-164886AA	3.83 OHMS	D-171862	279 OHMS
D-167026*	13,500/10,500 OHMS	D-171863	591 OHMS
D-162025AT*	1400/135/270 OHMS	D-164286*	10,000/15,000/62,000 OHMS
D-164285*	40,600/1500 OHMS	D-164284*	100,000/50,000 OHMS
D-166860FL	1155 OHMS	D-172241*	400/600/700/750 OHMS

ALL RESISTORS ARE SPOOL-WOUND, NON-INDUCTIVE ..... EACH **69c**

* TAPPED AT VALUES SHOWN.

POWER TRANSFORMERS

Comb. Transformers—115V 50-60 cps Input

CTJS-2-600VCT	.2A, 5V/6A		$5.95
CT-19A	590VCT .098A 6.3V/.6A, 6.3V/1.8A		2.85
CT-168	4200V .002A/12KV Test, 5VCT/3A/12KV Test, 6.3V/0.6A 5400V Test		12.95
CT-341	1050 10 MA—625V @ 5MA, 36V @ 4.5A 2x2.5V/3A, 6.3V @ 3A		10.95
CR 829	380VCT .340A	6.3VCT 3.0, 6.3VCT/3A	3.95
CT-826	1500V .160A	2.5/2, 30/100	9.95
CT-071	110V .200A	33/200, 5V/10, 2.5/10	4.95
CT-367	580VCT .050A	5VCT/3A	2.25
CT-99A	2x110VCT .010A	6.3/1A, 2.5VCT/7A	3.25
CT-403	350VCT .026A	5V/3A	2.75
CT-931	585VCT .086A	5V/3A, 6.3V/6A	4.25
CT-456	350VCT 30 MA	6.3V/1.3A, 5V/3A	3.45
CT-160	800VCT 100 MA	6.3V/1.2A, 5V/3A	4.95
CT-931	585VCT 86 MA	5V/3A, 6.3V/6A	4.99
CT-442	525VCT 75 MA	5V 2A, 10VCT 2A, 50V/200 MA	3.85
CT-720	550-0-550V/250 MA, 6.3V/1.8A		8.95
CT-43A	600-0-600V/.08A, 2.6VCT 6A, 2.6VCT 1A		6.49
CT7-501	650VCT/200MA, 6.3V/6A, 6.3V/5A		5.49
CT-444	230-0-230V/.085A, 5V/3A, 6V/2.5A		3.49

Filament Transformers—115V50-60 cps Input

ITEM	Rating	Each
FT-38A	6.3V/2.5A, 2.5V/7A, 2.5V/7A, 7500 VDC Test	$3.45
FT-674	6.1V 1.5A	1.10
FT-157	4V/16A, 2.5V/1.75A	2.95
FT-101	6V/.25A	.79
FT-924	5.25V/21A, 2x7.75V/6.5A	14.95
FT-824	2x26V/2.5A, 16V/1A, 7.2V 7A, 6.4V 10A, 6.4V/2A	8.95
FT-468	6.3VCT 1A, 5VCT 3A, 5VCT 3A	5.49
FT-55-2	7.2V/21.5A,6.5V/6.85A,5V/6A,5V/3A	9.95
FT-986	16V @ 4.5A or 12V @ 4.5A	3.75
FT-A27	2.5V/2.5A, 7V/7A, TAP 2.5V@2.5A, 16KV Test	18.95
FT-608	6.3V/3A 750 Test	1.79
FT-873	4.5V/5A, 7V/7A	2.19
FT-899	2x5V A 5A, 29kV Test	24.50

INTERPHONE AMPLIFIER

Easily converted to an ideal Inter-Communications set for office, home or factory. Original. New w/conversion diagram **$4.75**

DYNAMOTORS

Type	Input Volts	Input Amps	Output Volts	Output Amps	Radio Set
PE86	28	1.25	250	.060	RC 36
DM41B	14	6.2	330	.170	RU 19
DM13A	28	7	540	.250	BC 456
PE101C	13/26	12.6	400	.135	SCR 515
		6.3	800	.020	
BD AR 93	28	3.25	375	.150	
23350	27	1.75	285	.075	APN-1
ZAO515	12/24	4.2	500	.050	
B-19 pack	12	9.4	275	.110	MARK II
			500	.050	
B-104	12		225	.100	
			440	.200	
BA-3A	28	10	300	.060	SCR 522
			150	.010	
			14.5	.5	
5053	28	1.4	250	.060	APN-1
PE73CM	28	19	1000	.350	BC 375
CW21AAX	13	12.6	400	.135	
	26	6.3	800	.020	
			9	1.12	
PE94	28	10	300	.300	SCR 522
			150	.101	
			14.5	.5	

INVERTERS

PE-218-N: Input: 23/28 vdc, 92 amp. Output: 115 v, 350/900 cy 1500 volt-amperes. New . . . $44.50

PE-206: Input: 28 vdc, 38 amps. Output: 80 v 800-cy, 900 volt-amps. Dim: 13"x5½"x10½". New . . . $22.50

LELAND No. 10536: IN: 28 VDC, 12A. OUT: 115V, 115VA, 400 CY 3 PHASE. EXC. COND . . . $70.00

Send M.O. or Check. Shipping Chgs. C.O.D.

COMMUNICATIONS EQUIPMENT CO.

131 Liberty St. Dept. N-5 New York City 7, N. Y.

A NOISE LIMITER DELUXE

By **J. J. HOEFER, WØIIJ**

A further improvement on recent designs, this compound full-wave noise limiter promises advanced performance.

WITH hundreds of new mobile rigs being installed each year, noise limiting is of increasing importance. One circuit recently described was that of the full-wave limiter circuit [1], which is used in at least one commercial receiver. However, slight changes will improve the limiting action.

The most that can be hoped for in a simple noise limiter is to prevent noise peaks from exceeding audio peaks, regardless of percentage of modulation. More clipping will result in flattening the audio peaks, distorting the sound. Noise silencers may succeed in reducing noise peaks to zero, but only with the addition of amplifiers and complicated circuitry, requiring more current from the overworked battery of a mobile installation.

The full-wave limiter is shown in Fig. 1A. The potentiometer resistance is such that the limiting may be adjusted for modulation percentages of 100 at *B* to 33⅓ at *A*.

In actual practice the potentiometer may be set for as much limiting as needed, fidelity being sacrificed to intelligibility.

Both diodes will be conducting if any negative voltage is developed at *A* by the second detector. Let us assume minus 12 volts d.c. developed at *A* by an unmodulated carrier. The voltages at *C* and *D* will then be minus 8 and minus 4 volts with respect to ground. If the potentiometer is set to *B* and the carrier modulated 100%, an 8-volt peak-to-peak voltage appears at *B*. The voltage at *D* will thus be swinging from 0 to minus 8 volts. Any additional negative swing, such as from a noise pulse, merely causes diode 1 to open and the noise is not passed. Any additional positive swing causes diode 2 to open, with the noise not being passed.

For a lower-percentage modulated signal the potentiometer is set nearer *A*. This increases the amount of audio, and again 8 volts peak-to-peak is applied at *D*. The output signal and noise are both attenuated in the voltage divider composed of diode 1 and,the 470,000 ohm resistor between *C* and *D*, section *X*, Fig. 1B. Under signal conditions the diode conducts, and the diode resistance is its forward resistance of approximately 200 ohms. Essentially all of the signal is passed (Section *Y*, Fig. 1B). With strong negative noise pulses present, the diode does not conduct and the diode resistance is its back resistance. This may be on the order of 500 megohms or higher. The noise is very greatly attenuated (Section *Z*, Fig. 1B).

Similar considerations exist for diode 2 and the 1-megohm resistor in the output of the limiter for positive noises pulses.

A vacuum diode is a necessity in this circuit for the above reasons. However, space limitations in existing car receivers may preclude the addition of another tube to the chassis. Additional battery drain is also a factor.

The final circuit, as shown in Fig. 2A, overcomes these difficulties. The only change from Fig. 1 is that two resistors have been replaced by diodes. This circuit is now a full-wave compound limiter. Diode 3 is normally non-conducting and a biasing voltage is applied through its back resistance of 500,000 ohms to the cathodes of diodes 1 and 2.

As in Fig. 1 the output signal and noise are both attenuated in a voltage divider now composed of diodes 1 and 3 (Section *X*, Fig. 2B). Under signal conditions diode 1 conducts and essentially all of the signal is passed

Fig. 1. (A) The full-wave limiter. (B) Attenuation network: basic circuit. X: diode conducting. Y: diode non-conducting. Z.

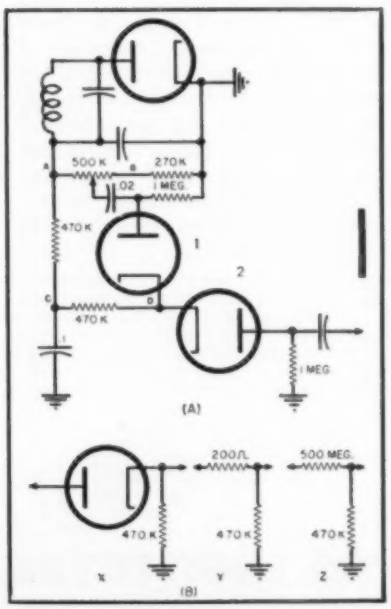

Get the jump on VHF, UHF service needs

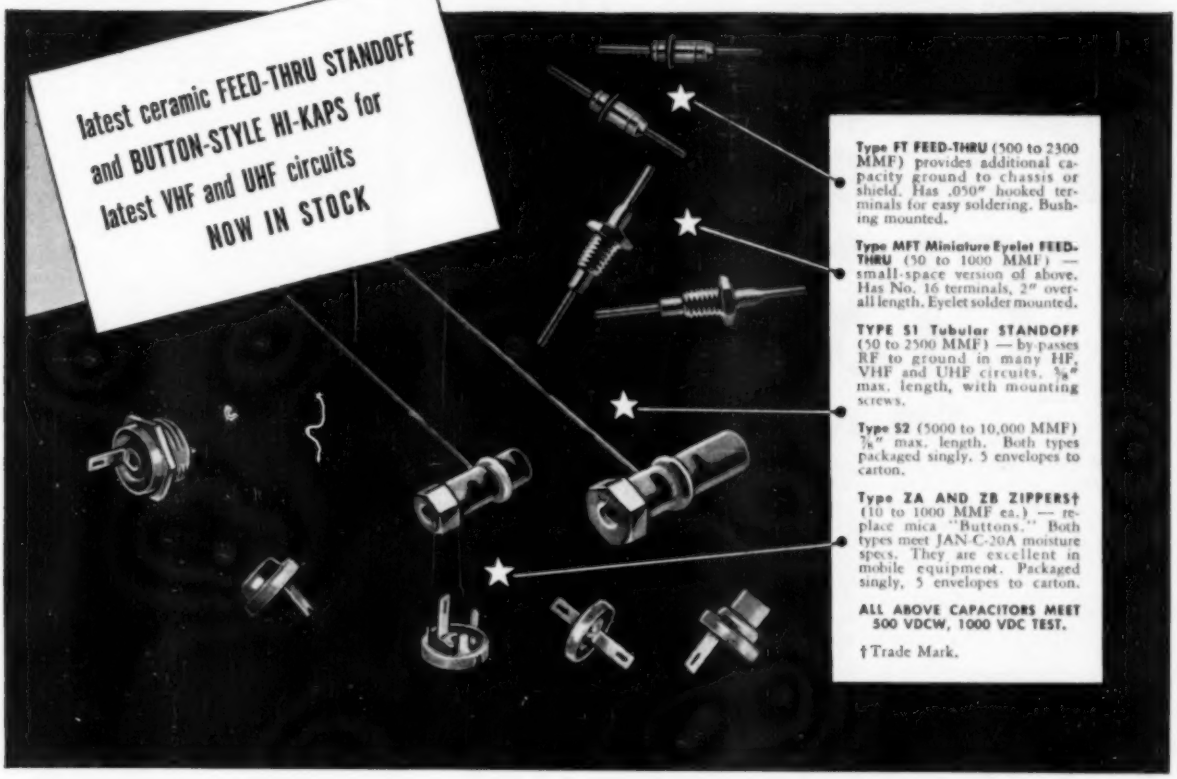
latest ceramic FEED-THRU STANDOFF
and BUTTON-STYLE HI-KAPS for
latest VHF and UHF circuits
NOW IN STOCK
Type FT FEED-THRU (500 to 2300 MMF) provides additional capacity ground to chassis or shield. Has .050" hooked terminals for easy soldering. Bushing mounted.
Type MFT Miniature Eyelet FEED-THRU (50 to 1000 MMF) — small-space version of above. Has No. 16 terminals, 2" overall length. Eyelet solder mounted.
TYPE S1 Tubular STANDOFF (50 to 2500 MMF) — by-passes RF to ground in many HF, VHF and UHF circuits. 5/8" max. length, with mounting screws.
Type S2 (5000 to 10,000 MMF) 7/8" max. length. Both types packaged singly, 5 envelopes to carton.
Type ZA AND ZB ZIPPERS† (10 to 1000 MMF ea.) — replace mica "Buttons." Both types meet JAN-C-20A moisture specs. They are excellent in mobile equipment. Packaged singly, 5 envelopes to carton.
ALL ABOVE CAPACITORS MEET 500 VDCW, 1000 VDC TEST.
† Trade Mark.

Keep plenty of these new Centralab capacitors on hand

TAKE a *good look* at these NEW Centralab Ceramic Capacitors. Chances are you'll be meeting a lot of them — soon. Why? Because these miniature Feed-Thru, Standoff and Button-Style (Zippers) Hi-Kaps are as up to date as the newest VHF and UHF circuits. And, in many cases, they're *actual replacements* for a vast majority of popular make sets. You'll find them simpler to install, mechanically stronger and longer lived than ordinary old-style capacitors. They have all the features you need to maintain customer satisfaction. What's more, they offer all the advantages of famous Centralab ceramic construction.

Helping you get the jump on this replacement business is another example of the close coordination between Centralab and you Service Engineers. One more reason why it pays to specify Centralab products every time. Remember, it's good business to be first with the *newest!* For full details, see your Centralab jobber, or use the coupon.

Why it pays to install Centralab Ceramic Capacitors

- ✓ **Highest dependability** — lasting permanence
- ✓ **Smaller** — ½ the size of ordinary capacitors
- ✓ **Impervious to moisture** — absorption .007 or less
- ✓ **Maintain capacity** — even at 80° C plus
- ✓ **Low power factor**
- ✓ **High accuracy** — exceptionally close tolerances
- ✓ **Exact temperature compensating qualities** where required.

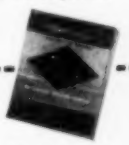

CENTRALAB, A Division of Globe-Union Inc.
910 E. Keefe Ave., Milwaukee 1, Wisconsin

I'd like a copy of Centralab's newest catalog No. 28, giving complete data on Types FT and MFT — S1 and S2 — ZA and ZB, plus other Centralab electronic components.

Name..... Position.....

Company.....

Address.....

City..... Zone..... State.....

Centralab

A DIVISION OF GLOBE-UNION INC.
Milwaukee 1, Wisconsin
In Canada, 635 Queen Street East, Toronto, Ontario

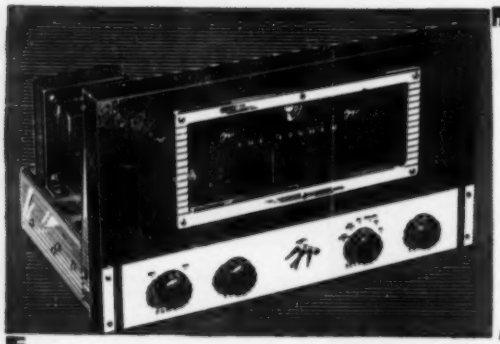

IT'S HERE!

IT'S THE BEST!

MODEL 50-R

FISHER

FM-AM TUNER

■ We haven't the space here to give you *all* the details on the new FISHER 50-R. However, we *can* tell you *there is no other like it*, anywhere, and at any price! FEATURES IN BRIEF: Armstrong system, dual limiters, two IF stages, cascode RF stage, full limiting even on only 1 microvolt signal. Sensitivity, 2 microvolts for 30 db of quieting. AFC on switch and adjustable for locality. *Adjustable selectivity* on AM. Separate AM and FM front ends, fully shock-mounted. Response uniform, 20 to 20,000 cycles. Distortion less than 0.04% for 1 volt output. Hum level more than 100 db below two volts output. Cathode follower output. Fully shielded; bottom cover, Aluminum chassis. 12 tubes plus tuning eye and rectifier. **$159.50**

"The very best!" —HIGH FIDELITY MAGAZINE

FISHER PREAMPLIFIER EQUALIZER

■ "Either of these two units is of the very best," says *High Fidelity Magazine* of the FISHER 50-C Master Audio Control and 50-A Amplifier. The 50-C can be used with *any* amplifier. Intermodulation distortion is virtually unmeasurable. Complete phono equalization, loudness control, 5 inputs, 5 input level controls, cathode follower outputs. Self-powered.

Chassis, **$89.50**
With cabinet, **$97.50**

FISHER 40-WATT AMPLIFIER

■ THE FISHER Laboratory Standard Amplifier Model 50-A is, beyond a shadow of a doubt, *the world's finest all-triode amplifier*—and yet moderately priced. FEATURES: High output—less than .3% harmonic distortion at 40 watts (.08% at 10 watts.) Intermodulation distortion below .8% at 40 watts. Uniform response within .1 db, 20-20,000 cycles; 1 db, 5 to 100,000 cycles. Hum and noise more than 96 db below full output. Quality components and beautiful workmanship throughout. **$159.50**

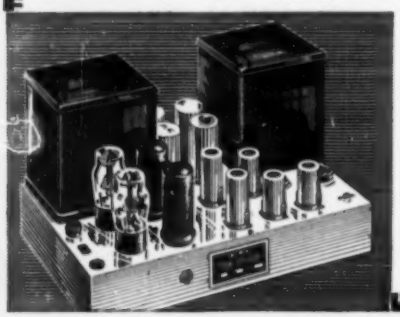

Write for illustrated brochure

FISHER RADIO CORPORATION
39 EAST 47th STREET • NEW YORK

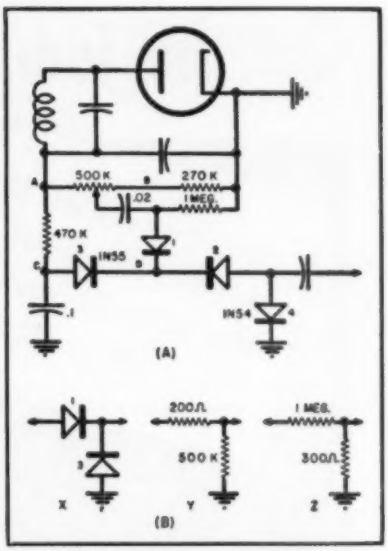

Fig. 2. (A) The full-wave compound limiter. (B) Attenuation network: basic circuit. X: signal conditions. Y: noise conditions. Z.

(Section *Y*, Fig. 2B). With strong negative noise pulses present, only diode 3 conducts (Section Z, Fig. 2B) and the noise is even more greatly attenuated than in section Z, Fig. 1B.

The action of diodes 2 and 4 is similar for positive noise pulses.

As diodes 3 and 4 have special characteristics only those specified will allow proper operation. Diodes 1 and 2 may be any of a number of different types including 1N54 and 1N55. The 1N54 is preferred as it is a high back resistance type.

It is recommended that the audio detector be replaced by a crystal diode. This eliminates noise leaking around the limiter through interelectrode capacities of the tube. Conventional duo-diode triode tubes simply won't keep the noise where it belongs, and the limiter cannot do its job properly.

The effectiveness of a compound limiter has been demonstrated [2], and it is logical to conclude that the full-wave compound limiter represents the ultimate. All that is needed now is a device to automatically set the potentiometer!

Besides its sheer effectiveness, the full-wave compound limiter offers the advantages of remarkable simplicity and negligible battery drain. Some experimenters may, of course, want to adapt this circuit to the home station receiver, especially in some urban locations where a vast "symphony" of noise, with crescendos and all, seems to be played 'round the clock.

Credit is due W9EDB for the initial design and for timely suggestions during the preparation of this article.

REFERENCES

[1] *Grenfell, W. S.; "A Noise Limiter for Everyone," CQ, August, 1952.*
[2] *Moses, R. C.; "Impulse Noise Limiters," Radio & Television News, REE Edition, June, 1951.*

-30-

BUILD YOUR OWN

Heathkits

- TEST INSTRUMENTS
- AMPLIFIERS
- RECEIVERS, etc.

1. Save by ordering direct from manufacturer.
2. All high quality standard band components
3. Increased knowledge through actual construction
4. Sound engineering insures excellent performance
5. Kit construction is fascinating and enjoyable

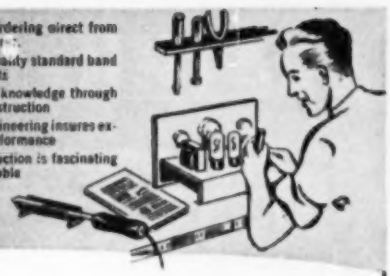

Heathkit MODEL O-8
OSCILLOSCOPE KIT

$43.50
Shipping Wt. 26 lbs.

The outstanding new 1953 model O-8 Heathkit Oscilloscope features the finest performance ever offered in this extremely popular kit instrument. Primarily intended as a general purpose oscilloscope for the faithful reproduction of actual wave forms and other electrical phenomena, it's vastly improved band width, good 100 KC square wave reproduction, three step vertical input attentuator, .025 volts per inch vertical sensitivity, etc., admirably qualify this instrument for TV and radio servicing, laboratory use, ham application and all general electronic development work. Improved vertical band width is obtained through the use of shunt peaking chokes with proper cathode compensation in the push-pull output stage. For additional flexibility of operation, provisions have been made for direct connections to the deflection plates, a Z axis input and a spot shape control for really fine focusing.

This beautiful kit is complete with all 10 tubes, including a 5" cathode ray tube, calibrated graph screen and flexible test leads. All necessary construction components, such as hardware, chassis, transformer, etc., and a detailed step by step construction manual, greatly simplify the assembly of this instrument.

Heathkit
VOLTAGE CALIBRATOR KIT

The use of a Voltage Calibrator will greatly increase oscilloscope usefulness. Provides a convenient method of making peak to peak voltage measurements by establishing a relationship between the unknown wave shape and the Voltage Calibrator. Voltage ranges .01-100 volts peak to peak. The Voltage Calibrator features direct reading scales and a regulated power supply system.

MODEL VC-2
$11.50
Shipping Wt. 4 lbs.

Heathkit
ELECTRONIC SWITCH KIT

The Heathkit Electronic Switch Kit will further extend scope usefulness by permitting simultaneous observation of two individually controlled traces. Continuously variable switching rates 10 cps to 2,000 cps in three ranges. Will also serve as a square wave generator over the range of switching frequencies.

MODEL S-2
$19.50
Shipping Wt. 11 lbs.

Heathkit VACUUM TUBE
VOLTMETER KIT

The beautiful new 1953 Heathkit Model V-6 VTVM, the world's most popular kit instrument, now offers many outstanding new features in addition to retaining all of the refinements developed and proven through the production of over 70,000 VTVM kits. The Heathkit VTVM now features extended voltage ranges with 50% greater coverage on the DC range. New 1½ volt low scale provides well over 2½ inches of scale length per volt permitting faster measurements with greater accuracy. AC and DC ranges are 0-1.5-5-15-50-150-500-1500 volts (1,000 volts maximum on AC). Ohmmeter ranges are X1, X10, X100, X1,000, X10K, X100K X1 meg. Measures .1 ohm to 1,000 megohms. Other features are db scale, center scale zero adjust and polarity reversal switch. High 11 megohm input resistance virtually eliminates circuit loading.

The low anti-inflation price of this tremendously popular kit includes all tubes, necessary constructional material, test leads and the construction manual.

MODEL V-6
$24.50
Shipping Wt. 6 lbs.

Heathkit AC VACUUM TUBE
VOLTMETER KIT

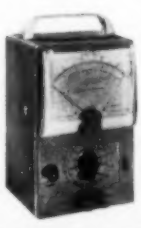

MODEL AV-2
$29.50
Shipping Wt. 5 lbs.

A new amplifier type AC VTVM that makes possible those sentitive measurements so essential in laboratory or audio work. Ten voltage ranges covering from .01 RMS full scale to 300 volts RMS full scale. Input impedance 1 megohm with frequency response 20-50,000 cycles. Ten DB ranges from −52 to +52 DB. Four diodes in meter bridge circuit for maximum linearity.

Heathkit
HANDITESTER KIT

MODEL M-1
$13.50
Shipping Wt. 3 lbs.

The ever popular Handitester is now supplied with a Simpson 400 microampere meter movement. Provides AC and DC voltage ranges 0-10-30-300-1,000-5,000 volts. Ohmmeter ranges 0-3,000 and 0-300,000 ohms. DC current measurements 0-10 and 0-100 milliamperes. A completely self contained portable instrument.

HEATH COMPANY · Benton Harbor 15, Mich.

HEATHKITS for the ENGINEER

Heathkit VISUAL AURAL SIGNAL TRACER KIT

MODEL T-3

$22.50 *

Shipping Wt. 10 lbs.

Designed especially for service applications in AM-SW-FM-TV repair work. RF and audio two channel input. More than adequate sensitivity—new noise locator circuit—calibrated wattmeter—substitution speaker—visual signal indication. Can be used with scope and VTVM, checks phono cartridges, phono mechanisms, microphones, tuners, etc. Let the Heathkit Visual Aural Signal Tracer help you.

Heathkit RESISTANCE SUBSTITUTION BOX KIT

Choice of 36 switch selected resistance values 15 ohms to 10 megohms. All standard RTMA 1 watt 10% resistors. Buy several for those lab and service applications.

MODEL RS-1

Ship. Wt. 2 lbs.

$5.50

Heathkit CONDENSER CHECKER KIT

An instrument designed solely for its particular job. Not a "sideline" of a multiple function instrument. Measures value and quality of unknown condensers and resistors. Capacity range .00001 mfd to 1,000 mfd. Resistance range 100 ohms to 5 megohms. Sensitive electron beam indicator—five polarizing test voltages—safety spring return leakage test switch. An amazingly accurate instrument at this low price.

MODEL C-3

$19.50 *

Shipping Wt. 8 lbs.

Heathkit AMATEUR TRANSMITTER KIT

MODEL AT-1

$29.50 *

Shipping Wt. 15 lbs.

Here is the long awaited Heathkit entry into the amateur radio field. The Heathkit AT-1 Transmitter kit is a well designed basic transmitter incorporating many desirable features and providing maximum overall performance.

Convenient band switching eliminates the bother and annoyance of plug in coils. It is merely necessary to switch to the desired frequency and plug in your favorite crystal or VFO. This transmitter features a self-contained power supply mounted on the same chassis and cabinet enclosed to minimize TVI. AC line by-passed to reduce radiation.

The coils supplied with the Heathkit AT-1 are pre-wound and adjusted for the necessary frequency coverage of 80-40-20-10 meters. The entire kit is supplied complete with all tubes, coils, punched and formed chassis and cabinet, as well as all constructional material required. A detailed assembly and operation manual is also furnished.

Heathkit SIGNAL GENERATOR KIT

MODEL SG-7

$19.50 *

Ship. Wt. 8 Lbs.

A service "must" is a reliable source of modulated (400 cycles) or unmodulated RF output. Frequency range 150 KC to 150 MC. Step attenuated and variable output—internal or external modulation. High output level and performance with low cost.

Heathkit GRID DIP METER KIT

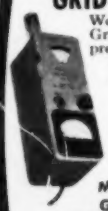

World's largest selling Grid Dip Meter. Five pre-wound coils—frequency coverage 2-250 mc. Simplified construction and operation

MODEL GD-1A

$19.50 *

Ship. Wt. 4 Lbs.

Heathkit TUBE CHECKER KIT

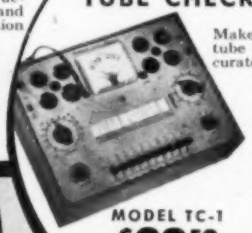

Make those all important tube tests quickly and accurately. Checks all tube types encountered in radio and TV work. Simplified setup and switching system provides fast checks for shorts, opens, individual elements and over-all quality. Portable cabinet available at slight additional cost. TV picture tube adapter also available. See order blank.

MODEL TC-1

$29.50 *

Shipping Wt. 12 lbs.

Revised Roll Chart .50

Heathkit SQUARE WAVE GENERATOR KIT

MODEL SQ-1

$29.50 * Ship. Wt. 12 lbs.

True square wave output with frequency range 10 cycles to 100 KC. High variable output voltage level 0-20 volts at 600 ohms output impedance. Provisions for external synchronization. The ideal instrument for TV service work and wide band amplifier circuit development.

Heathkit LABORATORY REGULATED POWER SUPPLY KIT

MODEL PS-2

$29.50 *

Ship. Wt. 17 Lbs.

A regulated variable 160-450 volt DC output power supply for the lab or service shop. Accurate voltage and current measurements with large Simpson meter. AC supply 6.3 volts at 4 amperes—standby switch eliminates warmup time. Low hum content—5 tube circuit. AC and DC output voltages isolated from panel for maximum operational flexibility.

Heathkit VIBRATOR TESTER KIT

Checks for starting and quality of interrupter and self rectifier type vibrators. Five sockets—checks hundreds of types. Operates from continuously variable type battery eliminator.

MODEL VT-1

$14.50 *

Shipping Wt. 6 lbs.

HEATH COMPANY · Benton Harbor 15, Mich.

SERVICEMAN · AMATEUR · STUDENT

Heathkit

IMPEDANCE BRIDGE KIT

Provides choice of Wheatstone, Capacitance Comparison, Maxwell or Hay bridge circuits. Measurement of resistance-capacity-inductance-dissipation factor-storage factor. 1% precision silver mica capacitance standard. ½% precision resistors.

MODEL IB-1B

$69.50

Shipping Wt. 15 lbs.

Heathkit

INTERMODULATION ANALYZER KIT

Intermodulation distortion analysis is one of the most satisfactory methods of checking audio equipment. The IM-1 features two self contained high frequency generators (3,000 and 7,000 cycles) a 60 cycle low frequency source, intermodulation section, AC VTVM, and power supply all in one complete unit. Direct reading IM percentages on 3 calibrated scales 30%—10%—3%.

Shipping Wt. 17 lbs.

MODEL IM-1

$39.50*

Heathkit

AUDIO OSCILLATOR KIT

MODEL AO-1

$24.50

Ship. Wt. 11 lbs.

Features sine or square wave coverage from 20-20,000 cycles in 3 ranges. Variable 10 volt output level at 600 ohms impedance. Thermistor controlled linearity—precision multiplier resistors—distortion less than .6%. An outstanding instrument value at this amazing low price.

Heathkit

DECADE RESISTANCE KIT

MODEL DR-1

$19.50*

Ship. Wt. 4 lbs.

Individual switch selection of twenty 1% precision resistors in 1 ohm steps from 1 to 99,999 ohms. Sturdy ceramic wafer switches featuring silver plated contacts and smooth positive detent action.

Heathkit

Q METER KIT

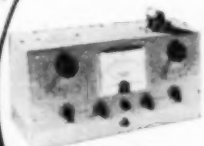

A typical Heathkit invasion of the laboratory instrument field. Here is the first successful low priced Q meter ever offered in kit form. Oscillator supplies RF in the range of 150 KC to 18 mc. Reads Q directly on calibrated meter scales. Measures Q of condensers, RF resistance and distributed capacity of coils. Calibrate capacitor with range of 40 mmf to 450 mmf with vernier ±3 mmf. All measurements made at the operating frequency.

MODEL QM-1

$39.50 Ship. Wt. 14 lbs.

Heathkit

AUDIO FREQUENCY METER KIT

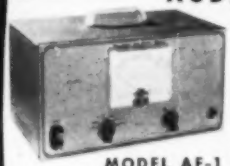

Indicates audio frequency on large 4½" Simpson meter. Ranges 10 cycles to 100 kc at input voltage level of 3-300 volts RMS. The input wave shape is not at all critical. Useful in production line testing—indicating square wave frequency—determining generator output. Operation entirely electronic, no vibrating reeds.

MODEL AF-1

$34.50

Ship. Wt. 12 lbs.

Heathkit

DECADE CONDENSER KIT

Switch selected 1% silver mica precision condensers providing capacity range of 100 mmf. to 0.111 mfd. in steps of 100 mmf.

MODEL DC-1

$16.50

Shipping Wt. 4 lbs.

Heathkit

AUDIO GENERATOR KIT

A new extended range 18 cycles—1 megacycle audio instrument at a remarkably low price. Five continuously variable output ranges—600 ohm output impedance—low distortion figure, less than .4% from 100 cps through audible range.

MODEL AG-8

$29.50

Ship. Wt. 11 lbs.

Heathkit

BAR GENERATOR KIT

MODEL BG-1

$14.50*

Ship. Wt. 6 lbs.

The Heathkit BG-1 Bar Generator represents another welcome addition to the fast growing line of popular Heathkits. The station transmitted test pattern is rapidly disappearing and the Bar Generator is the logical answer to the TV serviceman's problem in obtaining quick accurate adjustment information.

The Bar Generator produces a series of horizontal or vertical bars on the TV screen. These bars are equally spaced and will quickly indicate picture linearity of the receiver under test. Since picture linearity is independent of transmitting frequency, it is unnecessary to provide coverage throughout the VHF range, thereby holding down instrument cost.

The Heathkit Bar generator is simple to use and is extremely portable, providing a quick means of checking the television receiver either in your workshop or in the customer's home.

Heathkit

TELEVISION SWEEP GENERATOR KIT

Frequency coverage 10-90 mc and 150-230 mc. Variable sweep width 0-12 mc, built in absorption type marker, step and continuously variable output and blanking circuit.

MODEL TS-2

Ship. Wt. 20 lbs. **$39.50**

Heathkit

BATTERY ELIMINATOR KIT

A variable 0-8 volt DC supply source rated at 10 amperes continuously and up to 15 amperes intermittently. Voltmeter, ammeter, automatic overload relay, fuse protection—heavy duty Mallory 17 disc rectifier.

MODEL BE-3

Ship. Wt. 17 lbs. **$24.50**

WRITE FOR *Free*

CATALOG

New 32 page 1953 Catalog lists all kits, specifications, schematics and latest price information.

HEATH COMPANY · Benton Harbor 15, Mich.

Heathkit
SUPERHETERODYNE
RECEIVER KITS

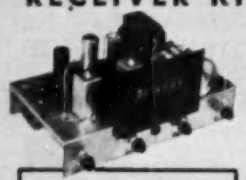

Broadcast Model BR-1 5 Tube-Broadcast Band 550 to 1600 KC coverage. Shipping Weight 11 lbs.
$19.50

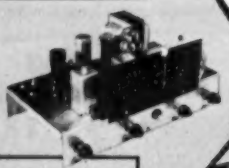

Three Band Model AR-1 6 Tube all wave circuit 3 Ranges, continuous coverage 550 KC to over 20 MC. Shipping Weight 11 lbs.
$23.50

NEW HEATHKIT WILLIAMSON TYPE
AMPLIFIER KIT

The ideal amplifier for custom high fidelity audio installations. Tops in performance, value, and flexibility of operation. Either Altec Lansing Peerless or Acrosound output transformers available. First Williamson type amplifier supplied with a matching preamplifier.

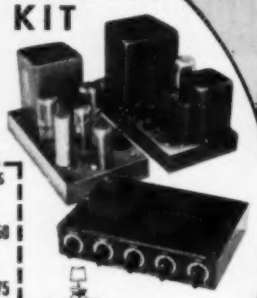

PRICES OF VARIOUS COMBINATIONS

W-2 Amplifier Kit (Incl. Main Amplifier with Peerless Output Transformer, Power Supply and WA-P1 Preamplifier Kit) Shipping Weight 37 lbs. Shipped express only	$69.50
W-2M Amplifier Kit (Incl. Main Amplifier with Peerless Output Transformer and Power Supply) Shipping Weight 29 lbs. Shipped express only	$49.75
W-3 Amplifier Kit (Incl. Main Amplifier with Acrosound Output Transformer, Power supply and WA-P1 Preamplifier Kit) Shipping Weight 37 lbs. Shipped express only	$69.50
W-3M Amplifier Kit (Incl. Main Amplifier with Acrosound Output Transformer and Power Supply) Shipping Weight 29 lbs. Shipped express only	$49.75
WA-P1 Preamplifier Kit only. Shipping Weight 6 lbs. Shipped express or parcel post.	$19.75

Heathkit FM
TUNER KIT

MODEL FM-2
$22.50*
Shipping Wt. 9 lbs.

Sensitive transformer operated 8 tube circuit. Frequency coverage 88–108 mc. Pre-assembled and tuned "front end." Vernier tuning with slide rule type dial.

Heathkit
ECONOMY 6 WATT
AMPLIFIER KIT

MODEL A-7
$14.50*
Ship. Wt. 10 LBS.

Dual inputs—separate bass and treble tone controls—output impedances 4–8–15 ohms.

A-7A ——— Amplifier with pre-amplifier stage for low level inputs... $16.50

Heathkit
HIGH FIDELITY 20 WATT
AMPLIFIER KIT

MODEL A-8
$33.50*
Shipping Wt. 16 lbs.

A high fidelity full 20 watt general purpose amplifier. Dual inputs and separate tone controls for maximum flexibility. Peerless output transformer 4, 8 and 16 ohms.

A-8A with additional preamplifier stage for low level cartridge, microphone, etc. $35.50

HEATH COMPANY · Benton Harbor 15, Mich.

ORDER BLANK

From _____

_____

_____

(PLEASE PRINT)

SHIP VIA
- ☐ Parcel Post
- ☐ Express
- ☐ Freight
- ☐ Best Way

QUANTITY	ITEM	PRICE		QUANTITY	ITEM	PRICE	
	Heathkit Oscilloscope Kit—Model O-8 (26 lbs.)	$43.50			Heathkit Square Wave Generator—Model SQ-1 (12 lbs.)	29.50	
	Heathkit Amateur Transmitter Kit—Model AT-1 (15 lbs.)	29.50			Heathkit AC VTVM Kit-Model AV-2 (5 lbs.)	29.50	
	Heathkit Bar Generator Kit—Model BG-1 (6 lbs.)	14.50			Heathkit Intermodulation Analyzer Kit—Model IM-1 (17 lbs.)	39.50	
	Heathkit Voltage Calibrator Kit Model VC-2 (4 lbs.)	11.50			Heathkit Regulated Power Supply Kit—Model PS-2 (17 lbs.)	29.50	
	Heathkit Electronic Switch Kit—Model S-2 (11 lbs.)	19.50			Heathkit Handitester Kit—Model M-1 (3 lbs.)	13.50	
	Heathkit TV Alignment Generator Kit—Model TS-2 (20 lbs.)	39.50			Heathkit Decade Resistance Kit—Model DR-1 (4 lbs.)	19.50	
	Heathkit Q Meter Kit—Model QM-1 (14 lbs.)	39.50			Heathkit Decade Condenser Kit—Model DC-1 (4 lbs.)	16.50	
	Heathkit Grid Dip Meter Kit—Model GD-1A (4 lbs.)	19.50			Heathkit Impedance Bridge Kit—Model IB-1B (15 lbs.)	69.50	
	Heathkit VTVM Kit—Model V-6 (6 lbs.)	24.50			Heathkit Resistance Substitution Box Kit—Model RS-1 (2 lbs.)	5.50	
	Heathkit Visual-Aural Signal Tracer Kit—Model T-3 (10 lbs.)	22.50			Heathkit F.M. Tuner Kit—Model FM-2 (9 lbs.)	22.50	
	Heathkit Condenser Checker Kit—Model C-3 (8 lbs.)	19.50			Heathkit Broadcast Receiver Kit—Model BR-1 (11 lbs.)	19.50	
	Heathkit RF Signal Generator Kit—Model SG-7 (8 lbs.)	19.50			Heathkit Three Band Receiver Kit—Model AR-1 (11 lbs.)	23.50	
	Heathkit Tube Checker Kit—Model TC-1 (12 lbs.)	29.50			Heathkit Amplifier Kit—Model A-7 (10 lbs.)	14.50	
	Heathkit Portable Tube Checker Kit—Model TC-1P (15 lbs.)	34.50			Heathkit Amplifier Kit—Model A-7A (10 lbs.)	16.50	
	Heathkit Portable Tube Checker Cab. only No. 365 (8 lbs.)	7.50			Heathkit Amplifier Kit—Model A-8 (16 lbs.)	33.50	
	Heathkit TV Tube Adapter No. 355 (1 lb.)	4.50			Heathkit Amplifier Kit—Model A-8A (16 lbs.)	35.50	
	Heathkit Battery Eliminator Kit—Model BE-3 (17 lbs.)	24.50			Williamson Type Amplifier Kit (Type:) Shipped express only		
	Heathkit Vibrator Tester Kit—Model VT-1 (6 lbs.)	14.50			WA-P1 Preamplifier Kit (6 lbs.) (Shipped exp. or p.p.)		
	Heathkit Audio Generator Kit—Model AG-8 (11 lbs.)	29.50					
	Heathkit Audio Oscillator Kit—Model AO-1 (11 lbs.)	24.50					
	Heathkit Audio Frequency Meter Kit—Model AF-1 (12 lbs.)	34.50					

Enclosed find ( ) check ( ) money order for
Please ship C.O.D. ( ) postage enclosed for pounds.

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

ON PARCEL POST ORDERS include postage for weight shown..... ORDERS FROM CANADA must include full remittance for merchandise.

MAKE YOUR OWN U.H.F. CHOKES

By E. J. GAUSS, WØEOS

An ingenious method for winding self-supporting u.h.f. chokes which are light in weight and have high "Q".

WITH increasing interest in v.h.f. and u.h.f. because of TV and other applications, the experimenter or amateur often finds that he needs small, efficient r.f. chokes. For coils whose inductance is sufficient to make the self-supporting method of winding impractical the conventional way has been to use a resistor for a coil form. A resistor of suitable physical size whose resistance was high enough to be ignored was selected. The inductor was then wound on the resistor. Unfortunately it is often difficult to find a proper resistor. Another objection to this method arose in the design of lightweight model airplane radio control equipment. The weight of the resistor seemed unnecessary.

To meet this problem a simple technique for making "air wound" coils was developed. First a smooth rod whose diameter was slightly smaller than the desired inside diameter of the coil was selected. It is necessary that one end of the rod be free of flanges so that the coil may be slipped off later. A very slight taper in the rod is helpful but is not required. The rod is then wrapped with *Scotch* tape with the sticky side out. (See *X* in Fig. 1A.) Only one layer is necessary and it should be wrapped loosely enough so that the resulting tube will slide freely on the rod. The desired coil is then wound. (See *Y* in Fig. 1A.) The ends of the wire may be secured by a small strip of tape. Spaced winding is easy if two wires are wound together and then one is removed; the wire holds its spacing because of the adhering qualities of the *Scotch* tape. Next the whole coil is covered with a layer of tape, this time sticky side down. (See *Z* in Fig. 1A). The coil is then slid off the end of the rod (Fig. 1B) and the edges are trimmed. If the tape is allowed to extend about ⅛ inch beyond the ends of the wire in the coil the top layer may be stuck to the bottom layer at the ends sealing the coil.

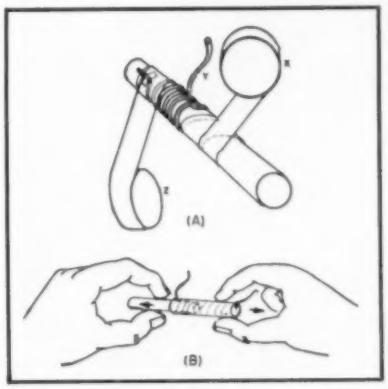

Fig. 1. (A) Steps in preparing rod and winding coil. (B) How coil is removed from rod.

If the coil will not slide off the rod either the wire was wound with too much tension or the first layer of tape was improperly wound. In either case the inductor should be rewound. By using this method anyone should be able to make a good choke in a few minutes with negligible cost for materials.

A one-meter miniature transmitter using isolation chokes of the type described.

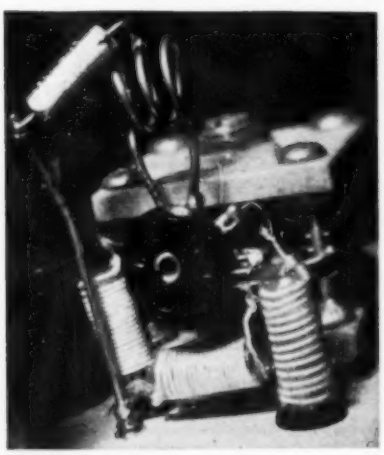

A light weight r.f. amplifier which incorporates the self-supporting chokes.

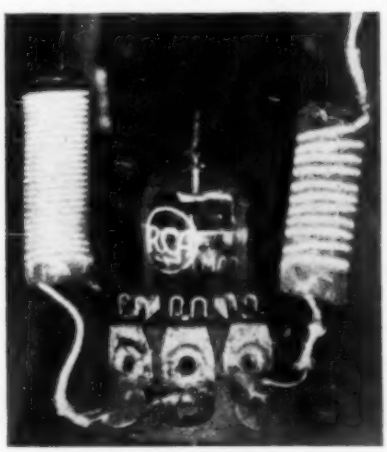

THESE BOOKS HELP YOU EARN MORE IN TV SERVICING

"How to Understand and Use TV Test Instruments"

Provides basic explanations of how each test instrument operates. Covers: VTVoltmeters, AM Signal Generators, Sweep Signal Generators, Oscilloscopes, Video Signal Generators, Field Intensity Meters, Voltage Calibrators. Describes each in detail; explains functions; tells proper use in actual servicing; shows how to avoid improper indications. Helps you get the most from your instruments; saves you time, helps you earn more. 148 pages, 8½ x 11".
ORDER **TN-1**. *Only*.....**$3.00**

"TV Servicing Short-Cuts"

Describes a series of actual TV service case histories, giving step-by-step explanations of how the service technician localized and tracked down each problem. Shows how these frequently recurring troubles can be tracked down and solved in *any* set. Explains how to apply proper time-saving servicing techniques — gives you the successful experience of experts, to make your service work easier, quicker, more profitable. 100 pages, 5½ x 8½".

ORDER **TK-1**. *Only*.....**$1.50**

"Servicing TV in the Customer's Home"

Saves you time, work and chassis-hauling on outside TV service calls. Shows you how to make successful repairs on the spot using these methods: employing VTVM and capacitor probe to trace down trouble; "tube-pulling" to diagnose trouble by observing audio and picture effects; performance tests through analysis of test pattern; adjustment techniques developed for field servicing. Saves time, avoids chassis removal. 96 pages, 5½ x 8½".
ORDER **TC-1**. *Only*.....**$1.50**

"Television Tube Location Guides"

VOL. 3. Shows tube positions and functions in hundreds of important TV sets. Helps save servicing time. Often, looking at the picture or listening to the sound, provides the clue to the trouble. Frequently, a tube failure is the cause. This guide, with its clear, accurate tube placement and function diagrams, makes trouble diagnosis and tube replacement quick and easy, *without removing chassis*. 192 pages. All new diagrams continuing coverage from Vol. 2.
ORDER **TGL-3**. *Only*.....**$2.00**
VOL. 2. Over 200 pages of tube placement diagrams not included in Vols. 1 and 3.
ORDER **TGL-2**. *Only*.....**$2.00**
VOL. 1. Over 200 pages of diagrams not in Vols. 2 and 3. ORDER **TGL-1**. *Only*.....**$1.50**

"Photofact Television Course"

A full, easy-to-understand explanation of TV principles, operation and practice. Covers Cathode Beam Formations and Control, Beam Deflection Systems, Beam Mod. and Synch.; analyzes CR tubes, camera tubes, voltage supplies, saw-tooth generators, sync. circuits, control functions, antenna circuits, RF input tuning, IF systems, AGC, DC restoration, etc.; with full bibliography and glossary. 208 pages, 8½ x 11".
ORDER **TV-1**. *Only*.....**$3.00**

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write direct to Howard W. Sams & Co., Inc. 2203 East 46th Street, Indianapolis 5, Ind.

My (check) (money order) for $..... enclosed. Send the following books:

☐ TN-1 ☐ TK-1 ☐ TC-1
☐ TGL-3 ☐ TGL-2 ☐ TGL-1 ☐ TV-1

Name.....

Address.....

City.....Zone....State.....

NOW at Newark PROFESSIONAL QUALITY TAPE RECORDING AT LOW COST!

THE **New** PENTRON TAPE RECORDER

Use 2 Ways FOR CUSTOM INSTALLATION OR AS A PORTABLE RECORDER

Available at last . . . a high fidelity recorder for the audio connoisseur, unbelievably low priced. Ideal as well for home, school, church or commercial use.

1 — FOR CUSTOM INSTALLATION

Model 9T-3M Tape Mechanism. 2 Speeds: 3.75" and 7.5" per second. 2 hours record-playback time. Super rewind-forward speeds—1200' in 40 seconds. Separate record-erase heads—removable pole, single or dual track. Flutter: ±0.3% at 7.5"—0.5% at 3.75". 74F909. Wt., 10½ lbs. NET 59.75

Model PRE-7 Pre-Amp. Push-pull supersonic bias-erase. Magic eye record level indicator. 5 Tubes. Exclusive oscillator circuit. Frequency response: ± 3 db, 50 to 11,500 cps at 7.5"; ± 3 db, 50 to 6500 cps at 3.75". Outputs: amplifier and headphones. Inputs: radio, phono and mike. 74F924. Wt., 8 lbs. NET 39.75

2 — FOR PORTABLE USE

Model PMC. Complete Portable Unit. Consists of tape mechanism and pre-amp above, in handsome carrying case, complete with reel of tape and take-up reel. Less amplifier, for use with your home music system or radio. 74F925. Wt., 25 lbs. NET 114.50

ALSO AVAILABLE

Model 9T3C. Complete Portable Tape Recorder. With built-in amplifier and speaker. (See Catalog No. 55).

Just Out! NEWARK'S New CATALOG No. 55

FREE! *196 Pages of the Latest Releases in Radio, TV, Industrial Electronics and High Fidelity.*

NEWARK ELECTRIC COMPANY

Department R-5
223 W. MADISON STREET
CHICAGO 6, ILLINOIS

ANOTHER OUTSTANDING JOBBER
GEO. D. BARBEY CO. Inc.
Lebanon, Pa. Reading, Pa.
Pottstown, Pa. Lancaster, Pa.

HAS THE SENSATIONAL NEW EICO 470-K 7" SCOPE KIT IN STOCK!

$79.95

AC-DC MUSIC AMPLIFIER

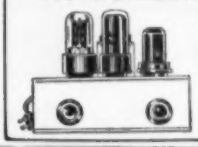

Volume and tone control.
1.5 w. output.
See your jobber.
MICHEL MFG. CO.
227 N. Water St.
Milwaukee 2, Wis.

Build Your Own Interior - Styled Cabinets

KITS by Cabinart

now available in select 5/8" white pine wood cut to size—takes a beautiful blond or mahogany finish

BASS REFLEX AND EQUIPMENT CABINETS

Ideal housing for hi-fi components . . . removable panels make future changes easier. Loudspeaker cabinet acoustically-designed for either 12" or 15" speaker.

Overall dimensions 33½", 23", 16"
Tuner Compartment: 20"H, 21¼" W, (inside dimensions) 15¼" D
Baffle volume 6 cubic feet

#80 ... 27.00* (equipment kit)
#8112 ... 18.00* (12" speaker)
#8115 ... 18.00* (15" speaker)

Corner Folded Horn Enclosures

Reproduces a quality of bass heretofore only possible through the use of far more expensive designs.

Baffle pre-cut for 12" or 15" speaker, Saran Plastic Acousticloth, Kimsul Acoustic Insulation, Assembly and finishing instructions, hardware, plastic wood, sandpaper and glue

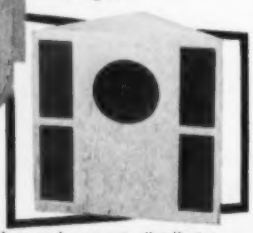

*Net prices, slightly higher West and South. Sold only thru parts distributors.

#61 (12" speaker) ... 19.95*
#63 (15" speaker) ... 23.95*

Write for free catalog and nearest distributor

G & H WOOD PRODUCTS COMPANY - 75 NORTH 11th STREET - BROOKLYN 11, N. Y.
Pioneers in radio furniture for high fidelity equipment.

Semi-quantitative tests were run to determine the relative "*Q*" of bare copper coils wound using this method. The comparison was made to self-supporting bare copper wire coils and similar coils wound on resistors. The results showed that the self-supporting coils had the highest "*Q*," closely followed by the cellophane-tape types. Poorest was the resistor - mounted style. —30—

OSCILLATOR BOOSTER FOR BATTERY SUPERHETS

By CHARLES ERWIN COHN

IN most battery superhets the oscillator is the most troublesome circuit, as it is in other sets as well. Many times a weak battery or tube will cause the oscillator to stop functioning, when the rest of the set is still operating normally, and force a premature replacement. This is especially bad if the set has short-wave bands.

This trouble can be overcome in the design of a new set by incorporating an oscillator booster tube, as shown in Fig. 1. The grid and plate of the booster tube (in this case a 1G6) are merely connected to the oscillator grid and anode respectively. Almost any tube is suitable for this purpose. A 1G4 single triode is good, or any r.f. pentode such as the 1N5 connected as a triode. Power output pentodes or beam tubes such as the 1A5 or 1C5 should not be used, as they will draw excessive plate current, being operated with zero bias.

The advantage of this hookup over using the tube as a separate local oscillator and the converter tube as a mere mixer is that the oscillator power obtained is that of the converter and the booster tube combined. For example, on the author's set neither the 1A7 nor the 1G6 alone would oscillate on the low end of the 7 to 15 megacycle band, but with both together in this hookup a strong oscillation was obtained. In sets using the 1R5 converter, the plate of the booster tube should be connected to the screen or wherever the plate winding of the oscillator coil goes. Most battery converter tubes use large grid leaks and instability might be noticed on the high end of a tuning range. In such a case, merely reduce the size of the grid leak until the instability is removed.

The application of this circuit will have two beneficial effects. First, it will provide considerable improvement in the performance of the set in those ranges where oscillation is weak or absent. Second, it will enable the oscillator to operate with lower battery voltages or tube emissions, and thus permit longer tube and battery life. —30—

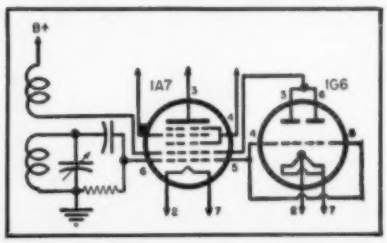

Fig. 1. Using a 1G6 as an oscillator booster. Many other battery-operated tubes will work in a similar circuit.

Here's how to increase your Auto Radio Repair Business!

There's one sure way to get ahead in the car radio repair business, and that's to be in a position to tap the vast market of Delco Radio-equipped cars and trucks that daily passes your door! To do this you need only sign up with Delco Radio, through your United Motors Electronics Distributor. Then, automatically, you have a reliable source for Delco Radio original equipment replacement parts, and for universal replacement parts. You will receive a complete and comprehensive Delco Radio Service Manual. You will regularly receive monthly issues of "Testing Tips," a bulletin giving the very latest factory information on testing and repairing Delco car radios. So if you want to increase your business—permanently—get on the Delco Radio team. Don't delay . . . contact your United Motors Electronics Distributor right away!

DISTRIBUTED BY ELECTRONICS WHOLESALERS EVERYWHERE

DELCO RADIO

DIVISION OF GENERAL MOTORS CORPORATION, KOKOMO, INDIANA

A GENERAL MOTORS PRODUCT — A UNITED MOTORS LINE

DELCO RADIO

COMPETITORS*

Team Up to Bring You One Great Electronics Firm Geared for Greater Values!

LOOK AT THESE BUYS!

TV CERAMIC CONDENSERS!

$10 Value • $1 Postpaid

Kit of 50 asstd. (25 mmf to .001 mfd) Brand new, standard brands; over half are temperature compensated.

PROP-PITCH MOTORS, NEW **$17.95**

See Feb. Radio-TV News page 66

MICRO SWITCHES, new **29c** ea. **4** for **$1**

Special Value Combination!

954 ACORN TUBES & SOCKETS

Brand New **29c** per set or buy **4** sets **$1**

LOOKING FOR RADAR EQUIPMENT?*

*parts also available

APS-3	SA	TPN-2
APS-4	AN/PPN1	APQ-13
APT-5	AN/PPN2	APS-15
SN	ARQ-8	APA-17

METER SPECIAL! 0-1 MA METER 2" round, new, boxed $3.95

ARC-4 complete with tubes, less dynamotor. Excellent condition $29.50

LIP MICROPHONES, MC-419, brand new .98

TUNING KNOBS FOR BC-454 and all Command Receivers, shipped ppd. ... ea. .59

RL-42B ANTENNA REEL MOTOR assembly. Brand new. Boxed. Quantity Available.

TELEPHONE HANDSET HANGERS, postpaid $1.98

ORDER WHAT YOU NEED!

Large Quantities Available*

*BK 22-ADF Relay Assembly $3.59

*ART-13 Band Change Motor 6.95

*BK35 Plate Circuit Relay 3.95

*QIA/3 2 & 5 ohm 100 w. Rheostat Assemblies ..... .98

PRICED FOR QUICK SALES!

SCR-284
MAB Walkie Talkies
BC-949A Range Calbrtrs.
BC-736B Interf. Red'cers.
BC-978A Trsg. Transmitters
BC-1203A Pulse Generators
BC-1212A Coupling Heads
JB-87A Radar Junct. Box
Wilcox 602A VHF Receivers

THESE HARD-TO-FIND ITEMS IN STOCK!

Parts & Equipment Available

BC-348	BC-342	ART-13
ARC-3	APN-9	LM
BC-221	BC-611	ARC-1

Attn: Schools, Labs, Hams!

WE PAY MORE

for Radio Parts & Equipment

Cash in on your surplus equipment—or we'll trade for something you really need. Write today! Available for TRADE—TV SETS, MOBILE EQUIPMENT!

Write for New Free Surplus Catalog!

HARJO SALES CO.

*Formerly CANDEE-AIRCO combined with ALVARADIO SUPPLY CO.

4109 BURBANK BLVD.,
P.O. Box 1187 Magnolia Park Station
BURBANK, CALIFORNIA

CABLE ADDRESS: HARJO Phone: ROckwell 9-2411

NEW TV STATIONS ON THE AIR

(As of April 5, 1953)

STATE, CITY	STATION	CHANNEL	FREQUENCY RANGE (IN MC.)	VIDEO WAVELENGTH (IN FT.)	VIDEO POWER* (IN KW.)
Alabama					
Mobile	WALA-TV	10	192-198	5.08	316
	WKAB-TV	48	674-680	1.45	270
Montgomery	WCOV-TV	20	506-512	1.94	88
Arizona					
Mesa	KTYL-TV	12	204-210	4.79	26.9
Tucson	KOPO-TV	13	210-216	4.65	316
	KVOA-TV	4	66-72	14.61	11
Arkansas					
Little Rock	KRTV	17	488-494	2.01	2.1
Colorado					
Colorado Springs	KKTV	11	198-204	4.93	250
Denver	KFEL-TV	2	54-60	17.8	56
	KBTV	9	186-192	5.25	240
Pueblo	KDZA-TV	3	60-66	16.06	16.6
Connecticut					
Bridgeport	WICC-TV	43	644-650	1.52	180
New Britain	WKNB-TV	30	566-572	1.73	20
Illinois					
Peoria	WEEK-TV	43	644-650	1.52	170
Rockford	WTVO	39	620-626	1.58	15.5
Indiana					
South Bend	WSBT-TV	34	590-596	1.66	170
Iowa					
Sioux City	KVTV	9	186-192	5.25	29
Louisiana					
Baton Rouge	WAFB-TV	28	554-560	1.77	216
Maine					
Bangor	WABI-TV	5	76-82	12.74	1.9
Massachusetts					
Holyoke	WHYN-TV	55	716-722	1.37	180
Springfield	WWLP	61	752-758	1.31	150
Michigan					
Ann Arbor	WPAG-TV	20	506-512	1.94	22.5
Mississippi					
Jackson	WJTV	25	536-542	1.83	180
Missouri					
Springfield	KTTS-TV	10	192-198	5.08	12.5
Nebraska					
Lincoln	KOLN-TV	12	204-210	4.79	26.9
New Jersey					
Atlantic City	WFPG-TV	46	662-668	1.48	18
North Carolina					
Asheville	WISE-TV	62	758-764	1.29	23
North Dakota					
Minot	KCJB-TV	13	210-216	4.65	29.5
Ohio					
Lima	WLOK-TV	73	824-830	1.19	20
Youngstown	WKBN-TV	27	548-554	1.79	160
	WFMJ-TV	73	824-830	1.19	175
Oklahoma					
Lawton	KSWO-TV	7	174-180	5.61	10
Oregon					
Portland	KPTV	27	548-554	1.79	88
Pennsylvania					
Altoona	WFBG-TV	10	192-198	5.08	316
Bethlehem	WLEV-TV	51	692-698	1.42	2.25
New Castle	WKST-TV	45	656-662	1.50	20.5
Pittsburgh	WKJF-TV	53	704-710	1.40	13.4
Reading	WHUM-TV	61	752-758	1.31	260
	WEEU-TV	33	584-590	1.68	225
Wilkes-Barre	WBRE-TV	28	554-560	1.77	1000
York	WSBA-TV	43	644-650	1.52	170
South Dakota					
Sioux Falls	KELO-TV	11	198-204	4.93	57
Texas					
Amarillo	KFDA-TV	10	192-198	5.08	56
	KGNC-TV	4	66-72	14.61	100
Austin	KTBC-TV	7	174-180	5.61	109.6
El Paso	KROD-TV	4	66-72	14.61	56.3
	KTSM-TV	9	186-192	5.25	64
Galveston	KGUL-TV	11	198-204	4.93	59
Lubbock	KDUB-TV	13	210-216	4.65	31
Wichita Falls	KFDX-TV	3	60-66	16.06	60
	KWFT-TV	6	82-88	11.8	70.9
Virginia					
Lynchburg	WLVA-TV	13	210-216	4.65	28
Roanoke	WROV-TV	27	548-554	1.79	1
	WSLS-TV	10	192-198	5.08	250
Washington					
Spokane	KHQ-TV	6	82-88	11.8	100
	KXLY-TV	4	66-72	14.61	47.9
Tacoma	KTNT-TV	11	198-204	4.93	29.5
Wisconsin					
Green Bay	WBAY-TV	2	54-60	17.8	100
Hawaii					
Honolulu	KGMB-TV	9	186-192	5.25	35
	KONA	11	198-204	4.93	117

*From Station CP application.
The frequency of the video carrier = 1.25 + channel lower freq. limit.
Total number of television stations now on the air: 166 (25 of which are u.h.f.)

Long Life—Low Maintenance
No Comebacks with the

FOR 50 YEARS Wiremaker for Industry

New 300 OHM TRANSMISSION CABLE by BELDEN

To You, Belden's Golden Anniversary Means

—product performance that can come only from a "know-how" that has grown through actual service since the inception of Radio.

—an ability to co-operate in pioneering new wires to meet or anticipate industry's growing needs.

In the years that follow

This Belden Program Is—

— TO BE CONTINUED

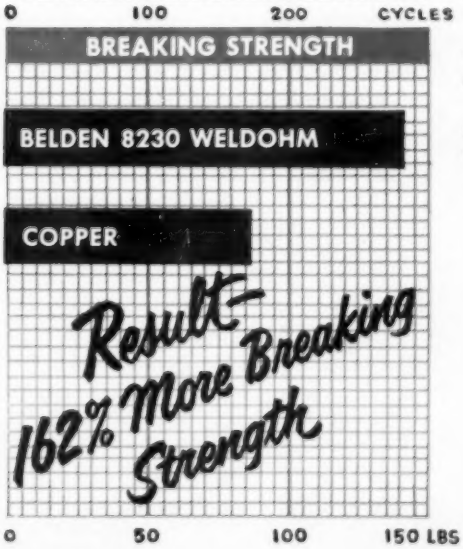

COPPER-SHEATHED 20-GAUGE STRANDED STEEL WIRE

Brown Polyethylene-Resists Weather and Oxidation

The new Belden Weldohm, 300-ohm Transmission Cable is the greatest advancement in television installation since television began.

Reducing TV lead-in conductor breakage to a minimum is easy. The new Belden Weldohm Cable has overcome the breakage point by 162%, that's 1½ times the strength of pure copper wire.

In actual test, Belden Weldohm Cable will withstand 254% more whipping or severe flexing than the average installation of 300-ohm copper lead-in wire.

There is no difference in the electrical characteristics between an all-copper conductor and the Belden Weldohm copper-coated steel wire. The web is 72 mils of 100% virgin polyethylene.

NEW
FOR U.H.F. INSTALLATION
BELDEN ULTRA-WELDOHM — 8235

BELDEN MANUFACTURING CO., 4681 W. Van Buren St., Chicago 44, Illinois

Belden Radio WIRE

AMERICA'S FINEST 28 WATT—50 WATT AND 10 WATT P.A. VALUES

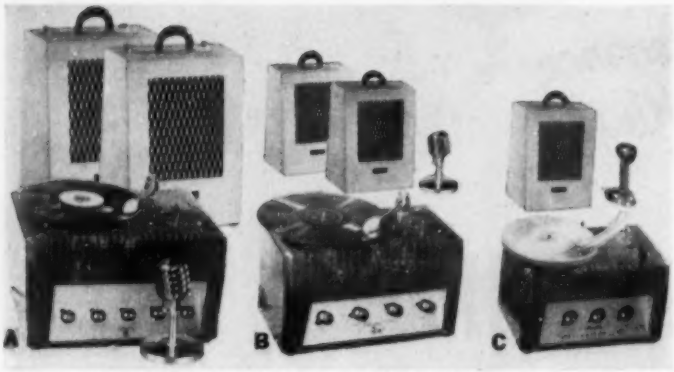

$69.95 BUYS A 28 WATT $150.00 LIST VALUE PORTABLE P.A. SYSTEM

(Illustration B)

3-SPEED PHONO TOP—TWO 12-INCH SPEAKERS
7-TUBES PUSH PULL 6L6'S HEAVY LEATHERETTE COVERED PLYWOOD PORTABLE CASES
CRYSTAL MIKE $8.95 EXTRA

STOCK No. AP-28X. Portable 28 watt public address system. You get a 7-Tube heavy duty push-pull 6L6 amplifier with inputs for 2 mikes either crystal or dynamic with separate mixing volume controls. One phono input. Fully variable tone control high fidelity, wide range frequency response. The heavy duty output transformer has taps for 4, 8, 16, 125, 250 and 500 ohm speaker connections. Two heavy duty 12 inch alnico V P.M. speakers, each with 25 feet of speaker cable. Each speaker is mounted in separate carrying cases. Each case has a snap on back and is large enough to give good speaker baffling. Each case is 21 x 16 x 13 inches. One is used to carry the amplifier. A 3-speed phono motor and pick-up is mounted in the top of the amplifier to play 33⅓, 45 and 78 RPM records.

This portable PA system will put out 20 watts all day long and 28 to 30 watts peak audio. McGee offers you this $150.00 list portable PA system at a terrific saving.

STOCK No. AP-28X complete portable PA system with 3-speed phono and speakers as pictured (less mike; ship. wt. 71 lbs. **$69.95.**

Electro Voice model 910 $28.50 list crystal mike with 20 feet of cable and desk stand **$8.95** extra.

Floor type mike stand instead of desk stand **$4.95** extra.

50-WATT PORTABLE P.A. ON SALE $99.95
3-SPEED PHONO TOP—TWO 12" SPEAKERS

(Illustration A)

10-tube portable 50-watt public address system. 4—6L6G (push-pull parallel) output tubes. Inputs for 2 microphones, either crystal or dynamic, with separate mixing volume controls. Twin bass and treble tone controls. High fidelity wide range output transformer with taps at 4, 8, 16, 125, 250 and 500 ohms. Complete with 2 super heavy duty 12" PM speakers and 25 ft. cables mounted in separate leatherette-covered carrying cases, 21"x21"x13". The amplifier fits in one of the cases for carrying. This amplifier will put out 40 watts all day long and 50 to 60 watts peak with ease. 3-speed turntable and pickup arm to play all records 33⅓, 45 and 78 RPM is mounted in the top of the amplifier. Stock No. AP-66X. 50 watt portable P.A. system similar to the 28-watt model pictured above, less microphone. Sale price, **$99.95.** Shipping weight, 100 lbs. Shipped via Express or Truck only. Regular $45.00 list Electro-Voice 610 dynamic microphone with 20 ft. cable and desk stand, **$11.95** extra. For floor stand instead of desk stand, add **$4.95.**

10-WATT PORTABLE P.A. ON SALE $42.95
3-SPEED PHONO TOP—10" ALNICO PM SPEAKER

(Illustration C)

5-tube portable 10-watt (14-watt peak) public address system. (Push-pull 7C5) U. L. approved amplifier with wide range response. Inputs for microphone and phono, with separate mixing type volume controls. Tone control. 10" Alnico V PM speaker is housed in a leatherette case 21"x16"x13" which holds the amplifier for carrying. 3-speed turntable and pickup arm to play all records 33⅓, 45 and 78 RPM is mounted in the top of the amplifier. List value, $90.00. Stock No. AP-10X. 10-watt portable P.A. system similar to the 28-watt pictured above, except it has only one case and one 10" speaker, less microphone. Sale price, **$42.95.** Shipping weight, 41 lbs. Shipped via Express or Truck only.

Crystal microphone with non-removable desk stand, **$3.95** extra when ordered with the AP-10X portable P.A. system.

BRUSH CRYSTAL EAR PHONE With Control $5.49

Simply clip on to the speaker voice coil of any radio or TV set or to an audio amplifier. No soldering necessary. Listen in privately to your favorite programs. The tiny Brush crystal ear phone fits your ear just like a regular hearing aid ear piece. A small remote control box enables using 20 ft. from the radio or TV set. Has its own separate volume control and small matching transformer built-in to operate the crystal from any speaker voice coil. Ideal for hospitals, homes, hundreds of other uses. 10 times more comfortable to wear than conventional earphones. Stock No. BH-500 includes Brush crystal ear piece, remote control box, 20 ft. of cable and instructions. Sale price, **$5.49** complete. Brush crystal earphone with 36" cord. Stock No. BR-51. **$2.95.** (You connect it like any crystal earphone, diagram furnished.) Accessory kit includes volume control with switch plus coupling capacity and instructions. **99c** extra.

INDIVIDUALLY CARTONED ELECTRONIC RADIO & TV TUBES

McGee offers you a wide selection of good quality TV and Radio tube types. Individually cartoned. Our private brand. These are not set mfg's. culls, but a carefully inspected private line of tubes with a full 6 months' guarantee. Types listed are in stock in good quantity at this time. Thousands sold. Order 50 tubes and take 10% off the listed prices.

0Z4	$0.59	6AT6	.49	6H6GT	.59	7H7	.79
1A7GT	.59	6AU6	.49	6K7GT	.69	7Y4	.69
1B3GT	.79	6AV6	.49	6L6G	1.09	12AL5	.59
1H5GT	.59	6AX4GT	.69	6S4	.59	12AT6	.69
1L4	.59	6BA6	.49	6SA7GT	.89	12AT7	.69
1R5	.59	6BA7	.69	6SH7GT	.59	12AU6	.59
1S5	.59	6BC5	.59	6SF5GT	.59	12AU7	.69
1T4	.59	6BD6	.49	6SK7GT	.59	12AV6	.59
1U4	.59	6BF5	.59	6SL7GT	.69	12AV7	.89
1U5	.59	6BF6	.59	6SN7GT	.69	12AX4GT	.59
3Q4	.59	6BG6G	1.29	6SU7GT	.69	12AX7	.69
3Q5GT	.69	6BH6	.79	6T8	.79	12BA6	.59
3S4	.59	6BJ6	.59	6U8	.79	12BE6	.59
3V4	.59	6BK7	.99	6V6GT	.59	12BE6	.59
5U4G	.49	6BL7GT	.99	6W4GT	.59	12BD6	.59
6A84	.69	6BQ6GT	.99	6X4	.39	12BF6	.79
6AK5	.89	6C4	.39	6X5GT	.49	12N8GT	.59
6AL5	.49	6CB6	.59	7A7	.69	12S7GT	.59
6AQ5	.49	6CD6G	1.49	7B6	.69	12SF5GT	.69
						12SJ7M	.59
						12SJ7GT	.59
						12SN7GT	.69
						12SL7GT	.79
						19BG6G	1.79
						25BQ6GT	.99
						25L6GT	.59
						32L7GT	.79
						35B5	.59
						35C5	.59
						35W4	.39
						35L6GT	.59
						43	.79
						47	.89
						50B5	.59
						50C5	.59
						50L6GT	.59
						70L7GT	.99
						117Z3	.39

UHF TELEVISION CONVERTER $34.95

Sutco UHF television converter with built-in booster. Continuously variable for channels 14 thru 83. Built-in wide band VHF booster for channels 2 thru 13. Self powered for 110 volt, 60 cycle AC operation. Selector switch gives choice of VHF or UHF antenna. VHF antenna may be fed thru the broad band booster or direct to the TV set. Stock No. 21A, shipping weight 7 lbs. Net price **$34.95.**

REGENCY RC-600 $49.95 LIST

Carefully engineered and of highest quality construction. Features extreme stability, air dielectric in the tuning element. Image rejection of VHF stations down 50 to 60 db. Converts all sets and is highly recommended for those having split sound and video. Tubes are 6AF4 oscillator, crystal diode mixer, 6BK7 dual triode IF amplifier and selenium rectifier. Front panel change-over switch for UHF or VHF. Input and output impedances 300 ohms. For 110 volt 60 cycle AC operation. Shipping weight 8 lbs. Stock No. RC-600, price **$49.95** each, lots of 3, **$37.46** each.

UHF-VHF ANTENNAS

VEE-D-X Ultra Q-TEE. One antenna for all channels 2 thru 83 with a single transmission line (tubular 300 ohm recommended, your cost 4c per ft.) List price $14.25, your cost **$8.38.**

Two stack Ultra Q-TEE antenna for fringe area. List price **$29.95,** your cost **$17.98.**

UHF ADAPTING BRACKET

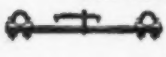

Permits addition of UHF antenna to existing VHF installation. Mounts three different ways to mast or antenna boom. List $1.50.
Your Net Cost..... **88c**

VEE-D-X MIGHTY MATCH

Model MM-30. Provides best method of combining VHF-UHF antenna systems with single transmission line. Automatic action. Printed circuit hi-efficiency.
List $4.00. Your Net Cost..... **$2.35**

30 FOOT TELESCOPING MAST $10.95

Famous Trio antenna rotator. Net **$26.43.**

5 wire rotator cable, 3c per foot. Deluxe 30 foot telescoping mast, Stock No. ST-30, $10.95. Complete kit of guy wire, guy rings and base mount for mast, $6.00 extra. Prices do not include Express charges.

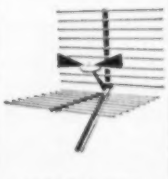

CORNER REF. UHF ANT. $8.95

Corner reflector antenna (less mast) for UHF only. As high as 10 db gain on channels 14 thru 83. (Tubular lead recommended, your cost 4c per ft.) With a Mighty Match you can connect this antenna with your present VHF antenna using only one lead to your set.

50-WATT BOOSTER AMPLIFIER

50-WATT BOOSTER AMP. $39.95

2-Mike Pre-Amp $12.95 Extra. Not a Kit, but a Manufactured Amp.

50-WATT BOOSTER A sensational value. 50 watt booster amplifier with push-pull parallel 6L6 output tubes. Use with your present amplifier as a booster or use with the PR-2X Pre-amp to add the use of 2 mikes and one low level input. The booster amplifier has one input jack and with 1 volt input gives 50 watts of audio. Booster has a 6 lb. potted case high fidelity output transformer, matches speaker with 4-8-16 ohm voice coil, also 60 ohm and 250 ohm line. Booster has a 225 mill power supply with 5U4 rectifier. Price includes tubes: 4 6L6, 7N7 and 5U4. The two variable controls are for master volume control and bass boost tone control. Size 8 x 6½ x 14½. Stock No. PA-55N, Shipping weight 26 lbs. Sale price $39.95 ea.

2-MIKE PRE-AMP. Pre-amplifier plugs in directly to the PA-55N Booster amplifier. It enables use of 2, Crystal or Dynamic Mikes plus one low level input. Furnished with 4 foot cables and plugs for remote control of the 55 watt Booster Amplifier. Small chassis size 5 x 3½ x 4". Stock No. PR-2X, with tubes 7F7 and 7N7. Net price **$12.95** ea.

McGEE'S $62.50 LIST 15" COAXIAL SPEAKER, $21.95
21 OZ. ALNICO V MAGNET—5" TWEETER

This is the finest 15" coaxial PM speaker value that we have ever offered. New 1952 production, of a famous manufacturer of fine speakers. The 15" speaker has a 21½ oz. Alnico V magnet; equal to 68 oz. of the Alnico 5 type magnet. The cone is free floating, of one piece construction. Will reproduce low frequencies down to 20 cps. The 5" tweeter is coaxially suspended and has a ridged cone to reproduce only the high frequencies. It will respond up to 17,500 cps. The high-pass filter is concealed under the pot cover, leaving only two wires to connect both the tweeter and woofer to any 8 ohm output transformer of a radio, or high fidelity music lover's amplifier. Stock No. P15-CX, shipping weight 13 lbs. Net price **$21.95.**

12" COAXIAL SPEAKER, $12.95

McGee offers the new 1952 model 12" coaxial PM speaker. Quality you would put in your finest sets if you were a manufacturer. 12" woofer has 6.8 oz. Alnico V magnet. Tweeter is coaxially suspended and has a metal diffuser. High pass filter is under the pot cover. Only two wires to connect to your radio or audio amplifier. 8 ohm with 18 watt peak and 10 watt average. Shipping weight 8 lbs. Response from 30 to 17,500 cps. Stock No. CU-14Y. Sale price **$12.95** each; 2 for **$29.00.**

12" JENSEN PM, $15.95

Another McGee Scoop! Jensen Concert 12", 14½ oz. Alnico V magnet PM speaker. 8 ohm voice coil. Will take 25 watt audio. You save dollars on this speaker. Just 1,000 to sell. Shipping weight 8 lbs. Stock No. P-12P. Sale price **$15.95;** 2 for **$30.00.**

G.I. 3-SPEED CHANGER WITH G.E. $22.95

VARIABLE RELUCTANCE TURN-ABOUT CARTRIDGE

Another tremendous McGee Scoop! Brand new General Instrument 3-speed automatic record changers. Complete with RPX-050 G.E. variable reluctance cartridge with turn-about stylus. Plays all 3 speeds automatically: 7", 10" or 12" records. Has reject button. Repeats last record. Base size, 12"x13¾". Shipping weight 14 lbs. Stock No. 700-GE. Scoop price, **$22.95.**

GI 3-speed changer same as above, but with Webster flip-over twin needle cartridge. Stock No. GI-700. **Sale price, $21.95 each.**

McGEE RADIO COMPANY Prices F.O.B. K.C. Send 25% Deposit with Order, Balance Sent C.O.D. With Parcel Post Orders, Include Postage

TELEPHONE VICTOR 9045. WRITE FOR FLYER
1422 GRAND AVE., KANSAS CITY, MISSOURI

TELEVISION BOOSTERS AND CONVERSION KITS ON SALE AT McGEE

GENUINE STANDARD COIL T.V. BOOSTER
Not Surplus, But Right From the Factory
$10.95

Latest Model B-51 Standard Coil Television Booster. McGee makes another lucky purchase and as usual, passes the saving on to you. The famous Model B-51, 12 Channel Standard Coil TV booster, which lists for $35.00, is offered to you for only **$10.95** each. Brand new, factory carton sealed and fully guaranteed by McGee. This top quality single stage booster utilizes printed high frequency circuits, for improved performance on all channels. Uses 6AK5 tube. Average gain, 6 to 7 volts on low channels and 5 or 6 on high channels. No distorting of picture or sound. Has extremely low noise factor. Continuous one-knob tuning and channel selector control switch for off-on and by-passing 300 ohm lead-in to set. Modern design, dark brown plastic cabinet, 8"x4½"x4½". Made for 110 volt, 60 cycle AC operation. Shipping weight 5 lbs. Model B-51. Sale price, **$10.95** each, or buy 2 for only **$20.00.**

FRINGE AREA TV RECEPTION IS BETTER WITH OUR McMURDO SILVER TV BOOSTER
$10.95—TWO FOR $20.00

Read the article on pages 52 and 53 of the December "Radio & TV News." You will see now a booster like the McMurdo Silver Super Sonic was used for fringe area TV reception. We can't guarantee this unusual reception, but we will guarantee this booster to be a sensational value. Continuously variable inductance type tuner from channel 2 including the FM band through channel 13. Self-powered for 110 volts AC operation. Incorporates a 6J6 tube. Input for 300 ohm TV line and 300 ohm output to TV set. Single knob tuning. Attractive plastic case. McMurdo Silver Super Sonic TV-FM booster. Stock No. GB-6B, shipping weight 5 lbs. Sale price, **$10.95** each or two for **$20.00.**

20 INCH CONVERSION KIT $29.95

YOU GET—
20HP4—20" PICTURE TUBE
20-INCH PLASTIC MASK
14 K.V. FLYBACK AND 70° YOKE

Our 20" conversion kit includes a 6-month guaranteed 20HP4, 20° rectangular blackface picture tube, plus a 14,000 volt G.E. built high voltage flyback transformer, plus a matched 70° cosine yoke, plus a 20° rectangular gold trimmed plexiglas mask and suggested diagram. The picture tube is the latest electro-static focus type that requires no focus coil. Shipped via express or truck only. Ship. weight, 40 lbs. Stock No. 20-TP, net price, **$29.95.** Price with Raytheon or GE 1 year guarantee picture tube, **$10.00** extra.

14-Inch Conversion Kit
$25.95

14-inch conversion kit: You get a 14-inch black face, 1 year guarantee G.E. 14CP4 picture tube, a 70° deflection yoke with matching 14,000 volt G.E. flyback and a 14" plexiglas gold trim safety mask, plus conversion instructions. Stock No. 14CC-G, sale price, **$25.95.**

17-INCH CONVERSION KIT $25.95
You Get—17BP4A 17" Picture Tube
17-Inch Plastic Mask
14 K.V. Flyback and 70° Yoke

17-inch conversion kit with a 17BP4A, 17" rectangular blackface electro-magnetic focus picture tube with 6 months' guarantee, plus a matched 70° cosine yoke, a G.E. built 14,000 volt flyback and a 17" rectangular gold trimmed plexiglas mask and safety shield. Suggested diagram furnished. Shipping weight, 30 lbs. via Express or Truck only. Stock No. 7-4X1, 17" conversion kit. Sale price, **$25.95.** Kit Price with GE or Raytheon 1 year guarantee picture tube, **$5.00** extra.

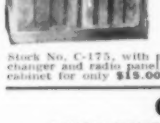

CAPEHART CABINET, $79.95
BLANK OR CUT TO FIT ESPEY CHASSIS

Buy this cabinet with Espey chassis and the VM changer at the left and have a fine radio-phono combination for less than the value of the cabinet alone. This beautiful cabinet was intended for a Capehart $800.00 combination. It is the finest possible furniture quality cabinet workmanship, 37" high, 40" wide and 21" front to back. Hinged top lifts in two sections, 25½" lid covers the changer compartment and 14½" is the width of the radio compartment. Changer mounting panel is furnished blank. Radio panel shipped ready cut to fit the 7-C Espey chassis. Baffle is cut to hold 2–12" speakers. Made of top quality walnut veneer, ⅝" material used throughout. Shipped via truck, rail or express only. Shipping wt., 160 lbs. Stock No. C-175, with panel cut to fit Espey 7-C, **$79.95.** Stock No. B-175B, with blank changer and radio panel, **$79.95.** Buy 2–12" 32 oz. Alnico "M speakers for use in this cabinet for only **$18.00 ($7.50 each).**

RCA 201E1 T.V. TUNER $7.95

Terrific buy on this RCA tuner. We have a limited quantity of the famous original 201E1, 13 channel completely wired and tested TV front end tuners. Ready to connect to your TV video I.F. strip. Offered at a sacrifice. Price was $44.00. Now only **$7.95** each, with tubes. Each tuner in good condition but has been repaired. Stock No. RCA-13P, TV front end tuner. Convertor coil type for separate sound as used in the famous 630 chassis. Complete with 3—6J6 tubes, **$7.95.** Specify shaft length desired, either 2" or 4".

RCA 201E-1 T.V. TUNER

Same as pictured above only new—with 2½" shaft. Stock No. 2Z01. Sale Price, **$11.95.**

3-TUBE SARKES-TARZIAN T.V. TUNER
$9.95

This popular Sarkes-Tarzian Type 3 tuner is widely used. 13 channel rotary type switch with individually tuned coils. Price is complete with diagram and three tubes: 6C4 osc., 6BH6 R.F. and 6AG5 mixer. Regular factory cost is twice our price. Each tuner is wired ready to hook up to a video and sound IF strip. May be used with either inter-carrier or separate sound IF circuits. Has built-on convertor coil, built in fine frequency control. Sarkes-Tarzian TV tuner, with 3 tubes. Net price, **$9.95** each. Specify shaft length, either 2½" or 4¾".

STANDARD COIL SUPER CASCODE TUNER $19.95
UHF STRIPS $9.40 EXTRA

The Cascode Circuit of the Standard Tuner offers a new development of this famous TV front end assembly which affords a 2-to-1 improvement in gain and a 35% to 50% reduction of noise over the pentode tuner. Other advances include: easy conversion to UHF reception by interchange of channel inductors; increased sensitivity for TV sets in fringe areas; elimination of booster use; and a high profit item for the serviceman as a replacement unit sale. Brand new factory TV-2000 TV tuner, compl. with tubes 6BK7 or 6BQ7 and a 6J6. Shaft length 3½". Scoop UHF (specify channel) strips supplied in pairs for above cascade tuner. **$9.40** per set. UHF strips for other models of the Standard Coil tuners specify channel and series; either F, G, K, Q, R, H or M as printed on the tuner, **$9.40** per set.

3 STATION INTERCOM MASTER $16.95
SUB STATION $3.95

3-station intercom master housed in chrome plated metal cabinet 7½"x6"x5" sloping front. Full 3-tube amplifier for 110 volt AC-DC operation. Press-to-talk switch on top of the cabinet and volume control with off-on switch and station selector switch are on either side. May be used with from one to 3 substations. (See matching cabinet chrome plated sub-station No. PM-A5). Master is quiet at all times except when press-to-talk switch is pressed at the master or call-back switch is pressed at the sub. Uses 3-wire intercom cable. 3-station intercom master MPM-A3, shipping weight: 10 lbs. Sale price, **$16.95** each, sub-stations extra. 3-wire plastic intercom cable, 100 ft. for **$1.95,** 500 ft. for **$8.95.**

INTERCOM SUB STATIONS $3.95

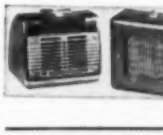

Chrome plated, with call back switch for 3-wire intercom master. Size 7½"x6"x5" sloping front. 5" Alnico V PM spkr. Intercom dealers buy at less than present production costs. Limited quantity. Stock No. PM-A5, ship. weight 7 lbs. Sale price, **$3.95** each or 3 for **$10.00.** Special 3-wire plastic intercom cable, 100 ft. for **$1.95,** 500 ft. for **$8.95.**

brown leatherette covered intercom sub-station with call back switch for use with 3-wire intercom masters. 5" square and 2½" deep. Has new plastic grill cloth, Alnico V PM speaker. A true McGee value. Stock No. NC-5, ship. weight, 1½ lbs. Sale price **$3.95** each or 3 for **$10.00.** 3-wire plastic intercom cable, 100 ft. for **$1.95,** 500 ft. for **$8.95.**

CAPEHART CABINET FOR 1000 SET—ONLY $99.95
BEAUTIFUL WALNUT

99.95

Beautiful, finest quality walnut combination radio-phono cabinet, 42" high, 42" wide and 22" deep. Made for Capehart's finest combination, selling for $1000 and up. Cabinet cost manufacturer over $200.00. Has highly polished matched walnut panels. Made of ¾" material. Top 11⅛" solid stock. This cabinet weighs approximately 175 lbs. The changer, radio and speaker grill all have hinged doors. Radio compartment on right hand side is 14" high and 11½" wide. Made to mount chassis vertically. Changer compartment is 14" high by 26½" wide. Large enough to hold any record changer or recorder mechanism. Front 10" of top over the changer compartment is hinged to fold back for easy access to the changer. Both radio and changer compartments come with uncut blank panels. Speaker baffle is cut for 12" speaker and the speaker compartment is completely enclosed. Shipping weight, 275 lbs. Stock No. C-275W Capehart combination cabinet. Net price, **$99.95.** Walnut.

COMPLETE RADIO, TELEVISION AND AMPLIFIER KITS AT McGEE

3-WAY PORTABLE KIT
$15.95

New 1952 Model 3-way personal portable radio kit. Operates on 110 Volts AC-DC or 67½ B plus 1½ volt self-contained batteries. Leatherette covered case size, 5½"x8¾"x8". Receives broadcast 550 to 1650 KC. A conventional 2-gang superhet circuit with 456 KC iron core IF's. Incorporates the new super gain stick loop antenna. All plated chassis. Lab. approved circuit—matched coil parts. Price includes all parts, tubes, diagram, Alnico V PM speaker. A factory quality kit. Stock No. PN-4T, shipping weight 12 lbs. Operates on 1½ batteries. **$15.95.** 67½V. B, **$1.99;** 1½V. A, **39c** extra.

Build Your Own Phono-Mike Broadcaster
$7.95

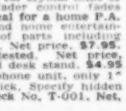

Kit Model DE-6R. With this simple kit, you can build a 3-tube phone oscillator that also has a mike input. Will broadcast over any radio within your home, about 75 feet from 1000 to 1500 kc. Inputs for crystal mike or crystal phono pickup. Fader control fades from mike to record. Ideal for a home P.A. system, baby listener and home entertainment. A complete kit of parts including tubes. Kit Model DE-6R. Net price, **$7.95.** DE-6RWT, wired and tested. Net price, **$9.95,** Crystal mike and desk stand, **$4.95 extra.** Concealed microphone unit, only 1" in diameter and ⅛" thick. Specify hidden mike when ordering. Stock No, T-001, Net, **$3.95** extra.

8-Tube Hi-Fi Amplifier Kit $29.95

A complete kit including tubes: 5-7E5, 2-12AX7, 2-6V6 plus rectifier diagram and photos. Inputs for radio tuner and any kind of phono pickup (crystal or G.E. variable reluctance) and either crystal or dynamic mike. Output matches 8 ohm voice coil. Two effects bass and treble tone controls with range selector switch for either juke box quality with heavy bass response or brilliant symphonic range. Response 18 to 20,000 cps. 8 tube all triode amplifier kit, complete with tubes. Shipping weight 25 lbs. Model 7X5. Net **$29.95.**

10-Watt Hi-Fi Amplifier Kit $14.95

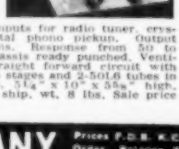

A complete kit of parts including tubes 12AX7, 12AU7, 2-5Q5L, plus rectifier, diagram and instructions to build a high fidelity twin tone control audio amplifier with bass and treble boost. Inputs for radio tuner, crystal and crystal phono pickup. Output matches 8 ohms. Response from 50 to 15,000 cps. Chassis ready punched. Ventilated cover. Straight forward circuit with twin triode gain stages and 2-5Q5L tubes in push-pull. Size, 9¼" x 10" x 5⅝" high. Model AP-10R, ship. wt. 8 lbs. Sale price **$14.95.**

10-TUBE RADIO KIT $29.95

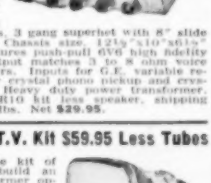

10 tube broadcast radio chassis kit, complete with tubes: 2-6SK7, 6SA7, 2-6SN7, 1-6SL7, 2-6V6 plus 5Y3 rectifier, diagram and instructions, 3 gang superhet with 8" slide rule dial. Chassis size, 12½"x10"x6½" high. Features push-pull 6V6 high fidelity audio. Output matches 3 to 8 ohm voice coil speakers. Inputs for G.E. variable reluctance or crystal phono pickup and crystal mike. Heavy duty power transformer. Model BK-R10 kit less speaker, shipping weight 18 lbs. Net **$29.95.**

17, 20" T.V. Kit $59.95 Less Tubes

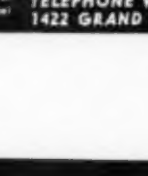

A complete kit of parts to build an AC transformer operated television chassis for use with a 16", 17" or 20" rectangular picture tube. The 12 channel Sarkes-Tarzian tuner is ready wired, as is the 4 tube video IF strip. Circuit is of the conventional design. Do not buy this unless you understand television. It is difficult to wire. We furnish a schematic, Kit Model WH-20. Ship. wt, 40 lbs, less all tubes. Net **$59.95.**

Kit of 22 tubes, less picture tube **$16.95.** 17" 17BP4A, **$19.95.** 20HP4, **$29.00.**

6-TUBE 2-BAND KIT $14.95

Popular with schools and colleges for training. 6 tube AC-DC, 2 band radio kit with plastic cabinet. Receives broadcast and 6 to 18 mc shortwaves. Full 2 gang superhet with 5" speaker and slide rule dial. A complete kit with tubes: 12SK7, 12K8, 12SK7, 12SQ7, 50L6 and 35Z5, diagram and instructions. Factory quality. Cabinet size 13"x6¾"x6¼". Shipping weight 12 lbs. Model ME6-2. Net **$14.95.**

5-TUBE AC-DC KIT $12.95

Model RS-5. A 5 tube AC-DC straight broadcast kit, housed in the same cabinet as ME6-2 above. Complete with tubes. Shipping weight 10 lbs. Net **$12.95.**

AC POWERED BROADCAST TUNER KIT $12.95

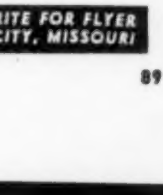

A self-powered, 3-gang superhet tuner kit with R.F. stage. This complete kit is furnished with a diagram, tubes and tubes: 6BA6 R.F., 6BE6 oscillator R.F., 6BA6 I.F. detector, 6AL5 diode, AVC, plus rectifier. Connect to any audio amplifier. Ideal for use with our S-2020 or 7x5 amplifier kits. Chassis size, 9½x4x4½" high. Shipping weight, 7 lbs. Broadcast tuner kit Model BT-38X. Net price, **$12.95.**

McGEE RADIO COMPANY Prices F.O.B. K.C. Send 25% Deposit with Order, Balance Sent C.O.D. With Parcel Post Orders, Include Postage

TELEPHONE VICTOR 9045, WRITE FOR FLYER
1422 GRAND AVE., KANSAS CITY, MISSOURI

NEW DATA in a famous service aid

Mandl's Television Servicing

THE NEW REPRINT of this widely used service guide includes new data on the cascode tuner, servicing of newer types of i.f. systems, automatically focused tubes, UHF station listings and antenna calculations, transistors and other recent developments. Everything you need to know for quick, efficient servicing is given here in the most practical, useful way. You'll learn simple signal tracing procedures, how to improve reception in fringe areas, how to use all test equipment, and many trade tricks for diagnosing troubles accurately and in minimum time. All faults likely to occur, including those hard-to-find troubles, are dealt with; there are hundreds of helpful illustrations, and a complete master trouble chart to help you pin point the cause of trouble from the symptoms and turn quickly to the specific directions for correcting it.

BASIC TV BOOKS

Television for Radiomen

By E. M. Noll. Very clear, nonmathematical explanation of the function and operating principles of every part and circuit in TV reception, and the techniques of installation, adjustment and alignment.

Television and FM Antenna Guide

By E. M. Noll & M. Mandl. How to determine which type of antenna is best for a particular site; how to install it to insure peak performance. Full accurate data on all types of antennas and allied equipment.

Do you know enough about hearing aids?

Hearing Aids

By Matthew Mandl

A rapidly increasing number of the 15,000,000 hard-of-hearing people in this country are turning to hearing aids and THEY ALL REQUIRE SERVICING! This book explains the operation of modern hearing aids, the differences between the various types of earpieces, amplifiers, batteries, etc.; what may go wrong with them; how to locate trouble, and how to make adjustments and replacements.

SEE THEM ON APPROVAL

The Macmillan Company, 60 Fifth Ave., N. Y. 11

Please send me the books checked below. I will either remit in full or return the books in ten days.

☐ Mandl's TV Servicing, $5.50 ☐ TV & FM Antenna Guide, $6.25

☐ Hearing Aids, $3.50 ☐ TV for Radiomen, $7.75

Signed .....

Address .....

.....

This offer good only within continental limits of U.S.A.

SPECIALIZE—FOR PROFIT

By **YVON O. JOHNSON**

Concentrate on servicing a single brand of TV receiver and cut inventory costs and overhead charges in general.

IF YOU have been wondering how to make your small TV service shop stand head and shoulders above the other shops in your locality, consider specializing in the repair of just one brand of receiver.

You should be able to increase your net profit through specialization if it is suited to you and your shop. Specialization can help you with customers, inventory, purchasing, and servicing.

Let's look at the advantages and disadvantages of specialization and then see how you can get started on it. This article applies to small shops doing service work as the main function with sales as a sideline, since the choice of the brand for repair work will determine the brand sold.

The Advantages

Increased customer acceptance. You'll probably agree that the shop which saves the customer money while rendering a quality service will prosper, providing it is operating at a profit.

When you specialize, you will become very familiar with the troubles of one brand. You'll be able to diagnose more sets in the home. You'll be able to repair more of them there because you can have the common replacement parts with you. Carrying parts for one set is fairly easy; for a couple of dozen, very difficult.

Customers will appreciate a shop that knows a brand well enough to service most sets in the home. Customers are reluctant to incur pick-up, shop, and delivery charges.

Of course, there will be many times when the set will still have to go to the shop, but you will have earned a reputation for doing shop work only when it is absolutely necessary.

Customers are impressed by specialization. Generally speaking, wouldn't you rather take your car to an auto repair shop specializing in your make rather than to a shop doing general work?

Better inventory. Your inventory and its turnover are favorably affected by specialization. Many tube types have a very slow turnover, yet it is necessary to stock them against the eventuality that they will be needed urgently at some future time. With one brand of TV, you'll have to stock only the tube types used by that manufacturer. The money that would be tied up in the slow movers can be used to maintain an adequate stock of the types needed.

Take a look around your shop and you'll probably find odds and ends of replacement parts which were ordered and, for various reasons, never used. And isn't each part for a different brand receiver? If you specialize, you'll avoid that problem as the chances are that you'll be able to use that replacement part soon.

You'll be able to maintain an adequate stock for one brand at the same or less expense than for maintaining an adequate stock for several makes.

Decreased purchasing time. The time that you spend in buying can be greatly reduced. You'll have to phone, write, or visit only one set distributor for exact replacement parts. You'll have to become familiar with only one manufacturer's part numbers and ordering procedure.

Parts warranties can be handled economically if you are doing it for one brand. You will not have to run around to several distributors, a tube here and there.

Increased shop efficiency. Unfortunately, all shop time is not productive. You should be able to cut down on diagnostic time when you specialize. You will know what voltages to expect at certain test points. You will know what the waveforms should look like on your oscilloscope. Often, in a repair job, much time is wasted by not knowing whether the voltage or waveform observed is within tolerance or is indicative of trouble.

Not only will you save diagnostic time, but you'll save alignment time. You'll know and remember the exact procedure to be followed. With this skill and speed in alignment, you will undoubtedly find it advisable to give every set that comes into the shop an alignment job. This will be feasible because you will have the necessary plugs, cables, etc., made up for that brand. You won't have to sort through a maze of other cables to find the ones you need.

Likewise, you can have a shop picture tube to avoid pulling the separate picture tubes from cabinets. This is most practical when you know that the shop deflection yoke and focus coil are exact duplicates of those in the home. What's more, they will have the proper plug attached!

You can easily have one or two shop speakers with the right plugs, transformers, and fields used by the one manufacturer in his models. This saves a few valuable minutes on each removal job. Such techniques are

The Picture Tells the Story

TV Antennas exist for one reason — to provide a clear, strong, sharp picture!

TRIO ZIG-ZAG* TV Antennas perform so well in this all important respect that they are America's most wanted.

Yes, a picture — the TV picture — tells the TRIO story more eloquently than anything else! Where all other antenna designs fail, high gain TRIO ZIG-ZAG TV Antennas consistently lock in sharp, clear pictures — from Maine to Texas, in city or country!

TRIO TV antennas look different, work different — provide a magnificent DIFFERENCE in picture quality!

*Patent Pending

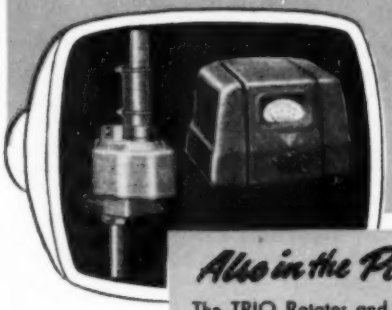

*New insulating sleeve, with longer leakage path and elimination of slit, does away with assembly errors — elements cannot short out. For maximum strength, new steel, electro-plated element clamps have been introduced.

Also in the Picture

The TRIO Rotator and Direction Indicator are the most dependable ever built. Developed after $50,000 research. Fully guaranteed for a FULL two years!

Best Buy in UHF Antennas

LOW IN COST — HIGH IN PERFORMANCE

NEW TRIO UHF BOW-TIE with reflector

Sturdy, broadband antennas of uniformly high gain that have been thoroughly field tested. Phasing strips installed, pre-assembled — a jiffy to attach reflector screen. Available in one, two and four bay models. Usual high-quality TRIO construction.

Model UBT-4 Supplied With 4 Foot Mast

Model UBT-1 Supplied With 2 Foot Mast

Model UBT-2 Supplied With 3 Foot Mast

NEW TRIO UHF MULTI-CHANNEL YAGI ANTENNAS

Broadband yagis developed by TRIO now successfully applied to UHF. Four models cover all UHF channels, rarely more than two needed for any one area.

These high gain six element yagis have sharper directivity, thereby eliminating ghosts. Thoroughly field tested. Entire antenna mounted in front of mast removes metal from field of reflectors or antenna elements. Mast clamp supplied. Completely assembled.

Model 6-UBY 14-26 for Channels 14-26
Model 6-UBY 27-42 for Channels 27-42
Model 6-UBY 43-60 for Channels 43-60
Model 6-UBY 61-83 for Channels 61-83

TRIO MANUFACTURING CO.

GRIGGSVILLE, ILLINOIS

3" RD 0-1000 MA DC..$ 2.95
4" SQ 0-50ua DC..... 12.95
1000 KC MOUNTED CRYSTAL 2.95

POLY-TECH

20 watt PP 6L6 output transformer t Standard VC, completely shielde.: upright cased.....79c

GOING MOBILE? CO-AXIAL 6 VDC RELAY. SPDT, WILL HANDLE UP TO 75 W. RF, uses standard co-ax connectors. Send your order in today b'cuz they'll go like hot cakes. Prepaid..... **$6.75**

MOBILE VHF ANTENNA MFD. BY G. E. 152-162 MC, complete with 12 ft. RG58U Coax cable, removable antenna rod, mount, 8318P (PL-259) Coax connector, installation hardware and instructions. Special, only..... **$2.45**

TELECHRON
3.6 RPM Synchronous 115v 60CY Motors. Special . **$1.95**

STRUTHERS-DUN
115 VAC 40-60CY. Relay, SPST, No. 1 Amp 115 VAC Contacts Quantity Ltd. **$1.95**

115V FILAMENT TRANSFORMERS 60 CY

2.5 VCT 10A, 10 KV Insulation	$4.50
5V 4A 2.5 KV Insulation	1.99
5.0 V 6A, 6.3 V 6A	3.95
5.0 V 12A, 2.5 KV Insulation	5.95
5.0 VCT 20A, 2.5 KV Insulation	6.85
6.3 VCT 3A, 2.5 KV Insulation	2.25
6.3 VCT 6A, 2.5 KV Insulation	3.15
6.3 V 10A	3.95
10 VCT 10A, 2.5 KV Insulation, cased	6.00
Dual 25V 1 Amp	1.95
14.7 V 500A, 230 V Primary	39.50

115V POWER TRANSFORMERS 60 CY

68 to 83 V Half Wave, 1.5A	$ 1.25
300 V Half Wave .03A	.75
.57 V Half Wave 3A	2.95
700 VCT 100 MA, 5V 3A, 2.5V 10A	2.25
740 VCT 185 MA, 6.3V 4A, 5V 3A	5.95
800 VCT 200 MA, 5V 2A	3.95
680 VCT 225 MA	2.95
750-800-0-600-750 VDC 225 MA	11.50
3200 VCT 350 MA	29.50

CHOKES

9 HY 95 MA, cased	$1.15
15 HY 100 MA, cased	1.95
10 HY 200 MA, cased	2.75
15 HY 250 MA, cased	3.75
5 HY 300 MA 70 OHMS, 2 FOR $4.95	
8 HY 400 MA 110 ohms, cased	$5.89
6 HY 500 MA 35 ohms, cased	7.25
.05 HY 3A 1 ohm	2.95
.02 HY 5A .5 ohm, cased	4.95

APG-17 Corner reflector ant.	$12.50
AS-27/ARN-5 Beam horn ant.	3.95
AS-31/APN-7 10 cm. antenna	12.95
J-44/APA-18 Junction box	4.95
J-48/APA-5 Junction box	29.00
JB-49-C Junction box (SCR-299)	29.50
C-17/APS-3 control box	35.00
C-47/APS-6 control box	6.50
C-121/AP control box	4.95
RD-3/AP	14.50
C-254/AR control box	9.95
MX-10/APS-3	14.50
C-197/ARC-3 control box	3.50
APA/10 Pan-Adapter manuals	2.95
TM-11-486 Communication manual, 600 P	6.50
BC-605 Intercom, New	6.95
BC-1068 Recvr. 150-200 MC., New	49.50
APS-13 With tubes	49.50
RM-29, TS-13 Handset, case (New	29.50
MC-385 High to Low Imped. Adapt. New	as
PE-94-CM., New	29.50
UPN 50-1200 cy. 115 V. Supplies	19.95
Mark II Headset & Mike, New	3.95

GE CONSTANT VOLTAGE TRANSFORMER. 115V ± 1% output at 50 VA. input 90-130 VAC 60 cy. 9" x 3" x 3", 6 ft. rubber cord & plug, receptacle output, wt. 7 lbs. Primary isolated from secondary. New each **$7.95**

DESK MICROPHONE
NEW W.E. (#1120-DA). High quality, single button mike, press to talk sw., stand, with cord & plug (W.E. PL-68). Perfect for airport, police commercial radio telephone installations. NEW BOXED each **$8.50**

GR 50-A Variac 115V in. 115V out @ 4A. Used ex. cond. ..only $95.00

Mallory Inductuner, 3 Section .. **$3.95**

DUAL 200ua CROSS POINT INDICATORS.. **$5.95**

1N34 DIODES
LIMITED QUANTITY
10 for only.... **$3.95**

Isolation or Bias Transformer, Prim. 117V. Sec 135V TAP, 6.3V 35W **$1.95**

OIL CAPACITORS

2 MF 600 VDC	$0.79
4 MF 600 VDC	.99
6 MF 600 VDC	1.15
10 MF 600 VDC	2.99
8 MF 1000 VDC	2.95
35 MF 1000 VDC	8.50
.1 MF 1500 VDC	.49
16 MF 1500 VDC	6.95
.1 MF 2000 VDC	.79
1 MF 2000 VDC	1.95
2 MF 2000 VDC	2.95
4 MF 2000 VDC	5.50
6 MF 2000 VDC	7.50
.5 MF 2500 VDC	2.15
.25 MF 3000 VDC	2.90
.5 MF 3000 VDC	3.15
3 MF 4000 VDC	9.95
4 MF 4000 VDC	13.50
1 MF 5000 VDC	5.95
2 MF 5000 VDC	10.50
2 MF 6000 VDC	12.95
.1 MF 7500 VDC	1.95
.25 MF 15KV DC	$2.50
1 MF 15KV DC	69.50

POLY TECH
Dept. E-3, 919 Dawson St., New York 59, N. Y.
Send for Bulletin
Murray Hill 6-2650

ANOTHER OUTSTANDING JOBBER
GREEN TELE-RADIO DIST.
472 Sutter Ave
Brooklyn, N. Y
HAS THE SENSATIONAL NEW EICO 470-K 7" SCOPE KIT IN STOCK!
$79.95

GET INTO TV SERVICING
Send for free 24-page illustrated booklet which tells you how to become a successful TV technician. America's leading TV servicing school offers you a specialized training program that omits non-essential math & design theory. You concentrate on radio & TV servicing only. You get professional training & experience right in our fully-equipped shops & laboratories. Send for this booklet today. Write Dept. R-53 No obligation—no salesman will call. Approved for Veterans
WESTERN TELEVISION INSTITUTE
341 W. 18th St. Los Angeles 15, Calif.

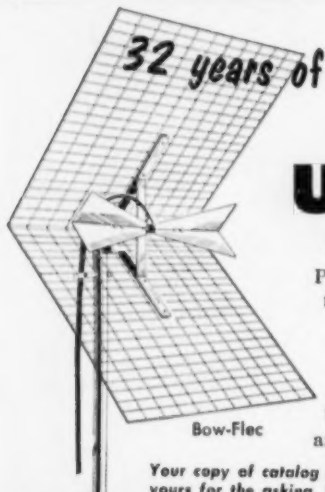

32 years of electronic leadership!
insuline
UHF-VHF ANTENNAS
Precision designed and field tested to provide the best TV reception under any condition. Insuline manufactures a complete line of UHF and UHF-VHF combination antennas and accessories.
Bow-Flec
Your copy of catalog No. T-752 UHF-VHF supplement is yours for the asking. Write Dept. N-5

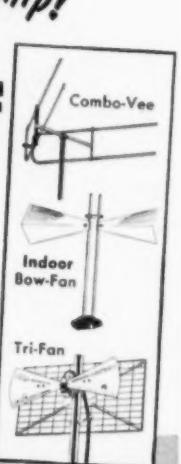

insuline CORPORATION OF AMERICA
INSULINE BUILDING • 36-02 35th AVENUE • LONG ISLAND CITY, N. Y.
West Coast Branch and Warehouse: 1335 South Flower Street, Los Angeles, Calif.
Exclusive Canadian Sales Agents: CANADIAN MARCONI COMPANY
Toronto • Montreal • Vancouver • Winnipeg • Halifax • St. John's (Nfld.)

shortcuts when you specialize, yet are impractical when you do general service.

The Disadvantages

Surely, the picture cannot be as rosy as it seems. There are definite disadvantages in this method of servicing.

First, there is the possibility that there may not be enough TV sets of any one desired brand in your area to make specialization practical. This, of course, is something that you must find out before you decide to specialize. Should you find there is little chance of keeping busy on one brand in your locality, then, by all means, do not specialize in just one brand. Should you find there is a large enough concentration of that make in your servicing area, then you may decide to go ahead with your plans.

It is improbable that you will be able to capture all the service work for that brand. Other service shops will have some faithful customers who will not think of changing. But it is doubtful that the majority of TV customers have fallen into that pattern. TV is still so new that most people seem to be shopping around for a competent—and inexpensive—service shop.

As a second disadvantage, you might say that specialization is like putting all of your eggs in one basket. Possibly it does not give you a broad enough base during slack seasons.

A partial answer to this is that you can accept any other servicing work that may come your way during the slack season to help compensate for the decreased business.

A third disadvantage is that another shop may decide to specialize in the same brand shortly after you make the same step. This will present a definite problem, but it should not be a hopeless one. If you are building up your customer relations and cutting down on inefficiency more than your competitor is, you should come out on top.

Closely allied to this disadvantage is another: What if the manufacturer or distributor should decide to do home servicing? It might be very difficult for you to compete. However, you might be able to compete successfully on the basis of personalized service.

How to Get Started

Determine the market. Your first job is to determine if the market for your specialized service is large enough to give you sufficient business. Let's say you are thinking of "X" brand TV. Will it be worthwhile?

One rough way to approximate the market is as follows: If the ratio of the number of "X" TV sets in your area to the total number of all TV sets in your area is equal to the ratio of your service jobs to all the service jobs in your area, then you could maintain your present service volume if you were to receive all the repair work on that brand.

This is stated in the form of a proportion:

Pipes that grew without getting bigger

Cross-section of coaxial cable. To triple capacity, Bell Laboratories and Western Electric engineers had to make 1000 amplifiers work perfectly in tandem . . . feed repeater power along the same cable that carries messages . . . put signals on and off the line at numerous cities along the route without distortion.

Pencil-size pipes carry telephone messages and television across country through the Bell System's coaxial cable. Once, each pipe could carry 600 voices, or one television program. Now it can carry 1800 voices, or 600 voices *plus* a broadcast quality television program.

Yet the pipes aren't any larger. They are being made into triple-duty voiceways by new repeaters, new terminal equipment and other transmission advances developed by Bell Laboratories engineers.

The conversion expense is less than the cost of laying extra coaxial cables. But it calls for highly refined manufacturing procedures, made possible only by close co-operation of Bell Laboratories and Western Electric, manufacturing unit of the Bell System.

In improving the coaxial cable system they created more than 20 years ago, engineers at Bell Telephone Laboratories devised a new way to give America still better telephone service, while the cost stays low.

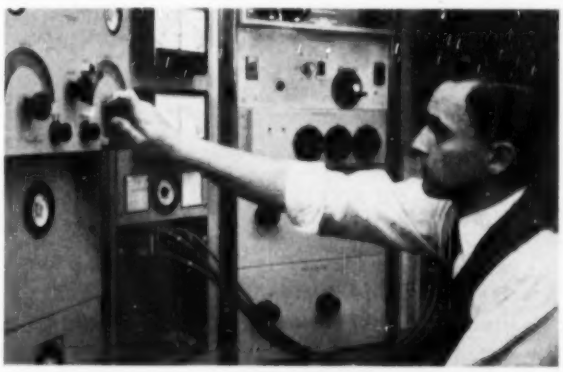

Laboratories engineer tests new triple-duty coaxial system. It marks the first time that telephone conversations and television can travel through the same pipes at the same time. With a wider frequency band being transmitted, big problem was to eliminate interference between the two types of signals.

BELL TELEPHONE LABORATORIES

IMPROVING TELEPHONE SERVICE FOR AMERICA PROVIDES CAREERS FOR CREATIVE MEN IN SCIENTIFIC AND TECHNICAL FIELDS

CREATED FOR
the Discriminating

MODEL 2430

TECH-MASTER
Custom-Built
TV CHASSIS

MODEL C-30

Model 2430: GOLD MEDAL TV Chassis

World's most powerful, most dependable TV receiver. Custom-designed and custom-built to provide the ultimate in sight, sound and value.

- Improved 630 type chassis.
- Advanced Cascode Standard turret tuner, adaptable to UHF without tools.
- Full 4 Mc. bandwidth.
- Quick action keyed AGC circuit.
- New, Hi-sweep auto-transformer system.
- 5 Microvolt sensitivity.
- Phono-input circuit.
- For all picture tubes from 16" to 24".

MODEL 2430: with quality PM speaker, all tubes less picture tube, universal picture tube mounting brackets. Equipped with audio take-off to feed sound through external amplifier, if desired **$189.50**

MODEL 2431P: Same as 2430, (less sound take-off), but with true fidelity Push-Pull audio amplifier **$199.95**

Model C-30: BLUE RIBBON TV Chassis

Custom designed, custom built, yet economically priced no higher than mass-produced models.

- Retains the outstanding characteristics of RCA-630 circuitry, namely 4-stage, full bandwidth picture IF strip, and 3 stage FM sound section.
- Latest synch and sweep circuits.
- Advanced Cascode turret tuner adaptable to UHF without tools.
- 5 Microvolt sensitivity.
- Permanent magnetic focuser.
- Double time constant AGC.
- 29 tubes (including 3 rectifiers).
- Phono-input jack (with front panel switch.)
- For all picture tubes from 16" to 24".

MODEL C-30: With quality PM speaker and all tubes (less picture tube), completely wired, aligned and tested **$149.50**

Watch for announcement of new Tech-Master chassis, Model 2439, featuring latest 90° deflection circuit for picture tubes up to 30 inches.

At all Leading Radio Parts Distributors

TECH-MASTER PRODUCTS CO.
443-445 BROADWAY, NEW YORK 13, N. Y.

$$\frac{\text{"X" TV sets}}{\text{all TV sets}} = \frac{\text{your jobs}}{\text{all jobs}}$$

("X" TV sets are included in "all"; your jobs are included in "all jobs." Your jobs and all the jobs are computed for the same period of time.)

Your chances of success are better if the ratio of "X" TV sets to all TV sets is *greater* then the ratio of your jobs to all the jobs. In other words, you won't have to get all the "X" TV business in order to maintain your present volume.

But if the ratio of "X" TV sets to all TV sets is *less* than the ratio of your jobs to all jobs, you had better select another brand for specialization. Perhaps you could specialize on two brands. This would give you benefits over general servicing, yet would not be as advantageous as having only one brand with sufficient volume.

You can see that the smaller the ratio of your jobs to all jobs, the greater the possibility for specialization. Specialization will be worth investigating if you are doing, say, about 10% or less of the servicing business in your area.

Obviously, your investigation will center on trying to determine the four factors in the proportion. You will have to find out how many "X" sets there are in your locality, how many sets of all kinds, how many service jobs you do weekly (or monthly or yearly), and the total of all service jobs for the same period of time in the same area.

The problem of determining the TV ratio can be taken up with sales managers of TV distributors or with a local distributors' association. Get several estimates and then view them in light of your own knowledge. The more accurate the figures, the better informed you will be.

You can compile the number of service jobs you did during a certain period. It may be difficult to get figures on the total number of service jobs performed in your servicing area during the same period. Talking to other shops or your local servicing association, if you have one, will often help. Perhaps it will be necessary to estimate the total number of jobs from the number of technicians that were employed in that area during that period of time.

Evaluate the competition. This is easier than determining the market. Who else is specializing in "X" brand in your area? Is the manufacturer or distributor doing home service work? Is the service work on "X" brand evenly divided among all shops? If it is, or if you have a lead, then you have a fighting chance.

See the distributor. In addition to helping you determine the market, the distributor's personnel can help you with information on the manufacturer's and the distributor's policies, parts ordering, and servicing and alignment techniques.

You may find that the distributor will be glad to hear of a reputable

Columbia
GEM OF THE SURPLUS

ARC-5 OR 274-N TRANSMITTERS

2.1-3 mcs. Brand new $19.95
4-5.3 mcs. With tubes 6.95
5.3-7 mcs. With tubes 6.95
7-9.1 With tubes 14.50

ARC-5 OR 274-N RECEIVERS

.19-.55 kc. $19.95
1.5-3 mcs. Brand new 24.50
3-6 mcs. Less tubes 6.95
3-6 mcs. With tubes 10.95
6-9.1 mcs. With tubes. Used 10.95
New 22.50
6-9.1 mcs. Used. Less tubes 8.95
MD-7 ARC-5 PLATE MODULATOR. Excel. cond. 14.95
BC-456 274-N Modulator. Less dynamotor. Excel. cond. 3.95
RACK FOR DUAL TRANSMITTER (274-N) 2.95
RACK FOR DUAL TRANSMITTER ARC-5. ..... 3.95
TRIPLE RECEIVER RACK. 5.00
DUAL RECEIVER CONTROL BOX. BC-496. New 2.95
BC-442A ANTENNA RELAY with 50 mmfd. condenser. Excel. cond. 3.95
COMMAND RECEIVER FLEX CABLE. 9-12 Ft. long 2.95
12 V. COMMAND RECEIVER DYNAMOTOR. New 12.95
COMPLETE AIRCRAFT INSTALLATION AVAILABLE ..... P.U.R.

SCR-522 VHF TRANSMITTER: 100-156 MC. Less tubes. Good cond. $12.95
SCR-522 VHF RECEIVER: 100-156 MC. Less tubes. Good cond. $19.95
4 FT. ANTENNA BALLOON: Brand new in can $1.19
THORDARSON SWINGING CHOKE: 4-24 henrys @ 300 ma. New $4.95
- **COLUMBIA 15 LB. Surprise Package**
- **Sensational bu**

$1.95

HS-33 LO-IMP HEADSET: Used cond. Checked out $2.49

METERS Special This Month!

0-1 ma. 2" Rd. Weston $4.95
0-25 ma. 2" Rd. Weston 2.95
0-35 ma. 2" Rd. Triplett 3.25
0-5 amp RF 2" Rd. G.E. 3.95
0-9 amp RF 2" Rd. Westinghouse 3.49

XED-13. VHF XCEIVER Freq. 420 mc, same as APS-15 except 12 V. system. Complete with 12 V. dynamotor. All tubes, etc. Excel. cond. ONLY $29.50
PROP PITCH MOTOR: 24 VDC input. Like new. ONLY $17.95

MARINE EQUIPMENT

COLUMBIA'S NEWEST HI-POWERED 1953 MARINE TRANSMITTER. Puts out max. power allowed by F.C.C. Contains all latest improvements & meets newest F.C.C. specs. Specify whether 12 or 24 V. frequency desired, and positive or negative ground. Full 90-day, unconstitional guarantee. Pre-tuned, ready to install $349.50
BC-223 25 W. TRANSMITTER & ARB RECEIVER: For 24 V. Inst. Receiver covers beacon, standard, and b'cast marine frequencies and amateur bands. This combo makes the finest LOW-COST marine installation on the market. Complete, checked out, ready to go. The whole deal ONLY $185.00
DU-1 LOOP makes ARB RECEIVER one of the best radio compass units made. With conversion dope. Used cond. $32.50
JEFFERSON-TRAVIS MARINE 5 W. RADIO-TELEPHONE. Made by Emerson Radio Corp. 2-channel crystal controlled receiver & transmitter. F.B. for small boats with 6 V. system or sail boat. Will run 48 hrs. on standard 6V. car battery. Complete with tubes, instructions, but less crystals and battery. NEW $79.50
CRYSTALS FOR ABOVE: Specify freq. Set of 4 needed. Per Set: $22.50
APN-4 LORAN SET. For PP-1 Radar. Complete inst. $135.00

All orders F.O.B. Los Angeles. 25% deposit required. All items subject to prior sale.

COLUMBIA ELECTRONIC SALES
822 South San Pedro St. Los Angeles 13, Calif.

Snyder
PHILADELPHIA

UHF TV AERIALS

UHF-3A — CHANNELS 14 to 48
UHF-3B — CHANNELS 27 to 62
UHF-3C — CHANNELS 47 to 83

Your Cost **$3.95**

● 8 Aluminum Elements ● Sturdy Aluminum Cross Arm for long life ● Quick, convenient U Clamp Mast Mounting ● COMPLETELY PRE-ASSEMBLED.

ALMO RADIO CO.
509 ARCH ST. & 6205 MARKET ST.
Philadelphia, Pa.
6th & ORANGE STS. • Wilmington, Del.
4401 VENTNOR AVE. • Atlantic City, N. J.
1133 HADDON AVE. • Camden, N. J.
317 Park Heights Avenue • Salisbury, Md.

shop which will specialize in his product. He may refer you to set owners who phone requesting the name of a shop expert on that brand.

Become factory authorized. While talking to the distributor, you can ask him how to become a factory authorized service agency for "X" TV. Being one will increase the punch in your advertising. It will impress customers to have decals and signs in your shop stating you are a factory authorized service agency.

If you have attended the manufacturer's service meetings, be sure to ask for a certificate stating that you have received his "factory training." People outside of the TV servicing business instinctively feel that the certificate represents a great deal of training.

Advertise correctly. If you have a fairly extensive advertising program, you probably will not want to switch overnight to a specialty appeal. It may be best to advertise your specialization in the classified section of the telephone directory first. Be sure to become factory authorized, as pointed out before, so that you won't have any trouble being listed under the manufacturer's name in addition to your own firm name.

Later, other advertising can be switched to this appeal. You might find you can get enough effective advertising from the distributor's and set owners' recommendations.

Use common sense. It is well to wade in gradually. Don't turn down other work until you have all the "X" sets that you can handle. As they increase, you can cut down on the other types. But don't be too slow or some other shop may recognize the potentialities and beat you to it.

To specialize or not to specialize, like many other problems, involves a management decision. The decision should be based on as many relevant facts as you can obtain, viewed in the light of your experience and the experience of other firms in the same business—plus an imagination to see the possibilities in something a little different.

—30—

TECH-MASTER Custom Built KITS

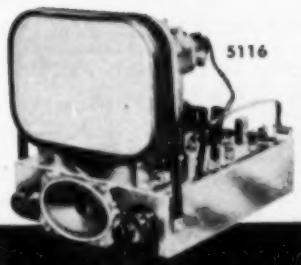

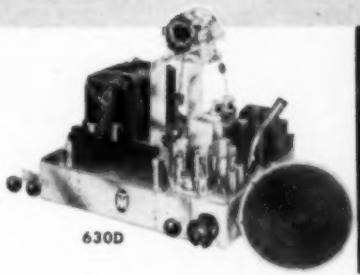

HIGH FIDELITY TV RECEIVERS and AUDIO AMPLIFIERS

Designed for the Discriminating Video and Audiophile

Model 630D: Deluxe 630-Type Circuit . . . World's Finest TV Kit.

All components used are best available. Rigid factory test standards assure years of trouble-free performance. Special Tech-Master schematic and pictorial diagrams guide every move.

- Advanced cascode TURRET TUNER adaptable to UHF without tools.
- Keyed AGC circuit.
- Full 4 Mc. bandwidth.
- 'Hi-Sweep' voltage multiplier system.
- 3-stage synch amplifier.
- 2-stage video amplifier.
- For all picture tubes, from 16" to 24".

MODEL 630D-24 (Deluxe). All principal components mounted. Complete with all components, picture tube mtg. brackets, speaker and all tubes, (less kine, wire and solder) **$159.50**

Model 5116: Universal AC/DC TV Kit. High quality TV at Low Cost.

- Advanced 12 channel Turret Tuner adaptable to UHF without tools.
- Latest hi-gain stagger-tuned IF system.
- Maximum signal amplification, even in fringe areas.
- New AGC system.
- For 14" and 17" rectangular picture tubes.

MODEL 5116: Complete with set of 16 circuit tested tubes, hardware, instructions and picture tube mounting brackets. (Less Kine, wire and solder) **$99.95**

Model TM-15A: UL* Williamson-Type Amplifier Kit.

Features a specially wound ALTEC LANSING Peerless audio output transformer. Kit furnished complete with punched chassis, transformers, tubes, all components and detailed wiring instructions.

Power Output ..... 15 watts undistorted
Output Impedance ..... 4-8-16 ohms
Input Impedance ..... High . . . for crystal pickups, tuners, pre-amps, etc.
Input Voltage ..... 1.1 VRMS (for 15W out)
Intermodulation and Harmonic Distortion .25% at 2W .45% at 5W
Hum and Noise Level: 70 db below rated output
Feedback ..... 20 db
Response 5 Watts 8 cps to 80,000 cps ± 1 db
10 Watts 12 cps to 56,000 cps ± 1 db
Tube Complement 2 6SN7, 2 5881, 1 5V4G
Power Requirements: 117 V., 50-60 cyc., 120 w
Dimensions ..... 9" x 12" x 6½"
Net Price (Kit of parts) $49.95

DELUXE PRE-AMPLIFIER KIT, Model TMD-15A, completely factory assembled, all major components mounted in place on chassis, ready to wire **$59.95**

***Ultra linear operation through use of screen-tapped primary output transformer.**

Model TM-15P: Four Channel Pre-amplifier Kit.

Complete with punched chassis, all components, tubes, cabinet, and detailed instructions.

4 Input channels
1—Low level-high gain . . . 3—Hi-impedance
Base and Treble Frequency controls:
± 15 db boost or attenuation at 20 cycles and 20 KC

EQUALIZATION CONTROL

POSITION	TURNOVER	ROLL-OFF
1	300 Cps	none-flat } for 78 RPM
2	500 Cps	none-flat }
3	400 Cps	12 db at 10 KC for 33⅓ and 45 RPM

Tube Complement ..... 1—12AX7, 1—12AU7
Power Requirement (from main amplifier)
125 volts DC at 6 ma, 6.3 volts at 600 ma
Dimensions ..... 10¾" x 4" x 4"
Net Price (Kit of parts) $19.95

DELUXE PRE-AMPLIFIER KIT, Model TMD-15P, completely factory assembled, all major components mounted in place on chassis, ready to wire **$29.95**

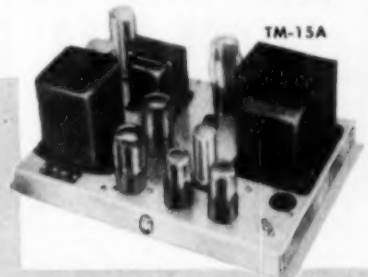

Sold by all Leading Radio Parts Distributors *Detailed Literature Upon Request*

TECH-MASTER PRODUCTS CO.
443-445 BROADWAY, NEW YORK 13, NEW YORK

If You Want Faster, Easier Installations at Lowest Cost—
BUY from NATIONAL ELECTRONICS—COUNTRY'S LEADING TV SPECIALIST

NEW SUPER FRINGE DIRECTRONIC

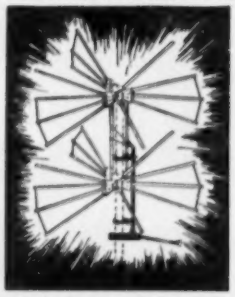

- 24 Hi-Tensil Aluminum Elements
- New High Gain
- No Motors
- Clearer Sharper Pictures
- Electronically Beamed in All Directions
- New low-loss Tubular Tri-X Cable
- Eliminates Ghosts — Interference
- New Six-Position Beam Selector

Model AX-824 as shown $26.95

New Improved Hi-Gain Super Fringe Directronic Motorless offers sensational advantages over motorized antennas—less installation cost—less upkeep. The new 24-element Directronic is beamed to any transmitter in fringe range by new 6-position Directronic Beam Selector, located at receiver. Twenty-four elements, including 6 multi-purpose reflectors, provide high gain in all directions. The newly developed low-loss Tubular Tri-X Cable minimizes attenuation of signal—permits longer transmission lines. New transmitters are coming on the air in all directions—the Super Fringe Directronic is the most efficient, least expensive, TV Antenna made for "'round the compass" reception today. Serviceman's kit contains 24 hi-tensil aluminum elements, including 6 reflectors, Directronic 6-position switch, 100 ft. Tubular Tri-X, 3 matched stacking bars, Universal U-Clamps.

SAVE WITH ROCKET 35 FOOT MAST KITS

Economy mast kit contains 3-10' seamless TRI-COATED 1¼" OD masts, one 5' mast, 500 feet of 6/30 galvanized steel guy wire, and every-thing else needed including guy rings, mast connectors, insulators, cable clamps, guy hooks, and swivel mounting base.

35-foot Mast Kit ..$15.95 25-foot Mast Kit ..$11.95

LOWEST PRICES ON ANTENNA ACCESSORIES

Mast Steel (Dualcoated 5' crimped) 1¼" O.D.	$1.08
Mast Steel (Dualcoated 10') 1¼" O.D.	1.98
Mast Connectors for 1¼" O.D. Mast	.59
Chimney Mount Complete with Straps	1.19
Peak Roof Saddle (will take up to 1½" O.D.)	1.59
Lightning Arrestor-TV	.69
Galvanized Steel Guy Wire—6/30	8¼c ft.
Rocket Twin-Lead—7/28 stranded	3c ft.
Mast Stand-off Insulators—3"	.10
Screw Type Stand-Off Insulators—3"	.03

NEW ROCKET 3 CHANNEL YAGIS

In many areas there is a real need for high gain Yagis covering 3 adjacent channels. For these requirements we offer these sensational new Rocket TRI-CHANNEL YAGIS covering Channels 2 to 13. In many cases only a high gain Yagi type will produce satisfactory pictures—and in these areas we recommend our tri-channel Yagi arrays as the most economical and satisfactory TV antenna type on the market today. Each array provides 1 reflector, 1 folded dipole, and 3 directors, designed for top sensitivity on the 3 channels covered. Offers simple-to-install quick-rig assembly—universal U-clamps for masts up to 1½" O.D.

Model CY-234	$8.50 Ea.
Model CY-345	8.50 Ea.
Model CY-456	8.50 Ea.
Model CY 7-9	4.95 Ea.
Model CY 9-11	4.95 Ea.
Model CY 11-13	4.95 Ea.

Note: Model numbers indicate channels covered.

NEW HIGH GAIN UHF YAGI

Good UHF reception in fringe areas now assured with new Rocket Broad band UHF Yagis. Compact, easy to stack for all the gain required anywhere. Three models cover all UHF channels. Rocket UHF Yagis are completely pre-assembled — you simply tighten mast clamp. Serviceman's array includes two reflectors, 2 dipoles, 4 directors and Universal mast clamp.

Model UHF-3A—Ch. 14 thru 48	
Model UHF-3B—Ch. 27 thru 62	
Model UHF-3C—Ch. 47 thru 83	
Single	$4.25 ea.
Lots of 6	3.75 ea.
Matched stacking bars—½ wave	.75 pr.

HI-GAIN SINGLE CHANNEL YAGIS

5 element—Ch. 2, 3, 4 ..$7.95 Ch. 5 or 6...$6.95
Ch. 7-13...$3.95

WRITE FOR NEW CATALOG
New Items—Lowest Prices—Best Selection

ALL PRICES F.O.B. CLEVELAND, OHIO
Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% deposit on all C.O.D. orders, please. Money-back guarantee. Prices Subject to Change Without Notice.

National Electronics
OF CLEVELAND
THE HOUSE OF TV VALUES
105 Delco Building Cleveland 3, Ohio

FREE

FREE — the latest issue of our "TV and ELECTRONICS NOTES". It presents

IMPORTANT FACTS EVERY SERVICEMAN MUST KNOW about

✓ **UHF**

Vital Serviceman's information regarding *Installation, Reception, Converting* existing Sets, *Tuners,* etc.

✓ **FRINGE AREA RECEPTION**

How to get *best* results at *lower* costs, improve performance, AND—

OTHER IMPORTANT SUBJECTS

Get this special FREE copy, or for regular subscription to "TV and Electronics Notes" send 50c.

RUSH THIS COUPON NOW

TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RN

☐ Send *FREE,* the latest issue of *"TV and Electronics Notes"* on *UHF, Fringe Area Recep.*,etc.

☐ Enclosed find 50c for regular subscription.

Name _____

Address _____

City _____ State _____

ROUND, SQUARE, KEY and "D" OPENINGS QUICKLY MADE with Greenlee Radio Chassis Punches

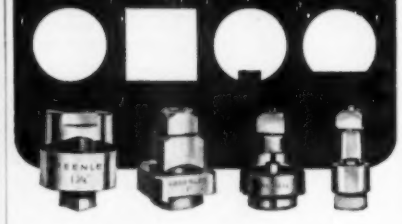

Save hours of hard, tedious work . . . cut accurate holes in chassis for sockets, plugs, controls, meters, panel lights, etc. with GREENLEE Punches. In 1-1/2 minutes or less make a smooth hole in metal, bakelite or hard rubber up to 1/16" thick. Easy to operate . . . simply turn with ordinary wrench. Wide range of sizes. Write for details. Greenlee Tool Co., 1885 Columbia Avenue, Rockford, Ill.

TOOLS FOR CRAFTSMEN
GREENLEE

DX-ING WITH THE ADMIRAL TV MODEL 19B1

By GEORGE R. ANGLADO

TELEVISION DX has become a new and exciting hobby among TV set owners. The months of January, June, July, and December are the best times for trapping the skip signals, however, reports show that signals have been received during the other months too.

Our recently-purchased 1953 Admiral receiver has been doing a good job of bringing in stations within a 300-mile radius, however, after reading reports on 1000 and more mile reception, we figured maybe something could be done to the set to enable it to get into this long-distance reception bracket.

Upon looking over the schematic for this receiver, we saw the possibility of revamping the circuit slightly to provide more gain for the long-distance stations we hoped to log.

These sets are equipped with a "DX Range Finder" control. The positions on the control are marked from 0 to 300, the 300 position being used for DX reception. With this control set in the 300 position, and using a booster with a push-pull 6J6 and rotatable yagi, we were not able to exceed the 300 mile radius.

After examining the schematic we finally pulled the chassis from the cabinet, hooked up the iron, got out a couple of resistors, and went to work. The set really performed. Not only did we hit the 1000 mile bracket—but farther—around 1200 or 1500 miles. The station logged was KRON-TV, Channel 4 in San Francisco—this from Biloxi, Miss. The miracle enabling us to pick up this station was the addition of three resistors!

Sounds too simple to be true? Sure, 1953 sets are a lot better on the whole than the 1952 line. The manufacturers are catering to the fringe area users in their later models but they can still be improved. An experimenter won't let up until it is improved, whether or not it means tearing the chassis apart and rebuilding it or buying two sets and using them both on the same chassis.

Although we didn't tear up the set, here are the simple changes that improved the long-range reception.

First, find test point "T" which is a socket located on the chassis. Using a 400,000 ohm resistor, insert one end in the test point "T" socket hole and ground the other end to the chassis. A good way to keep the resistor lead in the socket hole is to solder it to a banana type plug or to an old tube socket pin. Caution: If you live in a strong signal area, the addition of this resistor will cause the picture to tear. One means of overcoming this is to wire a toggle switch on the back of the set with one lead going to the bare end of the resistor that goes to ground and the other lead of the switch going to ground. In this way the resistor can be cut in or out of the circuit.

The second change involves unsoldering and taking out the two ratio detector resistors whose values are 10,000 ohms and replacing them with two 30,000 ohm resistors. This change improves detector action and gives greater sound output.

Good DX-ing!

—30—

A NEW CBS-HYTRON CTS-RATED* TUBE

*CTS-RATED: Rated for Continuous Television Service. In TV receivers, five tubes work . . . like transmitting tubes . . . *hard!* Account for almost 90% of your replacements. You know them: rectifiers, deflection amplifiers, damper diode. Larger-screen sets aggravate this problem. CBS-Hytron recognizes your need for huskier tubes for these sockets. Brand new designs, not just improved tubes. CTS-Rated 5AW4 . . . another CBS-Hytron first . . . is your answer for the low-voltage rectifier socket. It is CTS-Rated: (1) For heavier average (250 ma. max. d-c) and peak (750 ma. max. d-c) currents, (2) With big safety margins at these currents. You can depend upon the 5AW4 for continuous, trouble-free service. Yes, more CBS-Hytron CTS-Rated tubes are coming. Watch for them.

MECHANICAL ADVANTAGES

PLATE — Note formed A-frame construction. Each plate of 5AW4 is formed into two cylinders containing the filament. Uniform filament-to-plate spacing and uniform filament performance avoid hot spots on filament, plate . . . and bulb. Oversize radiating fins and extra large surfaces between formed cylinders dissipate heat faster. Sturdy structure is rigidly supported at eight points.

FILAMENT — Massive, heavy-duty, 20-watt filament offers generous reserve of emission. Cuts burn-outs due to ionization attack and back emission. Transmitting-type filament hook and spring suspension prevent sagging — yet reduce stresses on filament. Permit mounting 5AW4 in any position. Useful filament area is contained within formed cylinders of plate . . . to minimize external voltage drops.

CBS-HYTRON 5AW4†

NEW HEAVY-DUTY WORK HORSE CUTS 5U4G CALL-BACKS

Worried about slumping TV set performance, because of heavily loaded 5U4G's? Forget it. Use new CBS-Hytron CTS-Rated* 5AW4. A replacement for the 5U4G, the 5AW4 recaptures . . . and keeps . . . that new-set sparkle. Maintains full voltage, despite heavy load. Minimizes burn-outs. Avoids filament shorts while testing chassis on side. Loafs on tough jobs. Gives long, long, trouble-free life. The 5AW4 will cut your call-backs. Boost your profits. See it . . . buy it . . . soon. At your CBS-Hytron jobber's.

†Patent applied for

COMPLETE 5AW4 DATA FREE

See your CBS-Hytron jobber. Or write direct today.

New...Free DECAL

sells for you! *Sells* your magic ability to recapture new-set sparkle. Let this decal pull customers to you. Get it from your CBS-Hytron jobber today.

CBS HYTRON
Manufacturers of Receiving Tubes Since 1921

CBS-HYTRON Main Office: Danvers, Massachusetts
A Division of Columbia Broadcasting System, Inc.

RECEIVING . . . TRANSMITTING . . . SPECIAL-PURPOSE AND TV PICTURE TUBES • GERMANIUM DIODES AND TRANSISTORS

READ ALL ABOUT IT !!
TM NEWS
TM NEWS
TELEMATIC ONE JOBALEMON ST. BROOKLYN 2, N. Y.
SENSATIONAL NEW UHF ANTENNA
The ULTRA MATIC
ULTRA
• SENSATIONAL
• DIRECTIONAL
• ECONOMICAL
• SENSITIVE
• HIGH GAIN
• LOW LOSS
• COMPACT
KEEP YOUR EYE ON TELEMATIC AND SEE THE DIFFERENCE!
AS-18
WT-28
The only complete line of corrective television aids designed for your televiewing pleasure. Laboratory engineered and tested to the point of absolute perfection. When servicing requirements call for UHF or VHF antennas, TVI correction, antenna switching, matching, receiver coupling, filtering or trapping . . . think of . . . insist on TELEMATIC!
UNCONDITIONALLY GUARANTEED!
WT-300
AM-62
Booth 211 May Electronic Parts Show CHICAGO
TELEMATIC INDUSTRIES INCORPORATED

Regenerative Circuit

(*Continued from page 49*)

ing L_1. This, in conjunction with the fixed condenser C_1 gives sufficient station separation for satisfactory tuning of the short-wave bands. If more bandspread is desired, this can be achieved by connecting a small variable condenser of about 30 $\mu\mu$fd. in parallel with C_2.

The coils were wound on old octal tube bases. This permitted the least modification of the broadcast receiver chassis used as a base. Of course, the constructor who is starting out with a new, blank chassis and all new parts could substitute a different socket and other coil forms, although the coil data would have to be recalculated for the different form diameter used. The diameter of an octal tube base is slightly over $1\frac{5}{16}$".

All the coils are closewound, and with the specified number of turns, the amateur bands will fall approximately in the middle of the tuning range. L_2 should be wound rather loosely so that its spacing from L_1 can be adjusted for best performance. Once the optimum spacing has been found, the whole coil should be coated with radio cement or coil dope. If 5/40 Litz wire is not readily available for the coils, #26 enameled or *Formvar* wire can be used.

L_1 and L_2 should be wound in the same direction and the relative polarity of the connections should be observed. This is the familiar precaution with regenerative sets, for, as is well known, if the polarity of the connections or induced voltages is wrong, the feedback will be degenerative and the set will not work. While this is an important matter its handling turns out to be very simple.

—30—

BUY TEST EQUIPMENT
ON THIS RADICALLY NEW
TIME PAYMENT PLAN

NO INTEREST!! - NO CARRYING CHARGES!!

USE CONVENIENT TIME PAYMENT ORDER BLANK BELOW

Superior's New Model 770

VOLT-OHM MILLIAMMETER

Sensitivity—1000 ohms per volt

Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. • Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range. • Housed in round-cornered, molded case. • Beautiful black etched panel. Depressed letters filled with permanent white, insures long-life even with constant use.

SPECIFICATIONS:

6 **A.C. VOLTAGE RANGES:** 0-15/30/150/300/1500/3000 Volts.
6 **D.C. VOLTAGE RANGES:** 0-7.5/15/75/150/750/1500 Volts.
4 **D.C. CURRENT RANGES:** 0-1.5/15/150 MA. 0-1.5 Amps.
2 **RESISTANCE RANGES:** 0-500 Ohms. 0-1 Megohm.

Model 770 is an accurate pocket-size V.O.M. Measures only 3⅛"x5⅞"x2¼".

$14.90 NET

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

Superior's New Model TV-11

TUBE TESTER

• Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary. • Uses no combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. • Free-moving built-in roll chart provides complete data for all tubes. • Phono jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose external connections.

Operates on 105-130 Volt 60 Cycles A.C. Hand-rubbed oak cabinet complete with portable cover .....

$47.50 NET

Superior's New Model 670-A

SUPER-METER

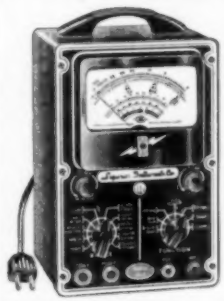

A *COMBINATION* VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts.
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms
INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
DECIBELS: —6 to +18 +14 to +38 +34 to +58

Comes housed in rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 6¼"x9½"x4½".

$28.40 NET

ADDED FEATURE:
The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

Superior's New

TV BAR GENERATOR

THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!

CONNECTS DIRECT TO ANTENNA POST

NO CONNECTION INSIDE RECEIVER

Features.—Can be used when no stations are on the air. • Provides linear patterns to adjust vertical and horizontal linearity • Provides vertical and horizontal sweep signals • Provides signal for testing video amplifiers.

TV Bar Generator comes complete with shielded leads and detailed operating instructions .....Only

$39.95 NET

Superior's Model 660-A—A NEW A.C. OPERATED

SIGNAL GENERATOR

Provides Complete Coverage for A.M.—F.M. and TV Alignment

• Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. • Accuracy and stability are assured by the use of permeability trimmed Hi-Q coils. • R. F. available separately or modulated by the internal audio oscillator. • Built in 400 cycle sine wave audio oscillator used to modulate the R. F. signal also available separately for audio testing of receivers, amplifiers, hard of hearing aids, etc. • R. F. Oscillator Circuit: A high transconductance heptode is used as an R. F. oscillator, mixer and amplifier. Modulation is effected by electron coupling in the mixer section thus isolating the oscillator from load changes and affording high stability. • A. F. Oscillator Circuit: A high transconductance heptode connected as a high-mu triode is used as an audio oscillator in a high-C Colpitts Circuit. The output (over 1 Volt) is nearly pure sine wave. • Attenuator: A 5 step ladder type of attenuator is used.

• Tubes used: 1—6BE6 as R. F. Oscillator, mixer and amplifier. 1—6BE6 as Audio Oscillator. 1—6M6 as Power Rectifier.
The Model 660-A comes complete with coaxial cable test lead and instructions .....NET

$42.95 NET

NEW TIME PAYMENT PLAN

ORDER BLANK

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. S-56, 38 Murray Street, New York 7, N. Y.

Please send me the units checked below. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

☐ **MODEL 770** .....Total Price $14.90
$2.90 down payment. Balance $2.00 monthly for 6 months.

☐ **MODEL TV-11** .....Total Price $47.50
$11.50 down payment. Balance $6.00 monthly for 6 months.

☐ **MODEL 670-A** .....Total Price $28.40
$7.40 down payment. Balance $3.50 monthly for 6 months.

☐ **TELEVISION BAR GENERATOR** .....Total Price $39.95
$9.95 down payment. Balance $5.00 monthly for 6 months.

☐ **MODEL 660-A** .....Total Price $42.95
$12.95 down payment. Balance $5.00 monthly for 6 months.

☐ I enclose $ ..... as down payment.

☐ Ship C.O.D. for the down payment.

Signature .....

Name .....

Address .....

City ..... Zone ..... State .....

SENSITROL RELAY

WESTON SENSITROL, coil sensitivity only 10 microamps! Built like meter. At 10ua, needle swings over into permanent magnet which grips it to close contacts rated 1 ampere. Perfectly damped; vibration will not close contacts. Built-in reset relay unlatches contacts when 12 or 24 volts AC or DC is momentarily applied to reset leads. The Sensitrol works directly from photocells, thermocouples, or any source of minute current. No electronic amplifier needed! A $69.50 precision device for only..... $12.95

SENSITIVE POLARIZED RELAY

This is the device that the services use to replace selsyns. Now offered to the public for the first time! SP-DT, both contacts normally open. The POLARITY of an applied 7½ VDC, 5 MA current determines which contact closes. Use for micro-positioning, remote control, model control, etc. Our free data sheet shows you just how to use it. In metal box with two other heavier duty relays. NEW, slightly dirty. $6.95
(Shipping weight, 4 lbs.)

SUPER SENSITIVE RELAY BK-7-B

Single pole, double throw. Coil 4000 ohms. Sensitivity accurately adjustable on calibrated scale. At 5 on scale sensitivity is ½ milliamp (1 milliwatt, 2 volts) and from 5 to 40 on scale the sensitivity decreases linearly to 1.5 ma (9 milliwatts, 6 volts). Thousands of uses: telemetering, voice-operated or capacity operated or thermocouple operated circuits, sequence circuits, etc. Fully encased, 1⅝"x3⅛"x 1¼" deep. Weight, 6 oz. With hinged contact-inspection door and screwdriver adjustable stationary contacts....Brand New. Only $2.95 each, 10 for $17.50
(Shipping Weight, each, 1 lb.)

A SENSITIVE RELAY!

Closes at 4 to 5 ma. (Extra set of SP/ST contacts for additional sequence, close at 5 ma. Coil 6000 ohms. Sensitivity easily altered by bending limit arm or changing spring. Only 1⅛" x 2¼" x 1⅝" overall; dozens of applications, now offered at a "stock no" price. Removed from clean equipment.
ONLY 98c each, 3 for $2.75
Boxed, reconditioned, like new..... $1.69

LOOKING FOR OIL FILLED CONDENSERS?
Send for our list of condenser bargains

12 CHANNEL T-V TUNER

Complete front end, famous make "Silver Circle." Furnished with original factory instructions, less tubes. Dozens of uses; receivers, converters, etc. The TV bargain of the year for builders, amateurs, students. These are factory rejected for minor damage..... ONLY $1.95 each, 3 for $5.00
(Shipping Weight, each, 3 lbs.)

6-9.1 MC Command Receiver, EXCELLENT, with tubes $6.95
(Shipping Weight, 8 lbs.)

274N PLUG. 7-prong male plug to fit back of command revrs, and xmtrs. This is the same plug as used in the racks. NEW each 21c, five for $1.00
Local Control Adapter Parts for 274N or ARC-5 revr. Exact pot, switch, knobs, etched plate, and instruction data. Ready to mount..... $1.29
SPLINE TUNING KNOB..... 75c

0-1 DC MILLIAMMETER

A hard-to-get meter at a hard-to-beat price. These are unused 2½" aviation type meters which we have modified for general use, including new white scale plate with large, easy to read calibration.
ONLY $4.50

ATTENTION, TELETYPE USERS

We buy and sell teletype equipment. Tell us what you want or what you've got, or both.

ANTENNA MAST SECTIONS, MS-49, 50, 51, 52, 53. New, original packing..... Each 39c

PRECISION CALIBRATED TUNER

Build a Q-meter or an audio oscillator, a signal generator, a VFO, an ultra-stable receiver, or — you name it! Lab-standard accuracy and resetability. 3 gang condenser assembly with 4" precision dial etched 1.5-12 mc in 3 bands plus 8 reference scale. Triangular plastic hairline indicator. 50:1 ratio drive assembly, all gears spring-loaded double-section. Has tuning lock. Plates are two single spaced 250 mmf, and one double-spaced 260 mmf section. Use double spaced section to eliminate drift.
(Shipping Weight, 6 lbs.)..... ONLY $4.95

BROADCAST BAND & AERO

MN-26-C Remote Controlled navigational direction finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC. 24 V. Self-contained dynamotor supply. Complete installation, including receiver, control box, loop, azimuth control, Left-Right indicator, plugs, loop transmission line, and flex. shafts. BRAND NEW, ORIG. PACK..... $69.50
(Shipping Wt. 75 lbs. Express Collect.)

SUPER HI-FI HEADSET BUYS

1. Uses annular grooved plastic fibre cones with voice coils as in speakers, and padded chamois ear muffs to obtain spacing for correct acoustical load. Gives finest music reproduction, far beyond upper and lower limits of auditory perception. Pair in series has measured impedance of 600 ohms at 1000 cycles, obtained with built-in high quality transformers. Checked out with freshly laundered ear pads.. $7.95
2. FOR AUDIOPHILES ONLY. Same general description as above except that these are made by America's leading hi-fi headset manufacturer, and currently sell for $45.00 the pair! Each set comes to you with response curves for each phone, as individually calibrated in our own lab. Satisfaction guaranteed. Complete, boxed..... $17.50
(Shipping weight, 3 lbs.)

6 V VIBRATOR KIT. Vibrator plus non-sync transformer, two outputs: 700 VCT, 145 ma for plates; 15 V for bias. Using 5R4G can deliver 300 V at 120 ma. (Shipping wt. 6 lbs.)
NEW $2.89

OUTPUT TRANSFORMER. 5000 ohms input to TWO outputs, 300 ohms or 3.5 ohms. Use as output for 12A6, 6V6, etc. or to match speaker or headset. NEW, potted, shielded 75c

EASY MONEY!

We're still buying surplus gear. Tell us what you've got, its condition, and your price. If we like it you'll get our check quick.

G. L. ELECTRONICS

905 S. Vermont Ave., Los Angeles 6, Calif.
All Prices F.O.B. Los Angeles. Calif. Buyers Add Sales Tax
SEND FOR OUR LATEST FLYER.

WHAT'S *New in Radio*

For additional information on any of the items described herein, readers are asked to write direct to the manufacturer. By mentioning RADIO & TELEVISION NEWS, the page and the issue number, delay will be avoided.

12-VOLT POWER SUPPLY

Electro Products Laboratories, Inc., 4501 N. Ravenswood Ave., Chicago 40, Ill. is offering a filtered d.c. power supply which provides adjustable d.c.

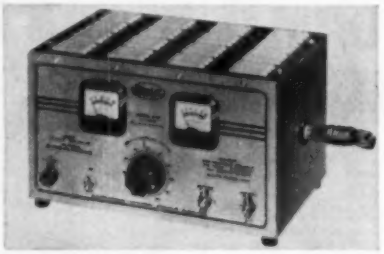

voltage (0-16) from an a.c. source, for all current loads from 1 to 8 amperes continuous output.

The C-12 incorporates a special filter circuit which reduces a.c. hum or ripple to less than 3% at 8 amperes.

Full performance data and information on your nearest distributor is available from the company on request.

TEST GEAR

A new frequency and modulation meter for use in the maintenance of two-way radio systems has been announced by the Electronics Division of *General Electric Company*, Syracuse, N.Y.

The meter, type ST-13-A, measures modulation swing and carrier frequency of FM transmitters and features both high and low r.f. output for receiver alignment. It is available with either one or two crystals, for servicing single or two-frequency systems, in the low (25 to 50 mc.),

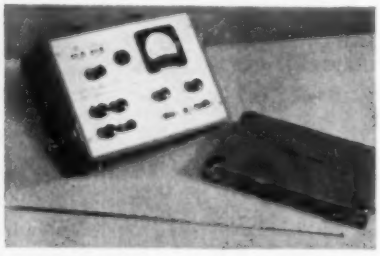

medium (72 to 76 mc.), and high (152-174 mc.) bands.

For complete data write Dept. N-14 of the Inquiry Section of the company.

STORAGE BINS

Akro-Mils, Inc., P.O. Box 989, Akron 9, O. has added a new 128-drawer model to its line of "Haz-Bin, Jr." storage units. The new cabinet has been designed to hold the hundreds of different small parts used in service shops and dealer outlets.

The cabinet provides maximum visibility and space economy. Clear plastic drawers make visual selection possible. The line is now available in nine models with 8, 12, 16, 24, 32, 48, 64, 96, and 128 drawers. Drawer size is the same in all models. The individual drawers can be subdivided into 2 or 3 separate compartments—lengthwise or crosswise. A built-in safety catch prevents accidental spilling of contents should drawer be pulled out too far.

ROTRON BLOWER

Rotron Mfg. Co., Schoonmaker Lane, Woodstock, N. Y. is in production on a new blower which is small, light-weight, direct-driven, brushless, and with axial flow.

Designed to be built into electronic and instrument cabinets whenever

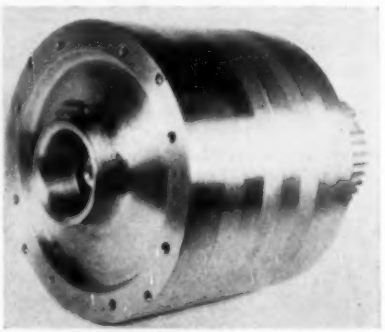

high air pressures are required in combination with relatively low volumes, these new units are powered by totally enclosed induction motors built on a single shaft with the blower.

Over-all diameter is 7¼" and length varies with number of stages and type of power supply. Pressures range from 5" to 28" of water.

RADIO PACKSET

Industrial Radio Corp., 428 N. Parkside Ave., Chicago 44, Ill. is in production on a portable, two-way radio packset for industrial, police, fire, utility, and conservation department applications.

The "Pak-Fone" consists of an 8-tube transmitter and 15-tube receiver and is completely self-powered. It conforms to FCC licensing regulations and is designed to provide two-way radiotelephone communication between other portable stations, mobile, or fixed stations.

The units are designed to operate in either the 25 to 50 mc. or the 152-174 mc. bands. A complete descrip-

tion and technical specifications are available from the company.

PRESELECTOR

Radio Mfg. Engineers of Peoria, Ill., is currently offering a new preselector for coverage of all amateur bands from 3.5 to 30 mc.

The DB23 has three neutralized push-pull stages employing 6J6 dual-

triodes in a novel combination of selected and wideband r.f. amplifiers. The manufacturer claims a constant gain of 25 db or more throughout all amateur bands (from 3.5 to 30 mc.) with an average image ratio improvement of approximately 12 db on 21 mc. and 25 db on all lower frequencies. Signal-to-noise ratio is said to be better than 7.5 db over that of the receiver itself.

The unit is completely self-contained and is housed in a streamlined cabinet measuring 5" x 7⅝" x 6⅛". Three easy-to-use controls for "On-Off," "Band Selector" and "Ant. Peaking" simplify operation.

MINIATURIZED CIRCUITS

Vacumet Inc., 1267 N. Clybourn Ave., Chicago 10, Ill., has developed a line of "in-bedded" circuits which offers new opportunities for miniaturization of circuits and components.

The "in-bedded" process consists of embedding solid metal conductors which are formed into any desired circuit pattern, into the face of a suitable insulating base. The base material can be plastic, glass, or ceramic and a special molding process makes the metal conductors and base an integral unit.

Conductor line widths as narrow as .001" can be produced and intricate designs are readily reproduced. "In-bedded" wiring .005" wide can handle a continuous current load of 250 ma. and the line width can be held to within ±.0002".

Circuit wiring, commutators, switches, inductors, and other components can be made by this process.

7" SCOPE KIT

Electronic Instrument Co., Inc., 84 Withers St., Brooklyn 11, N. Y., is in production on the Model 470, a 7" oscilloscope which is available in both kit and wired form.

Features of this new scope include boosted vertical sensitivity of 10 mv. r.m.s./in.; extended flat frequency response from 10 cps to 1 mc., ±2 db; three-step frequency-compensated attenuator input to vertical channel; push-pull outputs for both vertical

by every test
ATR is best!
ATR
AUTO RADIO
VIBRATORS
Have Ceramic Stack Spacers
A COMPLETE LINE OF VIBRATORS
Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life. Backed by more than 22 years of experience in Vibrator Design, Development, and Manufacturing.
"A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators
✓ NEW MODELS
✓ NEW DESIGNS
✓ NEW LITERATURE
ATR
Free
See your jobber or write factory
AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA—U. S. A.

1 MAN TURNS A CRANK... AND UP GOES THIS LOW-COST REINFORCED TOWER

Penn's special hoist permits 1-man erection of this new telescoping tower to heights of 45 feet.* No elaborate equipment required. Mount adjustable to all antenna rotors . . . mast can always be centered over tower. Tower clamp—reinforced at section joints.

The Standard Teletower

Rugged steel braces that reinforce tower also serve as climbing rungs. Straight top design makes climbing easier. Base adjustable to either flat or sloping surfaces. Competitively priced.

Write today for free bulletins and price list.

*Using 20 ft. pole

PENN Telescoping Tower

PENN Teletowers Tenna-Mast Hardware

PENN BOILER & BURNER MFG. CORP., LANCASTER, PA.

ANOTHER OUTSTANDING JOBBER

CLAYTON RADIO PARTS

3749-51 N. Ashland Ave.
Chicago, Illinois

HAS THE SENSATIONAL NEW EICO 470-K 7" SCOPE KIT IN STOCK!

$79.95

New Electronic Headquarters—

VAN SICKLE RADIO SUPPLY CO.

1320 So. Calhoun St. Phone E-4136

FORT WAYNE 2, IND.

Please note new address. Eugene Van Sickle, Owner

RADIO & TV RECEIVING

Windsor TUBES

TESTED and GUARANTEED for PEAK PERFORMANCE!

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
1A7GT	$ .61	6BU8GT	.89	12AT6	.48
1B3GT	.63	6BE6	.46	12AT7	.68
1L4	.57	6BF5	.60	12AU6	.43
1N5GT	.57	6BF6	.39	12AU7	.53
1R5	.58	6BG6G	1.34	12AV6	.37
1S4	.61	6BH6	.57	12AV7	.79
1S5	.47	6BJ6	.68	12AX7	.61
1T4	.56	6BK7	.88	12BA6	.45
1T5GT	.71	6BQ6GT	.89	12BD6	.46
1U4	.55	6BQ7	.84	12BE6	.47
1U5	.48	6C4	.37	12BH7	.63
1X2A	.67	6C8G	.53	12SA7GT	.52
2X2	1.50	6CD6G	1.85	12SK7GT	.50
3Q4	.60	6J5GT	.40	12SL7GT	.61
3Q5GT	.65	6J6	.62	12SN7GT	.54
3S4	.55	6K6GT	.41	12SQ7GT	.42
3V4	.56	6L6GA	.80	19BG6G	1.39
5R4GY	.91	6U7GT	.50	19T8	.79
5U4G	.40	6X8	.46	25BQ6GT	.89
5V4G	.75	6X8GT	.66	25L6GT	.48
5Y3GT	.39	6SA7GT	.52	25W4GT	.48
5Y4G	.39	6SF5GT	.60	25Z6GT	.42
6AB4	.40	6SH7GT	.47	35B5	.48
6AQ5	.54	6SK7GT	.50	35C5	.46
6AK5	.98	6SL7GT	.62	35L6GT	.47
6AL5	.40	6SN7GT	.54	35W4	.30
6AQ5	.46	6SQ7GT	.42	35Z5GT	.30
6AR5	.38	6T8	.77	50B5	.47
6AS5	.80	6U8	.78	50C5	.47
6AT6	.38	6V6GT	.46	50L6GT	.47
6AU6	.43	6W4GT	.45	117Z3GT	.39
6AV6	.37	6W6GT	.57	0A2	.88
6BA6	.45	6X4	.34	5654	1.50
6BA7	.60	6X5GT	.33		
6BC5	.53	6Y6G	.58		

To merit your confidence—to insure your satisfaction—Every tube we ship has been tested in a radio or TV set for PEAK PERFORMANCE. Each tube is attractively packaged in individual carton—and, Each WINDSOR Tube you buy carries the full RTMA GUARANTEE!

25% Deposit with Order. All Merchandise F.O.B. New York City. For orders less than $10, add $1 handling cost. Deduct 2% if full remittance accompanies order. All merchandise subject to prior sale and price change without notice.

DEPT. N-5

Windsor ELECTRONIC TUBE CO.

1515 SHEEPSHEAD BAY ROAD, BROOKLYN 35, N. Y.

and horizontal amplifiers; wide range gain and sweep control; internal voltage calibrator for peak-to-peak voltage measurement; internal retrace blanking; and provision for direct connection to CRT plates.

In kit form the new scope is designated as the Model 470-K. Further information is available from the company on request.

NEW V.T.V.M.

Elliott Laboratories, 50-34 201st St., Bayside, N. Y., has released its Model 940 v.t.v.m. to the trade.

Peak-to-peak or rms voltages with a frequency response of 25 to 10,000 cycles are obtainable. The input resistance of 16.5 megohms will not cause the circuit under test to be overloaded.

The unit uses a dual-triode balanced bridge circuit. Six a.c. ranges (3, 15, 30, 150, 300, and 1500 volts) and six d.c. ranges (same voltages) are included. Resistance is measured in five ranges from 0-1000, 10,000, 1 megohm, 10 megohms, and 1000 megohms while decibels may be read on five ranges.

The meter is housed in a bakelite case measuring 5¼" x 6⅞" x 2¼".

AMPLIFIER KIT

Philmore Mfg. Co., Inc., 113 University Place, New York, N. Y., has introduced a 20-watt high-fidelity amplifier in kit form.

The preamplifier and amplifier are built onto the same chassis. Four separate jacks are provided for magnetic pickup, microphone, crystal pickup, and radio or TV. Volume, bass, and treble control switches are on the front panel. The rear panel carries

while others plunged
WE WAITED

while others promoted
WE TESTED

while others gambled
WE ENGINEERED

NOW VEE-D-X

GUARANTEES YOU
THE *finest*

BOW TIE

OF THEM ALL

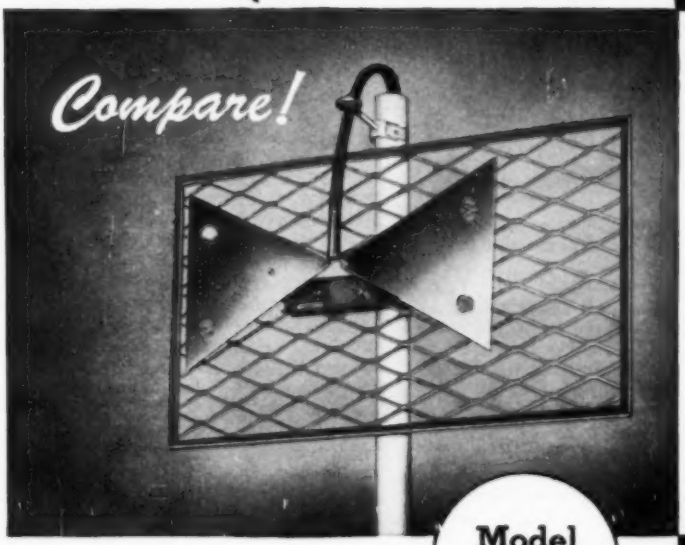

Model BT-U

- Precision-built
- Easiest to install
- Brilliant performer
- 8 db gain across the entire UHF band
- 50% additional gain on stacked arrays
- Engineered for super sharp picture reception from 470 to 890 mcs.
- Assembled in less than a minute
- Weather-resistant finish
- Compact packaging — only 12" by 20" by 1½" deep
- No insulators required

The Aristocrat of Bow Ties

BASED ON A COMPLETELY *New Antenna Formula*

- Eliminates insulators
- Permits all-metal construction
- Higher gain
- Flatter response over the

ENTIRE **UHF** BAND

EXCLUSIVE VEE-D-X FLEX-CLAMP

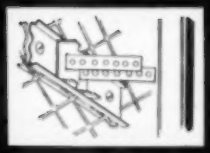

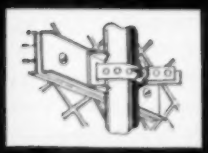

This exclusive VEE-D-X feature makes mounting of the BT-U amazingly fast and easy; especially when adding to existing installations at rooftop. No more fussing or fumbling with U-Bolts — just one screw to tighten and FLEX-CLAMP holds the antenna with a vise-like grip. FLEX-CLAMP completely facilitates probing — just loosen the screw and the antenna can be moved up or down the mast with ease. Will accommodate up to 1½" mast.

VEE-D-X STACKED BOW TIE

For fringe area reception

This stacked array provides 50% additional gain on all UHF channels. A special phasing harness, VEE-D-X screen clips, plus exclusive FLEX-CLAMP, permit fast, easy installation of this unit. Order stacking harness Model BTH-U.

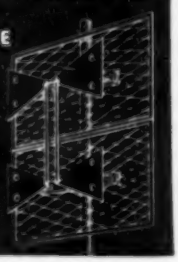

La Pointe ELECTRONICS INC.
ROCKVILLE, CONNECTICUT

May, 1953

NOW!
TEST SERVICE
12v. AUTO RADIOS
Electro
ELECTRONIC EQUIPMENT
New DC Power Supply
Model C-12
0-16 Volts from 0-8 Amperes Continuous Output. Up to 12 Amperes Intermittently

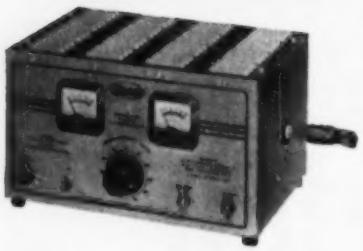

Only 3% Ripple at full load!

Completely variable output, makes it possible to test equipment under any voltage input condition. Provides filtered adjustable DC voltage for testing and servicing 12 volt and 6 volt auto radios from AC lines. Operates electronic equipment used on trucks, tanks and other mobile units; low voltage devices. Utilizes Superior Powerstat Voltage Control (Model 10) for extremely fine voltage adjustments.

See Your Nearest Parts Jobber!

Write for FREE BULLETIN!

MODEL BJ	6 Volts, 1-12.5 Amps. 5% Ripple
MODEL B	6 Volts, 1-20 Amps. 3% Ripple
MODEL N	0-28 Volts, 1-15 Amps. 8% Ripple
MODEL NF	0-28 Volts, 1-15 Amps. 1% Ripple

ELECTRO PRODUCTS LABORATORIES
4501-Nc No. Ravenswood Ave., Chicago 40, Ill.
CANADA: Atlas Radio Corp., Ltd., Toronto, Ont.

a switch with three preamplifier inputs.

This kit is illustrated and described in the company's 16-page 1953 catalogue which is available on request.

NOISE SUPPRESSOR

A new model "dynaural" noise suppressor, the Type 111-B, has been added to the line of audio equipment made by *Hermon Hosmer Scott, Inc.* of 385 Putnam Ave., Cambridge 39, Mass.

The new unit features redesigned dynamic noise suppression circuits, providing improved operation with LP records and extended bass-response loudspeaker systems. In addition, the effectiveness of low-frequency rumble suppression has been increased substantially.

The Type 111-B is designed to be used with the company's Type 214-A remote control amplifier but may also

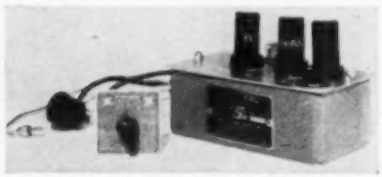

be used with amplifiers of other manufacturers. A free bulletin will be sent on request.

WIDE-ANGLE TRUMPET

University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N. Y., has developed a wide-angle trumpet which features a pair of exponential horns having twin air columns in a single assembly.

The "Cobreflex-2" is designed so that the wave fronts from each mouth form a single, uniform arc which results in a smooth radiation pattern free from the usual cancellations. Sound dispersion is 120 degrees horizontally and 60 degrees vertically. Low frequency cut-off is 250 cycles for maximum penetration of high noise levels without low-frequency masking effects.

WELDING UNIT

Precision components for transistors may be produced in quantity with variations of a new machine developed by *Kahle Engineering Co.,* 312 Seventh St., North Bergen, N. J.

The automatic lead wire welding machine (Model 2148) was designed and built to make 12,000 three-piece leads per hour for miniature receiving tubes. This machine is the basis of another version which is capable of turning out leads for transistors.

The company will supply complete details on the Model 2148 and other machines in its line which are adaptable to transistor production.

FM-AM TUNER

A new FM-AM radio chassis for built-in installations has been introduced by *Arthur Ansley Mfg. Co.* of Doylestown, Pa.

Using 10 tubes, including rectifier, and a straight a.c. circuit with power

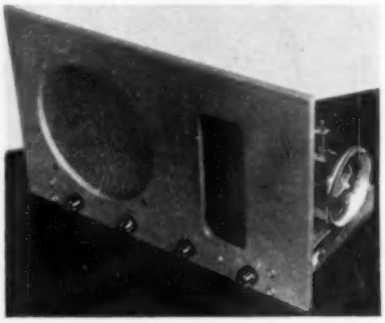

transformer, the set, known as the Model R-1 chassis, gives 5 watts' output. It is equipped with a phono jack and a phono position on the bandswitch for use with a record changer or player.

The complete set, with 8" speaker, is mounted on a natural-finish birch panel which measures 10" x 16". Behind-the-panel depth is 8".

MIDGET TAPE RECORDER

Mohawk Business Machines Corp., 47 West Street, New York, N. Y., has introduced a complete recording-playback system which weighs less than 6 pounds and is only 6 inches in length over-all.

The "Message-Repeater" uses an endless plastic tape enclosed in a cartridge the size of a pack of cigarettes. The unit contains a microphone and *Alnico* V speaker and through use of an amplifier booster and external speaker can be used as a public address system.

Messages up to two minutes in length can be recorded or the two-minute interval can be broken down into shorter messages. Previous recordings are automatically erased when a new message is spoken into the microphone.

NEW CARBON INK

Electrochemical Laboratories, 1430 Terrace Drive, Tulsa, Oklahoma has introduced a new carbon ink which, it is claimed, has very unusual qualities.

The carbon suspension has the covering power of India drawing ink, but is so stable that it can be used in some fountain pens and withstands freezing and thawing without harm.

Good adhesion on glass, smooth cellulose acetate, cellulose nitrate, etc. is claimed. It is a two-minute drying ink. Work done with this ink can be rendered water resistant by a brief heat cure at 180 degrees F.

It can be used for marking recording tapes, etc. Full details on this new product are available from the company on request.

CBS-HYTRON TRANSISTORS

CBS-Hytron, Danvers, Massachusetts is now in mass production on two point-contact type transistors—the PT-2A for amplifying and the PT-2S for switching.

Both units are moisture resistant, are available as plug-in or solder-in styles, have sturdy triangular basing, polarized base connections, are auto-electrically formed, are thoroughly stabilized, and operate at temperatures up to 55 degrees C.

Data on the PT-2A, the PT-2S, and the associated T-2 socket is available from the company on request.

AUTO VIBRATOR

P. R. Mallory & Co., Inc., 3029 E. Washington St., Indianapolis 6, Ind., has introduced a new vibrator which is designed to meet the special requirements of automobile radio sets which operate on 12 volt systems.

The new vibrator is the G874, produced as a replacement for original equipment vibrators in audio radio sets used in 1953 *Cadillacs*, *Buicks*, *Oldsmobiles*, and *GMC* trucks.

The G874 measures 1½" x 3¼" and has a unique pin arrangement which serves as a guide for quick insertion of the vibrator into the set. It also prevents it from being plugged into a 6 volt set by mistake. The pins are arranged in triangle formation with the longer pin connected to the reed.

"LOK-BLOK" SCREWDRIVER

Upson Bros., Inc., of Rochester 14, N. Y., is offering a new type of screwdriver whose resistance to torque and penetrating force has been increased beyond normal requirements for such units.

This increase in resistance to two of the most important factors contributing to screwdriver failure has been made possible by a new blade locking method.

The new "Hold-E-Zee" line features a precision-molded hexagonal block of extra hard plastic which drive-fits with extremely close tolerance into a hex cavity in the insulating handle. This permits the blade and block to freeze for utmost sturdiness.

POWER RHEOSTATS

Tru-Ohm Products, 2800 Milwaukee Ave., Chicago 18, Ill., has added three new power rheostats to its line. Available sizes now include 50, 75, 100, and 150 watt units.

Each of the models incorporates an extra deep ceramic core on which the resistance wire is toroidally wound and bonded in place with vitreous enamel. Positive and constant brush

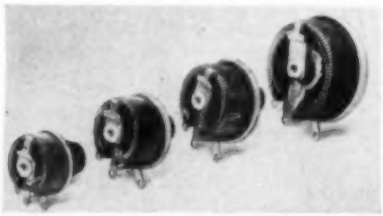

pressure is provided with an exclusive torsion spring assembly.

Standard and special versions of these power rheostats are available. For complete information write the company direct. —30—

Choose a McIntosh Amplifier for the HEART of your system.

Just as your *heart* sends life-giving blood surging through your body, so the amplifier acts as the pump, the power, the *heart* of your sound system. Your amplifier must accept and build up all tones and send them on their way to your loudspeaker. A McIntosh Amplifier does this best because it is better engineered. McIntosh's patented circuit and unity coupled output transformer make it more efficient. You get more power with the same size tubes and power input. McIntosh is built with better components, for example, grain oriented steel cores. Better designed . . . better engineered . . . with but one thing in mind . . . *greater listening pleasure for you.* McIntosh Amplifiers are used by leading radio stations, laboratories and recording studios throughout the world. If you're planning better music, make your amplifier a McIntosh.

LOST INSTRUMENTS

Send for McIntosh's interesting and informative 32 page booklet explaining high fidelity reproduction. It's available free upon request. Send for your copy of "Lost Instruments" today!

McIntosh LABORATORY INC.
326 Water Street • Binghamton, New York

BECOME AN

ELECTRICAL ENGINEER

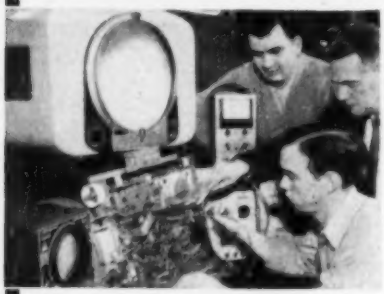

Bachelor of Science Degree in 36 months.

Major in Electronics or Power. Now, prepare for a career in these rapidly expanding fields.

This school will prepare you to become an engineer, technician or service man. Previous military, academic or practical training may be evaluated for advanced credit.

Enter Both Radio and Television

In 12 months you can attain the *Radio-Technician's* certificate. An added 6 months course qualifies you for the *Radio-TV Technician's* certificate and the Degree of "Associate in Applied Science." The Technician's course is the first third of the program leading to a Bachelor of Science Degree in Electrical Engineering with a major in Electronics.

Also offered: 12-month Radio-TV service course; 12-month Electronics or Electro Technician Courses; 6-month Electrical Service Course and 3-month refresher and general preparatory classes.

Terms Open April, July, Oct., Jan.

Famous for its Concentric Curriculum. Faculty of specialists. 50,000 former students. Annual enrolment from 48 states and 23 overseas countries. *Non-profit. 50th year.* Courses approved for Veterans.

MILWAUKEE

SCHOOL OF ENGINEERING

MILWAUKEE SCHOOL OF ENGINEERING
Dept RN-553, 1025 N. Milwaukee
Milwaukee 1, Wisconsin

Send: ☐ Free 160-page Catalog describing Electrical Engineering Courses; ☐ Booklet on Careers in Radio-TV.

I am interested in.....
name of course

Name.....Age.....

Address.....

City.....Zone.....State.....

If veteran, indicate date of discharge.....

SERVICE HINTS ON DU MONT TV SETS

RA-103D, 104A, 106A, 108A, & 110A

Low or no high voltage.

Sometimes the corona shield stand-off insulator in these sets cracks when the screw holding it to the shield is drawn too tight. Moisture entering the crack produces high-voltage leakage which eventually carbonizes the insulator.

Check this insulator and replace it if defective.

RA-109A

Audio hum.

This may be caused by faulty lead dress.

Shorten black lead (A) connected

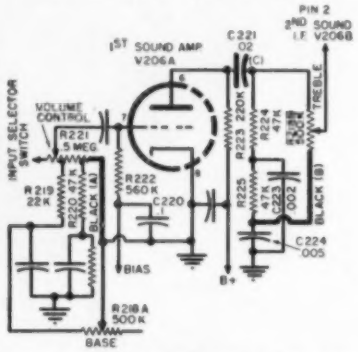

to ground side of the volume control by about 2¼ inches.

Shorten black lead (B) connecting tone control to C224 by 1 inch.

Dress C221 (C) located near tone control so that flat side is not facing chassis.

RA-109A, 112A, 113, 116A, & 117A

Repeated blowout of high-voltage fuse.

An intermittent short in the 5U4G low-voltage rectifier may be the cause, especially if a check of the high-voltage circuits indicates normal operation.

Strike the 5U4G; if it is intermittent it will usually produce a bright flash.

Replace the tube if it is defective.

RA-109, 116, 119, 130, & 133

Erratic a.g.c. action.

This may be due to intermittent opening of L216 (video peaking coil) at the grid of V216 sync amplifier.

Check the signal at the grid of V216 with an oscilloscope; if L216 is open the signal on the scope screen will reverse phase about 15 seconds after the probe is connected to the circuit. If the condition is intermittent, leave the scope in the circuit until it recurs.

If L216 is at fault, replace it with *Du Mont* part No. 21006621.

RA-109A, 116A, & 119A

Vertical shrinkage intermittently.

This may be due to intermittent open of the decoupling condensers in the plate circuit of the vertical saw-tooth generator.

Check condenser C294 and replace it with a 40 μfd., 350 v. electrolytic if it is faulty.

RA-109A, 116A, & 119A

Intermittent loss or complete loss of sync.

This may be due to an increase in the value or an open in bleeder resistor R283C. Replace this resistor with a new 1975-ohm unit if it is faulty.

RA-109A & 130A

Unstable horizontal sync.

When this condition is accompanied by a disappearance of the bias voltage at the grid of the reactance tube (V225) with the antenna disconnected, the probable fault is a shorted C265, negative voltage filter condenser.

Replace this condenser, if faulty, with a 10 μfd., 25 v. electrolytic.

RA-112A & 113

High frequency whistle.

This may be caused by loose terminal board on the flyback transformer.

Tighten the screw which mounts the flyback terminal board onto the transformer.

RA-112A, 113, 117A, & 147A

No vertical or horizontal hold.

When this condition is accompanied by an overloaded picture the fault is probably an open in L214, video peaking coil at the grid of the narrow band sync amplifier V212 (6BA6).

Replace this with new part (*Du Mont* part No. 21006621).

RA-112A, 113, 117A, & 147A

Pull at top of picture.

This may be due to a faulty coupling condenser between the second sync clipper (V220A) and the horizontal a.f.c. tube (V214).

Check condenser C264 and replace it with a 180 μμfd., 500 v., 5% mica if it is faulty.

RA-119A

White and dark horizontal bars.

Alternate white and dark horizontal bars about ¼" wide may be caused by microphonic vertical deflection amplifier tube. This effect is similar to that caused by a low frequency interfering signal

MAIL YOUR ORDER TODAY—OLSON WILL RUSH IT RIGHT AWAY!

GIANT AKRAD "LOADMASTER" CONDENSER KIT

STOCK NO. AS-20

$16.95

4-DRAWER STEEL CABINET FREE!

69 PIECES List $52.00

Here's your chance to get 69 By-Pass and Electrolytic Olson Akrad "LOADMASTER" Condensers all packed in a Big 4-Drawer Chest (10" x 11½" x 10") which we give you absolutely FREE. Treat yourself to a supply of these high-quality Condensers and see for yourself why 150,000 Radio Repairmen insist upon Akrad.

42 "LOADMASTER" By-Pass Condensers

Qty.	Cap.	Volts	List. ea.	Total
2	.001	600	$ .25	$ .50
2	.002	600	.25	.50
2	.005	600	.25	.50
5	.01	600	.30	1.50
5	.02	600	.30	1.50
10	.05	600	.40	4.00
10	.1	600	.45	4.50
2	.005	1600	.60	1.20
2	.008	1600	.65	1.30
2	.01	1600	.65	1.30

27 Akrad "LOADMASTER" Electrolytic Condensers

Qty.	Cap.	Volts	List. ea.	Total
2	10	25	$1.00	$2.00
2	25	25	1.00	2.00
5	20	150	1.20	6.00
5	40	150	1.35	6.75
4	20-20	150	1.65	6.60
5	8	450	1.25	6.25
4	16	450	1.40	5.60

69 Condensers List Value $52.00

SETS A RECORD—BUT GENTLY

BRAND NEW 3-SPEED GENERAL INSTRUMENT AUTOMATIC RECORD CHANGER

Changes All Sizes—7", 10" and 12"

All Speeds—33⅓, 45 and 78 RPM

Imperial Deluxe Model

STOCK NO. RA-69

Equipped with single needle, with precious metal long-lasting tip. Plays all speed records, 33⅓, 45 and 78 RPM. Regular retail price $17.50. Shpg. wt. 15 lbs.

Single, each $19.99. In lots of 3, each, only..

$18.99

This famous model is Olson's All-Time Best Seller in Record Changers. For good reasons, too. Records slide gently down the center spindle—no chance of damaging your valuable records. Simple to operate and factory adjusted to insure years of trouble-free service. Connects to any radio, amplifier or TV. Clever "Touch-Plate" allows you to reject or skip a disc if desired. Precision-engineered by craftsmen with years of experience, these General Instrument Changers are Brand New, in Original Factory-sealed Cartons and 100% Guaranteed by the Manufacturer and Olson. Operates on 115 V. AC, 60 cycle. Base size 12" x 12½" x 5⅛" above plate and 3½" below.

BUILD YOUR OWN 3-TUBE POWER AMPLIFIER

STOCK NO. AMP-11

$7.95 LESS TUBES

Olson Super Bargain. Kit includes punched chassis, sockets, condensers, power transformer, choke, 2 controls, 2 connectors, all hardware and complete wiring diagram. 115V AC. Input for any crystal, dynamic or ribbon mike and separate input for phonos. Shpg. wt. 10 lbs.

KIT OF TUBES FOR AMP-11: 6X5, 6SL7, and 6V6GT. STOCK NO. AS-80—$2.59.

OUTPUT TRANSFORMER FOR AMP-11: Matches 6V6 to any 3.2 ohm voice coil. STOCK NO. T-57—69c.

12" Magnavox Speaker and Baffle Close-Out

Stock No. AS-66

Get both for only....

$7.95

In lots of 4 sets. One set for $8.95.

You get Magnavox's fine 12" PM speaker with Alnico 5 magnet. (Same as you'll find in those expensive Magnavox Super-Radio-Phono Combinations.) Power output 8 watts. Voice coil fully waterproofed. Impedance 6-8 ohms. In addition you get a walnut Speaker Baffle to bring out the full rich, rounded tones of the Magnavox Speaker. Baffle may be mounted on a wall or it will stand on a table. Here's the ideal combination for extension speakers for porches or other rooms. Can be connected to any radio or amplifier. Order 4 or more sets and install them in restaurants, auditoriums, halls, etc. Shpg. wt. 12 lbs.

CRYSTAL MIKES

Astatic high output crystal mike for PA systems and recorders. Equipped with handle base and 7' shielded cable. Shpg. wt. 3 lbs.

STOCK NO. M-67.

$5.95 each

STOCK NO. M-66, same but with on-off switch built into handle.....

$6.95

BIG INSULATED RESISTOR KIT

OLSON SPECIAL PRICE

Contains a carefully selected assortment of 100 insulated resistors. Standard RMA color code. Included are 70—½ watt, 20—1 watt and 10—2 watt resistors. Handsomely packed in a durable plioblin bar. Regular List Price $15.80. Shpg. wt. 2 lbs.

$2.99 Stock No. AS-32

COMPLETE TV ANTENNA

A complete stacked array. Made by a famous manufacturer whose name and brand is on every factory sealed carton. Look what you get: 2 Six-element conical bays, 1 pair "Q" bars, 2 Five-foot mast sections, 60 ft. 300 ohm twin lead, 5 Standoff insulators, 1 mounting base, 1 guy ring, 1 clamp, hardware. Elements are highest quality aluminum. Reg. list price is $31.95. Shpg. wt. 15 lbs. Express only.

Stock No. AU-24

$11.99 Complete Set

FREE! OLSON'S BIG NEW BARGAIN CATALOG

Get Olson's LOWER-than-wholesale prices from this famous book. STANDARD BRANDS—FRESH STOCK. IMMEDIATE DELIVERY. Catalog is two colors—40 full pages of unbelievable bargains. A new catalog mailed Bi-Monthly—with new low bargains each mailing. Simply note on your order or write today for your free copy from: OLSON RADIO WAREHOUSE, 275 E. MARKET ST., AKRON 8, OHIO.

OLSON STORES TO SERVE YOU IN:

CLEVELAND, OHIO
2020 Euclid Avenue

★

CHICAGO, ILLINOIS
623 W. Randolph Street

If you live in or near either of these cities visit our Bargain Stores where you'll find these and hundreds of other Olson Buys.

OLSON HAS OVER 150,000 SATISFIED CUSTOMERS

REG. LIST $95.00

NEW MASCO WIRELESSFONE 2-STATION WIRELESS INTERCOM

COMPACT • PORTABLE • VERSATILE

Stock No. AMP-14

FOR ONLY... $57.00 PR.

Extra Stations Order AMP-15 $28.50 each

No Wires or Interconnecting Cables Required. Just plug line cord into socket and Wirelessfone is ready to operate. Noise-Silencing Control, pre-set at factory, keeps system quiet until in actual use. Additional Stations may be added. Pilot Light On-Off Indicator. Ideal for Home, Farm, Commercial, Professional and Institutional Users. No interference with radio sets. May be used on AC or DC current. FEATURES: A Complete System Ready to Operate. No Installation Cost. Unbreakable Cast Aluminum Housing. Powerful sound amplification of 2½ watts. Ta'k-Listen-Dictate switch, a 3-position switch. "Dictate" position enables a secretary to take notes of a conference without actually being present and is ideal for baby-sitting. Shpg. wt. 11½ lbs.

CONVERT 6V DC to 110V AC

Now you can have all the advantages of a 110v AC power supply IN YOUR OWN CAR! Converts 6v DC to 110v AC 60 cycle with capacity to 45-50 watts. Fully filtered. Just plug in cigar lighter and operate portable phonos, radios, dictating machines, lights, electric shavers, etc. Only slightly larger than cigarette pack! Ideal for picnics, camping, summer traveling pleasure. Shpg. wt. 3 lbs.

Stock No. RA-104

$10.63

Stock No. M-80

TELEPHONE PICKUP

$4.50

Record or amplify both sides of a telephone conversation. No connection to telephone necessary. Just lay pick-up under any cradle type phone and connect lead to hi-impedance input of any disc, wire or tape recorder or any amplifier. Operates by induction. Shpg. wt. 1 lb.

CONDENSER KIT

$1.99 YOUR COST ONLY

Stock No. AS-83

50 POPULAR BY-PASS CONDENSERS

Contains values from .001 Mfd. to .05 Mfd. All brand new. Famous manufacturers' overstocks. List price $9.85. Shpg. wt. 2 lbs.

WEN Soldering Gun STOPS SOLDER-JOB HOLDUPS

Stock No. TL-22

$9.71 EACH

Pkg of 6 tips for gun. STOCK NO. TL-23 ... 89c

Fastest, most convenient way to solder. Heats almost instantly; economical trigger control saves on electric bills; built-in spot-light and "long reach" replaceable tip combine to make the tightest corner solder job easy. Sturdily constructed—heat and shock resistant, fully guaranteed. 250 Watts 120 V—AC. Shpg. wt. 6 lbs.

RELAYS

Small fast acting relays for dependable operation. Pure Silver Contacts. Choice of 2 models. About 1½" square.

STOCK NO. SW-29

6000 Ohm Coil

Operates in Plate series circuits. Pulls in at current to drawn. Double Pole—Double Throw.

CHOICE

$1.99 EACH

30 Ohm Coil

Operates on 6 Volts or less. Single Pole—Double Throw. Shpg. wts. each 4 oz.

STOCK NO. SW-30

WILCOX-GAY RECORDIO TAPE RECORDER

2 Full Hours of Recording or Play-back • Automatic-Foolproof Push-Button Controls • 2-Speeds • Records • Plays Back • Erases • Portable

BRAND NEW REG. $149.50 NOW ONLY..

$99.50 Stock No. AMP-10

Order your Wilcox-Gay Tape Recorder for less than Dealer's Cost! This is the finest Recorder Olson has ever offered—at a price that is really give-a-way. We made a real deal and you get the benefit.

Five "Preest-o-matic" Push-button Controls allow instant choice of all operating functions—fast forward and reverse, record, stop, and playback. The easiest of all recorders to operate. Handles up to 7" reels. Full range of recording times—7" reel records for a full hour at 3.75" per second, plus another hour on other half tape; and at 7.5" per second you get a full recording hour on both halves of tape. Rewinds in less than 3 minutes.

Automatic records from FM or AM radio, phonograph, TV or mike. Plays back through powerful built-in amplifier and 5" x 7" elliptical speaker. Frequency response—70-8500 cps at 7.5" per second, and 90-6000 cps at 3.75" per second. Output—2 Watts. Maximum Fidelity gained by Automatic Speed Selector.

Complete with Controlled Reluctance Mike, Record Lock Button, External Speaker Jack, Full Range Variable Tone and Volume Control's. 4 Tubes—6SJ7, 6AQ5, 12AX7, 6X4 Rectifier, 7 ft. Cord. Neon Recording Indicator. Handsome Removable Cover. Ideal for Office, School, Church, Club, Home, etc. Lightweight, only 23 lbs. complete. Portable size 12" x 14" x 9". 110-120 Volt 60 cycle AC, U.L. Approved.

PLASTIC BASE 600 FT. REEL

STOCK NO. X-275

Single, ea. $1.49

Lots of 10 $1.29 each

1200 FT. REEL

STOCK NO. X-249

Single, ea. $2.19

Lots of 10 $1.99 each

FULLY GUARANTEED BRAND NEW FIRST CLASS RECORDING TAPE NATIONALLY KNOWN NAME BRAND

Get the buy of your life. Save up to 64% on high quality RECORDING TAPE. A large manufacturer had to sell his inventory and he unloaded the whole deal. Olson now offers you this high grade recording tape at prices which defy competition. Standard ¼" wide, 600 and 1200 ft. lengths. Frequency response 50 to 8,000 cy. Plastic Reel included with each. Shpg. wt. ea. 1 lb.

6J6

Reg. List $2.50

Single, ea., 99c

Lots of 10, 69c ea.

MOST POPULAR TV TUBES—Discount Over 72%

INDIVIDUALLY BOXED • BRAND NEW

MADE BY LARGEST MFR. • 100% GUARANTEED

Here's the inside story on how Olson bought these fine brand-new tubes. America's largest tube manufacturer made them and was ready to ship to a big company when they suddenly got a cancellation. Olson stepped in and made a deal and bought a terrific quantity. Then we had our "Akrad" brand put on every tube. They're individually boxed and carry the usual 100% Olson Money-Back Guarantee. Order Plenty at This Price.

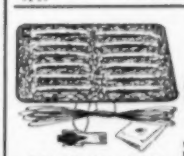

REAR DECK AUTO SPEAKER KIT FOR ALL CARS

$2.95 EACH

Install a rear seat speaker in any car, any radio. Complete Kit of parts furnished with easy instructions. Includes beautiful grille and 3-way dashboard switch for operation of front and rear speakers separately or together. Supplied less speaker. Requires popular 6" x 9" size speaker. Shpg. wt. 5 lbs.

STOCK NO. AS-81

SPEAKER FOR AS-81 KIT

Heavy duty—high volume PM 6"x9" speaker with 3.2 ohm voice coil for AS-81 installation. Shpg. wt. 6 lbs.

STOCK NO. S-114

$3.39 EACH

DON'T THROW AWAY OLD PICTURE TUBES

BOOST BRILLIANCE WITH THIS TV TUBE BOOSTER

$2.95

Completely automatic. Easy to install—no tools needed. Just plug into old picture tube that is starting to dim and watch the big change. Works on any Tube—10" to 30" in all AC parallel circuits. Adds months and months of service to those old tubes. Reg. $5.95. Shpg. wt. 1 lb.

Stock No. T-100

OLSON RADIO WAREHOUSE

275-A EAST MARKET ST., AKRON 8, OHIO

CONCORD Slashes TUBE Prices

60% OFF LIST

Most complete tube stocks in America!

ALL STANDARD BRANDS

● NEW — BOXED — GUARANTEED*

KITS

"All-American" TUBE KIT
12SA7, 12SK7, 12SQ7, 25Z5, 50L6 — $2.99

"Miniature" KIT
12AT6, 12BA6, 12BE6, 35W4, 50B5 — $3.15

"Portable" KIT
1R5, 3S4, 1T4, 1S5 — $2.95

FREE
TOOL STEEL Tube Pin Straightener
For 7-pin Miniatures, FREE with each order of 25 Tubes or more. Worth $3.95!

Tube No.	Net Each	Tube No.	Net Each	Tube No.	Net Each	Tube No.	Net Each	Tube No.	Net Each
0Z4	.66	6AL5	.72	6BQ7A	1.60	6SN7GT	.88	12SK7GT	.74
1A7GT	.88	6AL7GT	1.16	6BZ7	1.68	6SQ7	.60	12SL7GT	1.00
1B3GT	1.02	6AQ5	.80	6C4	.68	6SQ7GT	.60	12SN7GT	.92
1H5GT	.68	6AQ6	.76	6CB6	.84	6T8	1.16	12SQ7GT	.64
1L4	.84	6AQ7	1.06	6CD6	3.96	6V6GT	.80	19BG6G	2.40
1L6	1.06	6AR5	.66	6D6	.88	6W4GT	.74	19C8	1.28
1N5GT	.84	6AS5	.84	6F6	.84	6W6GT	.88	25BQ6GT	1.36
1S5	.76	6AS7G	3.95	6F6GT	.66	6X4	.62	25L6GT	.68
1T4	.84	6AT6	.62	6F8G	1.34	6X5GT	.62	25Z5	.66
1T5GT	1.04	6AU6	.72	6H6	.66	6Y6GT	1.00	25Z6G	.54
1W4	1.06	6AU7	.88	6H6GT	.74	7N7	.88	35A5	.72
1W5	.88	6AV6	.62	6J5	.60	12AT6	.62	35B5	.80
1X2A	1.06	6B4G	1.28	6J5GT	.60	12AT7	1.16	35C5	.80
3Q5GT	1.00	6BA6	.76	6J6	1.00	12AU6	.72	35L6GT	.68
3S4	.80	6BA7	1.00	6K6GT	.64	12AU7	.96	35W4	.50
3V4	.80	6BC5	.80	6K7	.74	12AV6	.62	35W5	.52
5U4G	.60	6BE6	.76	6L6G	1.25	12AV7	1.16	35Y4	.72
5V4G	.98	6BF5	.94	6L6GA	1.42	12AX7	1.00	50B5	.80
5Y3G	.54	6BQ6G	1.92	6S4	.68	12BA6	.76	50C5	.80
5Y3GT	.44	6BH6	.84	6SA7	.70	12BA7	1.00	50C6G	1.16
6AB4	.80	6BJ6	.84	6SA7GT	.74	12BE6	.76	50L6GT	.68
6AC7	1.16	6BK6	.60	6SJ7	.66	12BZ7	1.20	80	.52
6AG5	.90	6BK7	1.28	6SK7	.66	12SA7	.70	117L7	1.56
6AK5	1.66	6BL7	1.16	6SK7GT	.74	12SA7GT	.74	117Z3	.62
6AK6	.94	6BQ6GT	1.36	6SL7GT	.98	12SJ7	.70	117Z6GT	1.00

5% ADDITIONAL DISCOUNT ON LOTS OF 100 OR MORE ASSTD.

*All Tubes Guaranteed for 90 days, excepting only burnouts and breakages.

Please include 25% deposit with order, balance C.O.D. FOB NYC. Minimum order $5.

Concord Radio
55 Vesey Street, New York 7, N. Y.
Phone Digby 9-1132

CONCORD 55-Q Vesey St., N. Y. 7 Dept. 165
Please include my name on your special bargain mailing list. Free of charge.
Name .....
Address .....
City ..... State .....

TUBES
All receiving and special purpose types. Real values that will save you 10 to 70%. Call or write today for special price list. State type & quantity for additional discount.
METROPOLITAN SUPPLY CORP.
1133 Broadway, New York 10, N. Y. — CH 3-1105

COLOR AMERICA'S MOST WANTED
Tele-COLOR-Vision Screen changes ordinary television pictures into beautiful, exciting, lifelike colors. It's Spectacular!
FREE Sample and Literature.
National Telecolorvision Screen Co.
Box 708-C Brownsville, Texas

opportunities AT BELL TELEPHONE LABORATORIES

A career for you with one of the nation's leaders in research and development in communications and military electronics.

ELECTRONIC TECHNICIANS DRAFTSMEN
ELECTROMECHANICAL TECHNICIANS

Openings require previous training at high school, armed service school, or technical institute level and in general 2 or more years of applicable industrial or military experience.

Other positions generally open for experienced Wiremen and Machinists for experimental development work.

Send your name and address for application, telephone collect within 100 miles for information, or visit us Monday through Saturday. Evening interviews arranged.

BELL TELEPHONE LABORATORIES
WHIPPANY, N. J. (Near Morristown)
WHIPPANY 8-1000 EXTS. 326, 300
MURRAY HILL, N. J. (Near Summit)
SUMMIT 6-6000 EXTS. 3259, 3381

at the grid of the video amplifier. Check by replacing the 6AU5.

RA-160 & 162

Horizontal jitter at top of picture, white streaks.

This condition is especially noticeable when receiving weak signals, and is due to internal corona in C501, the anti-ringing condenser connected across part of the horizontal deflection yoke.

Replace this condenser with a 68 μμfd., 2 kv. unit.

RA-160 & 162

No high voltage, buzz in sound, no a.g.c.

This is probably due to shorted condenser C231 in the cathode circuit of the a.g.c. gate (V209B). This will cause R264 and R239 to burn out.

Replace C231 with a 120 μμfd. condenser.

RA-160 & 162

To improve horizontal sync and increase brightness.

Check R348B, the power supply voltage divider, for open or intermittent.

Replace it with a wire-wound, 2900 ohm, 10 w. unit.

RA-160 & 162

Sync buzz.

Probably due to improperly adjusted oscillator slug. If buzz persists after slug adjustment, check

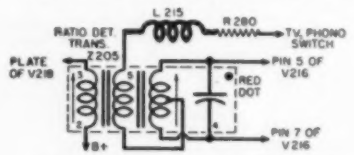

for the presence of L215, fixed inductor, connected between pin 5 of the ratio detector transformer, Z205, and one end of resistor R280 (270 ohm, ½ w. carbon). If L215 is present, remove it and connect R280 directly to pin 5 of Z205.

RA-164 & 165

To eliminate horizontal line displacement with noise.

Do the following to increase the immunity of the a.f.c. circuit to short duration noise pulses, especially when receiving weak signals:

Replace C228 with a .01 μfd., 20%, 200 v. condenser.

Replace C268 with a .05 μfd., 20%, 200 v. condenser.

Replace R241 with a 220 k, 10%, ½ w. resistor.

RA-164 & 165

To reduce picture noise and increase sync stability.

Reducing the source a.g.c. voltage, especially the a.g.c. voltage fed to the tuner, improves picture quality in weak signal areas. To effect this improvement do the following:

a. Remove the blue lead from the

ADVANCE! Raise your earning power – learn RADIO-TELEVISION-ELECTRONICS by SHOP-METHOD HOME TRAINING

GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for *you* in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!

Trained technicians are in growing demand at good pay —in manufacturing, broadcasting, television, communications, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.

EARN WHILE YOU LEARN

Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Spare-time Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.

MASTER ALL PHASES!

Get Master Shop-Method Home Training from an Established Practical Resident School with its own Training Shops, Laboratories, Studios — almost 50 Years of Successful Experience in Training Ambitious Men.

We Bring National Schools To You!

Superheterodyne Receiver

Signal Generator — Audio Oscillator — T.R.F. Receiver

LEARN BY DOING

You receive and keep all the modern equipment shown above, including tubes and valuable, professional quality Multitester. *No extra charges.*

FREE! RADIO-TV BOOK AND SAMPLE LESSON!

Send today for National Schools' new, illustrated Book of Opportunity in Radio-Television-Electronics, and an actual Sample Lesson. No cost—no obligation. Use the coupon now—we'll answer by return airmail.

National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto radios are being sold daily—more than ever before. Television is sweeping the country, too. Co-axial cables are now bringing Television to more cities, towns, and farms every day! National Schools' *complete* training program qualifies you in all fields. Read this partial list of opportunities for trained technicians:

Business of Your Own • Broadcasting
Radio Manufacturing, Sales, Service • Telecasting
Television Manufacturing, Sales, Service
Laboratories: Installation, Maintenance of Electronic Equipment
Electrolysis, Call Systems
Garages: Auto Radio Sales, Service
Sound Systems and Telephone Companies, Engineering Firms
Theatre Sound Systems, Police Radio
And scores of other good jobs in many related fields.

APPROVED FOR VETERANS AND NON-VETERANS
Check coupon below

Both Resident and Home Study Courses Offered!

TELEVISION TRAINING

You get a complete series of up-to-the-minute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our modern and complete Television broadcast studios, laboratories and classrooms!

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905
IN CANADA: 193 E. HASTINGS STREET, VANCOUVER, B.C.

FIND OUT NOW—MAIL COUPON TODAY!

NATIONAL SCHOOLS, Dept. RH-53
4000 South Figueroa Street
Los Angeles 37, California

Mail in envelope or paste on postal card.

Send FREE Radio-TV Electronics book and FREE sample lesson. I understand no salesman will call on me.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

☐ Check here if released from service less than 4 years ago.
☐ Check here if interested in Resident School Training.

HARVEY
The House of Audio

25th ANNIVERSARY YEAR

THE ORIGINAL WILLIAMSON HR-15 AMPLIFIER KIT

The famous, original Williamson HR-15 . . . still acclaimed the leader . . . in kit form, with the original Partridge output Transformer. Assemble this kit, and in 3 hours or less, enjoy the finest sound you ever heard. Operates from a tuner, phono-preamp, crystal pick-up, or other signal source. Absolute gain is 70.8 db with 20 db of feedback. Frequency response: ± .5 db, from 10 to 100,000 cps. Output impedances to match all speakers from 1.7 to 109 ohms. Kit is complete with 5 tubes (1-5V4, 2-6SN7, and 2-5881 (or 807 if requested), 2-Punched Chassis, 2-Resistor Mounting Strips, Sockets, Partridge WWFB Output Transformer, Assembly Instructions, and All Other Necessary Parts for Amplifier and Power Supply. **$76.50**

PARTRIDGE OUTPUT TRANSFORMERS — Available Separately. WWFB..... **$26.00**

HR-15T WILLIAMSON Kit—Furnished as above, with TRIAD Transformers and Chokes **$69.50**

NOTE: HR-15 and HR-15T Kits may be had with British KT-66 Output tubes for $3.00 additional.

R-J SPEAKER ENCLOSURES

BOOKSHELF MODELS

The new famous R-J cabinet developed to new dimensions. Small enough to permit it to be inconspicuously mounted on a bookcase shelf. Reproduces amazingly clean, smooth, bass fundamentals while permitting direct radiation of high frequencies. An ideal system where space is at a premium or as an extension reproducer in an extra room. May be finished to match the decor.

Model S-8-U for 8 inch speakers (11" high x 10" deep x 23½" long)..**$24.50**

Model S-12-U for 12 inch speakers (24" high x 10" deep x 21" long)..... **29.50**

WESTERN ELECTRIC
8" PM SPEAKER 755-A

A remarkable value, ideal for use with the RJ Model S-8-U. Provides full frequency range coverage and wide angle high frequency distribution.

SPECIAL $24.60

HARVEY is the House of Audio

Whether you require equipment, instruments or components . . . for recording or playback . . . for disc or for tape . . . in fact, anything you might need in audio, you will find in HARVEY'S stocks available for immediate delivery. Write, phone or wire.

NOTE: Price Net, F.O.B., N.Y.C. and subject to change without notice.

hrc **Harvey**
RADIO COMPANY, INC.
103 W. 43rd St., N.Y. 36, N.Y. • LU 2-1500

junction of R203 (330 ohm) and R222 (82k) and connect it to the white-green lead from the tuner. Disconnect this latter lead from C201 (5000 μμfd.).

b. Connect a 27k, 10%, ½ w. resistor between the junction of R201-R203 and the junction of the blue and white-green leads.

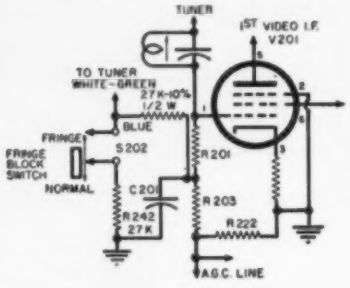

c. Replace C218 (.01 μfd.) with a .02 μfd., 20%, 600 v. condenser and C221 (.01 μfd.) with a .02 μfd., 20%, 400 v. condenser.

d. Replace R230 (1.8 meg.) with a 3.9 meg., 10%, ½ w. resistor, R226 (27k) with a 22k, 10%, ½ w. resistor, R227 (27k) with an 18k, 10%, 1 w. resistor, and R242 (39k) with a 27k, 10%, ½ w. resistor.

RA-164 & 165

Hook in picture.

This can be caused by leaky C225, coupling condenser between the 2nd sync clipper (V206A) and the horizontal phase detector (V207). Replace C225 with a new 1000 μμfd., 450 v. ceramic condenser.

RA-164 & 165

To increase picture drive and contrast range.

Remove C219 (.01 μfd.) and R214 (22 ohm) at cathode of V204 (12BY7 video amplifier).

Connect pin 1 of V204 to the junction of R218 (470 ohm) and R290B (contrast control). See (A).

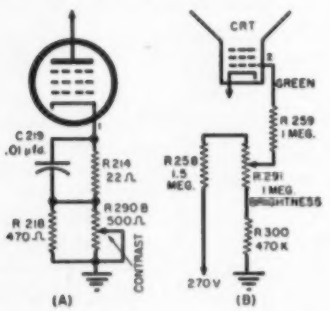

Remove R258 (1.5 meg.) and replace it with a 1.2 meg., 10%, ½ w. unit. See (B).

Remove R300 (470k) and replace it with a 390k, 10%, ½ w. resistor.

ALL SETS

Snow in picture.

Snow appears after set is in operation for some time. Grid-to-cathode leakage in one of the a.g.c. controlled video i.f. stages will

TERRIFIC "G & G" BUYS

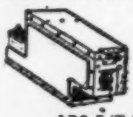

ARC-5/R-28 RECEIVER

2 Meter superhet, 100 to 156 Mc in 4 xtal channels. Louvred alum. cabinet 7⅛ x 4⅞ x 14". Complete with 10 tubes **$27.95**

ARC-5/T-23 TRANSMITTER

Companion for above. Brand New..... $59.50

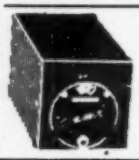

BEACON RECEIVER BC-1206-C

Receives A-N beam signals. Tunes 195 to 420 Kc. Size 4 x 4 x 6⅝". Wt. 4 lbs. Complete with 5 tubes.

BRAND NEW..... **$13.50**

Used..... $8.95

HEADSETS

	Excellent USED	BRAND NEW
HS-23 high impedance	$2.95	$4.75
HS-33 low impedance	2.45	5.75
HS-30 low imp (featherwt)	1.49	2.45
H-16/U high imp (2 units)	....	4.95
CD-307A cords, with PL55 plug and JK26 jack, 8' long	....	1.19

SCR-274N COMMAND & ARC-5 EQUIPMENT

Type		Excellent USED	BRAND NEW
BC-453	Rcvr 190-550 Kc.	$28.50	$44.50
BC-454	Rcvr 3-6 Mc.	12.50	24.95
BC-455	Rcvr 6-9 Mc.	12.95	17.95
BC-456	Modulator	2.75	5.75
BC-457	Xmtr 4-5.3 Mc.	18.50	29.50
BC-458	Xmtr 5.3-7 Mc.	9.75	37.50
BC-459	7-9.1 Mc.	19.95	24.50
BC-450	3-rcvr control box	1.49	2.45
BC-451	Xmtr control box	1.25	1.95
3-Receiver rack		1.79	2.95
2-Transmitter rack		1.59	3.25
Single Transmitter rack		....	3.25

DYNAMOTORS

TYPE	INPUT Volts	OUTPUT V	OUTPUT A	Excellent USED	BRAND NEW
PE-86	28	250 @	.06	$ 2.95	$ 5.50
DM-28	28	224 @	.07	3.50	5.95
PE-101C	12,24	400 @	.13	2.75	4.85
DM-53A	28	220 @	.08	2.75	6.50
PE-103	6,12	500 @	.16	22.50	39.50
PE-94	28	300 @	.2	4.95	7.95
DM-32	28	250 @	.06	2.50	6.50
DM-21	14	235 @	.09		16.50
BD-77	12	1000 @	.35		23.50

BC-645 TRANSMITTER-RECEIVER

15 Tubes 435 To 500 MC

Set can be modified to use for 2-way communications, voice or code, on following bands; ham band 420-450 mc, citizens radio 460-470 mc, fixed and mobile 450-460 mc, television experimental 470-500 mc. 15 tubes (tubes alone worth more than sale price!): 4—7F7, 4—7H7, 2—7E6, 2—6F6, 2—955 and 1—WE316A. Now covers 460 to 490 mc. Brand new BC-645 with tubes, less power supply in factory carton. Shipping weight 25 lbs.

BRAND NEW **$49.50** each

CONVERSION DIAGRAM INCLUDED!

PE-101C DYNAMOTOR for above BC-645..... $4.85

UHF ANTENNA ASSY, for above BC-645..... $2.45

MICROPHONES

	Excellent USED	BRAND NEW
T-45 Lip Mike, navy type	$0.49	$1.45
T-30 Throat Mike	.45	.85
T-17 Hand Mike	4.50	....
T-32 Desk Stand Mike	....	4.95

BC-221 FREQUENCY METER

Reconditioned, PERFECT! Complete with tubes and crystal **$129.50**

J-38 TELEGRAPH KEY $1.19

WILLARD 6-VOLT MIDGET STORAGE BATTERY

3-amp hr. Brand new. 3⅝" x 1-13/16" x3⅛". Uses standard electrolyte. **$2.65**

WILLARD 2-VOLT STORAGE BATTERY

30 AMP HR. BRAND NEW **$2.69**

1-QUART ELECTROLYTE FOR ABOVE... ENOUGH FOR TWO CELLS....BOTTLE **$1.45**

7-PRONG 2-VOLT VIBRATOR, FOR PORTABLE AND FARM SETS (GE LB530).... **$1.49**

Please include 25% Deposit with order—Balance C.O.D. MINIMUM ORDER $3.00. All Shipments F.O.B. Our Warehouse N.Y.C.

G&G RADIO SUPPLY COMPANY Dept. N-5

51 VESEY STREET • NEW YORK 7, N. Y.

cause the i.f. a.g.c. voltage to drop and the r.f. a.g.c. voltage to increase.

Locate the defective tube by substituting good ones for those in the i.f. stages.

ALL SETS

Microphonic sound, tubes O.K.

This may be due to loose clip on top of adjusting screw of the sound discriminator transformer. Solder clip to top of transformer can. —30—

CURING "BRAKING" IN ROTARY BEAM MOTORS

By JACK WATT, W8HYQ

THE propeller-pitch motors widely used as rotators for amateur rotary beam antenna systems are often subject to a violent "braking" action when the control switch is thrown "off" after being in the "reverse" position. The braking is very severe on the smaller-sized motors, and when they are used with anything as large as a 20-meter array, the action could eventually wreck the most ruggedly-built beam.

When the control switch is opened and the power is removed from the system, two things happen: the reversing relay returns to its "normal" position, and the field of the stepdown transformer collapses. The motor inertia tends to keep it turning in its original ("reverse") direction. Since the reversing relay has returned to the "forward" position, the collapsing field sends a surge through the motor which has a tendency to turn it in the opposite direction. The result is a terrific jerk to the beam structure.

By inserting a time-delay circuit (see diagram) the reversing relay is energized for about five seconds after the power is cut off, allowing the motor to come to a complete stop before the relay returns to its normal position. The time delay can be varied by substituting different sizes of resistors and condensers for the ones shown.

The time-delay circuit is installed at the operating position, so it is still possible to have complete reversing control with only three wires. The stepdown transformer remains right at the motor and the control wires are still fairly light, a necessity if the beam is a long way from the operating position. —30—

Wiring diagram of the time-delay circuit.

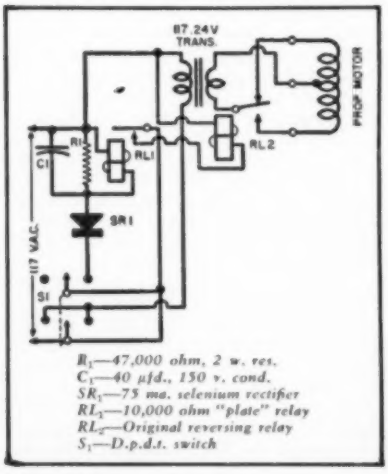

R_1—47,000 ohm, 2 w. res.
C_1—40 μfd., 150 v. cond.
SR_1—75 ma. selenium rectifier
RL_1—10,000 ohm "plate" relay
RL_2—Original reversing relay
S_1—D.p.d.t. switch

Instant HEAT

that's "QUICK ON THE TRIGGER" and "RIGHT ON THE TARGET"

USE THE

WALL TRIG-R-HEAT SOLDERING IRON

READY TO SOLDER IN SECONDS

$11.95

HEAT-CONTROL Thermostatic Action guaranteed for the life of the iron, or double your money back!

Yes—the heat is QUICK! Just touch the trigger, and in seconds TRIG-R-HEAT is ready to solder. Heat is RIGHT, too! An amazing, exclusive thermostatic action (*without the use of transformers or fragile thermostats*), quickly brings TRIG-R-HEAT to "on-the-target" soldering temperature and keeps it there. Iron is never too cool for efficient work—never too hot for the good of the tip. The result—solder doesn't fuse to iron, so tips last two to three times as long as those on irons without this exclusive feature. A built-in spotlight makes dark, hard-to-reach places easy to solder. Wattage starts at approximately 400 watts and idles at about 100 watts. Operates on 115-120 volts, AC or DC. Get Wall TRIG-R-HEAT at your dealer's *today!*

OVER 20,000,000 SOLDERING PRODUCTS SINCE 1864

WALL SOLDERING PRODUCTS Fine, Safety Irons SINCE 1864

WALL MANUFACTURING CO.

GROVE CITY • PENNSYLVANIA

OF COURSE
YOU CAN
BUY
YOUR HI-FI
at Famous
Federated
Purchaser

IF we've neglected to remind you lately, here's why:

As preeminent suppliers of electronic equipment to everyone, including huge industry, armed forces and home hobbyists, we've naturally taken it for granted that our friends *know* we sell the very best in high-fidelity equipment and give the very best high-fidelity advice.

5 convenient branches across the nation!

Visit our special Audio demonstration rooms in New York City, Newark, N. J., and Allentown, Pa.

Franchised Distributors for all major high-fidelity equipment manufacturers.

Free literature available.

Federated Purchaser
INC.

New York 7, N. Y. • 66 Dey St. • Digby 9-3050
Newark, N. J. • 114 Hudson Street • MArket 3-0035
Allentown, Pa. • 1115 Hamilton St. • Hemlock 3-7441
Easton, Pa. • 925 Northampton Street • Easton 4258
Los Angeles, Cal. • 911 S. Grand Ave. • Trinity 1781

MANUFACTURERS' LITERATURE

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO & TELEVISION NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

MINIATURE TUBE GUIDE

Hytron Radio and Electronics Co., Danvers, Massachusetts now has available copies of the Sixth Edition of its "*CBS-Hytron* Reference Guide" covering miniature tubes.

Pertinent characteristics data is given for 250 miniatures, 87 of them new since the Fifth Edition was published. The Guide also includes 111 basing diagrams and indicates similar larger prototypes.

Data is as complete as possible and includes operating conditions for individual tube types.

The material is presented in tabular form in order to provide the maximum information for the service or electronic technician in the most usable style. Copies of the Guide are available on request.

CONCORD CATALOGUE

Concord Radio, 55 Vesey Street, New York 7, New York, has recently issued a 36-page catalogue covering various types of electronic equipment.

Catalogue 153 lists tubes, audio equipment, test equipment, kits, antennas, converters, TV accessories, tools, parts, ham gear, etc. Copies are available upon request to the company direct.

SPEAKER ENCLOSURES

Bud Radio, Inc., 2118 E. 55th St., Cleveland 3, Ohio, now has available a four-page pamphlet describing a complete line of metal speaker enclosures for hospitals, auditoriums, stadiums, school rooms, restaurants, airports and railroad stations, department stores, industrial, and commercial applications.

Complete information is given on each model including mechanical specifications, finishes, and prices.

MAIL ORDER CATALOGUE

Radio Shack Corporation of 167 Washington St., Boston 8, Mass., has published an 8-page sale bulletin which lists junction-type transistors, u.h.f. television antennas and converters, a TV-FM booster, wire, tubes, blowers, transformers, condensers, resistors, and sale-priced high-fidelity tuners and amplifiers.

Copies of this bulletin are available on request.

BOGEN EQUIPMENT

David Bogen Company, 29 Ninth Ave., New York 14, N. Y., has issued a 24-page booklet covering its line of amplifiers, p.a. systems, television boosters, and allied equipment.

Entitled "Electronics for Audio-Radio-Television," the new publication gives design features, specifications, and prices on the equipment. The amplifier section includes p.a. units ranging in output from 10 to 70 watts. Three mobile amplifiers are also listed for 6 volt d.c. or 117 volt a.c. input; two broadcast quality preamps, one designed for mixing and fading up to five inputs; and 125 watt and 50 watt booster amplifiers are also covered.

Copies of this booklet are available without charge from the company.

STEEL SHELVING

Precision Equipment Co., 3712 N. Milwaukee, Chicago 41, Ill., is offering a copy of its new catalogue covering steel shelving, lockers, etc., as well as other storage and maintenance equipment for industrial use.

Various items of interest to the radio and television service shop owner are illustrated and described. A copy of this 32-page booklet is available on request.

JENSEN PUBLICATION

Jensen Manufacturing Co., 6601 Laramie, Chicago, Ill., has issued its "Technical Bulletin No. 4" which describes the company's four-channel, ultra-fidelity system as demonstrated at the two 1952 Audio Fairs and at the February 1953 Audio Fair in Los Angeles.

Included is construction information on the "Transflex" bass reflex transmission line unit and associated 45-cycle crossover network for the frequency range adjacent to the lower limits of audibility.

RECORDING EQUIPMENT

Audio & Video Products Corp., 730 Fifth Ave., New York 19, N. Y., is offering a 4-page illustrated catalogue with detailed specifications and prices on the complete line of *Ampex* recording equipment and audio accessories handled by the firm.

The publication includes details on the new *Ampex* playback which allows up to 8 hours of continuous play with automatic reversal and on pre-recorded music-on-tape for use with these machines.

CLAROSTAT MANUAL

Clarostat Mfg. Co., Inc., Dover, N. H., has announced the availability of the Second Edition of its "TV Control Replacement Manual."

This publication carries over 262 pages of factual control replacement information by set model and chassis

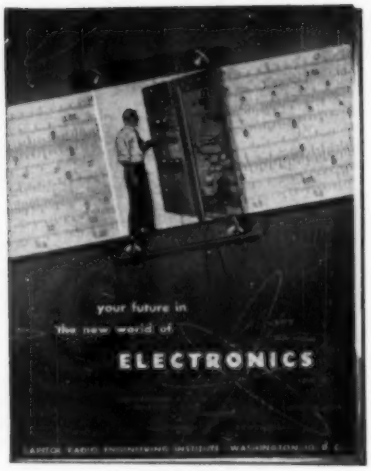

RADIO—TV—ELECTRONICS

will these fast-growing industries leave you behind . . . or skyrocket you up with them?

Send for this free CREI booklet today . . . and find out!

When you find success in your chosen field, you may look back on one small incident that changed the course of your career. It may be a conversation you had. It may be the day your father bought you a radio kit, or the day you applied for a job just when somebody was needed. It may well be (as it has for thousands) the day you took two minutes to request the free CREI booklet called "Your Future in the New World of Electronics."

When you read this fact-packed booklet, you will get a complete picture of the electronics industry: where it is going, and what you can do to rise with it. For here is a field expanding so rapidly that the most optimistic experts fall short in their predictions.

Consider the 109 TV stations now operating, and the 2,000 more made possible by the recent FCC "unfreeze." Consider the 20,000,000 TV sets and more than 100,000,000 radios now in operation. Consider the gigantic defense orders for electronic equipment and installations.

Consider the thousands of radio-equipped fire and police departments; the radio-equipped railroads; the hundreds of cities with 2-way radio service for cars and cabs; the wide-ranging field of aviation communications—radio-controlled aircraft, navigation-and-traffic control, airport stations.

Consider the maritime world with its radar and navigation aids, fathometers, ship-to-shore and ship-to-ship communications. Think of electronic heating, Fax and ultra-Fax, electronic medicine, electric computers, and all the industrial applications of electronic know-how.

Then think of the unlimited number of positions to be filled—in development, research design, production, testing and inspection, manufacture, broadcasting, telecasting, and servicing. Luck won't get you a job. Contracts won't. Knowledge *will*. You will have knowledge if you prepare now—if you are alert enough and ambitious enough to obtain that knowledge—if you take two minutes to send for "Your Future in the New World of Electronics" and then follow the plan it describes.

This helpful book shows you how CREI Home Study leads the way to greater earnings through the inviting opportunities described above. However, being an accredited technical school, CREI does not promise you a "short-cut." You must translate your willingness to learn into salable technical knowledge—via *study*. CREI knows what it means to grow along with a booming industry. This year CREI is celebrating its 25th Anniversary, having started in 1927 in the early days of radio-electronics. Since then CREI has provided thousands of professional radiomen with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms use CREI courses for group training in electronics at company expense; among them are United Air Lines, Canadian Broadcasting Corporation, Trans-Canada Airlines, Sears Roebuck & Co., Bendix Products Division All-American Cables and Radio, Inc., and RCA-Victor Division and Macklett Laboratories. CREI courses are prepared by recognized experts, in a practical, easily-understood manner. You get up-to-date study materials; your work is under the personal supervision of a CREI Staff Instructor who *knows* and *teaches you* what industry needs. You choose your own hours of study *at home*. Upon completion you join the many CREI graduates who have found their diplomas keys-to-success in Radio, TV and Electronics. CREI alumni hold many top positions in America's leading firms.

CREI resident instruction (day or night) is offered in Washington, D. C. New classes start once a month.

VETERANS: If you were discharged after June 27, 1950—let the new G.I. Bill of Rights help you obtain CREI resident instruction. Check the coupon for full information.

At your service is the CREI Placement Bureau which finds positions for students and graduates. Although CREI does not guarantee jobs, the bureau now has many more requests for personnel than can be filled. Talk to men in the field and check up on CREI's high standing in electronics instruction. Determine for yourself right now that your earnings are going to rise with your knowledge—and that you will rise *with* this booming industry. All this CREI offers you, provided you sincerely want to learn. Fill out the coupon and mail it today. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—your future—is up to you.

MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE
Dept. 115, 3224 16th St., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK FIELD OF GREATEST INTEREST
- ☐ Practical Radio Engineering
- ☐ Aeronautical Radio Engineering
- ☐ Practical Television Engineering
- ☐ Broadcast Radio Engineering (AM, FM, TV)
- ☐ TV, FM & Advanced AM Servicing

Name .....

Street .....

City ..... Zone ..... State .....

Check ☐ Residence School ☐ Veteran

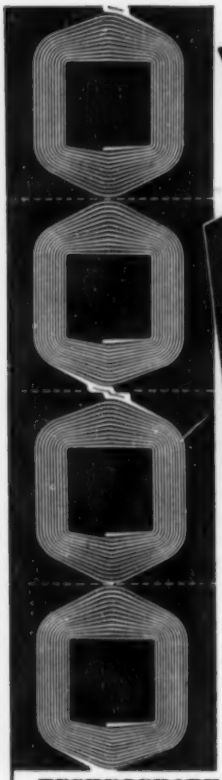

Just released... $1.00

THE TECHNOGRAPH SYSTEM OF PRINTED CIRCUITS fully explained

in 48 pages of clear text and illustrations by the originators and holders of the basic patents . . . Technograph Printed Circuits, Ltd. (Henderson & Spalding) of England.

Valuable reading for Engineers and Businessmen alike . . . The key to future development of many electronic components.

48 pages 5½" x 8½" with attractive hard cover.

MAIL COUPON TODAY

CONTENTS:
- Origin and Early Development
- The Technograph System Described
- Advantages of Printed Circuits
- Economic Aspects

TECHNOGRAPH
PRINTED ELECTRONICS, INCORPORATED
191 Main Street • Tarrytown, New York

TECHNOGRAPH PRINTED ELECTRONICS, INC.
191 Main Street, Tarrytown, New York, Dept. E5
Gentlemen:
Please send me postpaid, _____ copies of your book, The Technograph System of Printed Circuits. I enclose $1.00 for each.
Name _____
Street _____
City _____ State _____

ANOTHER OUTSTANDING JOBBER
RADIO PRODUCTS SALES CO.
1237 - 18th St
Denver 2, Colorado
HAS THE SENSATIONAL NEW EICO 470-K 7" SCOPE KIT IN STOCK!

$79.95

SCHEMATICS—CONVERSIONS
FOR SURPLUS GEAR
NEW LIST! MANY ADDITIONS!
Send stamped, self addressed envelope for List C. Add 25c for chart explaining AN nomenclature.
R. E. GOODHEART
BOX 1220 BEVERLY HILLS, CAL.

Your One Complete Speaker Source
UTAH REPLACEMENT SPEAKERS
Export Dept. Rocke International Corporation, N. Y. C.
utah
RADIO PRODUCTS CO., INC.
HUNTINGTON INDIANA
A WHOLLY OWNED SUBSIDIARY OF NEWPORT STEEL CORPORATION

UTAH WANTS TO SEE YOU
YOU WILL WANT TO SEE UTAH
at Booth 880 - Display Room 603 A
ELECTRONICS PARTS SHOW MAY 18-21

designation, the set manufacturer's part number, the *Clarostat* catalogue number, and the function of the control. Several cross indexes serve as additional checks in determining the right replacement.

The manuals are available at $1.00 each from distributors or the company direct.

FREE PUBLICATION

Allied Radio Corporation, 833 W. Jackson Boulevard, Chicago 7, Ill., has released the first issue of the *"Allied* High-Fidelity Auditioner," a four-page quarterly publication containing information about new products and developments, especially in the field of high fidelity.

An interesting feature is a column called "Hi-Fi Clinic," with questions and answers about typical problems encountered with hi-fi equipment.

This new publication will be sent without charge to audio technicians, hi-fi installers, experimenters, and hobbyists. To be placed on the mailing list send your request to "High-Fidelity Auditioner" at the company address.

"SCOTCH" TAPES

Minnesota Mining and Mfg. Co., 900 Fauquier St., St. Paul 6, Minn., has announced an 8-page booklet describing applications of seven *"Scotch"* brand paper-backed electrical tapes in electric motor, coil, and transformer construction.

The physical and electrical properties of all applicable tapes, together with the electrolytic corrosion factors of each are listed in the book, copies of which are available from the manufacturer.

CONSUMER BOOKLET

The receiver division of *Allen B. Du Mont Laboratories, Inc.,* has issued a comprehensive consumer booklet on cabinet design, construction, and styling.

This purse-sized booklet breaks TV cabinet styles into four distinct categories; traditional, contemporary, modern, and mixed and contains an exhaustive description of each of the styles.

The booklet will be distributed to consumers through the company's authorized "Teleset" dealers.

TUBING COMPONENTS

Uniform Tubes, Inc., 1220 Level Rd., Collegeville 2, Pa., is currently offering copies of a four-page booklet describing a wide variety of miniature and subminiature metal tubing for use as component parts of transistors and other advanced electronic equipment.

Manufacturers' inquiries are invited by the company.

THERMAL RELAYS

A copy of *G-V Controls Inc.'s* new catalogue covering its miniature and octal size thermal time delay relays is now available from the company at 28 Hollywood Plaza, East Orange, N. J.

Publication #30, a 4-page, 2-color

Let me show you how EASY it is to

LEARN TV

the practical way--

ASSEMBLE A **TRANSVISION**

TV KIT

Pay as You Wire

$39 Down Payment

I WILL HELP YOU to start learning TV the *practical way* — by assembling a TRANSVISION TV KIT in EASY STAGES. For only $39 you get PACKAGE #1 (standard first pkg. for all of our kits). This package gives you the BASIC CHASSIS and over 450 TV COMPONENTS with *complete Instructions.* When ready, you order the *next* stage (pkg. #2), etc. All stages (or packages) are low priced, making your complete kit a terrific buy! Your completed **chassis is a** *superb 25 tube set* (22 tubes and 3 rectifier tubes) with 6"x9" p.m. speaker — a custom-chassis worth up to 100% above your investment.

EDUCATIONAL:

No previous technical knowledge required. With PACKAGE #1, you get my handy 70-page plastic-bound *Instruction Book* which includes a *20-page Service Section.* Also *12 full size (17"x22") Drawings and Photographs,* a 64 page *Service Booklet,* and 1 year's subscription to my *"TV and Electronics Notes".*

AIDS CAREER:

Do you plan to be a *TV Technician, Service-Dealer,* or *Engineer?* You'll benefit by assembling a Transvision TV Kit.

PROFIT 3 WAYS:

You profit by *gaining valuable practical knowledge . . .* by *saving on servicing costs . . .* and by producing a *TV chassis worth up to 100% above your cost.*

FEATURES

given only in new Transvision TV Kits:

No previous technical knowledge required . . . Easiest to assemble . . . **New A4 circuit gives finest picture and sound** . . . Ideal for fringe areas . . . Has Automatic Frequency Control . . . Automatic Gain Control . . . Retrace Elimination . . . **Never obsolete** because color and other developments can be added easily . . .

Choice of **6 Kits.**

UHF and **REMOTE CONTROL** may be had at small additional cost.

EXPORTERS: Foreign system of 625 lines can be accommodated.

For complete line of TV Cabinets, ask for folder.

Used in Naval Reserve Training Program.

FAMOUS EDITOR of a national science magazine says: *. . . my own assembly (of the kit) produced top-quality results,* comparable with any set I've seen and *better than most . . .*"

FREE CATALOG describes 6 great new Transvision TV Kits.

Write to D. GNESSIN, EDUCATIONAL DIRECTOR, at:

TRANSVISION, INC., Dept. RN5K **NEW ROCHELLE, N. Y.**

MAIL THIS COUPON TODAY

Mr. D. Gnessin, Educational Director
TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RN5K

☐ I'm enclosing $_____ deposit. Send standard kit PACKAGE #1, with all Instruction Material. I'll pay the balance C.O.D.

☐ Send FREE copy of your new TV Kit Catalog, Cabinet Folder, and Price Lists.

Name_____

Address_____

City_____ State_____

brochure includes cutaway views of the stainless steel mechanism and metal shell, a complete set of curves of operating characteristics, and detailed specifications on the six time ranges now in production. Delay intervals range from 3 seconds to 5 minutes.

SERVICE MANUAL

Sylvania Electric Products Inc. has announced the publication of a new service manual, covering all of the company's TV models from 1950 to 1953.

Superseding the three former volumes issued since 1949, the new manual omits all duplicate information on each chasis as it was built. Condensed and revised schematics, waveforms, alignment procedures, and replacement parts lists for all models through the 508-510 chassis, in addition to code changes in the bridge, chassis, and model numbers, are featured.

In addition to the manual, the company is offering a one-year subscription to all of its TV technical information. The manual and subscription will sell for $2.00 each. Contact your *Sylvania* distributor for further information.

RAILROAD RADIO DATA

New heavy-duty railroad radio equipment is described in an 8-page booklet currently available from *Westinghouse Electric Corporation,* Box 2099, Pittsburgh 30, Pa.

The booklet, B-5787-A, describes features of the equipment that enable it to readily fulfill the five basic needs of railroad radio communication: end-to-end; train-to-train; wayside-to-train; dispatcher-to-any-wayside or train; and bridging wire-line breaks in an emergency.

The electrical and mechanical description of the equipment includes ratings, dimensions and weights, and power requirements.

The equipment covered is the company's Type FE. —30—

CAPSULE RADIO CONTROL

THE first master test unit of a revolutionary capsule radio control for municipal street lighting systems, invented by Broadway Maintenance Corp., has been installed in New York. The inexpensive new control is expected to save American cities millions of dollars annually in lighting and maintenance costs.

It also provides the city with instantaneous emergency control of its street lights without additional equipment of any kind, should such control become necessary.

The capsule control, approximately the size of an electric bulb, is so inexpensive that it can be replaced rather than repaired. It is a monitor-type receiver which monitors a steady radio signal and switching assembly. It can be controlled from any standard commercial radio transmitter. In this way all street lights can be operated simultaneously without the malfunctioning now encountered with the astronomical time clock or photoelectric cells currently in use. —30—

L. Veltri, busy service-dealer of Westchester, N. Y., reports:

I SAVED $940*

by making a $59 INVESTMENT in a Transvision **FIELD STRENGTH METER**

Says Mr. Veltri: ". . . The way I figure, in the last 6 months I saved that much money in installation time alone . . ."

FIELD STRENGTH METER

Saves 50% of Installation Cost

Pays for itself on 3 or 4 jobs

NO TV SET NEEDED

Works from antenna . . . Measures actual picture signal strength *directly from antenna.* Shows antenna orientation maxima. Compares gain of antenna systems. Measures *TVI* on all channels. Checks receiver radiation (local oscillator). *Permits one man antenna installation.*

Eliminate variables, insure accuracy with direct meter readings on the FSM.

PREVENT WASTE OF SERVICING TIME! By checking antenna performance with the *Field Strength Meter,* the serviceman can determine whether the *TV set* or *antenna,* or *both,* are the source of trouble. *Call backs are eliminated.*

Don't lug sets. The Transvision FSM makes installation easy.

Wide range: Measures field strength from 10-50,000 microvolts. Has *Fringe Area Switch* for weak signal areas. 13 channel selector. Individually calibrated on every channel.

ADAPTABLE for UHF

Model **FSM-2,** for *110V AC only.* Complete with tubes. Wt. 13 lbs. ..... **net $59.**

Model **FSM-3B,** for *110V AC and Battery Operation* (all batteries and cables included). Wt. 22 lbs. ..... **net $79.**

Order direct from factory:

TRANSVISION INC., NEW ROCHELLE, N. Y.

FREE: Sample copy of **"TV and Electronics Notes".** Or send 50¢ for year's subscription.

10 DAY TRIAL

Buy and try this fine instrument for 10 DAYS. Then, if you wish, you may return it. Your purchase price less 10% (our cost of handling and re-packaging) will be promptly refunded.

TRANSVISION, INC.
DEPT. RN-53F NEW ROCHELLE, N. Y.

( ) Send me_____Model FSM-2; _____FSM-3B

( ) Enclosed find $_____deposit. Balance C.O.D.

( ) Enclosed find $_____in full.

I accept your 10 Day Trial terms.

Name_____

Address_____

City_____ State_____

24 HOUR
DELIVERY
FROM STOCK!
RELAYS
Our stock of more than a million relays — in over a thousand different types — is the world's largest. Don't delay your production for want of large or small quantities of relays of any type.
Telephone, wire or write for quotations.
ALLIED CONTROL CO. INC. N.Y.C. U.S.A.
TYPE
SINGLE RELAY DIV.
NEW AND MORE COMPREHENSIVE
1953
RELAY SALES
CATALOG
NOW READY
Be sure to send for your copy
Relay Sales
1953 CATALOG
Telephone
SEeley 8-4146
Relay Sales
833 W. CHICAGO AVE.
DEPT. 8, CHICAGO 22, ILL

QRM-Cutting Selectivity

(Continued from page 62)

The front and rear panels were similarly formed from sheet aluminum, as was the wrap-around case and cover. Note that the front panel is slightly larger than the rear one, to permit the wrap-around and cover to go inside the lip of the front and outside the rear. It can thus be slid off over the rear cover by removing the sheet-metal screws holding it in place. The parts of the disassembled case are shown in the photograph Fig. 3. To save space, no socket is used for the pilot light. Its only function is to indicate whether or not heater power is on the unit, and a 12-volt bulb, operating on 6 volts and soldered in place by its base behind a small hole in the panel was found to do the job admirably, and without glare. The hole may be seen between the knobs in the photograph, Fig. 5.

External Connections

Fig. 6 shows the connections that need to be made between the converter, the i.f. strip, and the broadcast receiver. Note that a d.p.d.t. switch is installed in the receiver and is used to switch both the audio input to the receiver gain control and the heater power. In one position, all BC receiver heaters are on, the converter and i.f. heaters are off and the gain control is connected to its original BC circuit. In the other, the BC receiver r.f. and i.f. tube heaters are off, power instead being supplied to the converter and i.f. strip heaters, and the input to the gain control is switched to the i.f. strip output. By thus switching heaters, it is possible to leave plate voltage on both the i.f. strip and the entire BC receiver at all times, since turning off the BC r.f. and i.f. tubes stops them from drawing plate current, and makes it available for the i.f. strip which requires approximately 30 milliamperes. Be sure to trace out the receiver 6-volt circuits, however, so that the audio and rectifier tubes (if any), the vibrator, and the speaker field, if operated at 6 volts, run all the time.

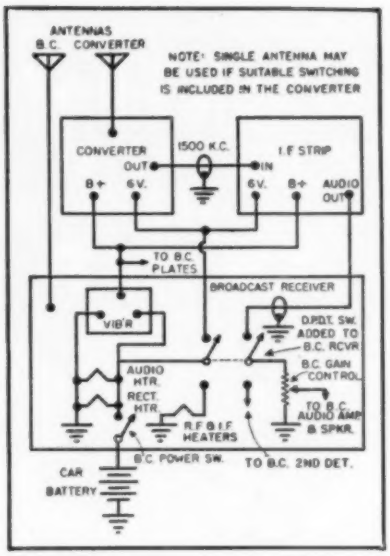

Fig. 6. External connection diagram. Most of the car receiver is disabled to save power when the attached equipment is used.

It is important to shield the audio output lead from the i.f. strip to the BC receiver, since otherwise it will be likely to pick up vibrator hash and feed it into the audio system. Other cables can also be shielded in the interest of minimizing ignition noise, although that has not always been found necessary.

No other changes need to be made in the BC receiver, and it can still be operated normally without any of the ham gear connected. This is a decided

Fig. 5. Front and rear views of i.f. strip. In the front view: clipping level adjustment knob (left) and selectivity control (right). Rear view at left: power and audio connector (bottom left), oscillator tuning slug (bottom center), S-meter jack J_2 (bottom right), input jack J_1 (above J_2), S-meter adjustment pot (center of panel).

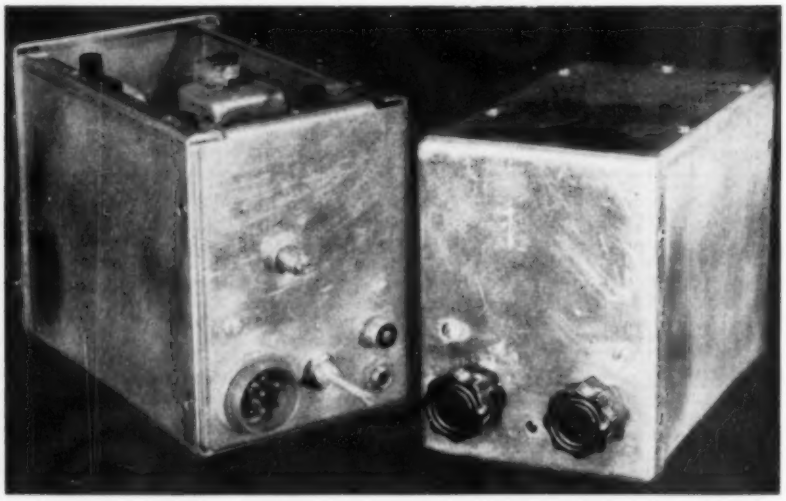

ONLY AT AIREX...THE MOST POWERFUL FRINGE AREA TV CHASSIS MADE

THE CHASSIS THAT TELEVISION ENGINEERS AND SERVICEMEN ARE BUYING FOR THEMSELVES

New 1953 630 FA-2*

This amazingly advanced 31 tube TV chassis is years ahead in engineering and gives you the ultimate in TV viewing and listening pleasure. To assure you trouble-free TV our engineering staff has incorporated into the "630 FA-2" design the experiences of hundreds of TV servicemen and engineers. Receiving range includes stations up to 200 miles away. Nothing has been spared to bring you the finest of TV chassis. Only the best and most expensive parts are used. There is no other chassis that compares with the "630 FA-2" * for fringe area reception.

TUBE MTG. BRACKETS—$6.50

3 MONTHS RMA GUAR. ON ALL PARTS

CHASSIS MFR. LIC. BY RCA

ONLY CHASSIS WITH PUSH-PULL AUDIO OUTPUT AT

$169.95 Less CR Tube

Complete with 12" ROLA Hi-Fi Speaker (Fed. tax incl.)

Detailed Service Manual & Schematic—$1

CHECK THESE EXCLUSIVE FEATURES

• 10 WATT push-pull audio output. Frequency range from 40 to 12,000 cycles • Standard Coil Cascode Tuner prevents radiation • Retrace Blanking Circuit allows you to raise the brightness without the annoying vertical retrace lines • Heavy duty front focus control • Automatic gain control potentiometer allows you to adjust the threshold sensitivity as low as 4 microvolts & still keep the full 4MC band width • Improved sync amplifier • Improved automatic brightness control • Set aligned for 21.9 MC. New Ham band will not interfere • Improved fused high voltage power supply gives full 14.5 KV under load • Will handle all picture tubes up to 24 inch with full sweep • Improved video amplifier has a gain of 40 • All moulded plastic condensers give long life & trouble-free operation • Easily adapted to new UHF stations in 2 minutes by just changing a strip in the tuner • Extra heavy duty power transformer with large safety factor • 6CB6 tubes in Video IF to give full gain • Extra filtering in power supply for hum & ripple free operation • Phono Connection & switch on chassis allows you to play your phonograph or tuner through the built-in 10 watt hi-fidelity amplifier • Extra heavy duty focus coil, which runs cool • Full focus cosine yoke.

TV PICTURE TUBE SALE

Standard Brands Factory New

Guaranteed 1 full year

- 10" Tube—**$18.95**
- 12" Tube—**$22.95**
- 16" Tube—**$25.94**
- 17" Tube—**$27.95**
- 19" Tube—**$36.95**
- 20" Tube—**$34.85**
- 21" Tube—**$39.95**
- 24" Tube—**$79.95**

Ring and Sleeve for 24"—**$7.50**

TV Gold Plastic Masks

16" and 17"—**$4.95**; 20" and 21"—**$7.95**; 24"—**$14.95**

SENSATIONAL CABINET BARGAIN FOR 630 CHASSIS

Beautiful, lustrous hand rubbed mahogany finished cabinet for 17"—20"—21" tube size. Price includes mask, glass & mtg. brackets. Reg. Mahogany Finish....$49.95 Blonde Mahogany Finish..$59.95

ALSO OVER 100 BARGAIN PRICED CABINETS FOR TV & AUDIO INSTALLATIONS

Send for free folder and price list. Full line table models, consolettes, consolettes and TV-Radio-Phono combinations. Many styles, mahogany, blonde, etc.

RECORD CHANGER SALE

Webster 3 speed 1953 Model Automatic Stop **$33.95**

GI 3 Speed....**$17.95**

Garrard RC 80..**$41.30**

HI-FIDELITY EQUIPMENT BUYS

- **ESPEY MDL 7C 12 TUBE FM-AM** with 12" Hi-Fi speaker.....**$64.95**
- **PILOTONE'S NEWEST HI-FI MODELS**
  Pilotone FM-AM Tuner Mdl AF821A with built-in preamplifier.....**$99.95**
  Pilotone FM-AM Tuner Mdl AF-723...**$79.95**
  Pilotone Amplifier Mdl AA901 with Williamson circuit **$89.95**
  Pilotone Amplifier, Mdl AA902.....**$44.95**
  Pilotone Pre-Amplifier, Mdl PA911...**$29.95**
- **RADIO-VISION FM TUNER** with power supply.....**$24.95**
- **FM-AM TUNER FOR "630"** Fits into well of chassis. Complete with instructions and escutcheon.....**$29.95**
- **ELECTRONIC AM TUNER FOR "630"** Fits into well of chassis.....**$14.95**
- **GENERAL HI-FI SPEAKER UNIT** Uses Baruch-Lang 4-speaker system. Complete in unfinished baffle.....**$24.95**
- Choice of finishes, mahogany or blonde **$29.95**
- **HALLICRAFTER ALL-WAVE RECEIVERS** Model S38C .....**$49.95** 8 Band World-Wide portable AC-DC..**$149.95**

We carry a complete line of Hallicrafters. Write for further details.

SUPER 630 DX 30 TUBE CHASSIS

Standard Coil Cascode Tuner. 12" RCA Hi-Fi Speaker. Fed. Tax Incl.....**$154.95**

Complete Service Manual for "630 FA2" or Super "630 DX".....$1

Send for free new TV parts & Hi-Fidelity Catalog.

TV BOOSTERS REDUCED PRICES

Supersonic, Mdl 107..**$12.95**
Regency, DB 520.....**$18.95**
Regency UHF converter, Covers complete UHF band **$37.50**
UHF Slug sets.....**$9.40**

LOW PRICED TV ANTENNA EQUIPMENT

10 element conical, all alum..**$3.95**
Double Vee **$3.95**
Above antennas stacked.....**$8.75**

300 OHM 14 STRAND TV WIRE

100 feet **$1.95**
1000 foot rolls.....**$14.95**

TV TELESCOPIC MASTS
Complete with Hardware

30 foot—**$14.95**; 40 foot—**$19.95**

ALLIANCE ANTENNA ROTORS

ATR—**$26.49**; DIR—**$26.29**

BARGAIN SPECIALS—BRAND NEW

- Standard Coil Cascode Tuner (Latest) .**$21.95**
- Airview Intercom, Master and 1 Slave.**$15.95**
- 2 Tube Amplifier (Less Tubes).....**$ 2.95**
  Kit of Tubes.....**$ 2.00**
- 3 Tube Amplifier (Less Tubes).....**$ 3.95**
  Kit of Tubes.....**$ 3.00**
- Picture Tube Rejuvenator.....**$ 3.95**
- TV Interference Eliminator .....**$ 2.95**
- Portable Phonograph Buys:
  3 Watt output, open top.....**$12.95**
  Same with cover.....**$14.95**
  3 Speeds, with cover.....**$18.95**
- Portable Phonocases .....**$ 2.95**

All merchandise is brand new, factory fresh & fully guaranteed. Mail & phone orders filled upon receipt of certified check or money order for $25 as deposit on TV chassis, 20% on other items. Balance C.O.D., F.O.B. N. Y. Prices & specifications subject to change without notice. No Fed. taxes to pay. Prices lower than OPS Regs.

AIREX RADIO CORP. SHOWROOM: 171 Washington St., N. Y. 7. Grammercy 7-9245 MAIL ORDER DEPT.: 400 Lafayette St., N.Y.3

SEND POSTCARD TO BE PUT ON FREE MAILING LIST

NEW
IT'S TERRIFIC!
EICO
7 MODEL 470 -INCH PUSH-PULL SCOPE

KIT $79.95
Factory Wired $129.50

- BOOSTED VERT. SENSITIVITY: 10 mv rms/in.
- EXTENDED FLAT FREQ. RESPONSE: 10 cps—1 MC (±2 db).
- 3-STEP FREQ.-COMPENSATED ATTENUATOR; cathode follower input.
- INTERNAL VOLTAGE CALIBRATOR; dir.-cal. screen.
- EXTENDED SWEEP RANGE: 15 cps—100 kc.
- INT. POS. OR NEG., EXT. & LINE SYNC.
- ON FRONT PANEL: sawtooth, 60 cps outputs; intensity mod. & ext. sync inputs.
- VAR. PHASING of int. 60 cps sweep.
- DIRECT CONNECTION TO CRT PLATES.

ORDER NOW!
For full specifications on Model 470 and the complete EICO line, write for latest catalog.

ALLIED RADIO
833 W. JACKSON BLVD., CHICAGO 7, ILL.

LEARN TELEVISION
ELECTRONICS and RADIO
Engineering Laboratory and Classroom Training. Day and Evening Classes.
Write for illustrated Catalog
ELECTRONICS INSTITUTE, Inc.
21 HENRY, DETROIT 1, MICH.

YOUR OWN ELECTRONIC MUSIC
How to build and play my latest model electronic organ without a knowledge of music.
Send stamp for details
JIM KIRK, W8DEG,
1552 Church St., San Francisco 14, Cal.

STANDARD BRANDS TUBES INDIVIDUALLY BOXED
STANDARD WARRANTY NEW LOW PRICES BRAND NEW!!

0Z4	$ .54	5Y3GT	$ .39	6BA6	$ .54	6F6GT	$ .54	6W4GT	$ .54	12SQ7GT	$ .63
1B3GT	.87	6AB4	.61	6BA7	.76	6H6	.57	6W6GT	.65	19BG6G	1.75
1L4	.65	6AC7	.98	6BC5	.65	6J5GT	.54	6X4	.49	19T8	.87
1R5	.59	6AG5	.64	6BE6	.57	6J6	.76	6X5GT	.43	25AV5GT	1.05
1S4	.76	6AG7	1.19	6BF5	.69	6K6GT	.54	12AT6	.47	25BQ6GT	1.08
1S5	.64	6AH6	1.05	6BG6G	1.69	6L6GA	1.05	12AT7	.76	25L6GT	.54
1T4	.64	6AK5	.88	6BH6	.72	6SA7GT	.61	12AU6	.54	25Z6GT	.49
1U4	.69	6AL5	.50	6BJ6	.61	6SC7	.76	12AU7	.65	35B5	.61
1U5	.61	6AQ5	.54	6BL7	.98	6SF5	.58	12AV7	.88	35C5	.61
1X2A	.75	6AQ6	.49	6BN6	.72	6SH7	.65	12BA6	.54	35L6GT	.61
3Q4	.75	6AR5	.69	6BQ6	1.08	6SJ7	.54	12BE6	.58	35W4	.41
3Q5GT	.72	6AS5	.62	6BQ7	1.08	6SL7GT	.64	12BH7	.82	35Z5GT	.39
3S4	.65	6AT6	.46	6C4	.49	6SN7GT	.69	12SA7GT	.62	50B5	.61
3V4	.65	6AU6	.54	6C5	.57	6SQ7GT	.49	12SG7	.61	50C5	.61
5T4	1.31	6AV5GT	1.05	6CB6	.65	6SR7	.49	12SH7	.49	50L6GT	.59
5U4G	.54	6AV6	.46	6CD6G	1.29	6T8	.79	12SK7GT	.63	117Z3	.54
5V4G	.98	6B4G	.98	6E5	.76	6V6GT	.57	12SN7GT	.73		

Many other types equally low priced—include all your tube needs with your order.
One of the largest stocks in the country!
Terms: 25% with order, balance C.O.D.
All prices subject to change without notice, F.O.B. New York City. Mail order division.

Television Materials Corp.
125 Cedar St., New York 6, N. Y. • COrtlandt 7-4307

advantage when the car is to be turned in, since it is bad enough to have to convert the BC receiver when the car is new, and worse to have to reconvert it when it's old and you'd much rather be cutting holes in the fenders of the new one with the three propeller spinners.

Alignment

The first step in putting the i.f. strip into operation is to set the oscillator on the correct frequency. It may be operated on either 1415 kc. or 1585, for 1500 kc. input, and either is satisfactory. If the *Millen* units are used, tune the oscillator to 1450 or 1550 kc. Its frequency can be checked quite closely by listening to it in a broadcast or communications receiver, and adjusting the slug as required. A 1500-kc. signal should now be fed to the input receptacle, either from a signal generator or, if not available, from a converter, and the i.f. transformers tuned. They should be tuned for maximum with their coupling adjustment rods pulled out as far as they will go, and the selectivity control in maximum selectivity position. The selectivity thus obtained is usually too sharp for phone work, however, and it can be broadened by increasing the coupling of T_2, T_1 or both. The control on T_3 will then provide additional control from the front of the panel. It has generally been found that the best results are obtained by coupling T_1 all, or almost all, the way in, and leaving T_2 all the way out.

If the 50-kc. *Millen* transformers are used, most of these considerations will not apply, of course. The builder may in that case decide to align the i.f. strip by the conventional method of working from the demodulator back to the mixer-oscillator stage.

The 50-kc. units are inherently sharper than the others, and since they do not have adjustable coupling, the builder may find that experiments with resistive loading and stagger tuning may be in order.

If means are available for checking the selectivity curve, either visually or point-by-point, some slight improvement in symmetry may sometimes be obtained by slight readjustments of the trimmer condensers after the coupling is adjusted, but this step is not necessary and may be omitted unless convenient, since the improvement is hardly noticeable to the ear.

The input transformer should, of course, be adjusted to 1500 kc., preferably with the converter with which the strip is to be used connected and a signal on appropriate frequency fed through it.

This unit has proved itself to be an outstanding improvement in the mobile station. It provides just about all the selectivity that can be used for phone operation, and actually outperforms a very high percentage of home station receivers. Similar units built by W2DZV, W2AIH, and others have been equally successful.

—30—

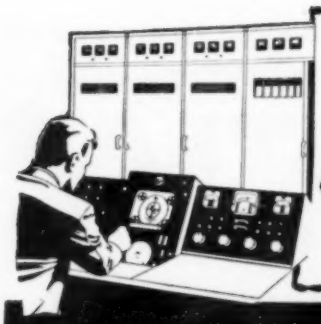

Where Will You Be in ELECTRONICS 6 Months from Today?

ADD TECHNICAL TRAINING to your practical experience

Get Your FCC License In A Hurry!

Then Use Our Amazingly Effective JOB FINDING SERVICE

Get This Valuable Booklet FREE

Money-Making FCC Commercial Radio Operator LICENSE Information

TV ENGINEERING INCLUDED IN OUR TRAINING & COACHING

TELLS HOW—

HERE IS YOUR GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing our course.

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL

YOU GET

YOUR FCC LICENSE

If you have had any practical experience —Amateur, Army, Navy, Radio repair, or experimenting.

TELLS HOW— *Employers make*

JOB OFFERS Like These to Our Graduates Every Month

Letter from nationally-known Airlines, "We would also appreciate if you would place the following additional advertisement in your bulletin—Wanted—Superintendent of Communications . . . Salary $666.66 per month."

Letter from nationally known manufacturer of high quality AM and FM transmitters, "We are very much in need at the present time of radio-electronics technicians and would appreciate any helpful suggestions that you may be able to offer. Salary up to $412 per month to start."

These are just a few examples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME in Spare Time.

Name and Address	License	Lessons
Lee Worthy 2210½ Wilshire St., Bakersfield, Calif.	2nd Phone	16
Clifford E. Vogt, Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerch, 38 Beucler Pl., Bergenfield, N. J.	1st Phone	38
S/Sgt. Ben H. Davis, 317 North Roosevelt, Lebanon, Ill.	1st Phone	28
Albert Schoell, 110 West 11th St., Escondido, Calif.	2nd Phone	23

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
CARL E. SMITH, E.E., Consulting Engineer, President
Desk RN-52, 4900 Euclid Bldg., Cleveland 3, Ohio

TELLS HOW—

Our Amazingly Effective JOB-FINDING SERVICE Helps CIRE Students Get Better Jobs

Here are a few recent examples of Job-Finding results:

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police."

Edwin P. Healy, 264 E. 3rd St., London, Ky.

GETS FIVE JOB-OFFERS FROM BROADCAST STATIONS

"Your 'Chief Engineer's Bulletin' is a grand way of obtaining employment for your graduates who have obtained their 1st class license. Since my name has been on the list I have received calls or letters from five stations in the southern states, and am now employed as Transmitter Engineer at WMMT."

Elmer Powell, Box 274, Sparta, Tenn.

OURS IS THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC-TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.

GETS CIVIL SERVICE JOB

"I have obtained a position at Wright-Patterson Air Force Base, Dayton, Ohio, as Junior Electronic Equipment Repairman. The Employment Application you prepared for me had a lot to do with me landing this desirable position."

Charles E. Loomis, 4516 Genesee Ave., Dayton, Ohio.

Your FCC Ticket is recognized in all radio fields as proof of your technical ability.

GET ALL 3 FREE! MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RN-52 4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)

B I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License Information."

Be sure to tell me about your television engineering course.

Name.....

Address.....

City.....Zone....State.....

Paste on 2-cent postcard or send air mail.

CHANGE 6 OR 12 VOLT D.C. TO 110 VOLT A.C. 60 CYCLE
Just plug into Cigar Lighter on Dash.

Trav-Electric Super
Model 6-71160
60 cycle
60-75 Watts
$37.95 LIST

Size 4"x5"x6"
Operates
- Wire Recorders
- Amplifiers
- Soldering Iron
- Dictating Machines
- Turntables
- Small Electric Drill

Trav-Electric Master
Model 6-51160
60 cycle
40-50 Watts
$24.95 LIST

Size 4"x5"x6"
Operates
- Curling Irons
- Radios
- Turntables
- Small Dictating Machines
- Test Equipment, etc.
- Portable Phonographs

Trav-Electric Senior
Model 6-1160
60 cycle
35-40 Watts
$15.95 LIST

Size 2½"x2½"x4½"
Operates
- Test Equipment
- Turntables
- Lights
- Short, Long Wave Radios
- Portable Phonographs
- Electric Shavers, etc.

Trav-Electric Midget
Model 6-11160
60 cycle
10-15 Watts
$10.95 LIST

Size 2"x2"x3½"
Operates Test Equipment, All Electric Shavers

Fully Guaranteed
See Your Jobber or Dealer

TERADO COMPANY
MFRS. OF PRECISION EQUIPMENT
1068 RAYMOND AVE. • ST. PAUL 14, MINN.
In Canada write: Atlas Radio Corp., Ltd. 560 King St. West, Toronto 28, Ont.
Export Sales Division: Scheel International, Inc., 4237 N. Lincoln Ave., Chicago 18, Ill., U. S. A.
Cable Address—*Harscheel*

Audio Equalization

(*Continued from page* 39)

recording work in a large variety of halls and rooms, each with its own set of audio characteristics, and since the monitor room at each of those recording sessions is likewise dissimilar, it is obvious that different sounding recordings will be issued by the same company!

Then what about the mastering? Isn't that where the recording equalization is inserted? Yes, that's correct. But what exactly happens? What is the procedure in the master-room where the final lacquer disc is cut for processing and pressing? Here are some of the simple facts: the master recording engineer plays the original tape *into his monitor speaker* and, using one of the various professional "program" type line equalizers, he accents or diminishes the bass and treble spectra. He equalizes for sound and, also important, for proper bass content, commensurate with the playing time of his particular selection, which determines the cutting pitch and, to an extent, the allowable cutting stylus' lateral excursions on the passages heavy with bass. Go back a few paragraphs, if you will, to our discussion of the difference in sounds in "your home and mine" and we wonder what would have been the equalization introduced, if the master recordist's monitor speaker had been located in my home, or in yours.

How, then, does the sincere recording company decide what to do for master equalization? It combines the several factors of its own discretion in hearing, conclusions as to what is good sound, experiences which have taught what its experts consider to be the "average sound," and an honest desire to manufacture a reputable product which pleases more than it displeases.

What does this leave the sincere high fidelity enthusiast? When and how does he arrive at proper playback equalization? We believe quite sincerely that he arrives at proper playback equalization when the sounds from his pickup, amplifier, and loudspeaker, combined with the audio characteristics of his home and the surrounding noise levels, give him the *maximum satisfaction*. Above all, when it pleases his own ears—*that's* when he has equalized the recording characteristic, which was never adjusted to please the "square" screen of an oscilloscope or the cold mind of a vacuum tube voltmeter, but was adjusted to meet certain physical and uncertain psychological conditions.

How does he achieve it? By availing himself of a playback equalizer with maximum flexibility in adjusting "tone balance"—the same effectual adjustments which the room, the conductor, the recording and re-recording engineers make. By using a preamplifier-equalizer with separate bass and

for dependable sound, INDUSTRY relies on ATLAS

DR Double-Reentrant Projectors

Paging & Talk-Back Speakers

ALNICO-V-PLUS Driver Units

Dual Speakers

FULL-GRIP, VELVET-ACTION Mike Stands

DEPENDABLE QUALITY: The latest electro-acoustic research and engineering—and over 20 years of manufacturing know-how—are behind every ATLAS product.

DEPENDABLE SERVICE: Coast-to-coast and around the world today—in every Industrial, Marine, Railroad, Military, Educational, Civic, U.S. and Foreign Government application—under every kind of climate and noise condition—ATLAS sound equipment is famous for highest efficiency and durability. That's the proof of ATLAS performance dependability.

DEPENDABLE DELIVERY: Yes, ATLAS gives our Government highest priority. And yes, we too feel the pinch of material shortages. But our customers will continue to get our usual dependable delivery—because we believe in equitable and dependable distribution to all ATLAS users.

DEPENDABLE PROFITS: Completeness of line, excellence of product, dependable delivery, right prices—that's the ATLAS combination that means high, steady Industrial Sound profits for You!

•

JUDGE for yourself, COMPARE ATLAS at your local Jobber today. See why ATLAS is the preferred line for utmost dependability. Write NOW for FREE latest Catalog 551

ATLAS SOUND
ATLAS SOUND CORP.
1446-39th Street, Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

BRAND NEW PE-103 DYNAMOTOR
The Answer To Your Mobile Station Power Supply

6 or 12 VDC Input and 500 VDC 160 MA Output. Ready to install. In original packing case. **$29.95** Cash With Order. Include Aprox. Postage. Excess Refunded. Calif. orders include 3½% sales tax.

L. A. HAM SHACK 1306 Bond St., at Pico Los Angeles 15, Calif.

ARKAY
world's finest radio kits
Write for free Brochure
RADIO KITS, INC., 120 Cedar St., N. Y. 6

treble spectra controls and a few selectable turnover frequencies. For maximum flexibility, the bass and treble controls should have an electrically infinite number of steps of spectra control over their usable ranges. A continuously variable control, such as the variation provided by a potentiometer, one for bass and another for treble, affords the infinite degree of desirable spectra control with the very minimum of circuitry that a switch selector cannot possibly provide. As for the turnover points, there is too little difference between a 250 and a 300 cycle, or a 400 and a 500 cycle, or a 800 and a 1000 cycle turnover, for example, to warrant the inclusion of all the 8 or 9 turnover points required to meet the needs of commercial records being manufactured today, here and abroad.

In conclusion, I would like to state that I do not believe that there is no exact science to the art of recording and equalization, nor do I infer that the same science could not be applied to the playback system. I am endeavouring to point out some of the human and physical elements which enter into the "art and science," and the human and physical elements which are the listener's lot to cope with. The ear and the mind and the aesthetic criteria of the human being are not as consistent as oscilloscopes or other measuring devices of the laboratory. Humans are measured by so called "averages." Laboratory instruments are measured according to "tolerances" and they, in turn, measure only electrical tolerances. Recordings are not made to be played for the pleasure of a laboratory's measuring devices.

—30—

WAGE-HOUR REPORT

VIOLATIONS of the overtime pay provisions of the Fair Labor Standards Act were the chief cause last year of back wage liabilities for firms in the communications industry, according to the recently-released annual report of the U. S. Labor Department.

Employers in the industry paid $149,935 in back wages to 1170 employees as a result of the division's activities.

Of the 486 establishments investigated by the division during the year 1952, 63 per-cent were found in violation of the overtime pay requirements. Twenty-nine per-cent had failed to comply with the statutory minimum wage. Violations of the Act's child-labor provisions were found in 3 per-cent of the investigated establishments.

The report emphasizes that the fact that 71 per-cent of the investigated establishments had violated one or more of these basic provisions of the Federal Wage and Hour Law should not be considered representative of compliance by the communications industry as a whole. Investigations are made on a selective basis with concentration on plants where complaints have been made.

The Act covers only those employees engaged in interstate commerce or in the production of goods for interstate commerce.

—30—

TO
ELECTRO-MECHANICAL
ENGINEERS
AND
DESIGNERS

with experience in

SMALL, PRECISION DEVICES

HUGHES RESEARCH AND DEVELOPMENT LABORATORIES, one of the nation's leading electronics organizations, is now creating a number of new openings for qualified electro-mechanical engineers and designers in important phases of its operations.

HOW TO APPLY

Write today to address below, giving details of qualifications and experience. Assurance is required that any relocation of an applicant will not cause disruption of an urgent military project.

THE COMPANY

The Hughes Laboratories, located in Southern California, are presently engaged in the development and production of advanced radar devices, electronic computers and guided missiles.

THE OPPORTUNITIES

Opportunities are offered for men who will perform interesting work on development of intricate new devices in close association with outstanding scientists. Activities will embrace a variety of challenging problems requiring originality and affording unusual possibilities of progress in learning.

FIELDS OF WORK

The work includes such fields as those involving Servo Mechanisms, Computers, Microwave Tubes, Pulse Circuitry, Solid-State Physics, Miniaturization, Antennas—Waveguides, Heat Transfer, Hydraulics—Gyros, Test Equipment, Subminiaturization, Stress Analysis, Instrumentation, Structures, and Precision Production Mechanisms.

YOUR FUTURE

Working experience in advanced techniques employing the above fields will increase your value to the Company as it further expands in development of electro-mechanical devices. Large-scale use of electronically controlled systems in business and industry is a certainty within the next few years.

HUGHES

RESEARCH AND DEVELOPMENT LABORATORIES

SCIENTIFIC AND ENGINEERING STAFF

CULVER CITY, LOS ANGELES COUNTY, CALIFORNIA

BUILD 15 RADIOS

AT HOME ONLY

With the New Improved 1953 Progressive Radio "EDU-KIT" **$19.95**

NOW INCLUDES

SIGNAL TRACER and CODE OSCILLATOR

- FREE TOOLS WITH KIT
- ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
- NO ADDITIONAL PARTS NEEDED
- EXCELLENT BACKGROUND FOR TELEVISION
- 10-DAY MONEY-BACK GUARANTEE

WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The Progressive Radio "Edu-Kit" offers you a home study course at a rock bottom price. Our Kit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction Practice expressed simply and clearly. You will gain a knowledge of basic Radio Principles involved in Radio Reception, Radio Transmission and Audio Amplification.

You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios.

You will learn code. You will receive training for F.C.C. license. In brief, you will receive a basic education in Radio exactly like the kind you would expect to receive in a Radio Course costing several hundreds of dollars.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio.

The Progressive Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used by the Veterans Administration for Vocational Guidance and Training.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. All parts are individually packed, and identified by name, photograph and diagram. Every step involved in building these sets is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" comes complete with instructions. These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Transmission, Radio Reception, Audio Amplification and servicing by Signal Tracing is clearly explained. Every part is identified by photograph and diagram. You will learn the function and theory of every part used.

The Progressive Radio "Edu-Kit" uses the principle of "Learn by Doing." Therefore you will build radios to illustrate the principles which you learn. These radios are designed in a modern manner, according to the best principles of present-day educational practice. You begin by building a simple radio. The next set that you build is slightly more advanced. Gradually, in a progressive manner, you will find yourself constructing still more advanced radio sets, and doing work like a professional Radio Technician. Altogether you will build fifteen radios, including Receivers, Transmitters, Amplifiers, Code Oscillator and Signal Tracer.

The Progressive Radio "EDU-KIT" Is Complete

You will receive every part necessary to build 15 different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, line cords, selenium rectifiers, tie strips, coils, hardware, tubing, hook-up wire, solder, etc.

Every part that you need is included. These parts are individually packaged, so that you can easily identify every item. Tools are included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided.

In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes. The "Edu-Kit" is a complete radio course, down to the smallest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the cost of the "Edu-Kit." Here is your opportunity to learn radio quickly and easily, and have others pay for it. Our Consultation Service will help you with any technical problems which you may have.

FREE EXTRAS IN 1953

• Electrical and Radio Tester • Electric Soldering Iron • Book on Television • Radio Trouble-Shooting Guide • Membership in Radio-Television Club • Consultation Service • Quizzes • Training for F.C.C. License.

The Progressive Radio "Edu-Kit" is sold with a 10-day money-back guarantee. Order your Progressive Radio "EDU-KIT" Today, or send for further information.

We pay shipping charges all over the world, if you send check or money order for $19.95 with your order. On C.O.D. orders, you pay cost of delivery.

PROGRESSIVE ELECTRONICS CO.

497 UNION AVE., RN-18, Brooklyn 11, N. Y.

NEW TV PRODUCTS on the Market

BUILT-IN ANTENNA

Arvin Industries of Columbus, Ind. has announced that all of the company's u.h.f.-equipped television sets now incorporate a built-in, all-channel antenna which accommodates both u.h.f. and v.h.f. reception.

Since approximately 80 per-cent of all of the company's TV production is now concentrated in sets equipped with the all-channel built-in tuner which was first introduced last Spring, the same percentage of *Arvin* sets is now all-channel antenna-equipped.

ALL-CHANNEL SET

Raytheon Television and Radio Corp. of Chicago is featuring one-knob, all-channel tuning in its 1953 line.

The single-knob tuning feature applies to both v.h.f. and u.h.f. bands. A single knob tunes all 70 u.h.f. channels. One of the models recently shown in the 1953 line was the Model C-2115, "Stockholm," which features

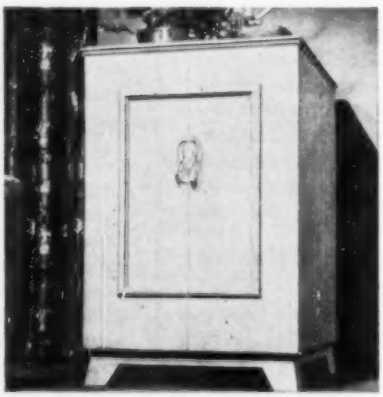

a 21-inch picture tube and is equipped with a pull-out drawer for optional phonograph equipment.

"T-V SERVISET"

Lee Electronic Labs. Inc. of Boston 19, Massachusetts has developed a compact circuit analyzer for the field or bench servicing of radio, television, radar, communication, and allied equipment.

The Model EC is completely self-contained, is simple to operate, will not load or detune the circuit under test, and does not employ tuning controls.

It may be used as an r.f. and a.f. signal tracer; r.f. and a.f. signal injector; an a.c. voltage indicator (0-60-550-20,000 volts); d.c. voltage indicator (same ranges); d.c. polarity indicator; low ohms continuity and short indicator; high ohms continuity and leakage checker; substitute and test for high capacity electrolytics and by-pass condensers; a substitution and test for high value grid, plate load,

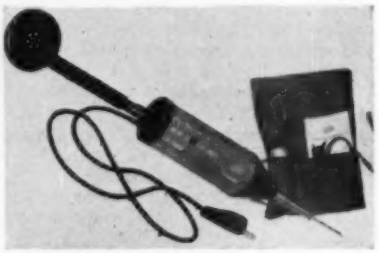

a.g.c., and a.v.c. resistors; substitution and test for medium value dropping, plate load resistors, etc.; substitution and test for low value cathode bias, current limiting resistors, filter chokes, etc.; and a dynamic checker for speakers, phones, etc.

The "T-V Serviset" comes complete with instruction manual, high-impedance, high-sensitivity *Alnico* phone, a special phone extension cord, a *"Klipzon"* type extension tip, a special high voltage adapter, kinkless test lead with built-in lamp remover, and fabric pouch which houses all accessories and the manual.

TV SERVICE SYSTEMS

Markem Service Systems, 145 Hudson St., New York, N. Y. has developed a special service systems package for television organizations.

Simple in operation and sufficiently flexible to apply to any type of service being rendered, the TV operator is afforded continuity and control in handling the service operation from the initial call to the point where the repair job has been completed and the technician returns.

The package consists of proportionate quantities of all the forms comprising the system, housed in a specially-designed desk tray. The company will provide complete details on request.

TV CONTROLS

International Resistance Co., 401 N. Broad St., Philadelphia 8, Pa., has added three new TV controls to its replacement line.

The Type 4WK is a universal 4-watt wirewound control which comes equipped with the company's "Knob Master" shaft, knurled, flattened, and grooved to fit most knob requirements without modification except for cutting to required length. Diameter is 1¾" with 11/16" depth behind the panel.

The Type 4WS is identical except for the shaft dimensions. The third

HOW LUCKY CAN WE BE?

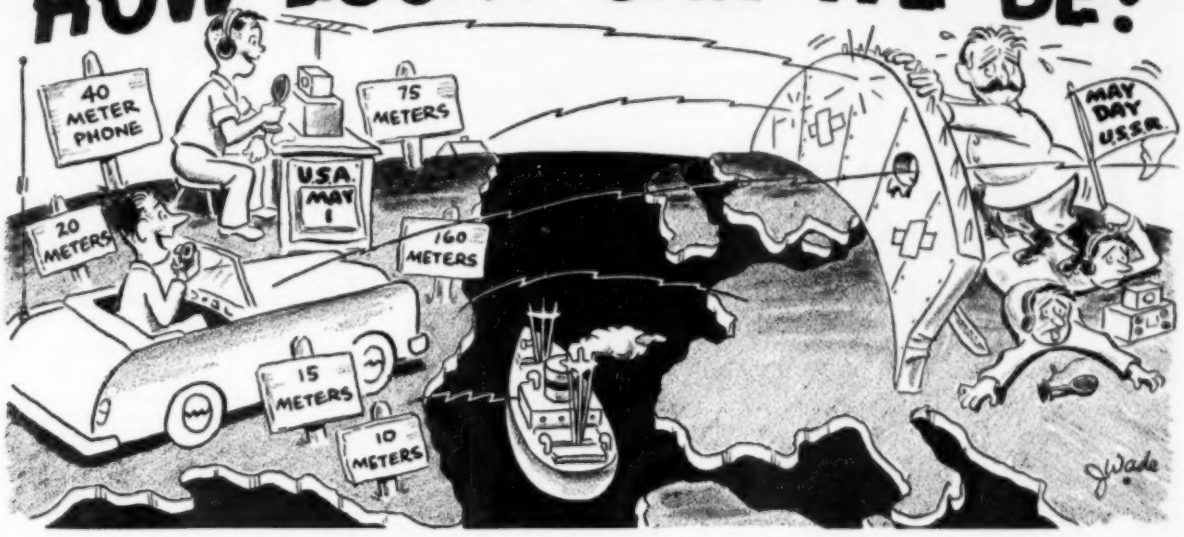

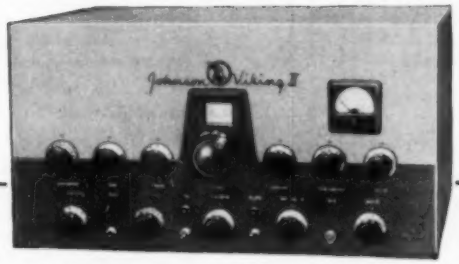

JOHNSON VIKING II TRANSMITTER KIT.
Shpg. wt. 85 lbs. Only $279.50

JOHNSON VIKING II Wired and tested.
Only $336.50

BOMBARD THE AIRWAVES...SPREAD THE WORD! IT'S EASIER THAN EVER!

There's no Iron Curtain here to put a damper on your activities. And our sensational "Surprise" trade-in allowances on used (factory-built) test and communication equipment are really something to cheer about. So go "all out" at less cost the easy Ashe way. Get your trade-in deal working today. Mail the handy coupon!

NATIONAL SW-54
Shpg. wt. 10 lbs. Only $49.95

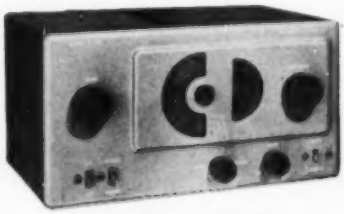

HALLICRAFTERS S-38C
Shpg. wt. 14 lbs. Only $49.50

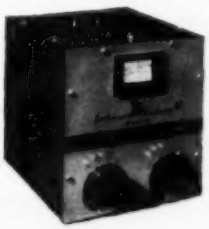

JOHNSON VIKING
VFO KIT less tubes
Shpg. wt. 6 lbs.
Only $42.75
Wired and Tested
Only $59.75

HALLICRAFTERS S-72
All-Wave Portable.
Less battery pack.
Only $109.95
Battery pack for S-72
Only $4.17

NATIONAL NC-125
with built-in
Select-O-Ject. Less
spkr. Shpg. wt. 36 lbs.
Only $149.50

All prices F. O. B. St. Louis
Phone CHestnut 1125

Walter Ashe RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

FREE CATALOG!

R-53-5

WALTER ASHE RADIO COMPANY
1125 Pine Street, St. Louis 1, Missouri

☐ Rush "Surprise" Trade-in-offer on my _____

for _____
(show make and model No. of new equipment desired)

☐ Send new 1953 Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

Send for your copy today

RIDER
TEK-FILE*
packaged tv service information—factory-authorized factory-approved for easy tv servicing... tailor-made for over 2800 receivers... only $2 per pack
(at your jobbers)
*dependable replacement parts listing beginning with Pack 57
JOHN F. RIDER
Publisher, Inc.
480 Canal Street
New York 13, N. Y.

unit is the Type VB, a two-watt carbon element high voltage control for use in television receivers employing electrostatic picture tubes.

Form S-081, available from the company, provides complete details.

CROSSOVER NETWORK

A new crossover network which combines u.h.f. and v.h.f. into a single antenna system is now available from *Eby Sales Co.*, Dept. K, 130 Lafayette St., New York 13, N. Y.

The network is an electronic filter which employs a high and low pass resonant circuit, designed to isolate the v.h.f. antenna from the u.h.f. antenna and to eliminate interference.

Housed in a weather-resisting plastic case, the crossover network can be installed on the mast or crossarm of the antenna by means of a clamp which is supplied. All elements and metal parts are of corrosion-resisting materials.

NEW U.H.F. ANTENNA

Radiart Corporation of Cleveland, Ohio, is offering a new and sturdy antenna for u.h.f. television reception.

The "U-4" is a broadband antenna of uniform gain covering the entire u.h.f. spectrum. It is completely factory pre-assembled for speedy installation and may be stacked, measuring 12" x 12" x 5".

Further information on the "U-4" is available on request.

PORTABLE VOLTMETER

A new, low cost, high voltage measuring device designed for busy TV service technicians has been announced by *American Research Corp.*

The "TV Voltprobe" enables the technician to measure the accelerating d.c. voltages on a TV tube from 4000 to 25,000 volts quickly, easily, and accurately.

The unit is 10" long, lightweight, and completely self-contained. In operation an alligator clip is connected to the chassis of the set. The probe end of the instrument is connected to the second anode by piercing the rubber protective cap.

The "TV Voltprobe" is being distributed nationally by *Clover House Products*, Dept. 61, Box 1107, Santa Monica, Cal. Write to the distributor for full details or information on dealer and distributor opportunities.

CR TUBE TESTER

Research Electronics of Roslyn, Pa., has developed a cathode-ray tube test set which will handle all television

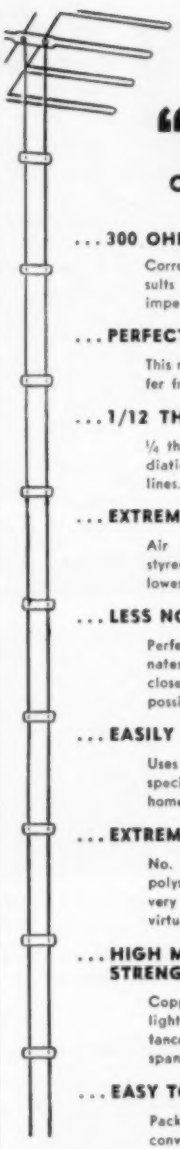

FOR VHF UHF TV INSTALLATIONS

LOW LOSS 300 OHM

"LL300"

OPEN WIRE LINE

PATENT APPLIED FOR

... 300 OHMS IMPEDANCE

Correct size wire and spacing results in 300 ohms characteristic impedance.

... PERFECT IMPEDANCE MATCH

This means maximum signal transfer from the antenna to set.

... 1/12 THE RADIATION LOSS

¼ the spacing means 1/12 the radiation loss of 450 ohm open wire lines.

... EXTREMELY LOW LOSS

Air dielectric plus clear polystyrene spacers results in the lowest possible loss of signal.

... LESS NOISE PICKUP

Perfect impedance match eliminates standing waves—this plus close spacing results in the lowest possible noise pickup.

... EASILY INSTALLED

Uses conventional stand-offs—no special hardware needed. Enters home through ½" hole.

... EXTREMELY LONG LIFE

No. 18 copperweld conductors, polystyrene spaces combined with very low wind resistance means virtually indefinite life.

... HIGH MECHANICAL STRENGTH

Copperweld construction plus light weight and low wind resistance make 200' unsupported spans possible.

... EASY TO USE SPOOLS

Packaged on 100, 150, 200, 250' convenient, easy to use spools.

All the above features mean: BETTER RECEPTION—LONG LIFE—EASE OF INSTALLATION PLUS LOW COST when you use LL-300 OPEN WIRE. Order through your Jobbers or write for free circular.

R. J. BUCHAN CO. BRICELYN 1, MINN.

RADIO ENGINEERING DEGREE IN 27 MONTHS

Radio engineering is a big field. There's room for you in it—if you're good. Get first-class training at Indiana Tech. Intensive specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, electronics. Modern laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. Government approved. Enter June, September, December, March. You can earn part of your expenses right here in Fort Wayne while you are studying.

INDIANA TECHNICAL COLLEGE
953 E. Washington Blvd., Fort Wayne 2, Indiana
Please send me free information on B.S. Engineering Degree in 27 months as checked.
☐ Radio-Television ☐ Aeronautical
☐ Civil ☐ Mechanical ☐ Electrical
Name .....
Address .....

picture tubes and magnetically deflected radar types.

This portable test instrument will measure all characteristics including emission, cut-off, gas ratio, heater-cathode leakage (positive and nega-

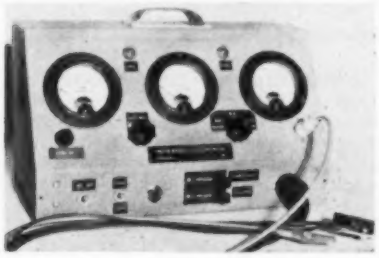

tive), grid-cathode leakage, A2 leakage, and G2 leakage. It features electronically-controlled and regulated circuits. The unit operates from 117 volt, 60 cycle a.c. lines.

OPEN LEAD-IN

Imperial Radar and Wire Corp., New York 66, N. Y., has developed a new open lead which is said to insure lower signal loss in u.h.f. and v.h.f. installations.

The new line has a nominal impedance of 250-275 ohms and can be used with 300 ohm equipment without mismatch. The narrower spacing for 250-275 ohms is said to be more desirable at u.h.f. Losses are .35 db per 100 feet dry at 500 mc.

Distributors are handling this line in spools carrying 100, 250, and 500 foot lengths.

LINE SPLICER

A new, solderless transmission line splicer designed to provide a constant

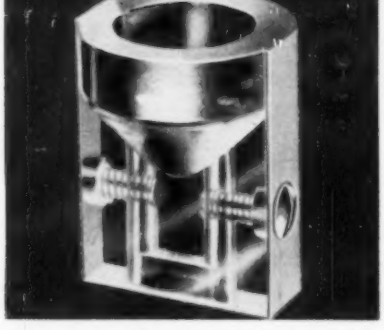

impedance splice for tubular type 300 ohm lines to flat types has been announced by *Mosley Electronics, Inc.*, 2125 Lackland Road, Overland 14, Mo.

The splicer, Catalogue No. 29-S, is intended for use with any of the currently-available tubular or oval types of line in use for u.h.f. installations.

TELESCOPING MAST

Alprodco, Inc. of Mineral Wells, Texas is offering a telescoping slip-up television mast to the trade.

Made of hot-dip galvanized heavy gauge tempered steel tubing, thumb bolts engage curved tube nuts for

SEE OUR AD IN MAY-JUNE ISSUE OF "SCIENCE & MECHANICS" FOR MORE LOW PRICE SPECIALS

RADIO STANDARD SURPLUS ELECTRONICS

RAFTS OF SURPLUS FROM STANDARD SURPLUS

MODEL GO-9 TRANSMITTER
ONLY A FEW LEFT
All brand New, 100 Watts CW, or MCW, emission. Operates from 110 V., 800 Cycle, easily converted to 60 Cycle operation. Low frequency range, 300 KC. to 600 KC. High frequency 3,000 KC. to 18,000 KC. using an E.C.O. We furnish complete conversion data with each transmitter. Complete with schematics..... $59.95

ARMY AMMUNITION CANS
Type M-3 50 Cal. Cans 12" Long x 6" Wide x 7½" Deep.
Type M-1 Cans 16½" Long x 3½" Wide x 6½" Deep.
All aluminum with Leather Handle and Hinged Top with hasp. Use for all your small parts or tools. O.D. Color, clean them and buff or paint..... Each $1.50

HI AMP. TRANSFORMER
11 Volt 65 Amp. Output—115 Volt 60 Cy. Input. Ideal for welding or Heavy Fil. Tubes or Heat. Approx. Wt. 50 Lbs..... SPECIAL at $15.95 Ea.

SCR-283 RADIO SET
Brand new—Consisting of 1—BC429 Receiver (similar to RU-16) and 1—BC430 Transmitter with Coils, and all Tubes, Intercommutator, Control Boxes, Mounting Racks, Instruction Book, Antenna, Relay, etc. Less Cables.
All New..... $39.95 set

ARC 5 EQUIPMENT:

TRANSMITTERS
4 to 5.3 MCS.. 8.95
5.3 to 7 MCS.. 7.95
All above complete with all tubes and crystal. In excellent condition.

RECEIVERS
190 to 550 KC $16.95
6 to 9 MCS. 9.95
All above Receivers complete with all tubes and dynamotor. In excellent condition.

R-4/ARR-2 RECEIVER—234-258 MCS
Complete with all tubes and dynamotor. Excellent condition..... $19.95

COMPONENTS
MOUNTING RACKS
Single Trans.... $1.00 Ea.
Double Trans.... 1.75 Ea.
Triple Rec.... 2.25 Ea.
RE-2/ARC-5 ANTENNA RELAY UNIT
Comp. with Meter and 50 MMFD vac. cond..... Ea. $4.50
MD-7 ARC-5—PUSH PULL MODULATOR UNIT
Comp. tubes and dynamotor. Exc. cond..... $11.50

DYNAMOTORS

TYPE	INPUT V.	OUTPUT V.	M.A.	PRICE
DM-19C	12	500	200	$14.95
BD-77	12	1000	350	19.95
PE-86	28	250	60	2.95
DM-16	28	220	80	4.95
DY-2	28	250	60	3.95
ARC-5	28	500	100	6.95
RU-16	28	330	135	6.95
	18	450	100	2.95

REVERSIBLE MOTOR
1/40 H.P. Ball-bearing 3450 R.P.M. in Blast-proof case. Needs only a capacitor for starting. All Brand New. 110 V., 60 Cy. Special Low Price. $4.95
Starting Capacitor..... $0.69 Ea.

ARC-4 TRANSCEIVER
140-144 MC. Ideal for 2 meters. Complete with 20 tubes and control box.
BRAND NEW..... $29.95

BC 357 MARKER BEACON
75 Mc. uses 1—12SQ7, 1—12C8 Tubes. Excellent condition. Less Tubes..... $2.95
With Tubes..... $.95

B-3A INTERVALOMETERS
This unit was used to release bomb loads at different time intervals and now can be used ideally for dark room timers, etc. Complete with two 2050 tubes; four sensitive relays and other related parts. Excellent Condition..... Each $6.95

CRYSTALS
FT-241 54th Harmonic Type. Fundamental Frequencies listed below in KC.

370	390	410	430	449	469	486	508
372	392	412	432	451	470	488	510
374	394	414	434	453	471	490	512
376	396	416	436	454	473	492	514
378	398	418	438	456	475	494	516
380	399	420	440	458	477	496	518
382	400	422	442	460	479	498	520
384	402	424	444	462	480	502	
386	404	426	445	464	482	504	
388	406	428	447	466	484	506	

Each Frequency..... 69c Ea.; 3 for $1.50
500 KC..... $1.50

12 VOLT BLOWER MOTOR
The famous Trade Winds Blower for use on Trucks, Boats, Etc. Ideal for Engine Room use as motor is completely enclosed and Sparkproof. 4" outlet.
All Brand New..... Each $9.95

SELENIUM RECTIFIER
I. T. & T. Type No. 5H2AM5. 36 Volt AC Input Max. Full Wave, 28 Volt DC Output Max. @ 8 Amps.
All Brand New..... Each $9.95

PROP PITCH MOTORS
For your Beam Antenna: 20 Volt to 32 Volt, A.C. or D.C. ¼ H.P. Motor; 114 RPM Gear Reduction, 9000 to 1.
ALL BRAND NEW. Each $16.95

MIDGET SELSYNS
AY6 type operates from 6-12 Volts 60 Cycle. Use as both transmitter and receiver. These compact little units draw almost no current and work fine for all remote position indicating applications. OD 2¼x2¼x2". Has spring return shaft. All New (Appr. wt. 1 lb.)..... Each $2.50
AY-5 Type, same as above but has a continuous rotating shaft. These compact units are all new. $4.95

SIGNALING BLINKER LIGHT
Same Light as used on U.S. Navy Ships for visual signaling between ships. 8" diameter with geared shutter. Use on 110 Volts. Complete with mounting yoke and spare bulbs and parts. All New..... Each $14.95

BRASS SELSYNS
Heavy Duty Bendix Selsyns, 110 volts 60 Cycles AC.
TYPE II—2 similar to type 6 Selsyns—New Cond. ..... Pr. $35.00

NEW 12 VOLT BATTERIES
For Mobile or light Airplanes, in original factory boxes. Weight: 37 Lbs. Size: 5½" wide x 10" long x 10" high. Signal Corps Type BB-53, 12 Volt, 34 Aft.
A real terrific surplus value while they last, all new..... Ea. $9.95

BC 375 TUNING UNITS
4500 KC-6200 KC; 6200 KC-7700 KC; 7700 KC-10000 KC; 10000 KC-12500 KC. With Vernier Dial and many parts which alone are worth 5 times our Low Price of..... $2.98 per unit
TU-5 2000 KC to 3000 KC..... $5.95

WILLARD 2 VOLT RADIO BATTERY
NEW. Uncharged (Appr. wt. 4 lbs.) TYPE 20-2..... Ea. $2.50
Complete set of three with Box and Connections to make a 6 volt, 20 Amp. Hrs. Battery Uncharged (Appr. wt. 15 lbs.)..... Set $8.95

2 VOLT VIBRATORS. VB8A Synchronous Type. Used in all portable radios having 2 volt wet cell supply. All new..... Ea. $1.00

AIRCRAFT HEATERS
Stewart-Warner Gasoline Heater with 24 Volt Blower Motor attached 8.5M B.T.U. Per Hour.
All in Excellent Condition..... Each $4.95

12 VOLT GENERATOR
Same generator as used in Trucks and Tractor Units. 12 Volt 25 Amp. with V-Pulley for connection to motor or engine. Used..... Each $12.50

SOUND POWERED HEAD AND CHEST SET
Use same way as Hand Set except you have freedom of hands. No Batteries or power source required for operation. Excellent Condition..... Per Pair $11.95

HOBBY MOTORS
Operates from 110 Volts, 60 Cy., AC. Geared Motors: 3 Speeds: 4,000 RPM., 200 RPM., 5 RPM. These motors can be used for Bar-B-Que spits, Home Work shops or any low speed application. Each speed on a separate shaft. Can be used separately or at the same time. All New. Each $12.95

CAPACITORS ● FIXED ● OIL FILLED
Solar, Pyranol, C.D., Etc.
ALL D.C. VOLTAGE RATINGS

2 MFD.	400 V..	$0.79	1 MFD.	1500 V..	$1.00
3X3 MFD.	400 V..	1.95	2 MFD.	1000 V..	1.29
10 MFD.	400 V..	2.95	8 MFD.	1000 V..	3.95
1 MFD.	600 V..	.79	10 MFD.	1000 V..	4.95
4 MFD.	600 V..	1.95	1 MFD.	1500 V..	1.50
5 MFD.	600 V..	1.98	4 MFD.	1500 V..	2.25
6 MFD.	600 V..	1.98	6 MFD.	1500 V..	2.95
7 MFD.	600 V..	1.95	1 MFD.	2000 V..	1.95
8 MFD.	600 V..	1.98	2 MFD.	2000 V..	1.95
8x8 MFD.	600 V..	2.25	3 MFD.	2000 V..	3.50
10 MFD.	600 V..	2.25	1 MFD.	3000 V..	3.95
15 MFD.	600 V..	2.95	1 MFD.	5000 V..	9.95
20 MFD.	600 V..	2.95			

CAPACITORS TRANSMITTING VARIABLE
K 1 MMFD. to 75 MMFD. ⅛" Spacing..... $1.98
*D 12 MMFD. to 125 MMFD. 3000 V. Peak..... 3.50
L 28 MMFD. to 110 MMFD. 5000 V. Peak..... 2.95
*F 12 MMFD. to 150 MMFD. 3000 V. Peak..... 1.50
A 7 MMFD. to 80 MMFD. 1500 V. Peak..... 1.00
* With National "Velvet Vernier" Dial.
All New Hammerland, Cardwell, Etc.

MICA CAPACITORS

CAP.	W. VOLTS	PRICE
.25	250	$1.95
.015	1000	.79
.002	1000	1.00
.005	1000	1.00
.07	1000	1.25
.1	1000	2.50
.035	1500	.79
.039	1500	.75
.05	1500	.75
.075	1500	.75
.093	2000	1.98
.01	2000	1.50
.02	2000	1.50
.03	2000	1.95
.000075	2500	.79
.00025	2500	.95
.0006	2500	.75
.025	2500	1.50
.0015	3000	1.00
.002	3000	1.00

CAP.	W. VOLTS	PRICE
.003	3000	$1.50
.005	3000	1.00
.015	3000	2.50
.006	3500	1.25
.0001	5000	1.50
.00015	5000	1.95
.0002	5000	1.75
.0003	5000	2.25
.00032	5000	2.25
.000375	5000	2.50
.0004	5000	2.35
.0005	5000	2.75
.0006	5000	3.25
.00072	5000	3.35
.00075	5000	2.75
.0008	5000	3.28
.001	5000	3.28
.0011	5000	2.95
.0015	5000	3.25
.002	5000	3.25
.004	5000	3.50
.005	5000	3.75
.0006	6000	3.50
.001	6000	3.50
.0001	7500	2.95
.001	7500	3.95

.00015	600	.35
.01	1000	.75
.01	1200	.75
.001	1200	.65
.005	1200	.80
.01	2500	1.50
.002	2500	1.00
.0005	2500	.65
.00025	2500	.75
.00005	2500	.75
.01	600	.65
.02	600	.75
.03	600	.85
.00005	600	.35

All Mail Orders Promptly Filled, F.O.B., San Francisco . . . All California Orders—Add 3% Sales Tax . . . Do not send postage stamps. Write for new 1953 free booklet listing our stock and prices on Radio, Electronics, Tools, Hardware, Motors, Wire, Meters, Batteries, Aluminum Sheets, etc. 20% Dep. on all C.O.D. orders. All items subject to prior sale and prices subject to change without notice. On purchases under $5.00, send full amount.

STANDARD SURPLUS 1230 Market St., San Francisco 3, Cal. Telephone HEmlock 1-3106

ERIE 413

HIGH VOLTAGE CERAMICONS®

Thousands and thousands are in use . . .

and not one has ever failed

ERIE 413 is fast becoming THE REPLACEMENT for high voltage TV filter applications

The ERIE 413 High Voltage Ceramicon is an innovation in capacitor design and has had wide acceptance by servicemen everywhere.

The Reason . . . ONE BODY, plus the correct combination of replacement terminals, permits any serviceman to carry a minimum stock, but at all times to have the correct replacement available. It's as simple as that and greatly reduces inventories. The illustrations on the left tell the story.

ERIE components are stocked by leading electronic distributors everywhere.

ERIE RESISTOR CORP.

ERIE RESISTOR CORPORATION . . . ELECTRONICS DIVISION

Main Offices: **ERIE, PA.**

Sales Offices: Cliffside, N. J. • Philadelphia, Pa. • Buffalo, N. Y. • Chicago, Ill. Detroit, Mich. • Cincinnati, Ohio • Los Angeles, Calif.

Factories: **ERIE, PA. • LONDON, ENGLAND • TORONTO, CANADA**

When answering Advertisements be sure to mention RADIO & TELEVISION NEWS

L. A. HAM SHACK SELLS FOR LESS

METERS—WESTON • SANGAMO
ALL NEW • ALL D. C. • 2" SQUARE

0–5 Ma, 0–15 Ma, 0–50 Ma, 0–100 Ma, 0–200 Ma, 0–300 Ma, 0–500 Ma — **$3.29 EACH** or **3 for $9.00**

0–2 Ma **$3.95**

Mfg'rs inquiries: lots over 100

Voltmeter. 2" sq.—0 to 20 Volts.....$3.29
DC Voltmeter. 2" sq.—0 to 300 Volts w/Ext. resistance. Complete $3.95.....3 for $9.95
RF Ammpeter. 2" sq.—0 to .5 Amp.....$3.95
Ammpeter. 2" rd.—0 to 50 Amps. $3.29
Ammpeter. 2" sq.—0 to 50 Amps. $3.29
3 for $9.00
3" Round Meters. DC. All New. 0—15, 0—30, 0—300 Mills. $4.95 Each.....3 for $11.95
Milliampmeters. 2½" rd. 0—30 Mills. Each $3.95
Milliampmeters. 2" rd. 0—50 Ma. 0 to 5 Ma. movement. Each $3.29.....3 for $9.00
Thermocouple. 2" rd. 350 Milliamp. HF. ...$3.29

"S" METER. Illuminated face. Full scale reading of 5 ma. A standard value for most "S" Meter Circuits. 2⅜". Black face. New $2.49
Amp Meter. No. 60-0-60. New $1.29

MODULATORS	Used	New
BC-456 with Tubes, less dyn. ...	2.95	
MD-7 Modulator Dynamotor, 28V	3.95	
BC-433 Receiver—with tubes...	24.95	
MN-26C Compass Receiver.....	24.95	$39.95
MN-26Y Compass Receiver.....	24.95	39.50
BC-357 Marker Beacon Rec. W.O. Tube		5.95

COMMAND AND/OR ARCS TRANSMITTERS and RECEIVERS

3-6 MC Receiver.....	Used $8.95—	New $17.95
6-9.1 Receiver	Used 7.95—	New 12.95
Triple Receiver Rack.....		1.95
V.H.F. ARC5 Transmitter or Receiver, Complete w/tubes	Used	24.95
	Used	New
4-5.3 MC Transmitter with tubes	$ 8.95	
5.3-7 MC Transmitter with tubes	8.95	
7-9.1 MC Transmitter with tubes	10.95	$19.95
3-4 MC Transmitter with tubes	18.95	
28V Receiver Command Dynamotors	1.95	

CIVIL AIR DEFENSE or 2 METERS

Modulation Transformer. BC-375.	New	$3.95
BC 306 Antenna Loading.....	New	3.95
FLB Filters—A's, B's, C's	New	1.95
FL5 Filters	New	.95
Hand Keys—J-38	New	1.95
Heineman Circuit Breakers	115 V., 20 amp. 115 V., 5 amp.	1.39 .97

TRANSFORMERS

12V 24V 2 am 110V primary.....$2.95
Code Tapes for TG-10 15 rolls. New..... 7.95

DYNAMOTORS

PE-103 **New Case** $29.95
PE-73 29V @ 20 amps. output 1000V @ .350 amps. .....New 9.95
PE-77 14V @ 40 amps. output 1000V @ .350 amps .....New 24.95

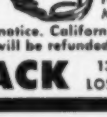

HEAD SETS HS-33.....New $4.95
HS-30 .....New $1.95
HS-23 .....Used $2.95
Matching Transformer for HS-30 .69

Cash with order. Prices subject to change without notice. California orders please include 3½% Sales Tax. Please include approximate postage—Excess will be refunded. What Have You in Surplus? Submit

L. A. HAM SHACK 1306 BOND STREET, at PICO LOS ANGELES 15, CALIFORNIA

easy finger-tip locking of joints. Notched bottom ends assure positive orientation, automatic joint locking clips, and erection safety. The unit features automatically- aligning mast sections with rotating guy rings and optional bases.

The "Custom-built" mast can be installed by one man.

AUTOMATIC IMPEDANCE MATCH

Rytel Electronics Mfg. Co., 9820 Irwin Ave., Inglewood, Calif., is marketing a new patented device which matches impedance automatically and exactly between antenna, lead-in, and receiver.

The "AIM" unit corrects impedance mismatch of greater than 10 to 1 ohmic ratios by means of a relatively simple-appearing, conductance-inductance coupling circuit. Use of special lead-ins to avoid mismatch is, therefore, eliminated.

The unit is attached to the receiver with which it is to be used thus making installation simple and easy.

TUBE CADDY FOR TV

Argos Products Co., 4753 N. Broadway, Chicago, 40, Ill., is on the market with a deluxe tube caddy which incorporates a convenient tool tray for television technicians.

Other features of the new model include heavier draw type clasps, a standup support for the cover, and black-and-white pebble-grain leatheroid covering. The deluxe model measures 18" x 14½" x 9¼". The company's regular and junior models are also available.

Price information and complete specifications on any or all of the units are available from the company.

HIGH-PASS FILTER

Bud Radio, Inc., 2118 E. 55th St., Cleveland 3, Ohio, is marketing a filter unit that will eliminate or greatly reduce television interference from broadcast stations, ham transmitters,

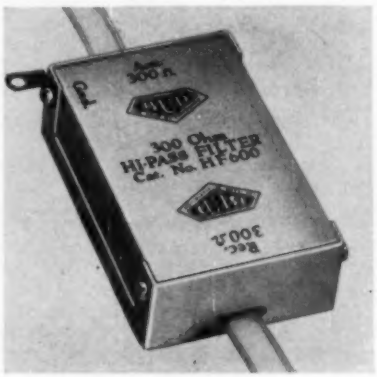

diathermy and ex-ray equipment, auto ignition systems, and many other interference-producing sources.

The high-pass filter is designed to have a cut-off frequency at 42 mc., thus rejecting signals from 0 to 42 mc. Since there is no attenuation above 42 mc. picture strength is not affected.

We have complete lines of AEROVOX capacitors, ATLAS Sound Systems, BOGEN Amplifiers, BUD Variable Capacitors, CLAROSTAT Controls, GARRARD Changers, MERIT Transformers, QUAM Speakers, RIDERS Publications, SAMS Photofacts and SIMPSON Meters which are exact replacement parts. Send us the name of set and model number and/or part number which you need. WRITE for completely illustrated CATALOG. We have complete lines of AEROVOX capacitors, ATLAS Sound Systems, BOGEN Amplifiers, BUD Variable Capacitors, CLAROSTAT Controls, GARRARD Changers, MERIT Transformers.

TUBES

ALL TUBES are guaranteed for one year . . . individually boxed. Very BEST BRANDS available for immediate delivery!

0Z4	59¢	3S4	.69	6AX5	.79	6Q6G	.95	6SN7GT	.69	7F7	.89
0Z4G		3V4	.95	6AX5	.69	6H6GT	.89	6SQ7	59¢	7F8	1.47
1A5GT	.79	5T4	1.40	6AY5GT	.89	6J5GT	.59	6SQ7GT		7G7	1.19
1A7	.69	5U4G	.59	6B4G	1.44	6J6	.79	6SR7GT	.59	7H7	1.05
1A7GT	.79	5V4G	.87	6B8GT	1.15	6J7G	.69	6SS7	.99	7J7	1.19
1B3GT	.95	5W4	59¢	6BA6	.59	6J8G	1.15	6T8	.89	7K7	
1B5	.29	5W4GT		6BA7	69¢	6K5GT	.69	6U5	.79	7L7	.79
1H5GT	.59	5Y3GT	.45	6BC5		6K6GT	.59	6U6GT	69¢	7N7	.69
1J6GT		5Y4G	.54	6BC7	1.05	6K7GT	.69	6U7G		7Q7	.79
1L4	69¢	5X4G	81¢	6BD5GT	.89	6K8GT	1.19	6U8	.89	7R7	1.19
1L6		523		6BE6	.59	6L5G	.95	6V3	1.29	7S7	1.19
1LA4	1.19	6A3	1.68	6BF5	69¢	6L6G	95¢	6V6GT	.69	7V7	.79
1LA6	1.19	6A7	1.21	6BF6		6L6GA		6W4GT	.59	7W7	1.19
1LC5	.69	6A8GT	69¢	6BG6G	1.69	6L7	1.19	6W6	.69	7X6	1.05
1LC6	1.19	6AB4		6BH6	69¢	6N6G	1.40	6X4	59¢	7X7	79¢
1LD5		6AB7	1.15	6BJ6		6N7GT	1.19	6X5GT		7Y4	
1LE3	1.19	6AC5GT	.89	6BK7	1.19	6P5GT	.69	6Y6G	.69	7Z4	.89
1LH4	1.19	6AC7	1.45	6BL7	.79	6Q7GT	.59	6Z4/84	.72	12A7	1.59
1LN5	1.19	6AG5	1.05	6BN6	1.19	6R7GT	.69	7A6	.95	12A8	.69
1N5GT		6AG7	1.49	6BQ6GT	.85	6S4	.59	7A5	1.19	12AH7	1.38
1P5GT	79¢	6AH6	1.89	6BQ7	1.29	6S7GT	1.15	7A6	.89	12AL5	.54
1Q5GT		6AK5	.89	6BZ7		6S8GT	1.25	7A7	79¢	12AT6	.59
1R5		6AK6	1.08	6C4	.59	6SA7GT	69¢	7A8		12AT7	.89
1S4	.99	6AL5	69¢	6C5GT		6SC7		7B4	.89	12AU6	.69
1S5		6AQ5		6C6	69¢	6SD7GT	.99	7B5	.89	12AU7	.79
1T4	69¢	6AQ6	.81	6CB6		6SF5	.59	7B6	.89	12AV6	.59
1U4		6AR5	.79	6CD6G	1.69	6SF5GT	.59	7B7	89¢	12AV7	.89
1U5	.59	6AT6	.59	6D6/78	1.10	6SG7	69¢	7B8		12AW6	1.19
1V	.88	6AS5	.90	6DB6	1.15	6SH7		7C5	.89	12AX4	.69
1X2A	.89	6AU5GT	1.29	6E5	.69	6SH7GT	.69	7C6	79	12AX7	.69
2A6	89¢	6AU6	.59	6F5GT	59¢	6SJ7	.79	7C7		12BA6	.59
2A7		6AV5GT	.89	6F6GT		6SJ7GT	59¢	7E5		12BA7	1.19
2X2/879	.74	6AV6	.59	6F7	1.59	6SK7GT		7E6		12BE6	59¢
3Q4	.69	6AX4	.69	6F8G	1.59	6SL7GT	.69	7E7		12BF6	

12BH7	.69	19T8	.89	38	88¢	75	.79
12BZ7	1.19	25AC5GT	1.04	38/44		77	.69
12F5GT	.65	25BQ6GT	1.15	41	.72	78/6D6	1.10
12H6	.89	25L6GT	.59	42	.68	80	.69
12J5GT	.75	25W4GT	.69	43	72¢	83	1.45
12K7GT	.69	25Z5	.69	45		84/6Z4	.72
12Q7GT	.89	25Z6GT	.69	45Z5	.69	VR90	$1.19
12SA7GT	.69	32L7GT	1.15	46	89¢	VR105	
12SC7	1.05	26	59¢	47		VR150	
12SF5	.69	27	.99	50A5	1.05	117L7	1.40
12SF5GT	.69	35A5	69¢	50B5	69¢	117N7	1.95
12SF7	.99	35B5		50C5		117P7	1.95
12SG7	.89	35C5		50C6G	1.39	117Z3	.59
12SH7GT		35L6		50L6	.69	117Z6	1.19
12SJ7GT	69¢	35W4	.59	50X6	.69	807	1.55
12SK7GT		35Y4	99¢	50Y6	.98	813	10.95
12SL7GT		35Z3		70L7		866A	1.49
12SN7GT	.99	35Z4	.75	70L7GT	89¢	2050	2.08
12SQ7	69¢	35Z5	.55	71A	.87	2051	1.15
12SQ7GT							
12SR7GT							
12Z3	.95						
14A7	1.05						
14AF7	.93						
14B6	89¢						
14B8							
14C5	1.25						
14C7	1.12						
14F7	1.05						
14F8	1.45						
14H7	1.12						
14Q7	1.05						
14W7	1.19						
14X7	1.19						
19BG6G	1.49						

FREE OFFER!

5 SMALL SCREWDRIVERS with rotating handle and handy case with purchase of $10 or more—or 5 lbs. of good usable radio service parts with order of 100 tubes or more—or a kit of assorted radio repair hardware free with purchase of 50 tubes or more.

IMPORTANT NOTICE

We at Premier have always felt that our duty to our customers extended beyond the simple job of selling parts. After all, lots of people sell and so what really sets one apart from the other is service.

As an extension of Premier service, we will publish here each month special items of interest to all servicemen. These will include service short-cuts, special speed-up methods, test equipment hints, and even offers of reprints of good service articles.

Like the reprint of the informative scope article that appeared in the January 1953 issue of RADIO NEWS. If you want a copy, drop us a line and one will be shipped to you post haste.

TELEVISION PICTURE TUBES

SEND US YOUR ORDER AND WE WILL SHIP FROM STOCK IMMEDIATELY

SIZE	PRICE	SIZE	PRICE
7 inch	$17.95	16 inch	$19.95
8 inch	31.50	17 inch	20.95
10 inch	12.95	19 inch	23.95
12 inch	16.95	20 inch	24.95
14 inch	17.95	21 inch	26.95
15 inch	19.95	24 inch	54.95

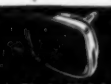

ONE FULL YEAR WARRANTY ON ALL TYPES

METAL TUBES $1.50 extra per tube
Electrostatic Tubes $1.50 extra per tube

WE PAY FOR YOUR DUD

Your worn out picture tube is worth money if it is not broken.

SIZE	WE PAY	SIZE	WE PAY	SIZE	WE PAY
7"	$1.00	14"	$3.00	19"	$4.00
8"	1.00	15"	4.00	20"	4.00
10"	2.00	16"	3.00	21"	5.00
12"	3.00	17"	3.00	24"	5.50

These allowances apply when you purchase the same size picture tube.

MODEL 300 PRECISE OSCILLOSCOPE

HERE IS THE BUY

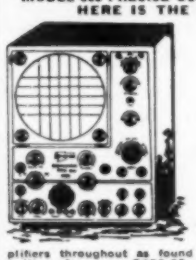

7" tube size, Sweep magnifier, complete push-pull from input through output. Vertical sensitivity 10.6 mv. R. M. S. per inch. Bandpass +0 — 3db — to FIVE mc, complete with phasing control, blanking control, intensity mod. and self-measurement peak to peak feature, with DC amplifiers throughout as found only in scopes selling for over $950.00. Exclusive easy maintenance feature: all small tubes mounted directly behind front panel. In kit form ONLY $94.95

VTVM PRECISE

Vacuum Tube Volt-Meter. 1% accuracy ceramic precision resistors; Coax DC connector; FM zero alignment scale; burn-out proof circuit. Rugged oversize 4½" meter.

Model 989, factory wired $44.98.
989K-Kit . only $25.98

MISCELLANEOUS BUYS

I. F. TRANSFORMER—456 Kc 19c
PILOT LIGHTS, Type No. 47
10 for 39c . . . . . 100 for $2.95
VOLUME CONTROLS with SWITCH, 2" shaft 1 meg, ½ meg, ¼ meg 34c
SINGLE ION TRAPS . . . . . ea. 15c
OUTPUT TRANSFORMER—for 50L6 29c
for 6V6 39c
UNIVERSAL OUTPUT TRANSFORMER, 12 watt 99c
CHIMNEY MOUNT for TV ant. 98c
6 foot LINE CORD UL . . . . . 10 for $1.95
TV INTERLOCK CORDS . . . . . ea. 49c

REGENCY UHF Converter

UNIVERSAL-CONVERTERS ALL SETS—the only converter recommended for the 5,000,000 split sound and video TV sets now in use as well as all intercarrier TV sets. NET $37.46

TV SET SPECIALS!

"FAMOUS NAME TELEVISION SETS"!

- Automatic Gain Control
- Standard Coil CASCODE TUNER—adaptable to UHF
- Best reception even in fringe areas

- Meet all Standard RTMA requirements
- Finished in luxurious mahogany
- Manufacturer Licensed under RCA Patents:

17" Table model, now only	$159.95
20" Table model, now only	$172.03
17" Console, mahogany	$172.03
21" Console, mahogany	$204.21
21" Console, blonde wood	$217.21

P. M. SPEAKERS

12" COAXIAL PM SPEAKERS $12.95 ea.
High Fidelity with high pass filter attached. 20 watt; 40-17500 cps. response; 8 ohm Voice-Coil.
8" COAXIAL PM SPEAKERS $9.95 ea.
Very best quality—NATIONAL BRANDS. Individually Packed.

3" ea.	$1.39	8" ea.	$3.23
4" ea.	1.59	10" ea.	5.10
5" ea.	1.59	12" ea.	5.95
6" SPECIAL PRICE	ea.		$1.79

RESISTOR KITS

Insulated ½w, 1 and 2 watt assortment of most used values, I.R.C. Ohmite, Stackpole, Speer, etc., 100 for $2.95

TUBE KITS

BEST BRANDS AT BEST PRICES

1V4, 1T4, 1R5, 1S5	$2.19
3Q4, 1T4, 1R5, 1S5. List Value $8.80. Tube Kit only.	$1.98
3S4, 1T4, 1S5, 1R5. List Value $7.80. 4 Tube Kit.	$1.98
1U4, 3S4, 1S5, 1R5. List Value $7.80. All Four Tubes for	$1.98
117Z3, 1U5, 3S4, 1R5, 1T4. AC-DC Portable Kit. All for	$2.49
12AT6, 12BA6, 12BE6, 35W4, 50B5. 5 Tubes for	$2.59
50L6GT, 35Z5GT, 12SQ7GT, 12SK7G, 12SA7G. 5 Tubes for	$3.22

NEW DAVIS SUPER-VISION TV ANTENNA

Unbeatable for fringe area and DX—The only television antenna with a money-back guarantee. With the new Electronic Dipole Separators, $20.55 less mast

5' aluminum mast heavy gauge 1¼" diam. with interlocking end. Slip two sections together for a ten footer . . . . . each $1.00

TV ANTENNAS

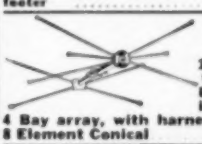

10 Element conical . . . rugged throughout . . . only $3.95
Double bay array, with stacking bars $7.75
4 Bay array, with harness and stacking bars . . . $14.95
8 Element Conical . . . only . . $2.95

TV ANTENNA KIT

Fringe Area DOUBLE "V"

High Gain, Best Pictures Possible . . . complete with 300 ohm line. Insulators, guy wire, hardware, full size antenna with double length 9 ft. mast . . . $6.95 Complete

300 OHM TWIN LEAD

55 MIL. 100 ft. . . $1.49 1,000 ft. . . $10.95
20 GAUGE 80 MIL 100 ft. $1.89, 1000 ft. $16.95
TUBULAR 300 OHM LINE 1,000 ft. $34.50
100 ft. $4.95

PREMIER T.V. RADIO SUPPLY

Division of Continental Corp.
3237 W. North Ave. • Chicago 47, Ill.
ARmitage 6-5550

TV PICTURE BRITENER

For correcting soft, dark or weak picture tubes. ONLY . . . . . $1.65 ea.

21" TV CONVERSION KIT

Consisting of rectangular tube, 70 DEGREE YOKE, Beautiful Mask and FLYBACK TRANSFORMER complete $31.95
20" TV CONVERSION KIT, as above, complete $28.95
17" TV Conversion Kit, as above, complete $23.95
24" Conversion Kit $59.95

TERMS 20% DEPOSIT with order, balance C.O.D. All shipments F.O.B. Chicago. ORDERS LESS THAN $5.00—$1.00 SERVICE CHARGE. CABLE ADDRESS: CONTULAB.

These prices supersede all previous advertised prices, subject to change without notice.

Special Offer On This Complete RADIO ENGINEERING LIBRARY

New, Up-To-Date Edition of Famous Library Covers Whole Field of Radio Engineering. Places Latest Facts, Standards, Data, Practice, and Theory At Your Fingertips.

The five big volumes of the new edition of the Radio Engineering Library now include the very latest facts, standards, data, and practice. This Library will help solve hundreds of problems for designers, researchers, engineers, and students in any field based on radio.

Written by leading radio engineers, these books cover circuit phenomena, networks, tube theory, vacuum tubes, amplification, measurements, etc.—give specialized treatment of all fields of practical design and application. They provide you with a complete and dependable encyclopedia of facts.

- *5 Volumes, 3872 Pages, 2770 Illustrations.*
- **Eastman's FUNDAMENTALS OF VACUUM TUBES, 3rd Edition.**
- **Terman's RADIO ENGINEERING, 3rd Edition.**
- **Everitt's COMMUNICATION ENGINEERING, 2nd Edition.**
- **Hund's HIGH FREQUENCY MEASUREMENTS, 2nd Edition.**
- **Henney's RADIO ENGINEERING HANDBOOK, 4th Edition.**

SEND NO MONEY

Special Low Price—Easy Terms

On this special offer you get this Library for $17.50, instead of $43.50 You save $6.00 and may pay on easy terms. Mail coupon below to examine the Library FREE for 10 days. No obligation. These books are recognized as standard works; you are bound to need them. So take advantage of this special money-saving offer. *Mail coupon at once!*

McGraw-Hill Book Co., Dept. RTN-5,
327 West 41st St., New York 36, N. Y.

Send for 10 days' FREE trial, the RADIO ENGINEERING LIBRARY. If not satisfied I will return books. Otherwise I will send $7.50, plus delivery charges, then; and $6 a month for 5 months. (Reg. price $43.50; you save $6).

Name.....

Home Address..... RTN-5

City & State.....

Employed by.....

☐ **We'll Pay Delivery Charges** if you enclose $7.50 first payment WITH coupon. Same return privilege for full refund. *(Offer applies to U. S. Only.)*

The unit measures 3¼" x 2⅛" x 1⅛" and is housed in an aluminum case which may be mounted at the rear of the TV cabinet.

U.H.F. CONVERTER

Granco Products, Inc., 36-17 20th Ave., Long Island City, N.Y., has developed a u.h.f. converter which features coaxial cavity tuning.

The Model CTU incorporates three coaxial cavities, two functioning as a bandpass preselector with the third controlling the local oscillator frequency. A cascode amplifier and a power supply complete the unit. The preselector is essentially an overcoupled, double-tuned transformer with a balanced 300 ohm antenna input and unbalanced output to the mixer. The local oscillator tunes below the signal frequency for double

superheterodyne or converter applications.

The unit is controlled by a single knob with the complete u.h.f. television band being covered by five turns of the tuning knob. The circular dial is calibrated directly in channel numbers. —30—

Noise Immunity Circuits

(*Continued from page 56*)

the video detector it would be susceptible to noise interference. On the other hand, if it were to receive the signal only from the output of the final video amplifier, synchronization would be hard to maintain on strong signals due to sync compression. By combining the signals from both points, good synchronization can be maintained over a wide range of input signals.

Next month's (concluding) article will describe the operation of several other noise immunity circuits.

(To be continued)

Fig. 10. (A) Schematic diagram of the G-E noise canceller circuit. (B) and (C) show the strength of the signals reaching V_{11A} over paths 1 and 2. See text for details.

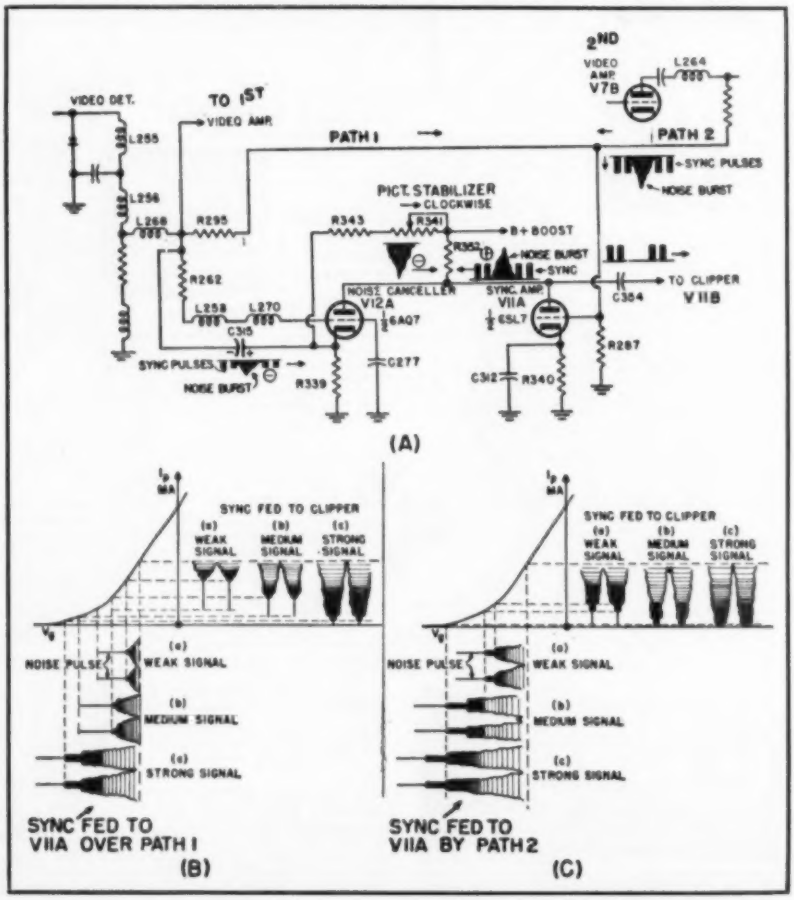

International Short-Wave

(*Continued from page 74*)

Calif.) Noted with *English* 1730-1800 on 7.500, 9.040 (best), 11.690A. (Sutton, Ohio)

Costa Rica—A *new* San Jose station is noted on 6.502A from around 2000 to as late as 2330; seems to announce "Radio Excelsior." (Robbins, Ind., URDXC)

Cuba—Some weeks ago, COBZ, *Radio Salas*, conducted *tests* in *English*-Spanish around 2300-2400 or later; asked for reports to Box 866, Havana, Cuba. (Riggs, Calif., others)

Cyprus—Sharq-al-Adna, Limassol, noted on 6.135, 6.170 around 0005-0015. (Niblack, Ind.) The 6.790 channel relays VOA in Greek 1530-1545. (WRH)

Czechoslovakia—Prague, 9.55, noted in *English* 1930-2000 for North America. (Beach, Mass.; De Hond, N. Y.)

Denmark—OZF, 9.52, noted at good level 2200-2300 to North America. (Littlefield, Mass.)

Dominican Republic—H11G, 6.130, Ciudad Trujillo, noted 2255 at excellent level; off 2300. (Niblack, Ind.)

Egypt—Cairo, 11.815, noted with news 1330. (Niblack, Ind.) With recordings 1445-1515. (Harris, Mass.) The Home Service lately has been carried on a *new* channel of 9.750A from around 1030-1430A closedown; all-Arabic, announces "Huna Kahera." (Pearce, England, Bellington, N. Y., others)

Ethiopia—ETAA, 15.047AV, now has *English* 1330-1430 sign-off. (Saylor, Va., others)

Finland—Helsinki has *English* 0700, 1430, 2200 over 9.55, 15.19, 17.80. (Lindholm, Sweden)

France—Paris, 17.850, noted at fair level 1045 in French.

French Morocco—*Radio Rabat*, normally closes 1800, but has been noted to 1830 Sat. (Pearce, England)

Germany—AFN, 5.470, Bayreuth, is scheduled 0000-1900. (ISWC, London)

(*Continued on page 130*)

IT'S A SHAME

to throw away that beautiful old Console . . . *replace the obsolete radio with a modern, easily-installed*

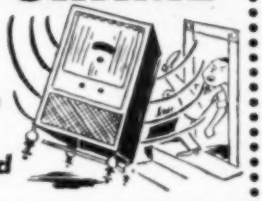

ESPEY AM/FM CHASSIS

(Enjoy Hi-Fidelity Reception)

It is not necessary to spend a large sum of money to modernize your old radio or to become a "High Fidelity" enthusiast. ESPEY chassis provide the Highest Quality at moderate prices.

Fully licensed under RCA and Hazeltine patents. The photo shows the Espey Model 511-C, supplied ready to play. Equipped with tubes, antenna, speaker, and all necessary hardware for mounting.

NEW FEATURES—Improved Frequency modulation circuit, drift compensated • 12 tubes plus rectifier, and pre-amplifier 12AT7 tubes • 4 dual purpose tubes • High quality AM-FM reception • Push-pull beam power audio output 10 watts • Switch for easy changing to crystal or variable reluctance pick-ups • Multi-tap audio output transformer supplying 3.2—8—500 ohms.

Write Dept. RN-5 for literature and complete specifications on Model 511-C and others.

Makers of fine radios since 1928

ESPEY MANUFACTURING COMPANY, INC.

TEL. YOrktelgar 9-7000

528 EAST 72nd STREET, NEW YORK 21, N. Y.

Compare... prove EMC superiority

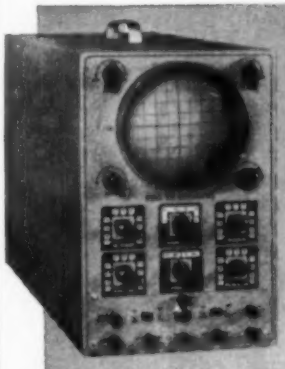

model 600

EMC MODEL 600 SCOPE features the use of a 5UP1 new 5 inch scope tube. The 2-stage, push pull, vertical amplifier has a sensitivity of .02 volts per inch and can be used up to 5 megacycles. A two step attenuator input is available. Synchronization is available on either positive or negative phase of input voltage through the vertical amplifier or from an external source. A multivibrator type of sweep from 15 cycles to 75 kilocycles is incorporated. Direct connections to scope plate available.

MODEL 600 (completely wired and tested)..... **$99.50**

model 106

VACUUM TUBE VOLTMETER

Check these features

SPECIFICATIONS

All functions completely electronic — meter cannot burn out.

DC VOLTAGE: Input resistance 16.5 megs or 1⅔ megohms per volt. Ranges 0 to 1.5, 10, 100, 300, 1000 up to 30,000 volts (with accessory probe).

AC VOLTAGE: Input resistance 2 megohms. Ranges 0 to 1.5, 10, 100, 300, 1000. Frequency response flat from: 25-100,000 cycles.

OHMS: 1000 — 10,000 — 100,000 —10 megohms, 1000 megohms.

COMPACT, portable bakelite case measures 4¼x5¼x2⅞".

MODEL 106 (complete with 1 meg isolating probe) $35.90

IN KIT FORM 23.90

MODEL HVP, 30000 Volt Probe for Model 106 .. 8.75

MODEL RFP, High Frequency Probe (useful to [illegible] megacycles) 4.95

—See them at your Jobber—

EMC

ELECTRONIC MEASUREMENTS CORP[illegible]ON

280 LAFAYETTE STREET * NEW YOR[illegible] Y.

EXPORT DEPARTMENT 136 LIBERTY STR[illegible] 6, N.Y.

Preferred for Original Equipment

Proven for Replacement

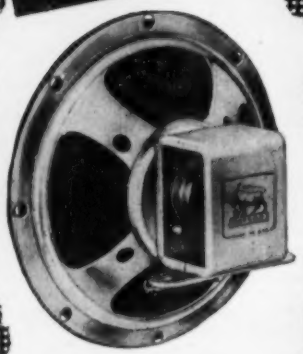

OXFORD

Speakers

There is an application for every Oxford Speaker . . . and an Oxford Speaker for every application.

OXFORD ELECTRIC CORPORATION

3911 S. Michigan Ave.
Chicago 15, Illinois

EXPORT: ROBURN AGENCIES, NEW YORK CITY

Greenland — Radio Angmagssalik, 7.570A, noted 0913-0951 closedown. (Pearce, England) Godthaab's OXI, 9.300A, noted from 1740, fair level in Ontario. (Bromley)

Greece—Radio Jannina, now near 7.090, noted closing 0200 (some days 0230); heard from opening 1500 to closedown 1700—with chorus. Athens, 7.300, has news 1430. Greek Forces Station, 7.050A, Athens, noted closing 1630. (Pearce, England) The VOA session in Greek 1530-1545 is now relayed over *all* Greek short-wave outlets. (WRH)

Haiti—4VEH noted Sun. on 9.710A at 1630-2130 sign-off. (Pfisterer, Pa.) By now should be using 9.667A daily 0630-0900 (or 0930).

4VCP, 6.385A, some days is strong around 2130, off 2154 with anthem; is "La Voix du Nord." (Bellington, N. Y.)

Honduras—HRP1, 6.351, San Pedro Sula, noted 2036-2101; HRQ, 6.125, San Pedro Sula, heard 2035-2054. (Patterson, Ga.)

Hungary—Budapest lists 6.248, 9.833, 7.220 for *English* 1700-1730, 1930 and 2300. (Lindholm) By now, however, may be using 11.910A instead of 6.248.

Iceland—Heard on 12.175 on Sun. *only* 1115-1130. (Bellington, N. Y.; Loven, Sweden)

India—VUB2, 4.840 and 7.240, Bombay, and VUC2, 4.880, Calcutta, noted closing 1230. (Hardwick, N. Z.) Delhi, 11.85, heard with news 0835. (Glick, Ind.)

Indo-China (Vietnam) — "Voice of Vietnam," 7.285A, excellent some days with news 0930. (Riggs, Calif.) *Radio France-Asie,* 11.925, Saigon, noted with news 0900, then with bilingual programs; heard on 9.754A from around 1035 with *English* 1100-1130 closedown (for Europe). (Pearce, England; Olsson, Sweden) Heard on 15.430 with news 0500. (Svensson, Sweden)

Iraq—Radio Baghdad, 6.135, noted with *English* 1415-1500 closedown. (Hardwick, N. Z.)

Israel—"Voice of Zion," 9.010A, has news 1515 (in *summer* may be 1415); announces news for 0645 over 9.010A, 6.830. (Pearce, England)

Italy—Rome noted daily in Italian 1100-1225 on 9.78, 11.81. (Gal, Calif.) With *English* for North America 1930-2000 on 9.575. (De Hond, N. Y.)

Japan — AFRS, Tokyo, announces schedule of 1600-0330, JKI, 11.825, JKL, 9.605; 0345-1000, JKI, 6.080, JKL, 4.860. (Riggs, Calif.) Kawachi, 4.940, noted 0410, good level; Nazaki, 4.910, heard 0415, excellent signal; Kawachi, 11.800, heard 1830, good level, moderate fading. (Ballou, Calif.)

Kashmir — Murree operates under the Kashmir Govt., scheduled 2130-2300 on 3.440; 0230-0400 on 6.250, 0630-1230 on 3.440. *Radio Kashmir,* Srinigar, operated by the Indian Govt., runs 2130-2330 on 3.277; 0200-0330 on 6.110, 0630-1200 on 3.277; relays news from AIR, Delhi, 2130-1030. (Radio Australia)

Kenya Colony—Nairobi, 4.855, noted closing 1500 with "God Save the

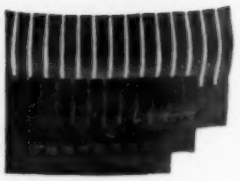

FINGER STOCK

Electrical Weather-Stripping by Eimac — *Now Available!*

Silver-plated, spring alloy, preformed finger stock especially suited for electrical "weather-stripping" for TVI-proofing cabinet access doors, etc. Also ideal for making coaxially constructed tube connections and many other uses. Available in 17/32", 31/32", and 1⅜" widths.

• *Write for new Eimac Catalogue Summary showing Eimac tubes and other accessories.*

Eimac

EITEL-McCULLOUGH, INC.
San Bruno, California

Now! HANDLE UP TO 90% OF TV TROUBLES by the easy PICTURE ANALYSIS METHOD!

PIX-O-FIX TV TROUBLE FINDER GUIDE

By Ghirardi & Middleton

Only $1.

Covers 24 common troubles identified by actual screen photos

• • • 190 possible causes of these troubles localized to receiver stage or section where they are most likely to occur.

• • • 253 step-by-step remedies for these troubles.

• • • 4,500 words in CAUSE AND REMEDY section to show exactly what to do.

Cut hours of tedious TV trouble-shooting to minutes! Make repairs twice as fast! Operation of Ghirardi's new PIX-O-FIX TV TROUBLE FINDER GUIDE is simplicity itself. Covers *all* TV receivers.

Just turn dial until actual TV screen photo appearing in PIX-O-FIX "window" matches distorted picture on set being repaired. PIX-O-FIX then gives you all possible causes for this trouble and just where in the receiver they are likely to be found. But that is only the beginning!

WHAT TO DO— HOW TO DO IT

Step-by-step repair instructions follow. Components likely to be faulty are specified. Quick tests are outlined. PIX-O-FIX guides you every step of the way!

Remember! PIX-O-FIX is NOT a "fix-it-yourself" gadget for consumers. It is a truly professional device for servicemen, apprentices and students—prepared by two of the nation's foremost service instructors—A. A. Ghirardi and R. G. Middleton.

MONEY BACK IF YOU'RE NOT SATISFIED!

Simply pin a $1 bill to this ad. Mail with your name and address to the publisher. If not satisfactory, return PIX-O-FIX in 10 days and your $1 will be refunded promptly. *(Price outside U.S.A. $1.25 same money-back guarantee).*

Dept. RN-53, RINEHART BOOKS, Inc., Technical Div., 232 Madison Ave., New York 32, New York

Queen," after time pips. (Pearce, England) Forces Broadcasting Service, East Africa Command, 7.265, Nairobi, noted 2300 with relay of BBC news. (Ferguson, N. C.)

Kuwait—Radio Kuwait, 5.000, noted around 1300-1401 closedown; all-Arabic. (Pearce, England) Uses 1 kw. and transmits 1130-1400 (*winter*) and 1230-1500 (*summer*) with additional period Fri. 0000-0200; programs are Arabic music, topical features (all-Arabic); Chief Broadcasting Officer and announcer is H. E. Shaikh Abdulla Mobarak; QRA for reports is The Broadcasting Officer, Radio Station, Security Department, Kuwait, Arabia. (Radio Amateur, London)

Madagascar—FIQA, 9.515, Tananarive, noted from 1130 in French. (Pearce, England) Heard opening on this channel 2230 in French. (Riggle, Ohio)

Mozambique — CR7BU, 4.918AV, noted signing on 2300 with *English* session. (Niblack, Ind.) Noted in Portuguese on 4.870A closing 1514 with "A Portuguesa." (Pearce, England)

New Zealand — Wellington, 9.54, noted 0225-0305. (Hyson, Md.)

Nigeria—Radio Nigeria, 4.800, Lagos, heard in Britain around 1300-1500 or later. Relays BBC news 1300, 1500. (Pearce, Catch)

Northern Rhodesia—ZQP, 7.200, Lusaka, is heard in Sweden around 1130. (GDX-aren, Sweden)

Outer Mongolia—Ulan-Bator can be heard on 6.325 from about 0400 to 1000 closedown. (WRH)

Pakistan — Radio Pakistan, 17.710, has news 0330, closes 0430; heard signing on 0630 on 15.270 to Indonesia (parallel 11.674); closes 0715. (Pearce, England) Noted on 3.320 with news 1015-1030, fair. (Hardwick, N. Z.) In parallel on 5.990A. (O'Sullivan, England) Noted closing 1600 on 7.010. (Sutton, Ohio)

Peru—OAX4Z, 6.082, Lima, is reported widely closing 2400 with announcements in Spanish, *English,* French. Robbins, Ind., notes OZX4B, *Radio Azul,* Cerro de Pasco, *moved* from 6.526 to 6.560, best *after* 2300.

Philippines — DZH3, 9.500, "Radio Philippines," Manila, lists schedule of 1600-1000; power has been raised from 250 watts to 1 kw. (Hardwick, N. Z.) DZH6, 6.030, Manila, fair to good around 0400. (Saylor, Va.) DZH8, 15.300, noted weekdays 0730-0800 with "Sacred Song Request" session. (Svensson, Sweden) DZH9, 11.855, noted 1845 weak level. (Bromley, Ontario) DZH5, 9.690, 250 watts, Manila, is scheduled 1700-2030 *only.* (Navarro, Philippines)

Poland — Warsaw has *English* for North America from 0600 on 9.55, 9.57. (Pearce, England) And from 0715 on 9.555, 11.740. (Saylor, Va.)

Portugal—CSB51, 12.875, heard well 1600. (Nilsson, Sweden) Lisbon, 15.125, noted signing off 1200. (Bishop, Ohio)

Portuguese Guinea — CQM4, 5.838, noted 1700-1800 closedown. (Osterblad, Finland)

Portuguese India—Radio Goa, 9.610, scheduled 2100-1230, heard in Germany

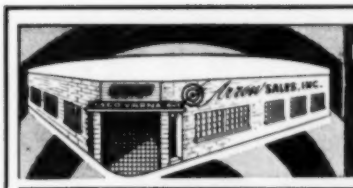

FOLLOW ARROW FOR BIGGEST STOCK AT LOWEST PRICES
- RADAR—TRANSMITTERS
- RECEIVERS — TUBES — PARTS

AN/APS-4
Airborne radar. New.
Complete ..... P.U.R.

AN/APS-6
Airborne radar set. New.
Complete ..... P.U.R.

AN/APR-4
RECEIVER & TUNING UNIT ..... P.U.R.

AN/APS-3
AIRBORNE RADAR SET. Now Complete .... P.U.R.

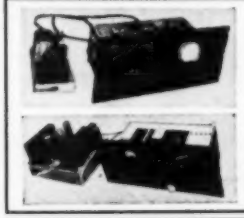

COMBO

BC-624 VHF RECEIVER
Freq. range 100-156 MC. Less tubes & crystals, with conversion dope. Used, good cond. **$19.95**

BC-625 VHF TRANSMITTER
Freq. range 100-156 MC. Less tubes & crystals, with conversion dope. Used, good condition.. **$12.95**
BOTH TRANSMITTER & RECEIVER. Per set **$29.95**

Monthly Specials!

RT-34/APS-13 420 MC. TRANSCEIVER with 5 stages of 30 MC. IF amplifier strip. Less tubes & R.F. section. With dynamotor.. **$6.95**

BC-604 30 W. FM TRANSMITTER. For 20-27 MC. band. Ideal for 10-11 meters. Complete with tubes, temperature controlled crystal oven and technical manual with all instructions for BC-603 and BC-604. Less dynamotor and crystals. Excel. cond. $12.95

INTERPHONE AMPLIFIER BC-709-B
A 2-position single stage audio amplifier. Uses 1 tube and operates from self-contained batteries. With Instruction Manual and Schematic. NEW (less batteries) **$3.95**

SCR-625 FAMOUS MINE DETECTOR
For prospectors, miners, oil companies, plumbers, etc. New.
WHILE THEY LAST! **$59.50**

COMMAND EQUIPMENT (SCR-274N)

		Used	New
BC-442	ANTENNA RELAY. Less cond. with cond.	$1.95	$ 3.95
BC-451	TRANSMITTER CONTROL BOX		1.50
BC-450	3-RECEIVER REMOTE CONTROL BOX		2.95
MC-215	MECHANICAL DRIVE SHAFT. Per length		2.95
BC-696	2-POSITION RECEIVER CONTROL BOX		2.95
BC-455	6-9 MC RECEIVER. With tubes	9.95	14.95
BC-454	(3-6 MC) With tubes	9.95	
BC-453	With tubes	$19.95	
MC-211	90° ANGLE COUPLING UNIT.		$0.95
FT-234	MOUNTING RACK for single transmitter	2.95	3.50
FT-226	MOUNTING RACK for 2 Command Xmtrs.		3.95
FT-221	MOUNTING PLATE for FT-220		1.50
FT-220	MOUNTING RACK for 3 receivers		2.25
FT-225	MOUNTING PLATE for BC-456		2.25
BC-456	MODULATOR. For SCR-274.		4.50
	Complete set of 4 tubes for transmitter		1.25

RADAR TEST EQUIPMENT
TS-3, TS-12, TS-13, TS-15, TS-33, TS-34, TS-35, TS-36, TS-45APM3.

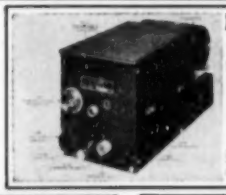

234-258 MC RECEIVER
11-tube UHF tunable receiver with schematic. Like new.
$17.95
Rack $3.50
Control Box.. 1.50

ARC-4 TRANSCEIVER
140-144 MC. Complete with control box, tubes, 12/24 VDC dynamotor with schematic. This is a special reduction for this month only.
Like new **$32.50**
MT 101 ARC-4 ..... $6.00

Miscellaneous Specials!

SURPRISE PACKAGE!
20 lbs. of good, useable radio parts $2.95

HS-16 HEADSET. 8,000 ohms. New $2.45
HS-23 HEADSET. High imp. New 4.95
HS-30 HEADSET. Featherweight type. Low imp. NEW ..... $2.49 USED 1.49
HS-33 HEADSET. Low imp. New 6.95
HS-38 HEADSET. USED, excel. cond 1.49
NEW 3.50
T-26 CHEST TYPE MIKE. New 2.75
T-32 DESK STAND MIKE. New 5.95
LIP MIKE. Navy type. New ..... .96

PE-125 POWER SUPPLY: Operates on 12 or 24 v. battery. NEW $17.95
CD-307 EXTENSION CORD. For HS-23-33. NEW 1.95
RS-38 MIKE. NEW 4.95
Used 1.75
BC-605 INTERPHONE AMPLIFIER. With dual noise input circuit. NEW 5.95
RM-13 COMPLETE REMOTE CONTROL BOX. For 3 separate transceivers. With handset, decibel output meter and FE-8 ringer unit. 110 V. AC operated. Excel. cond. 29.50
FL-8 RANGE FILTER 1.95

TUBES!		TUBES!		TUBES!		TUBES!		TUBES!	
16JP4	$19.95	304TH	$8.95	5CP1	$4.95	3FP7	$3.25	9002	$ .89
16AP4	24.95	304TL	8.95	5BP4	4.95	4AP10	1.49	9001	.99
16DP4	19.95	830-B	2.75	5FP7	2.25	211D	.69	9003	1.69

MP-22 MOBILE ANTENNA. MOUNTING RACK. Complete with hardware. New ..... $ 3.95
TU-17 TUNING UNIT. (2-3 MC.) For BC-223 Xmtr. Used 2.95
I-70 "S" TUNING METER. NEW 2.50
WOBULATOR. See p. 43 Dec. '51 RADIO NEWS 5.95
BC-1023 75 MC. MARKER BEACON RECEIVER. Complete with tubes, mtg. rack. NEW 10.95
TU-25 TUNING UNIT. (3.3-5.2 MC.) For BC-223 Xmtr. Used 2.95

IN-4A L R TUNING METER. Used ..... $ 3.95
FL-8 RANGE FILTER 1.25
TS-10 SOUND POWERED HAND SET—Used, excel. cond. For Pair 14.50
BC-1033 75 MC MARKER BEACON RECEIVER. Complete with tubes ..... P.U.R.
FIELD TELEPHONE. EE-8. Complete BRAND NEW. SPECIAL. ONLY 27.50

TUBES! NEW! ORIGINAL BOXES!
Limited Quantities Available
250TL....Ea. $11.50 250TH.....Ea. $14.50

INDUSTRIAL CORPORATIONS
We carry one of the most complete stocks in U. S. of Military Electronic Equipment, Test Equipment, and Aircraft Electronics. Call or write for free catalogue.

$5.00 MINIMUM ORDER ACCEPTED. All items subject to prior sale. All shipments F.O.B. warehouse. Calif. residents add tax with remittance. 20% deposit required. Please specify shipping instructions with order. **EQUIPMENT WANTED!** Highest prices paid for all types of Electronic Gear!

ARROW SALES, INC.
Cable Address: ARROWSALES POplar 5-1810
Mailing Address: P. O. Box 3878-R, N. Hollywood, Calif.
Office-Warehouse: 7460 Varna Ave., N. Hollywood, Calif.

STAN-BURN
S-P-A-R-K-S

CATHODE RAY TUBE SPECIALS
One Year Guarantee

G. E.		STAN-BURN	
5TP4	$44.95	10BP1A	$11.00
7JP4	17.10	12LP4A	14.20
10BP4A	19.25	14CP4	17.00
10FP4A	24.00	15DP4	19.50
12KP4A	27.10	16AP4	21.60
12LP4A	21.70	16FP4	19.60
12UP4B	28.25	16GP4	21.60
14CP4	24.50	16EP4A	22.60
16AP4A	30.95	16DP/HP4	19.60
16DP4A	28.20	16DP/HP4A	20.60
16GP4	31.25	16KP4	18.50
16KP4/16RP4	28.20	16LP4	20.60
17BP4A	23.90	16LP4A	21.60
17CP4	23.90	17BP4	18.50
19AP4A	39.45	17CP4	21.60
20CP4	24.75	19AP4	23.90
20LP4	37.50	19AP4A	25.90
21EP4A	37.35	20CP4	29.50
24AP4A	76.50	21EP4	32.50

ANTENNAE SPECIALS

	1-11	12 or more
DOUBLE V ½	$2.98	$2.20
DOUBLE V ½ Dowel	3.45	2.45
DOUBLE V ½ Dowel	3.95	2.95
10 Element Conical ½	3.55	2.55
Folded Hi Straight Low Quick Rig ½ elements	4.25	3.25
WINDOW CONICALS	4.95	3.75
MASTS		
5 FOOT SWEDGED	.79	.69
10 FOOT PLAIN	1.39	1.29
TV WIRE		
42 Mil.	$ 9.95 M Ft.	
55 Mil. 300 OHM	14.95 M Ft.	
72 OHM COAXIAL	38.00 M Ft.	

4 Prong Vibrators, each ..... $ 1.49
Lots of 12 or more 1.19
12" Heavy Slug Speaker ..... Special 3.98

CHASSIS 630 REGAL with Cascode Tuner $149.50
OPEN FACE CABINET 42.00

WIRE RECORDERS IN STOCK
WILCOX GAY—Model 2A1D ..... $ 89.97
PENTRON — Model 9T3C — 2-speed Tape Recorder ..... Write for Prices
RADIO CRAFTSMAN
Model C400—Hi-Fi Amplifier ..... Net 42.90
Model C10—AM-FM Tuner ..... Net 131.50
Model C500—Williamson Amplifier ..... Net 99.50
We also carry MASCO—BOGEN—PILOT, etc., Amplifiers, Pre-Amps, FM Tuners and WEBSTER Tape Recorders.

6x9 PM Speaker	$ 3.98	630 Vert., output	
7" PM Speaker	3.98	potted	1.29
711 G.E. Flyback	1.98	630 Vert. Blocking OSC. XForm	.89
70° Yoke	1.98	Casco Tuners	19.95
630 Vert., output upright	1.98	Standard Tuners	17.95
		Dumont 31.25 mc	14.95

AUTHORIZED DISTRIBUTORS for General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

We carry a Complete line of HI-FIDELITY and sound equipment. Send us your requests.
We also carry a complete line of popular makes of Radio at 50 10 discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations.
Terms: 20% with order. Balance C.O.D. All prices F.O.B. NEW YORK Warehouse. Minimum order $5.00.
Write for our latest price list and Hi-Fi catalog to Dept. RN-5.

STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

around 1000. (ISWC, London) Has religious broadcasts in *English* some days 1030. (Pearce, England)

Roumania — Bucharest noted with *English* 1500-1545 on 9.252, 6.210 (no longer says "Radio Romana Libera" for this channel). (Pearce, England) Noted closing 1630 on 9.252. (Chatfield, N. Y.)

Sao Tome—Noted on 17.677A with good level Sun., Thur. 0700-0800 in Portuguese. (Svensson, Sweden)

Saudi-Arabia — Djeddah (with programs from Mecca) uses 752 kc. and 3.970 for Ryadi (Central Arabia) and the Persian Gulf; 7.245A for Egypt; 6.100 for Syria and Lebanon; 11.850 or 11.950 for Indonesia. (Radio Amateur, London)

South Africa—Springbok Radio, Johannesburg, is being heard at weak level most days on 4.945, with *English* around 2320-2345 fade-out. (United 49'ers) Johannesburg, 4.895, heard opening 2345 in Afrikaans with trumpet fanfare, then setting-up exercises to piano accompaniment. (Niblack, Ind.) Heard closing 1130 on 11.937, at 1200 with SABC news on *new* channel of 9.595A. (Pearce, England)

South Korea—HLKA, Seoul, is reported on 9.555 parallel Pusan, 7.935A. Not reported to *ISW DEPARTMENT* yet as heard in USA.

Southern Rhodesia—Salisburg, 3.320, noted 1300 with BBC news relay. (Pearce, England)

Spain—Radio Falange de Valladolid, 7.006A, noted with music 1400-1800. (Nilsson, Sweden) *Radio S.E.U.*, 7.093V, Madrid, noted 1435 with music. *La Voz de Falange*, 7.380A, Madrid, heard 1445 with music. (Pearce, England) *Radio Nacional de Espana en Malaga* has *moved* to 6.980 from 6.950A; closes daily 1830A. (Kary, Pa.) Madrid, 9.363, good 1800 and 2215 in *English* for North America. (Annala, Ore.)

Spanish Morocco — Radio Tetuan, listed 6.067, sent daily schedule of 0800-1000, 1400-1800 Spanish, 1000-1200 Arabic. (Kary, Pa.)

Sweden—Radio Sweden, 9.535, noted with *English* 2300-2330. (Osburn, Calif.)

Switzerland—United Nations Radio, 6.675, Geneva, carries "U. N. Album" Mon., Wed., Fri. in *English* and Tue., Thur. in French 1315-1330; *except* Sat., Sun. has news 1330-1345, and news in French 1345-1400. (ISWC, London) Berne, 6.165, good 2030-2100. (Barras, La.) Noted on 15.305 at 0828 in *English*, strong. (Machajewski, N. Y.)

Syria—Damascus, 7.145, noted 1515 with Arabic session. (Pearce, England) Still has news 1715, closes 1730 on 11.915A. (Sutton, Ohio)

Tahiti—Radio Tahiti, 6.135, Papeete, is coming through with weak level around 0000-0130 closedown. (McPhadden, Calif.)

Taiwan—"The Voice of Righteousness," BEV34, operates on 7.400 at 0200-0300 in Chinese, 0300-0400 in *English;* "The Voice of Salvation," BEC26, uses 7.400 at 0630-1030. (Radio Australia) "The Voice of Free China," Taipeh, operates to Europe and Middle East over BED4, 11.800, at 1400-1600 (*English* 1420); in *English* for USA over 15.235, 11.735 at 2300-2400; relays VOA to China 1700-1730 daily over 11.920. (ISWC, London, and others)

Tanganyika—Dar-es-Salaam hopes to have a 20 kw. transmitter in service by mid-1954. (Ridgeway, South Africa)

Tangier — Pan-American Radio, 7.300, noted 1400-1500. (French, Mass.) Signing off 1900 in Spanish, French, *English*. (Niblack, Ind.) *Radio International*, 6.110, noted from 1530. (Ballington, N. Y.) *Radio Africa*, 7.126, noted 1000 with popular songs in French, Spanish. (Pearce, England, and others)

Thailand — Bangkok, 6.240, noted 0553, good level; started fading 0645.

LARGEST SELLING BOOSTER
at any price!

burton browne advertising

(Riggle, Ohio) Noted on 6.240 at 1845 with American recordings, identified 1900 in Thai, *English*, then continued in Thai. (Mercier, France)

Trinidad—VP4RD, 9.625, noted 0650 at fair level. (Harold, Wisc.)

Turkey—TAT, 9.515, good level 1815-1900 with *English* to North America. (Dadson, Mich.)

USI—"Voice of Indonesia," 9.710 (*new* 50 kw. transmitter), Djakarta, now has *English* 0600-0700, 0930-1030 (news 0945); also used for Europe, New Zealand from 1200A. (Radio Australia) In the 0930-1030 period is parallel with 4.910. (Pearce, England, others) YDF7, 11.770, noted with *English* 1400-1500. (Hardwick, N. Z.)

Vatican—Currently, HVJ has *English* 1000 over 9.646, 11.740, 15.120; 1315-1345 over 9.646, 7.280, 5.968. (ISWC, London)

Venezuela — Radio Rumbos, YVLK, 4.970, Caracas, noted signing off 2400. (McPhadden, Calif.) Has *English* daily 1800-1900.

Yugoslavia — Belgrade announces *English* for 0130 on 6.100, 9.505; 1200 on 6.100; 1315, 1645 on 6.100, 6.150. (Pearce, England, others)

Press Time Flashes

The Fiji Islands' short-wave station is now on the air from Suva with 500 watts, to serve those portions of the Fiji group which are not adequately covered by the 2 kw. medium-wave outlet, ZJV. Has been *testing* on frequencies in the vicinity of 6.000 (6.005, 5.995, 6.130), and more recently on 7.195; in verifying for Rosenauer, Calif, said times of *test* transmissions are 1900-2100, 0030-0500 daily which are the hours of the medium-wave transmitter; when the final frequency has been established, an additional transmission will be 1400-1600. *Wants reports* to Fiji Broadcasting Company Limited, Victoria Parade, Suva, Fiji. On tests, Rosenauer found the 7.195 channel *best* (heard from 0300 fade-in to 0500 sign-off), despite slight ham QRM.

The Milwaukee Radio Amateurs' Club, Inc., recently celebrated its traditional "Old Timers Night" and its 35th year of existence; claims to be the oldest continuously active radio club in the world.

The annual outing of the United 49'ers Radio Society will be held July 19 at the home of James Pickering, Hightstown, N. J.; Pickering is treasurer of the club. (Boice, Conn.) The World Friendship Society of Radio Amateurs, England, is conducting a membership drive, particularly to enroll members in USA; details can be had from representative Gary Ripton, 47 Lake St., Le Roy, N. Y.

Tests are scheduled to begin shortly from Apia, Western Samoa, 6.040, relaying medium-wave ZM2AP, 1420 kc.; the last series of tests planned a year or so ago was cancelled.

Radio Free Asia is now relayed daily *except* Mon. 0645-1015 over DZI4, 6.110, DZI5, 11.940, Manila, and by Guam, 9.490; heard best in Britain on

NOW..Wire Lead Micas with 500 times better moisture resistance than ever before!

Sangamo HUMIDITITE* Mica Capacitors

When you use Sangamo HUMIDITITE molded Mica Capacitors, you gain all the advantages of an amazing moisture seal that offers previously unheard-of moisture resistance characteristics for compression molded plastic-encased mica capacitor components.

*what is HUMIDITITE?

Humiditite is a remarkable new plastic molding compound, developed by Sangamo, that gives Sangamo Mica Capacitors moisture resistance properties far superior to any others on the market.

HERE'S THE PROOF . . . The standard moisture resistance test described in MIL-C-5A (proposed) Specification requires mica capacitors to offer at least 100 megohms of insulation resistance after ten 24 hour cycles in a humidity chamber at 90% to 95% relative humidity. The best competitive micas barely meet this requirement . . . but Sangamo HUMIDITITE Micas, *under the same conditions*, all tested in excess of 50,000 megohms! Continued tests, over and above requirements, with the same HUMIDITITE Micas, proved them capable of withstanding from 21 to 52 cycles (from the smallest sizes to the largest) before failure.
Humiditite is just another example of the advanced engineering that enables Sangamo to meet the existing and future needs of the electronic industry. For additional information about HUMIDITITE, write for Engineering Bulletin No. TS-111.

Those who know... SANGAMO choose Sangamo

SANGAMO ELECTRIC COMPANY
MARION, ILLINOIS

5C53-5A

SPEAKER RECONING
Complete line Cones, Spiders, Rings and Voice Coils. Custom Built Voice Coils. Low prices. Write for Parts List and Reconing information.
WESTERN ELECTRONICS CO.
3104 West Colfax Denver 4, Colo.

ON-THE SPOT BATTERY RECORDER
WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK
Continuous, permanent, accurate, indexed recording at only 5c per hr. Instantaneous, permanent playback. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with "hidden mike"! Write for Detailed Literature.
MILES REPRODUCER CO., INC.
812 BROADWAY Dep't RN-5 NEW YORK 3, N.Y.

ANOTHER OUTSTANDING JOBBER
BURROUGHS RADIO Inc.
711 Second Street N.W.
Canton, Ohio
HAS THE SENSATIONAL NEW
EICO
470-K 7" SCOPE KIT
IN STOCK!

470K KIT $79.95 WIRED $129.50

TV Technicians—
Show your Skill
Let your Customers SEE that GOOD service is your business. Your skill is your most precious asset. Dress it up with the right tools to make sure its appreciated.

NEW
De Luxe tube caddy
$14.95*

Carries TOOLS and TUBES; Saves TIME, MONEY
PAYS for ITSELF
Technicians who carry the Tube Caddy make the right impression. Handy top tray for tools, soldering gun, or meter. Regimented drawers give tube inventory at a glance. Slip-apart hinges on cover, with clips inside for price list or mirror.
Its efficiency saves time, its neatness inspires confidence—builds business. Can pay for itself in three weeks time. Size 18 x 14½ x 9¼ in. Ask your Parts Jobber or write.
*Net to Dealer. Higher on West Coast. Other Models $13.50 and $7.75.

Craftsmanship in Cabinets
Argos
PRODUCTS COMPANY
310 MAIN STREET • GENOA, ILLINOIS

11.940. (Pearce) Noted on 6.110 with news 0945. (Balbi, Calif.)

A *new* Broadcasting Center of *four* short-wave transmitters of 100 kw. each is now under construction at Cairo, Egypt; when put into service, will beam programs to Asia, America, Europe. (WRH)

The *new* station *Radio Emisorra de Piratininga*, 6.025, Sao Paulo, Brazil, has been logged by Niblack, Ind., with good signal as early as 1800; call seems ZYR63.

According to Wadia, Japan, *Radio Japan* will shortly begin a transmission for South America.

A *new* transmission for South West Africa (not to be confused with the African Service) is aired by SABC, Johannesburg, over 9.680 Sun.-Thur. 2345-0130, 0315-0715, 0900-1605; Fri. 2345-0130, 0315-1650; Sun. 0055-0130, 0315-1605. (WRH)

When this was compiled, press dispatches from Germany indicated that a *new* short-wave station, "Radio Liberation," had just taken to the air from Munich to broadcast to Iron Curtain countries.

After quite an absence, TGWA, Guatemala City, has returned to the air; schedule is believed 0730-1900 on 15.170 and 1900-2400 on 9.760; has "Belize Program" (*English*) 1900 in parallel over TGWB, 6.180A.

On Mon. *only*, YVKO, 6.17, Caracas, Venezuela, has *English* session 1815. (Chatfield, N. Y.)

Radio Jamaica lately has been using 3.305A (replacing 3.360) at 0600-0700, then 4.950 to around 1600, when again uses 3.305A to 2300A sign-off. (West, Va., Bellington, N. Y., others)

Radio Clube de Angola, Luanda, Angola, has returned to 9.470 after using 9.092A for a few days. (Bellington, N. Y.)

Radio Belize, British Honduras, has been noted on its *new* 6.100 channel parallel with 4.951 at weak level around 1830-2100 sign-off with "God Save the Queen"; best around 1900. (Stark, Texas)

ZNB, Mafeking, Bechuanaland, is using both 8.232 and its "old" channel of 5.900 (which had been inactive) in parallel 0600-0700, 1200-1430; relays SABC news 0615, 1200. (Ridgeway, South Africa)

A *new* Spanish station is *Radio Juventud de la Coruna*, heard Sun. 1205 on 7.035. (Mercier, France)

The East Coast North America "morning" beam from *Radio Australia*, VLA11, 11.84, is now at 0700-0855; DX session Sundays is now 0840.

According to announcement, TGNA, 9.668, 11.850, should have changed schedule for *English* to 2200-2300 daily. (Bellington, N. Y.)

Radio Nederland, Hilversum, Holland, now has *English* 0445-0525, 21.48, 17.775, 15.22, 6.025; 1100-1140, 11.73, 9.59, 6.025; 1630-1710, 9.59, 6.025; 2130-2210, 9.59, 6.025.

Revised schedule from *Radio Japan* is 0000-0100 to North America, JOA6, 15.135, JOB4, 11.705; 0600-0700 to North China, JOA3, 9.675, JOB2, 7.180;

this FREE booklet
CONTROLS and the AMPLIFIER
will help you plan your music and your music-playing system

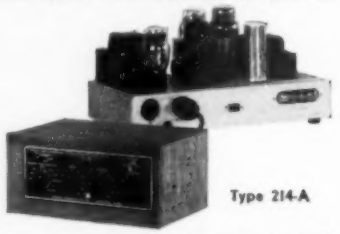

Type 214-A

Are you confused by too-much too-technical music equipment? You are not alone. Controls are to music systems as steering wheels are to autos. Why are our 210-B and 214-A Amplifiers the standards against which others are compared? Only because H. H. Scott Amplifiers give you better music under *all* conditions, not just ideal ones. Write today for your copy of free non-technical booklet AM 5, to sift fact from fancy.
Dept. RN553

HH SCOTT
HERMON HOSMER SCOTT INCORPORATED
"PACKAGED ENGINEERING"
385 PUTNAM AVE. CAMBRIDGE 39, MASS.

WAREHOUSE CLEARANCE SALE
ALL SURPLUS MUST GO!

BC706D Switch Boxes	3 for	$1.00
35MMFD Double Spaced Var. Cond.	3 for	1.00
CD716 Cords W/PL55 & JK56	3 for	1.00
BC-347 Interphone Amp.—less tube		1.00
Telescoping Whip Ant., 3-ft.		1.00
Telegraph Key JK-38		1.25
Telegraph Key—knee mount		.75
Elevator Servo Amp. with tubes		3.95
Navy CW Xmtr. 85-105MC, less tubes		2.50
Ant. Relay Unit—BC442A		3.95
5BP4 Cathode Ray Tube		3.95
2-Gang Variable Cond. from SCR-522		1.29
3-Gang Variable Cond. from SCR-522		1.59

Special Purchase! FM Radio Chassis

88-108 MC—Complete with 6 tubes, built-in antenna and speaker. Product of famous radio and TV maker whose name we promised not to mention $16.95

TWO-STATION INTERCOM SYSTEM

Consists of master and remote station, 20-ft. of 3 wire cable, 115 V operation, AC or DC. Extra wire .05 per ft... $17.95

NOTICE TO ALL HAMS
TRADE-IN your used communications gear on new Hallicrafters, National, RME, Hammarlund, Sonar, Elmac, Gonset, Etc. equipment. Write for FREE ESTIMATE, attention "Pick" —W3PFQ.

FREE QUOTATIONS on hi-fi equipments yours on request. All famous brands of amplifiers, tuners, changers, pick-ups, speakers, etc. Just tell us how much you want to spend and we'll recommend the best matched system your budget will allow!

SUN PARTS
DISTRIBUTORS
520 10th ST. N.W. • WASH. 4, D.C.

0700-0800 to Central China, JOA3, 9.675, JOB2, 7.180; 0900-1000 to Philippines-Indonesia, 1030-1130 to India-Pakistan, JOA3, 9.675, JOB4, 11.705. (Scheiner, N. J.)

All broadcasts from Lusaka, Northern Rhodesia, are directed to the African population of the three Central African territories of Northern and Southern Rhodesia and Nyasaland, while programs for European listeners are transmitted from Salisbury, Southern Rhodesia. The Lusaka station has plans for extending its operations considerably in 1953 when a *new* station is to be erected; the ultimate aim is to have two simultaneous transmissions in African vernaculars and simple *English;* the hours will be further extended also. (Radio Amateur, London)

* * *

Acknowledgment

Thanks for the fine reports! Keep them coming to 948 Stewartstown Road, Morgantown, West Virginia, USA. . . . . K.R.B.

Spot Radio News

(*Continued from page* 16)

force and by setting in motion a series of events that must be productive of harmful future consequences upon our radio and television services. There is no disguising the fact that such consequences will hamper and stunt the growth of that most vigorous and flourishing competitive broadcast system which the American people need and deserve. . . ." Continuing her angry rebuttal, Madam Commissioner said that she failed to . . . "see any real need or substantial justification for the Commission's approval of the merger."

THE POSSIBILITY that very low-priced (640 and 1240-kc.) portables may be made for Conelrad emergency use for family protection during air raids was reviewed recently during a special conference of set makers and officials of the Federal Civil Defense Administration in Washington. Under the Conelrad plan, to be placed in operation when there is danger of an enemy air attack, AM stations would transmit, under limited power on the 640 and 1240 kc. bands, raid information.

FCDA and the Bureau of Standards are preparing specs for a basic small dual-frequency receiver which would become available to everyone in industry.

Among those at the meeting were Lewis Clement, *Crosley;* Dorman Israel, *Emerson Radio;* Don Gaertner, *Admiral;* Leonard Sutton, *National Alert Co.;* W. A. Moore, *Packard-Bell;* K. B. Anderson, *General Electric;* W. F. Chaffee, *Philco;* James D. Secrest, RTMA, and members of FCDA, NPA, and the Commission.

RECOGNIZING THAT THE COMMISSION is not too keen about granting an exclusive allocation of 360 mc.

ANNOUNCING THE NEWEST, MOST ADVANCED MOBILE RADIO EQUIPMENT EVER DESIGNED!

Now being made by Platt Manufacturing Corp. Get all the facts. Write for illustrated catalog sheets today!

VISIT PLATT'S BRANCH STORE at 159 GREENWICH ST., N.Y.C. You'll find many bargains not listed here.

MN-26C INSTALLATION

A 12 tube remote control manual direction finder desirable for commercial type navigation on boats and planes. Has a frequency range of 150 kc to 1500 kc in 3 bands. This frequency covers the beacon and standard broadcast bands. Operates on 28 V DC input. Complete installation consists of:

MN-26C Receiver—Brand New	$39.95
MN-26K Rotable Loop	9.95
MN-28 Remote Control Box	10.95
2 Flex Shaftings	7.00
1 Antenna Cable	2.95
2 Plugs	5.00
1 MN-32 Azimuth Control Box	3.95

SPECIAL! Complete Installation $79.95 (You save $9.80)

BEACON RECEIVER BC-1206

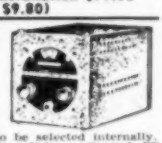

Frequency Range—195 KC to 420 KC. IF Frequency—135 KC. Receiver Sensitivity—3 Microvolts for 10 Milliwatts output. Output Impedance—500 Ohms and 4000 Ohms to be selected internally. Power Output—230 Milliwatts. Volume Control—RF Gain Control. Power Supply—24-28 Volts Aeroplane Battery. Current—.75 Amperes.

BRAND NEW—ONLY **$16.95**

Field Telephones

Army surplus, completely reconditioned and electrically tested, using 2 flashlight cells and a pair of interconnecting wires. GUARANTEED—like new. Only $22.95 NEW **$28.95**

FL-8 RADIO FILTER

Range or Voice for 1020 cycles. Audio Switch mounted on Filter. Excellent for CW. Brand New! SENSATIONALLY PRICED AT ONLY **$1.79**

FL-8 Radio Filter—$1.29

ARC-5/R-28 2 MTR RCVR

$25.95

Here is the 2-meter superhet you have been looking for! Absolutely one of the BEST available today! Tunes from 100 to 156 Mcs. In four crystal channels. (Easily converted to continuous tuning.) Tube lineup is as follows: 717A—R.F., 717A—Mixer, 2-12SH7—1st and 2nd I.F. 16.9 Mc. 12SL7—Det. AVC Squelch, 12SL7—1st audio-squelch amplifier. 12A6—2nd audio, 12SH7—R.F. Osc.—4th Harmonic Gen. 717A—Trip. 12th Harmonic Gen. 717A—Dblr.—12th Harmonic.

Excellent, used $25.95

PRE-AMPLIFIER MODEL K-1

The K-1 is used to amplify output level for microphones and phonographs. Operates on 24-28 VDC, can be converted to 110 AC. Comes complete with PL 55 plug and 2-foot 119-B cord. 2 terminal blocks and instruction book.

BRAND NEW . . . . . SPECIAL! **$3.95**

ARMY TEST UNIT 1-236

Meter is contained in a metal box 5½" long x 3⅝" wide x 3¼" deep. Comes complete with test leads and instruction book. Can be used for testing between AC and DC measuring resistance of circuits, checking fuses and testing capacitors.

SPECIAL **$4.19**

MINIMUM ORDER $2.00

Immediate Delivery — Send 25% deposit on C.O.D. orders. All shipments F.O.B., N.Y.C. (N.Y.C. residents add sales tax to your remittance.)

Special-of-the-Month!

Radio City Products Model 449

VOLTOHMMETER

5000 ohms per volt, AC-DC output 1000 V. ohmage up to 2 megs. In metal case with zero adjusting knob on front panel. Ready for use. (List Price $24.95) OUR SPECIAL PRICE **$9.95**

TUBES BRAND NEW! JAN! BOXED! **TUBES**

1B22	69c	30/44	29c	841	29c
1B23	$3.75	100B	49c	845	17c
2B22	49c	114B	29c	864	19c
2C26	09c	215A	09c	954	15c
2C26A	09c	221A	29c	1625	29c
3B22	$1.19	304TH	$5.95	1626	19c
3C24	98c	316A	29c	7193	09c
3D6	39c	388A	59c	9002	69c
7C4	39c	471A	$1.19	E1148	49c
10Y	19c	532A	$1.19	RK34	99c
12KBY	39c	722A	99c	VR92	14c
15R	39c	801A	19c	VT127	19c
		826	39c		

HEADSETS

HS-33 Good, used	$1.95
HS-33 low impedance with cord and plug, used, fine condition	3.79
HS-23 high impedance, BRAND NEW with ear pads	5.95
HS-33 low impedance, BRAND NEW with ear pads, cord and PL-54 plug	6.45
HS-33—BRAND NEW—Western Electric	7.25
CD-307A Cords, 6 ft. NEW	1.49
H-16/U high impedance. Includes two receiving units	3.95
HS-16 high impedance—used	.98

BC-221 Frequency Meter

Real Value! QUANTITY IS LIMITED —so first come, first served. They are just like new, with original calibration charts. Range 125-20,000 KC with crystal check points in all ranges. Complete with crystal and tubes **$129.50**

MODULATED TYPE $150.50

MODULATED TYPE with AC Power Supply 179.50

These Frequency Meters are factory tested, checked for frequency alignment and GUARANTEED.

SCR-274N COMMAND and ARC-5 EQUIPMENT

	USED	EXCELLENT USED	NEW
RECEIVERS			
BC-453—190 to 550 KC	$29.95		$49.95
BC-454—3 to 6 MC			24.95
BC-455—6 to 9 MC		$13.95	19.95
1.5 to 3			14.95
TRANSMITTERS			
A-998—2.1 to 3 MC			29.95
BC-457—4 to 5.3 MC		14.95	
BC-458—5.3 to 7 MC	7.95	8.95	17.95
ARC5-T-19—3 to 4 MC		24.95	34.95
BC-459—7 to 9.1 MC			24.95
T-15 ARC 5—500 to 800 KC			29.95
ADDITIONAL EQUIPMENT			
BC-456 Modulator	3.49	4.25	7.29
BC-450 Control Box (3 Receiver)	1.49	1.95	2.75
BC-451 Control Box (Transmitter)	1.29	1.79	2.39
BC-442 Relay Unit (ANT)			5.69
Plugs: PL 147, 148, 151, 152, 153, 154, 156—EACH		1.25	
Flexible Shafting with gear to fit receivers			2.69
3 Receiver Rack	1.79	2.29	2.98
2 Transmitter Rack	1.69	2.39	3.97
Single Transmitter Rack			1.97
DM-27 Dynamotor for Command Set		1.95	5.95
DM-33 Dynamotor for Command Set		2.95	3.95
Mounts for 2 Trans. Rack, 3 Rec. Rack, Modulator, & Antenna Relay Unit		1.95	

ELECTRIC MEGAPHONE SYSTEM

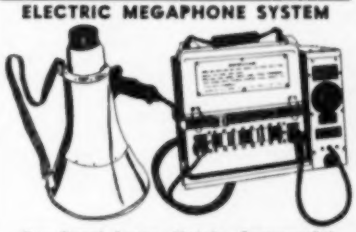

For Rural Areas, Hotels, Commercial Steamers, Ball Parks, Etc.

U. S. NAVY Type PAE-1 Electric Megaphone equipment is designed for voice reinforcement in much the same manner as, but to a greater degree than, the familiar acoustic megaphone. Consists of Megaphone Unit (which combines a microphone and reproducer in a single assembly), Portable Amplifier which electrically amplifies the output signal of the microphone section of the megaphone and feeds this amplified signal to the reproducer section. Charging Rack for recharging the self-contained storage battery of the portable amplifier. BRAND NEW—A TREMENDOUS VALUE! DEMONSTRATION GIVEN AT EITHER OF PLATT'S STORES **$149.50**

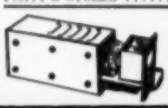

TURBO AMPLIFIER

4 tube Amplifier used by U. S. Air Force. 115 V. input at 400 cycles. Without tubes—EXCELLENT. SPECIAL **$1.19**

PLATT ELECTRONICS CORP.

DEPT. A, 489 BROOME ST., NEW YORK 13, N. Y.

PHONES: WO 4-0827 and WO 4-0828

Examine FREE

Prentice-Hall
ELECTRONICS & UHF LIBRARY

Edited by W. L. EVERITT

5 VOLUMES — 1662 ILLUSTRATIONS

Pay Easy Installments If You Keep Set

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logicaly arranged, profusely illustrated.

Electronic Fundamentals and Applications
By Prof. John D. Ryder, Univ. of Illinois

Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) characteristics of vacuum tubes, (c) all basic tube circuits. Includes: Electron Ballistics. Cathode-Ray Tubes. Emission of Electrons. Space Charge in Vacuum Tubes. Diode Rectifiers. Triodes. Multi-Element Tubes. Small-Signal Amplifier Circuits. Audio-Frequency Amplifiers. Radio-Frequency Amplifiers. Oscillator Circuits. Modulation Systems. Wave-Shaping Circuits. Gaseous Conduction. Gas Diodes. Gas Control Tubes and Circuits. Photoelectric Cells. Solid-State Electronics.

Electromagnetic Waves and Radiating Systems
By Prof. Edward C. Jordan, Univ. of Illinois

Covers entire field of electromagnetic engineering. Includes propagation as well as radiation and transmission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

Ultra High Frequency Engineering
By Thomas L. Martin, Univ. of New Mexico

Theory and technique of ALL the new fields of electronic engineering: Radar, Telemetering, Electronic computing, Facsimile, Television, Flind landing systems, Pulse-time modulation, Ionosphere measurements . . . and the others.

Networks, Lines and Fields
By Prof. John D. Ryder, Univ. of Illinois

Network transformations and theorems. Resonance. Impedance transformation and coupled circuits. Filters. General transmission line. High-frequency line. Equations of the electromagnetic field. Radiation. Transmission and reflection of plane waves at boundaries. Guided waves between parallel planes. Wave guides.

Elements of Television Systems
By George E. Anner, New York University

Complete basic theory, **plus** current practice, covering: Closed TV Systems. Commercial Telecasting Systems. Color TV Systems. Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

SEND NO MONEY — EXAMINE FREE

Just mail coupon below to get complete 5-Volume Set on 10 DAYS' FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only $5.35 down and $8 a month for five months until full price of $45.35 is paid. Decide for yourself—without risk or obligation—just mail coupon to examine Library ten days free.

PRENTICE-HALL, Inc., Dept. M-RN-553
70 Fifth Avenue, New York 11, N. Y.

Send me the Prentice-Hall ELECTRONICS & UHF LIBRARY (5 Volumes) for ten days' free examination. If fully satisfied in ten days I will send you $5.35 plus few cents postage and then $8 a month for five months until full price of $45.35 is paid. Or I will return the Library in ten days and owe nothing.

Name .....

Address .....

City and State .....

in the 5925-6875 mc. band for theater TV, exhibitors and motion picture interests have entered a compromise proposal asking for the use of common carrier frequencies by a limited common carrier. The plan also suggested that existing common carriers cooperate with the theater TV carrier, presently, because of a lack of national-networking facilities.

No specific company was named to serve as a theater TV carrier, although it appeared as if a cooperative company would be set up, similar to Aeronautical Radio, for the purpose.

FCC'S timetable calling for over 40 grants a month was once again on schedule during the second month of the new year, bringing the total of post-thaw approvals to 274; 87 for very-high and 187 for ultra-high stations.

Grants are well scattered now, as the table on page 148 illustrates, with even northern New England areas receiving a share of the new u.h.f. approvals. North Adams, for instance, in Massachusetts, will eventually have a Channel 74 outlet, which may serve Pittsfield, too, if permission is granted to place an antenna atop Mount Greylock, a peak mountain point in the state. And Portland, Maine, was awarded Channel 53, whose operators have indicated that they might be able to begin telecasting in the early fall of the year. Texas continued to receive the lion's share of grants, with five being awarded to Dallas, Longview, McAllen, Midland, and Texarkana. Missouri also appeared as a winner of a number of authorizations, four going to Hannibal, St. Louis, Clayton (area of St. Louis), and Sedalia. Most of the approvals for the month were for ultra-high stations.

EDUCATIONAL TV received quite a jolt in New York recently when the temporary State Commission on the Use of Television for Educational Purposes, rejected a 10-station statewide network plan, noting that such a program was neither necessary nor desirable at this time.

The state commission declared that the cost of constructing and operating such a system would be staggering. They estimated that the construction cost for ten stations would be at least $6,000,000, the operating costs a minimum of around $8,000,000, and an additional $10,000,000 outlay would be necessary if half of the classrooms in the state were equipped with TV receivers costing about $250 each. Another $4,000,000 would also be necessary for special films which might be produced at the rate of five per week for 40 weeks, with each film costing about $20,000.

The report of the state commission added that if the . . . "major use of educational television is to be the showing of educational film . . . there was no reason why this could not be accomplished through the simple use of motion picture projectors and

New Guaranteed TUBES Standard Brands

0A2	$1.00	6ARG	2.75	815		2.90
0A3/VR75	1.10	6AS6	2.30	828		9.95
0B2	1.40	6F4	4.50	829		9.95
0B3/VR90	1.10	6J4	6.95	829B		11.95
0C3/VR105	1.00			832		2.75
0D3/VR150	.90			832A		9.95
1A3	1.00			833A		34.95
1B22	2.00			836		3.45
1B23	6.95			837		1.45
1B24	9.50			845		8.50
1B27	12.50			849		24.50
1B32	3.10			851		39.50
1N21B	2.75			852		19.95
1N22	1.25			860		3.75
1N23	1.25			861		19.95
1N23A	2.25	6K4	3.50	866A		1.50
1N23B	3.49	C6L	12.95	872A		3.25
1N34A	.79	15R	.89	874		1.10
1N38	1.80	100TH	9.50	884		1.40
1N40	8.50	250R	8.95	931A		5.50
1N58A	1.25	250TH	18.00	954		.33
1N63	2.39	304TH	7.95	955		.49
1N69	.89	304TL	7.95	958A		.69
2C39	21.00	307A RK75	4.25	959		2.95
2C40	7.25	310A	5.75	1005		.69
2C43	13.95	350B	3.95	1616		.90
2C44	1.19	393A	8.95	1624		1.45
2C52	4.95	394A	3.95	1625		.39
2D21W	2.49	417A	8.50	1626		.39
2K25	29.50	446A	1.19	2050		1.40
2K26	99.50	464A	10.95	2051		1.40
2K28	32.00	702A	2.75	5559	FG57	15.95
2K29	29.00	703A	4.50	5560	FG95	29.00
2K2	.99	705A	1.80	5561		
1A4	.75	707B	14.95		FG104	29.95
3A5	1.25	715B	8.95	5635		8.95
3B24	4.95	715C	19.95	5637		6.50
3B24W	7.50	717A	.98	5638		8.50
3B26	3.50	722A	1.95	5645		8.95
3B28	7.50	723A/B	18.95	5646		8.95
3BP1	4.95	724B	2.75	5651		2.75
3C22	75.00	726A	12.50	5654		2.00
3C23	9.95			5670		4.30
3C24 240	1.50			5672		1.20
3C33	9.95			5676		1.65
3C45	14.95			5686		4.25
3DP1	3.95			5687		4.25
3E29	13.95			5694		2.60
3FP7	1.95			5702		3.50
3QP1	3.95			5704		2.25
3HP7	3.95			5718		8.95
4B24	6.95			5719		8.95
4E27	13.00			5726		2.70
4-125A	25.00			5744		1.95
4X150A	25.00	728B	59.50	5749		2.25
4X500A	85.00	801A	.39	5814		2.50
5BP1	4.50	803	3.95	5823		2.95
5BP4	4.50	804	10.95	5844		4.50
5CP1	4.50	805	3.25	6026		2.25
5C22	42.50	807	1.65	8005		4.95
5D21	19.95	807W	9.95	8012		1.95
5FP7	1.95	809	2.95	8025		4.95
5R4GY	1.40	810	9.95	9001		1.25
6AK5WE	1.50	811	2.90	9002		.98
6AL5W	1.50	813	11.95	9003		1.50
6AN5	2.75	814	2.95	9004		.69

WE PAY HIGHEST PRICES FOR YOUR SURPLUS !

Vacuum Capacitors

50-15	$5.95
50-20	10.00
50-32	12.50
12-32	10.00
100-20	14.50

Complete line of Receiving Tubes. Thousands of other types of Transmitting Tubes. If you don't see it, WRITE. Prices subject to change without notice. Californians add sales tax. Add postage to order.

jsh SALES CO.

ELECTRONICS
Dept. R-21
7552 Melrose Ave.
Los Angeles 46, California

PREMAX

Sell and Install the Lowest Cost Copper Plated

GROUND RODS

Don't take chances! Buy and install the finest, most efficient, lowest price copper plated Ground Rods made. 3/8" diameter in 4', 6' and 8' lengths, with quick, secure screw clamp that takes No. 4 to No. 14 ground leads. Solid steel, copper plated and pointed for easy driving. Send for prices today. Make this extra profit.

PREMAX PRODUCTS
DIVISION CHISHOLM-RYDER CO., INC.
5304 HIGHLAND AVE. NIAGARA FALLS, N. Y.

screens now available in most schools."

The FCC was asked to continue for . . . "at least five to ten years, the allocation of the channels . . . for educational purposes . . ." since more time was necessary to study the possibilities of the service. Development of television for educational TV was favored, but private funds available through non-profit organizations, can be more effectively used at present, it was said, particularly for pilot stations, following the pattern adopted in Los Angeles, San Francisco, Houston, and Dade County, Florida.

In Chicago, a fund of at least $500,000 was being sought for an educational Channel 11 TV outlet. According to Edward L. Ryerson, chairman of the committee seeking funds, it . . . "would be a disgraceful episode in the history of Chicago, if . . . we failed to make use of the channel."

THE 90TH BIRTHDAY of the Signal Corps celebrated at Fort Monmouth, a few weeks ago, was a festive event with Major Gen. George I. Back, chief signal officer opening the birthday program with an address to 900 Signal Corps officers stationed at the post, now under the command of Major Gen. Kirke B. Lawton. At a reception-dinner, guests included former chief signal officers Major Gen. Joseph O. Mauborgne and Major Gen. George Van Duesen.

Congratulations poured in to the Fort, and tribute was paid to Major Gen. Albert J. Meyer, under whose command the Signal Corps was established on March 3, 1863. The general, a physician, invented the famous flag wigwag system as a means of communication for the deafened, which became a standard means of communication. The nation is indeed grateful to Gen. Meyer and his brilliant successors for their continued contributions to the art . . . . . L. W.

CR TUBE SHORTS

By WILBUR J. HANTZ

CATHODE-TO-HEATER shorts in picture tubes are constant headaches to the service profession. In many cases the manufacturer refuses to replace these tubes during the set warranty period.

It is entirely possible to use the a.g.c. keyer tube filament winding to supply the picture tube heater if it can stand the extra current drain. In receivers of the transformerless type, something else must be done.

Some technicians apply high voltage between the kinescope cathode and filament which in some cases does clear up the short. A more positive method is to apply a source of low voltage, high current. Practically all service shops have a 6-volt A-battery eliminator which they use for servicing car radios and this is a good source of low voltage and high current. Connect a 500 μfd. electrolytic condenser across the A eliminator output and intermittently flash the picture tube with this unit. You will find that cathode-to-heater shorts clear up faster and stay clear longer with this technique. —30—

PE-101C DYNAMOTOR
6 or 12 Volt

(Reprints of original CQ conversion articles — Oct. and Dec., 1952 issues, furnished.)

• This is the Dynamotor the Hams have been talking about! Easily adapted to supply 625 V. @ 150 MA. and 325 V. 125 MA. at 12 Volts—or 300 V. 90 MA. and 160 V. 110 MA. at 6 Volts. (Illustration shows modified.) NEW: $4.95

BATTERY SWITCHING UNIT and METER Used to switch load from one battery to another—or 6 to 12 Volts. Contains Weston 2" Meter—0-15 Volt DC Scale for reading battery voltage. 20 Amp DPDT Switch and Indicator. Case size: 4" x 6¼" x 2¾" ..... NEW: $2.95

TRANSFORMERS AND CHOKES

TRANSFORMERS—110 V. 60 CYCLE PRIMARIES:

5 Volt CT-25A—10,000 V. Ins. OPEN FRAME—6" x 5" x 4½" $7.95

6.3 V. 1 Amp. ....1.25 — 24 V. 1 Amp. 1.95

24 V. ½ Amp. ....1.50 — 24 V. 6.5 Amp. 5.95

6—24—or 30 Volt 8 Amp 5.95

Two 12 V. 4 A. windings, gives 12 V. 8 A. or 24 V. 4 A. 5.95

325-0-325 V. 50 MA—6.3 V. 2.5 A; 6.3 V. .6 A (Rect. 6x5) Half Shell—2⅞"x3⅛"x3"—No. T-23-28 ..... 2.75

175-0-175 V. 40 MA—6.3 V. @ 2.4 A; 6.3 V @ .6 A; Halfshell 2⅝"x2 3/16"x2⅝"—No. T-23-40 .. 1.75

350-0-350 V. 90 MA—6.3 V. @ 3 A; 5 V. @ 3 A; Upright—3⅛"x3⅛"x3⅞" 3.25

CHOKES

15 Henries—165 MA. 125 ohms $2.95

5 Henries—150 MA. 85 ohms DC—Res. Cased 1.95

8 Henries—150 MA. 200 ohms 1.95

5-20 Henries—300 MA. 110 ohms, 1000 V. Ins. .. 3.95

AIRCRAFT CONTROL CABLE

3/32"—7x7 Strand, Weatherproofed, Galvanized, Preformed, 920 lb. test. Ideal for Television Guying and many other uses. Prices:

4½c per Ft.—1000 Ft. or more @ 4c per Ft.

POWER SUPPLIES

VIBRATOR TYPE—6 Volt DC input; output 230 Volt DC 50 MA.—not filtered—w/tube. Ideal for Command Receiver operation as receiver is filtered internally. Size: 4½" x 4¼" x 3½" $5.95

PE-157 POWER SUPPLY—2 Volt Vibrator Supply, operates from BB-54 2 Volt Battery mounted in Case. Output voltage 1.4 V. ½ Amp. 125 V. 50 MA. Less Battery, Speaker, & External Power Cord—with Vibrator ..... Used $4.95

MP-28 BA Power Supply & Modulator f/TA-12—New: 29.95

BLOWERS—115 VAC 60 CYCLE

SINGLE TYPE: (Illustrated at left) 100 CFM. 2½" intake: 2" outlet. Complete size: 5" x 6". Order No. 1C939 ..... $8.95

DUAL TYPE: 100 CFM. 4" intake: 2" Dia. Each Side. Complete Size: 8" x 6". Order No. 1C880 ..... $13.95

COMPACT TYPE: 100 CFM. Motor built inside squirrel cage. 4½" intake; 3⅜" x 3" Dia. Complete size: 4¼" W x 8⅝" H x 8⅛" D. Order No. 2C867 ..... $14.50

FLANGE TYPE: 140 CFM. 3½" intake; 2½" Dia. Complete size: 7½" W x 7½" H x 6¾" D. Order No. 1C807 ..... $13.95

FLANGE TWIN: 275 CFM. 4½" intake; 3¼" x 3" Dia. Complete size: 11¾" W x 8⅝" H x 8-1/16" D. Order No. 2C069 ..... $21.95

BC-645 TRANSCEIVER
Antennas • Plugs • Mounts
Parts, Etc.

TRANSCEIVER—Easily converted to 420 to 500 MC Bands. Instructions furnished for 460-470 MC Citizen Band. Complete with PE-101 Dynamotor, Control Box, Tubes, and Mount $32.95

ANTENNA TWO UHF ¼ WAVE with Set of 8 Plugs $7.95

MOUNTINGS For: Transceiver: $1.50—Dynamotor: 75c Control Box 50c

CONNECTOR PLUGS—Set of 8 ..... $4.00

SET OF COILS—1-2-3-4th IF, Oscillator, Ant., Loop, Assy.; Guide and L Rod Assy., etc. $5.95

COAXIAL CABLES:

RG-8/U COAXIAL CABLE: 1 to 100 ft. 9c per foot —100 to 500 ft. 8½c per ft.—500 ft. or more 8c per ft.

RG-34/U COAXIAL CABLE: 71 ohm—125 ft. $15.00

ANTENNA EQUIPMENT

MAST BASES—INSULATED:

MP-132 BASE—Illustrated at left—1" heavy coil spring, 2" insulator. Overall length: 11½." Weight: 2½ lbs. Price $3.95

MP-S-33 BASE—Insulated type with heavy coil spring and 3" dia. insulator. Requires 2" hole for mounting. Weight: 9 lbs. $5.95

MAST SECTIONS FOR ABOVE BASES

Tubular steel, copper coated, painted, in 3 ft. sections, screw-in type. MS-53 can be used to make any length with MS-52-51-50-49 for taper. Any section ..... 50c Each

Larger Diameter Section: MS-54 ..... $1.25

TELEPHONE WIRE

3 Conductor, copper & steel, 525 ft. $4.75

COMMAND EQUIPMENT

BC-459 Transmitter—7 to 9 MC.—Used 14.95

BC-455 Receiver—6 to 9 MC—Used 10.95

BC-456 Modulator NEW: $5.95—Used 2.95

Transmitter Rack—Single: $1.50—Dual 2.00

Rec. Rack—Triple: $2.50. Modulator—Mtg. 1.50

Rec. Dyn.—Used: $2.95. Trans. Dyn.—Used 2.95

TRANS.—REC.—AMPLIFIERS

RA-10 DA RECEIVER ..... NEW: 49.95

TA-12B TRANSMITTER with Tubes—Used $39.95

R1/ARR-1 Receiver—easily converted to 220 MC. (See R.N. Jan. '49) Complete w/Tubes. NEW $4.95

RT7/APN-1 Transceivers—420 MC. Complete with Tubes & Dyn. ..... NEW: $24.95—USED: $19.95

ARC-4 Transceiver—140-144 MC. w/Tubes—Used: $29.95

BC-1206—200-400 KC. Delco, w/Tubes 9.95

BC-605—With Tubes, Used 3.95

BC-709—W/Tubes—New: $4.95 ..... Used: 3.95

BC-347—Less Tubes—New: $2.95 ..... Used: 1.95

REVERSIBLE MOTOR

Motor Reversible—3.7 RPM. 40 lb. torque. 24 Volt DC or AC. Motor size: 5½" x 4-1/32" x 3-5/16". Shaft size: 21/32" x 5/16". Philco No. 441-1008 ..... NEW: $5.95

110 Volt AC TRANSFORMER to operate above motor. NEW: $4.95

RECEIVER AND TRANSMITTER

RECEIVER BC-225 — TRF Receiver with 3 Plug-in Coils to cover Freq. Range 201 to 398, 2500—4700, 4150—7700 KC. With 6 Tubes: 1/37—1/38—3/39. Power Supply required, 6 or 12 Volt & 250 Volts. Size: 15"x8"x7". Schematic included **$8.95**

TRANSMITTER BC-230—Voice modulated Trans. with 3 Plug-in Coils to cover Freq. Range 2500 to 7700 KC. With 4 Tubes: 2/10y—2/45 & RF Meter 0-1.5 Amps. Power Supply required, 6 or 12 Volt & 350 Volts. Size: 13"x8"x7". Schematic included **$8.95**

SPECIAL BUY—BOTH RECEIVER AND TRANSMITTER **$15.00**

BC-223 EQUIPMENT

CABLES w/PL-150 ea. end ..... NEW: $ 2.50

POWER SUPPLY PE-125-AX 20.95

MOUNTING for Transmitter 1.75

OPERATING MANUAL 2.50

TUNING UNIT—TU-17—2 to 3 MC.—NEW, in Case 4.50

BC-223 TRANSMITTER—Less Tubes, Meter, and Front Panel 4.95

DYNAMOTORS

DYNAMOTOR and BLOWER: 9 Volts DC input; output 450 Volts 60 MA. 4800 RPM. At 6 Volts DC input; output 260 Volts 65 MA. 3000 RPM. Price **$4.95**

INPUT:	OUTPUT:	STOCK No.:	PRICE:
14 V. DC	600 V. 300 MA.	BD-86	$9.95
12 V. DC	220 V. 70 MA.	DM-24	6.95
12 V. DC	220 V. 100 MA.	DM-18	4.95
14 V. DC	375 V. 150 MA.	DM-375	8.95
14 V. DC	330 V. 135 MA.	DM-330	7.95
14 V. DC	500 V. 500 MA.	PE-59	14.95
12 or 24 V. DC	275 V. 110 MA.	USA-0516	5.95
12 V. DC	250 V. 50 MA.	DM-25	8.95
12 or 24 V. DC	500 V. 50 MA.	USA/0515	3.95
12 or 24 V. DC	440 V. 200 MA. 225 V. 100 MA.	D-104	14.95
28 V. DC	250 V. 60 MA.	PE-86	5.95

Address Dept. RN • Minimum Order $5.00 • Prices F.O.B., Lima, O. • 25% Deposit on C.O.D. Orders

FAIR RADIO SALES 132 SOUTH MAIN ST. LIMA, OHIO

"In music, listening quality is everything..."

It is the No. 1 MUST. Without it everything else becomes meaningless. The AUDAX CHROMATIC has that quality to a degree not equalled by any other pickup" . . . *Sarser of amplifier fame* (Toscanini's NBC Symphony).

Be it diamond or sapphire, every stylus has a limited life-span; the diamond lasts the longest. Obviously, then, replaceability of the stylus—at home, is of the greatest importance. AUDAX is engineered for easy replaceability of the stylus—at home. Of further importance is the fact that each AUDAX CHROMATIC stylus is replaceable *independently* of the other.

The magnetic attraction between pick-up and a steel turntable is known as the "Hidden-Pull."* Today, with point-pressure under 10 grams, an additional 10 or 20 grams of "Hidden-Pull" becomes a very serious factor . . . The Audax CHROMATIC has no "Hidden-Pull."

Only YOU can decide what sounds best to you. Therefore, See and Hear the Audax CHROMATIC and—You be the judge . . . Audax costs no more than ordinary pickups.

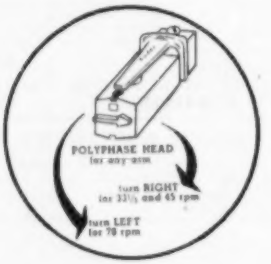

Available with the new Compass-Pivoted Audax arms and to fit the high quality record changers.

Only Audax has individually replaceable sapphire or diamond styli.

** 484 in 1953 ELECTRONIC phono facts obtainable from your dealer*

AUDAK COMPANY
500 Fifth Avenue, New York 36
Creators of Fine Audio-Electronic apparatus for over 25 years

"The Standard by Which Others Are Judged and Valued"

U.H.F. Test Equipment

(Continued from page 41)

could be used. Similarly, for Channel 83 (884 to 890 mc.) the fundamental will be 221 to 222.5 mc. and the fourth harmonic will be used. One important thing to consider in the use of harmonics is the increased sweep width due to the tripling or quadrupling. This requires adjustment of the sweep width and horizontal scope controls. If the fundamental sweep width is 10 mc., then at the third harmonic the width will be 30 mc. Since the i.f. bandpass of 3 mc. or so is the one actually observed on the scope, this will appear very narrow unless the sweep width is reduced accordingly.

From the above procedure it becomes apparent that the use of v.h.f. equipment for u.h.f. alignment is neither simple nor efficient. If only one or two u.h.f. channels are received optimizing the u.h.f. tuner for these channels with v.h.f. generators is quite feasible, but if more stations are received, u.h.f. equipment is required.

U.H.F. Sweep Generators

Although a number of test equipment manufacturers are now designing u.h.f. sweep generators, only four are currently selling these units. These are: *Tel-Instrument Co., Kay Electric Co., Polytechnic Research and Development Co.*, and *RCA*, the last offering two models. All of these generators cover at least from 470 to 890 mc. through continuously tuned networks. All of them have adjustable sweep width, internal blanking, and a sine wave voltage for horizontal scope deflection. Their prices range from $575 for the *Kay Electric* "Mega-Sweep" 111A to about $1500 for some of the other models.

Kay Electric Model 111A: This unit is basically the same as the standard "Mega-Sweep" made by this manufacturer. Two klystron oscillators are used, one is frequency modulated, the other is tuned over the range and the beat resulting from the two is fed out as the r.f. sweep signal. The new model 111A features 300-ohm output over the u.h.f. TV band with maximum available sweep width of 60 mc. Output voltage is stated as 0.3 volt across 300 ohms. The main drawback of this unit is the fairly complex tuning, tracking, and frequency determination inherent in klystron operation. A great deal has been written about the original "Mega-Sweep" and most of it applies equally well to this later model. One distinctive feature of this unit is that it can be used for v.h.f. and i.f. alignment as well. Its list price is $575.

Polytechnic Type 907: The outward appearance of this sweep generator is shown in Fig. 1. Its controls are fairly simple and feature a well calibrated, vernier-type dial covering from 35 to 900 mc. While this unit has no internal marker, provisions are made for

pfff...
REDUCE CORONA LOSS
STOP ANTENNA CORROSION

with CHAMPION Sprayon CLEAR PLASTIC (ACRYLIC BASE)

Improved and patented non-clogging nozzle sprays clear plastic coating on TV components. This Acrylic Base Plastic dries quickly, lasts indefinitely. Its natural high dielectric strength reduces corona loss in high voltage coils and circuits, insulation, rectifier sockets and other parts. Antennae and lead-ins coated with Champion Acrylic Base Plastic resist reception-damaging corrosion. The result, all-around better TV performance.

Also available in bulk, undiluted, with special Plastic Reducer.

Complete range of Sprayon colors including Chrome Aluminum, Gold — Copper — Lacquers, etc.

Write for descriptive bulletin.

CHAMPION BRONZE POWDER & PAINT CO., INC.
2526 W. Van Buren St., Dept. K, Chicago 12, Ill.

Editors and Engineers PUBLICATIONS

Book No. E&E-RL1 **RADIOTELEPHONE LICENSE MANUAL**

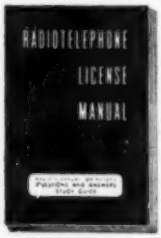

Now, in one convenient volume, complete study-guide questions with clear, concise answers for preparation for all U.S.A. commercial radiotelephone operator's license examinations.

$3.75 per copy •

BETTER TV RECEPTION (in fringe and low-signal areas). NEW SECOND EDITION. The standard guide for installation technicians. A popular text for TV enthusiasts.
Book No. E&E-TR2.....$2.50*

ANTENNA MANUAL. A practical, comprehensive book on antennas, for everyone interested in transmission and reception. Over 300 pages.
Book No. E&E-AM1.....$3.50*

RADIO HANDBOOK. GIANT 13TH EDITION. A one-volume library of radio information with extensive, simplified theory. Detailed how-to-build-it data on dozens of items of practical radio equipment. Book No. E&E-RH13...$6.00*

RADIO HANDBOOK, 12TH EDITION. Selected constructional items only. English edition.
Book No. E&E-RH12.....$3.00*

SURPLUS RADIO CONVERSION MANUAL. VOL. 1. Practical conversions. Write for list of contents. Book No. E&E-SM1.....$2.50*

SURPLUS RADIO CONVERSION MANUAL. VOL. 2. Companion to Volume 1.
Book No. E&E-SM2.....$2.50*

***Plus any tax.**

BUY FROM YOUR DISTRIBUTOR
ADD 10% ON DIRECT MAIL ORDERS TO
EDITORS and ENGINEERS, Ltd.
BOX 689A, SANTA BARBARA, CALIF.

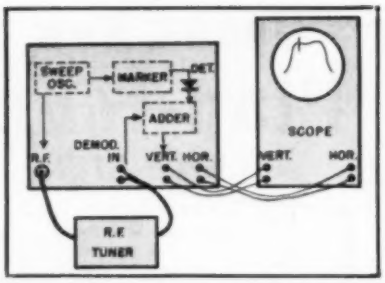

Fig. 4. Visual alignment setup using u.h.f. sweep generator which adds marker to detected sweep signal after it comes from tuner.

adding external markers through circuitry in the unit itself. This network is explained in detail in connection with the *RCA* WR-40A. The output impedance of the Type 907 is 75 ohms and the r.f. output can be varied from 10 microvolts to 1 volt. The internal construction of the generator using a 6F4 u.h.f. triode oscillator is shown in Fig. 3. The complex mechanical structure is required to assure good stability and accuracy over this wide frequency range. List price of this unit is $625.

Tel-Instrument u.h.f. sweep generator: Primarily designed for TV manufacturers, this sweep generator features crystal-controlled internal markers of adjustable amplitude. These crystal markers are located at every 36 mc. to permit simple identification of the particular section of the u.h.f. band. The sweep width is said to be adjustable up to 50 mc. The sweep frequency dial is calibrated in 36 mc. steps and a maximum output of 1 volt across 75 ohms is available. This unit is priced at $950 f.o.b. plant.

RCA: The *RCA* Model WR-40A u.h.f. sweep generator is probably the most complete u.h.f. instrument available. In addition to a continuously tuned sweep output from 470 to 890 mc., it also provides an accurate, tunable marker and a set of crystal controlled markers at 1 mc. and 10 mc. intervals. The amplitude of each of these three sets of markers is variable. Fig. 1 shows the complete unit. A very ingenious and slightly complex system is used to combine the sweep output with the markers. This is accomplished inside the generator, but after the sweep r.f. has passed through the unit under alignment. A block diagram of this scheme is shown in Fig. 4. The sweep output goes through the r.f. tuner and is then detected as in most visual alignment systems but, instead of going directly to the scope, it goes to the "adder" section of the generator. At the same time, a portion of the sweep signal is fed to the marker oscillator, the combination is detected and also fed to the "adder" section. In the "adder" circuit the two detected signals, essentially now 60 cps, are combined and connected to the vertical scope terminals. The advantage of this system is that it makes the sweep and marker amplitudes independent of each other. The same principle of

SPACE RESERVED!

for RCP Model 808A "Do-All" Tube and Set Tester

Because the Radio City Products Model 808A gives you more than just the facilities of a Tube Tester. It fills the need for a TV-Radio-CR Tube Tester and VTVM—with all this extra value designed into one unit.

Five Times Better Because It Is Five Instruments In One!

A TUBE TESTER—All the features of the famous 323 Dynoptimum free point tube tester—protected against obsolescence—tests all modern standard, miniature, naval base and subminiature tubes. Easily read on 4½" meter.

A CATHODE RAY TUBE TESTER—Will check all magnetic deflection type Television Picture tubes. Locates and isolates all shorts or leaks.

A REACTIVATOR—Revives and Reactivates many otherwise Dim or Bad Television Picture tubes. Can also be used on other tubes.

A VT VOLTMETER (A C-DC)—This really outstanding 17 Range instrument is a VT Voltmeter for AC as well as DC. Balanced bridge type push-pull circuit. Draws negligible current due to high Impedance of 25 megohms. Accuracy ±3% DC, ±5% AC. Discriminator alignment scale with zero center. AC & DC volts 0 to 5-25-100-250-1000;db — 20 to 16, —6 to 30, 6 to 42, 14 to 50, 26 to 62.

AN OHMMETER—Reads all Resistances 0.2 ohms to 1000 megohms on 5 ranges. Use this instrument also to check condensers for leakage and shorts.

Equipped with a double rollindex and enlarged, easy to read letters and numbers, the new RCP 808A is so designed as to simplify each operation. Truly a professional instrument for the professional technician.

The RCP 808A is housed in a handsome hand-rubbed oak carrying case and features an attractive, highly visual panel. Compartment available to hold test leads, isolation probe, batteries, etc. Size 12⅛" x 12¾" x 4¾". Weight 12 lbs. Complete, ready to operate at..... **$99.95**

Understand why so many servicemen agree that RCP is The Best For Test. Ask your local distributor for a copy of the latest Radio City Products Catalogue or write to us, in care of Dept. RN-5

RADIO CITY PRODUCTS CO., INC.
152 WEST 25th STREET • NEW YORK 1, N. Y.

STRIP-IT *A New Precision Tool*

For Removing Insulation from Wire and Cable
Designed for the Electronic Industry

- Fits in Tight Spots
- Cuts as Well as Strips
- Speedy, Efficient, Rugged
- Tool Steel Blades for Long Life
- INSTANT Adjustment to All Wire Sizes

Economically Priced **$1.95** net

The simple design and fool-proof operation of STRIP-IT makes this a tool that will become indispensable for electronic technicians and assemblers. Held in the palm of the hand, the operation is merely to bite into the insulation, twist, pull, and the wire is ready for the terminal connection. The sliding adjustment bar is set with a touch of the finger. STRIP-IT is engineered for thousands of operations, using only one set of blades.

THE C and M MANUFACTURING COMPANY

SEE YOUR LOCAL DISTRIBUTOR, OR WRITE

Norman R. Mac Innis, 1430 Mass. Ave., Cambridge, Mass., National Sales Representative

LOWEST PRICES

SPECIAL OF THE MONTH

100,000 Ohm, 150 Watt Resistors, Vitreous enamel. Only..... $.55 ea. 10 for $4.50

MOBILE DYNAMOTORS

MADE BY PIONEER AND EICOR

6 Volts input, 425 Volts at 375 MA Output, 6¾" Long, 4" Diameter. Weight 10 lbs. List Price Approx. $70.00. BRAND NEW, ONLY..... $27.95

CARTER SUPER DYNAMOTOR

12 Volts Input, 400 V. Output @ 200 MA Continuous or 375 MA Intermittent. Model B420. Designed for Police, Aircraft and Marine Use. Small, rugged and efficient. BRAND NEW, ONLY..... $24.95 Each

MOTOR DRIVEN TIME DELAY

Adjustable from 5 to 45 seconds, in 5-second steps. 115 Volt, 60 cy. sync. motor. SPDT switch, 10 Amp. contacts. Made for Western Electric. Only..... $4.95

PLATE TRANSFORMER BARGAIN

Primary 115 Volt, 60 Cy. Secondary 435-0-435 Volts @ 300 MA., 5V @ 3A., 5V @ 3A., 6.3V @ 10A. Electrostatic Shield, Fully Cased..... $5.95 ea.

G. E. RELAY CONTROL

(Ideal for Model Controls, Etc.)

Contains a sigma midget 8,000 ohm, relay (trips at less than 2 MA), high impedance choke, bimetal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total low price of... $1.25 Each 10 for $9.90

Panel Meters

NEW GOV'T SURPLUS STANDARD BRANDS

3" METERS

0-200 Microamps	$6.95
0-400 Microamps	5.95
0-500 Microamps	5.95
0-10 Milliamp	4.50
0-50 Milliamp	4.50
0-150 Milliamp	4.50
0-200 Milliamp	4.50
0-250 Milliamp	4.50
0-1000 Milliamp	4.50
0-10 Volt DC (1 MA)	4.95
0-15 Volt DC (1 MA)	4.95
0-50 Volt DC (1 MA)	4.95
0-150 V. DC (1 MA)	4.95
0-1.5 Volts AC	4.95
0-3 Volts AC	4.95
0-150 Volts AC	7.50
0-1.5 KV DC w/ multiplier	6.95

4" METERS

0-200 Microamps	$8.95

METER BUY OF THE YEAR!

2" Simpson Meters

Round bakelite case. Brand new, original cartons.

0-1 MA DC..... $3.95

0-300 Volts DC, 1000 Ohms/v (1 MA)..... $3.95

DB Meter —10 to +20..... $3.95

ANY 3 METERS $11.50

FILTER CONDENSER BARGAIN

8 x 8 M.F.D. 600 VDC Oil Compound Filled. NEW, but scratched. ONLY... $.95 each

BAKELITE CASED MICAS

MFD	VDC	Price	MFD	VDC	Price	MFD	VDC	Price
.001	600	$ .18	.01	1 KV	$ .45	.02	2 KV	$ .90
.002	600	.24	.002	1200	.35	.005	2800	.55
.01	600	.26	.024	1500	.65	.002	2500	.45
.02	600	.28	.033	1500	.75	.004	2500	.50

WIRE WOUND RESISTORS

5 Watt Ohms: 25-50-84-200-250C..... $ .09 ea.
10 Watt Ohms: 25-40-125-2K-4K..... .15 ea.
20 Watt Ohms: 150-300-750-1K-1.5K, 2.5K, 2.7K-10K-20K..... .20 ea.
30 Watt Ohms: 100-2500-4500-18K..... .22 ea.

1 MEGOHM, 1% W.W. PRECISION RESISTORS, SHALLCROSS. List Price Approx. $9.50. ONLY..... 97¢ ea.; 10 for $8.95

1% PRECISION W. W. RESISTORS IRC—SHALLCROSS

OHMS: 110, 1K, 2K, 2.5K, 2.8K, 5K, 9.5K..$ .35 ea.
OHMS: 25K, 50K..... .49 ea.
MEGOHMS: .5, 1..... .69 ea.

OIL CONDENSERS

3.75 mfd 660VAC	$2.45
1 mfd 2500VDC	1.75
1 mfd 3600VDC	1.95
.1 mfd 7500VDC	1.75
.5 mfd 7500 VDC	4.95
1 12KV DC	2.95
01x .01 12KV DC	2.95
5 mfd 660 VAC	2.95
7 mfd 800 VDC	1.75

GE KV METER

0-15 KV DC, 3½" Bakelite Case, 500 UA movement. Includes 30 Meg. 1% Ext. Multiplier..... $9.95

FILTER CHOKE BARGAIN

6 Hy 500 MA. Fully Cased..... $4.95

5 VOLT, 190 AMP.

Transformer, 105-125V. tapped 60 cy. Pri., 3.9 KV ins. Amertran..... $29.95

MICRO SWITCH

SPST, normally open, 10 Amp. contacts. .37 ea., 10 for $3.25

HEAVY DUTY FILTER CHOKE

4 Hy. 1 Amp, 10KV ins. Fully Cased..... $19.95

PIGTAIL MICAS

MMF: 5, 20, 50, 80, 100, 250, 300, 400, 500, 750, 800, 1000, 2000, 3000, 4000, 5000, 6000, 10000..... $0.09 ea.

PEAK ELECTRONICS CO.

66 West Broadway, New York 7, N. Y.

Phone WOrth 2-5439

combining the detected signals is employed in the *Tel-Instrument* and *Polytechnic* sweep generators, although the latter does not have a built-in marker. The *RCA* model WR-40A retails for $1450, a price in accordance with the special features of two sets of crystal-controlled markers and an accurate variable marker.

To reach a wider market and supply a simpler instrument *RCA* also produces the model WR-41A u.h.f. sweep generator. This unit is shown in Fig. 1. It does not contain the crystal-controlled or the variable marker portions, but otherwise performs the same as the more expensive edition. Both sweep generators contain a built-in detector which permits monitoring the r.f. output. To use this feature a short coaxial cable is connected between the r.f. output and the demodulator input terminal. The demodulator output can then be connected to the vertical scope terminals for presentation. The model WR-41A sells for $595 and adjustable marker units are sold as accessories with it. It is possible to use a maximum of four of these absorption type, presettable units. They are inserted into the sweep oscillator box and cause dips in the response curve at the desired frequencies.

Use of U.H.F. Sweep Generators

The basic connections for using the u.h.f. sweep generator are the same as for v.h.f., except where marker addition requires some changes. In aligning u.h.f. networks the same principles apply as in v.h.f., but some of the effects hardly noticed in v.h.f. assume major importance when dealing with u.h.f. With the exception of the *Kay Electric* "Mega-Sweep" model 111A, all other units have an output impedance of 75 ohms. This means that if a u.h.f. tuner is aligned which has the same impedance as the v.h.f. section, i.e., 300 ohms balanced, the 75 ohm unbalanced output from the sweep generator will have to be matched to the tuner. Several types of matching devices are available for u.h.f. and their performance will greatly influence the alignment and the appearance of the response curve. If the impedances are not matched closely, standing waves will result which can materially distort the response curve pattern. In trying to align the r.f. tuner then, it is actually possible to ruin the tuner response curve, while a good curve appears on the scope. For this reason it is essential that there be a proper impedance match between sweep generator and tuner. Some u.h.f. tuners use 50-ohm or 75-ohm coaxial input networks so that the problem of matching is much simpler. In any event, before aligning a tuner its input impedance and whether it is balanced or not should be ascertained.

Impedance matching devices which transfer from a balanced to unbalanced system are often called "baluns." There are several types on the market and some are available with the sweep

Handy, New Pfan-Tone PICK-UP KIT!

Discover the hidden music in your records—untapped by standard phonograph pickup equipment. Let amazing new Strain-Sensitive PFAN-TONE Pickup bring out the best in your records—old and new.

✓ **Exclusive New Principle Modulates** current from preamplifier—reproduces faithful electrical image.

✓ **Free From Hummmmm**—No coils to pick up induced current from turntable motor.

✓ **Easy to Install**—Now in handy KIT form. No soldering necessary.

Ask your radio supply man or write today for FREE INFORMATION. If you use a single play, professional turntable, ask about the new functional PFAN-WOOD TONEARM.

Pfanstiehl
CHEMICAL COMPANY
100 Lake View Avenue Waukegan Illinois

WANT THE BEST IN CAPACITORS?

Type UMP

• Many, many notable advances in the art of capacitor design and manufacture have been made by the ILLINOIS CONDENSER COMPANY. As an example, ILLINOIS CONDENSER COMPANY has recently been awarded a patent on their unique and exclusive molded capacitor construction as featured in the UMP types.

For almost two decades, ILLINOIS CONDENSER COMPANY has been building quality capacitors and regular users include most all of the largest manufacturers of TV and radio sets. Their names literally compose the "blue book" of electronics.

To meet the ever increasing demand for ILLINOIS electrolytic capacitors, ILLINOIS CONDENSER COMPANY has built new plants and greatly increased production. Why don't you, too, discover why ILLINOIS capacitors are "first choice" of so many!

Write for Catalog!

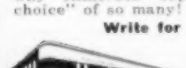

ILLINOIS CONDENSER CO.
1616 NORTH THROOP STREET • CHICAGO 22, ILL.

generator. *Polytechnic Research* manufactures a very good 50 to 300 ohm "balun" which sells for approximately $30. *RCA* supplies a matching pad which matches their 75-ohm generator to a 300-ohm system by means of a resistor network.

Many service technicians will remember the early days of television when alignment of the r.f. tuner was a major operation and required all sorts of tricks and precautions. We are now in the same stage as regards u.h.f. Aligning a u.h.f. tuner requires an accurate knowledge of the characteristics of the particular tuner as to bandwidth, input impedance, tracking, and peaking adjustments as well as familiarity with u.h.f. test equipment. With time, however, the familiarity and experience will come and as tuners and test equipment become more standardized, u.h.f. alignment will become just as routine a service job as present v.h.f. work. —30—

GDO TIP

By LEON CARTER

THE low-cost surplus "S" meters now on the market can be used to advantage in grid dip oscillators despite their relatively low sensitivity (3 to 5 ma.), by connecting them in a simple v.t.v.m. circuit as shown.

The oscillator grid leak is a carbon pot and the slider is connected to the triode grid through a 1 megohm isolating resistor. The tube can be a general-purpose triode capable of handling the full-scale meter current. R, should be the correct value for providing full-scale current through the meter with zero volts on the grid of the tube. 50,000 ohms is a good value as a starter.

Set the pot slider at the grounded end for this adjustment. Full scale is to the left of the scale with "S" meters, to the right with other types of meters. When the GDO is operating, increasing the pot setting will place a negative voltage on the triode grid, from the oscillator grid leak, and reduce the meter current. This adjustment gives a good reading on the meter as the oscillator amplitude falls off normally on the higher ranges and the dip is more easily seen.

When the instrument is used as an absorption wavemeter, the pot slider is set up toward the grid end to take advantage of the full voltage across the grid leak. Adjustment of the pot has a slight effect on the oscillator frequency up to 40 mc. but this is negligible. At v.h.f. it may become objectionable.

The v.t.v.m. tube may be half a twin triode with the other half serving as the oscillator, if desired. The GDO should be calibrated with the pot set to give a normal scale meter reading on each frequency range. —30—

Increasing "S" meter sensitivity.

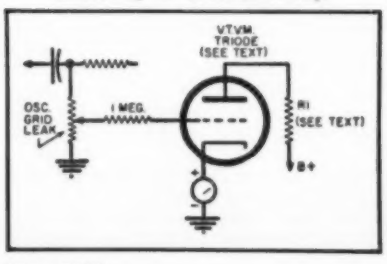

EVERYBODY'S TALKING ABOUT NEWCOMB'S

"AUDI-BALANCE"

PATENT APPLIED FOR

"The greatest amplifier improvement in recent years" . . . A godsend to both owner and service man." . . . "It used to take me hours to do what Audi-balance does in seconds." . . . "Does even better than I've been able to do with meters, this balances tubes dynamically." . . . "The problem has plagued us for years, it is now possible to keep perfect balance in output tubes consistently for lowest distortion." . . . "Audi-balance is the perfect solution."

Just one of the features that make the brand new Classic amplifiers by Newcomb so exciting. Write for catalog of 8 completely new home music amplifiers priced from $39.50 to $269.50 audiophile net.

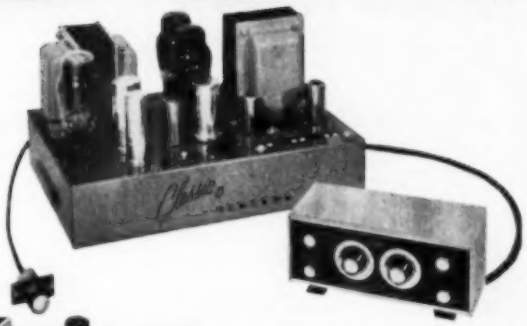

The Classic 25

For the sound thrill of a lifetime this superb new 25 watt custom amplifier has every practical operational feature electronic engineering can offer you. Even more important is the incomparable listening pleasure it provides.

The Classic 15

This outstanding 15 watt amplifier is unique in luxury features and technical perfection at a surprisingly moderate cost. Its smartly designed remote control unit is a superlative piece of engineering, beautifully finished in brushed brass.

Substantial Installation Savings

Savings of as much as, or more than, the entire cost of these fine amplifiers are being reported by enthusiastic purchasers. This is due to their unique design which removes the usual necessity of a remote control being near the amplifier, tuner and changer. These items can now be installed in a hall closet or any similar out of the way location leaving only the beautiful remote control and the speaker, with no messy confusion of wires, in the living room. No accessories connect directly to the remote control. All inputs connect only to the main amplifier. The savings in cabinetry and of installation labor are obvious and very real to those who take advantage of this new complete remote control design

Write for Catalog

NEWCOMB

DEPT. F 6924 LEXINGTON AVENUE, HOLLYWOOD 38, CALIF.

15 years of quality leadership

HARRISON HAS IT!
Famous
Aerosound ★
ULTRA LINEAR
OUTPUT TRANSFORMERS

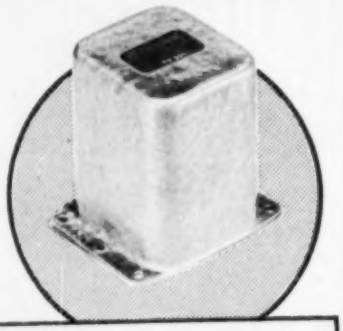

Using a Williamson?

Double Your Power Output ...Reduce Distortion by 50%!

ACRO TO-300

One of the world's finest transformers! Specifically designed to obtain maximum performance from ultra linear circuits.

- Undistorted Power: 40 watts, 30 to 20,000 cps
- Frequency Response: +1 db, 10 to 100,000 cps
- Unequalled Square Wave Performance
- Resonance-Free Response
- Low Phase Shift
- Output Impedances: 4, 8, 16 ohms
- Fully potted steel case: 3⅛x3¼x4¼"H.

$24.75

TO-305. Same as TO-300, PLUS 125 and 500 ohm output impedances **$30.75**

TO-310. Same as TO-300 except 20 watts. For converting popular 10-watt 6v6 amplifiers to Ultra Linear operation **$18.75**

TO-290. 20 watts. For original Williamson using 807, 5881 or KT66 as triodes **$15.75**

FREE! 12-page brochure on ultra linear output transformers, amplifier circuits and specs.

If COD, send 25% Deposit.

Mail Your Order TODAY! Immediate Shipment

HARRISON
RADIO CORPORATION
225 Greenwich St. • N. Y. 7, N. Y.

Please send me the following transformers as checked below (include postage; weight approximately 8 lbs. each):

☐ TO-300 ☐ TO-305 ☐ TO-310
☐ TO-290 ☐ Free Data Sheets

Amount Enclosed $ _____

NAME _____

ADDRESS _____

RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

IF YOU operate a service business, whether it is radio, television, audio, or mobile equipment, have you ever given any serious thought as to *why* set owners should select *you* to handle their service? What facilities or special abilities do you have that will permit you to give better or more satisfactory service than, for example, the dealer who originally sold the equipment? Is there some good, solid reason why service customers should patronize you in preference to your competitors?

Or do you feel that since you are *in* the service business customers should turn to you for service for no special reason except that you are in the business? Do you feel that somehow or other service customers in your area have some sort of an obligation to have you do their electronic service work? Or do you harbor the thought that the industry generally has a responsibility to help you *individually* make a success out of your service business?

These are soul-searching questions but they pose the fundamentals that must underlie sales planning in any business that hopes for long range success in the sale of service. When you set up any business to serve the public your major problem is effective sales promotion carried out at a cost that your volume of business will support. Without such a program carefully planned and consistently carried out, your business venture will flounder during seasonal lulls. If you do not have a planned service sales program geared to the needs of your specific locality or area you are not guiding your business through management; you are merely drifting along with the economic tide which will eventually land you on the rocks of failure.

Service Customers and You

In its tours about the country the TTLB staff comes in personal contact with many set owners and especially owners of television receivers. The essence of the information gleaned from these contacts is that set owners are more confused than dissatisfied with TV service. They have little idea about the complexities of TV circuitry and probably less about what good service should cost. Another problem that confuses them is, "How do you pick out a good, reliable service company from all the listings in the telephone directory?"

In order to gather factual information on the dormant market for electronic service and set owner attitudes toward independent service operators, the Bureau arranged to conduct a series of consumer surveys in various parts of the country. The first of these surveys has just been completed. It reveals some very interesting information.

To get a true cross-section of opinion in a selected area the surveys were set up to blanket the chosen section. Interviewers contacted set owners in a house-to-house program and gathered information on all electronic home instruments including television, radios (broken down into consoles, table models, battery portables, and auto), and record players. One hundred homes were covered in the first survey.

The cardinal point crystalized in this study merely emphasizes with facts a sad failing of independent service operators that has been pointed out many times in this department: Independent service operators are failing to sell themselves and their know-how and service facilities to the set owning public.

Despite the fact that manufacturers have made exceptionally good service selling promotional material available to service operators, so little of this is being used that it hasn't made even a dent in public opinion. All too often service people read a new public relations booklet on service made available to them by some manufacturer and say, "Gee, this is swell." Then what happens? Nothing. The only way these fine promotional pieces will ever be read by set owners in your area will be for *you* to order them and either mail or distribute them house-to-house.

Take the RTMA—BBB consumer booklet on television and service as an example. Probably a quarter of a million of these booklets have been

ordered and distributed. There are twenty million TV set owners. Just think of it—only one booklet has been distributed for every 80 set owners!

A Few Set Owner Facts

Of the first 100 homes covered in the TTLB set owner survey, 84 have television receivers. Twelve of these have required no service to date, 8 have had one service call under warranty, and 4 are serviced by the owners themselves.

The average "in service" life of the 60 receivers on which service costs were obtained is 20.1 months per set. These sets have required a total of 176 service calls for which the owners paid $959.25. This averages 2.9 calls per set at $5.45 per call.

Forty-five of these set owners said they preferred to call the dealer from whom they bought the set when it needs service. Four sets are serviced by part-time TV service technicians and only eleven are handled by independent TV service companies! TV service operators who have been afraid that radio and appliance dealers will get into the service field more aggressively should study this next fact.

Eight of the dealers who handled most of the sales involved in this survey maintain service departments. However, all of these dealers are interested in service only to the extent of maintaining customer good-will. They would prefer that independent service operators take over the servicing after the sets are out of warranty. But they will not assume the responsibility of recommending an individual service company to their customers. They feel that is a selling obligation of the service company who wants the service business.

Yet no independent TV service company has been able to capture the interest of an appreciable percentage of these people so they will call him for service.

Price Advertising?

A weekly community newspaper is distributed to every home in this area. Each week there are four or five ads in it offering TV home service at prices ranging from $2.50 to $4.00. Evidently none of this advertising is effective for not one of these advertisers was mentioned by set owners as their source of TV service.

When set owners are properly sold on what good service can accomplish in maintaining top picture quality the cost of service becomes secondary to the caliber of service rendered. The sales promotion necessary to sell the facilities, qualifications, and know-how of independent service companies is a responsibility of the service company itself—no one else can or will do that job for him.

After-Market Sales

The city in which this TTLB survey was made is a primary signal area on Channel 6 and a fringe area for a Channel 10 station. A good signal can

ends low line voltage hazard

CREST LVB-117 Line Voltage Booster

ACCURATE VOLTAGE BOOST!

A unique Line Voltage Booster engineered to restore peak performance to any TV set or electrical equipment. Insures full strength, width, and height of the picture when low line voltage weakens or shrinks picture. Corrects intermittent sync and oscillator drift caused by low line voltage.
350 Watt Rating . . . ample for most requirements on line voltages from 90 to 135 Volts.
Simple external Plug-in . . . 10 second installation aids over the counter sales.
Automatically operated . . . turns on and off with set or appliance. Multi-tap selector switch . . . permits exact voltage boost.
Visual Indicator . . . assures exact selection of required boost.
Overload fuse protection . . . minimizes hazards of unsafe line increases.
Dealer Net Price $10.77—List Price $17.95

VARIABLE INDUCTANCE

Universal Substitution Kit

TO SAVE VALUABLE SERVICE AND DEVELOPMENT TIME . . .
Now available for the first time . . . a complete Variable Inductance . . . Universal Substitution Kit.
For Vidio Peaking . . . IF Circuits.
The unique replacement set of 8 variable inductance coils cover a range from 1 to 590 μh.
Q-Max impregnation.
Full data enclosed on L min., L max., Q's, R, C dis., Freq. self-res.
Individual Calibration Charts permit adjustment to requirements of inductance value without test equipment.
Complete set Model 200K . . . Net Price $4.75
Single Set Replacements Available

CREST LABORATORIES, INC.
84-11 Rockaway Beach Blvd., Rockaway Beach, N. Y.
NEptune 4-3328

Just Out!

bigger — better

17TH edition

Radio's MASTER

- 1220 pages
- 80,000 items
- 8,000 illustrations
- 8" x 11"—5 lbs.

Publisher's price $6.50—your price through your regular parts distributor

$1.95

The right part when you need it for service

This permanent, hard cover Official Buying Guide of the electronic-TV parts and equipment industry with its comprehensive detailed index, eliminates the need for maintaining files of small catalogs and manufacturers' literature. RADIO'S MASTER catalogs 90% of TV and electronic equipment. Not merely part number listings — complete descriptions, specifications and illustrations written and compiled by each manufacturer. Enables you to make comparisons or substitutions right now!

UNITED CATALOG PUBLISHERS, INC.
110 Lafayette St., New York 13

Don't Gamble....

ON ULTRA HIGH FREQUENCY

"RECEPTION"

..you can count on the....

MI-TEE RAY

UHF

ANTENNA

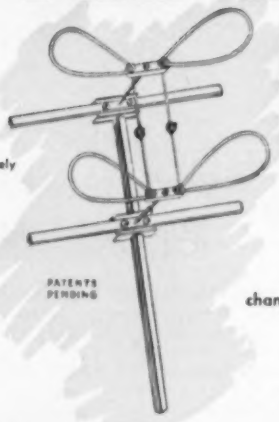

- designed and engineered exclusively for UHF
- all aluminum sturdy construction
- minimum space requirements
- matchless reception
- nationally advertised

PATENTS PENDING

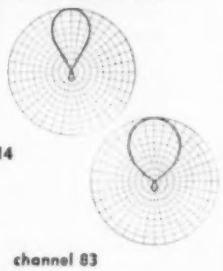

channel 14

channel 83

List Price $5.95

Fretco INCORPORATED

Pittsburgh 19, Pennsylvania

PAY LESS FOR TUBES

INDIVIDUALLY BOXED · FULLY TESTED · EACH TUBE GUARANTEED FOR SIX MONTHS

Type	Price	Type	Price	Type	Price	Type	Price
1B3GT	$ .69	6AS5	$ .50	6K6GT	$ .41	12AZ7	$ .70
1H5GT	.46	6AT6	.38	6L6G	.80	12BA6	.45
1L4	.57	6AU6	.43	6L6GA	.80	12BE6	.47
1N5GT	.57	6AV6	.38	6S4	.46	12BH7	.63
1R5	.56	6B4G	.96	6SA7GT	.52	12BZ7	.75
1S5	.47	6BA6	.45	6SJ7GT	.47	12SA7GT	.52
1T4	.56	6BC5	.53	6SK7GT	.50	12SK7GT	.50
1T5GT	.71	6BD5GT	.89	6SL7GT	.62	12SL7GT	.61
1X2	.67	6BE6	.47	6SN7GT	.54	12SN7GT	.54
3Q5GT	.65	6BF5	.60	6SQ7GT	.42	12SQ7GT	.44
3S4	.55	6BG6	1.34	6T8	.78	19BG6	1.39
3V4	.56	6BH6	.57	6U8	.85	19C8	.94
5U4G	.43	6BJ6	.48	6V6GT	.46	19T8	.79
5V4G	.73	6BK7	1.10	6W4GT	.45	25BQ6	.89
5Y3G	.34	6BL7	.83	6W6GT	.57	25L6GT	.48
5Y3GT	.30	6BQ6	.89	6X4	.34	25Z6GT	.42
6AB4	.46	6BQ7	1.10	6X5GT	.33	35A5	.48
6AF4	1.40	6BZ7	1.10	6Y6G	.59	35B5	.47
6AQ5	.54	6C4	.34	7N7	.52	35C5	.47
6AK5	.95	6CB6	.53	12AT6	.38	35L6GT	.47
6AK6	.63	6CD6	1.85	12AT7	.68	35W4	.31
6AL5	.40	6F6GT	.45	12AU6	.43	35Z5GT	.30
6AN4	1.30	6H6GT	.49	12AU7	.55	50B5	.47
6AQ5	.46	6J5GT	.40	12AV6	.38	50C5	.47
6AQ6	.42	6J6	.62	12AV7	.80	50L6	.47
6AR5	.38			12AX7	.61	117Z3	.39
		Motorola Ballast Tube 217A485459.....	.30			117Z6	.68

Each tube is performance-proven. 25% deposit must accompany all orders. Balance C.O.D. All prices F.O.B., N.Y.C. If remittance is made with order, you can deduct 2%. $1.00 handling charge for orders under $10.00. Subject to Prior Sale. Importer inquiries invited.

PHILLIPS TUBE COMPANY

2281 Nostrand Ave.
BROOKLYN 34, N. Y.
CLoverdale 3-8010-1-2

be picked up from the latter station from a properly selected and installed antenna system. Almost all set owners in a single station area tire of the programs available from the one station after a few months of set ownership and are good prospects for the necessary equipment that will permit them to receive a second station.

But only 11 sets out of the 84 covered in this study have outdoor antennas that permit them to get Channel 10!

Just consider the dollar volume of business that is waiting in this area for the sales promotional activity that will crystalize it into sales on antenna systems. Good sales promotion and follow-up salesmanship would interest a large part of these set owners in a deluxe antenna installation which would include a booster and a rotator in addition to a deluxe type fringe area antenna. This type of installation would give the TV service company a gross return of $150.00 per set. In the handful of homes covered in this survey there is a potential of more than $10,000 worth of antenna equipment and installation income.

Sales Promotion Service

At the present time, TV set dealers are not interested in the after-market sale of accessory equipment that requires installation. Dealers' sales programs are usually geared to the sale of new units and once a sale is completed and the set installed to the customer's satisfaction the average dealer is content to wash his hands of the account until it becomes a prospect for other new units that he handles.

As u.h.f. telecasting expands its coverage and present v.h.f. stations increase their power, many original primary signal areas will become fringe areas for new stations or for present v.h.f. stations with increased power. Thousands of set owners who bought sets for single or dual station reception with indoor antennas will become prospects for substantial antenna systems to add to the stations available to them.

But the majority of these people will remain *prospects* until some one *sells* them on the increased pleasure available to them from the stations they could get with properly selected and installed antenna systems.

Who is going to do this selling?

The set manufacturer has nothing to gain income- or profit-wise by promoting the sale of supplementary antenna systems and accessories to customers who already own his receivers. Neither has the set dealer who does not maintain a service department as a profit-producing function of his business have anything to gain by after-market sales of equipment that requires specialized installation.

The two industry elements which stand to gain everything in the sale of after-market equipment are the parts distributors and the independent TV service companies. So if these new

markets for antenna systems and associated accessories are to be properly exploited they will have to do it.

Sales Responsibility

The fundamental difference between a "jobber" and a "distributor" is that the jobber performs only a warehousing function through financing substantial quantities of the products he handles and jobs them in smaller quantities to the dealers or service companies that use them. A distributor not only handles this warehousing function but he also assumes some of the merchandising responsibility for getting his suppliers' products into the hands of its ultimate end market.

The tremendous expansion of the TV equipment after-market which will follow in the wake of u.h.f. expansion will throw local promotional responsibility squarely in the laps of parts distributors and their major service accounts. While some antenna manufacturers will expand the consumer advertising campaigns that have been tried in a few metropolitan areas it is highly questionable whether they will extend them into other than densely populated areas.

Merchandising-minded parts distributors will not wait for manufacturers to take the lead in exploiting the TV set after-market equipment sales. They will develop cooperative promotional sales programs with their major TV service accounts which will keep market control in their own hands.

The immediate need for such programs will probably become apparent to many distributors before the coming summer arrives. The TV-viewing boom that started with the political conventions last year and continued through the campaigns and the inauguration last January apparently has been gradually subsiding as indicated by reports from many of the older TV areas.

What About Radio Service

It has been apparent for a long time that service companies in TV areas have focused their promotional efforts entirely on television and have neglected radio service completely. At TTLB business meetings during the past few months many TV service operators have reported a growing number of set owners who have asked their technicians to fake radio sets back to the shop with them for repairs.

The set owner survey provides factual proof of the vast field of radio service that has been neglected. Twenty of the set owners interviewed said they had radio sets that need repairs and they did not know who to call for service.

The one hundred householders reported ownership of 218 radio sets. This included 48 consoles, 147 table models, and 23 battery portables. Four users said their battery portables needed complete sets of batteries.

These facts revert again to the original premise that if service operators

STANCOR *Exact* REPLACEMENT

FLYBACK TRANSFORMERS

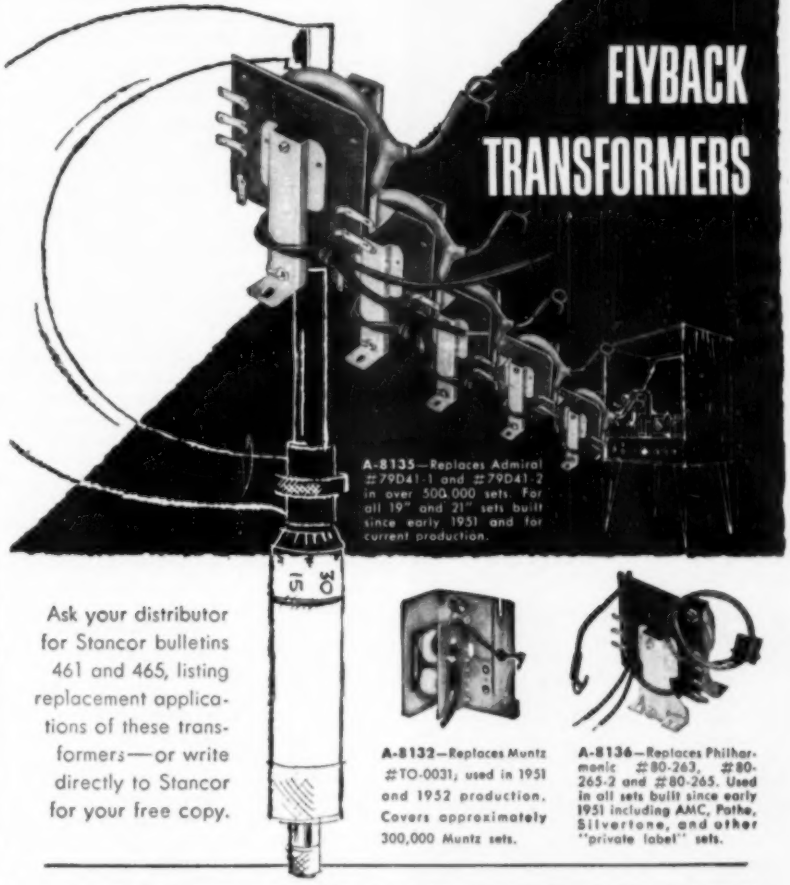

A-8135—Replaces Admiral #79D41-1 and #79D41-2 in over 500,000 sets. For all 19" and 21" sets built since early 1951 and for current production.

Ask your distributor for Stancor bulletins 461 and 465, listing replacement applications of these transformers—or write directly to Stancor for your free copy.

A-8132—Replaces Muntz #TO-0031, used in 1951 and 1952 production. Covers approximately 300,000 Muntz sets.

A-8136—Replaces Philharmonic #80-263, #80-265-2 and #80-265. Used in all sets built since early 1951 including AMC, Pathe, Silvertone, and other "private label" sets.

Stancor Transformers are listed in Howard W. Sams' Photofact Folders, John W. Rider's Tek-Files, and the Howard Company's Counterfacts.

STANDARD TRANSFORMER CORPORATION
3584 ELSTON AVENUE • CHICAGO 18, ILLINOIS
EXPORT SALES—
Roburn Agencies, Inc., 39 Warren St., New York 7, N.Y.

RADIO COURSES
• RADIO OPERATING • CODE
• RADIO SERVICING • ELECTRONICS
• F.M. TELEVISION
• PREPARATION FOR CIVILIAN, MARITIME, ARMY AND NAVY LICENSE REQUIREMENTS.
Write for Catalog T.S.
YMCA TRADE & TECH. SCHOOL
19 W. 63 St., N. Y. 23 LAdison 2-8117

ANOTHER OUTSTANDING JOBBER
VAN SICKLE RADIO SUPPLY CO.
1320 S. Calhoun St.
Ft. Wayne, Indiana
HAS THE SENSATIONAL NEW EICO 470-K 7" SCOPE KIT IN STOCK!

$79.95

REMOTE CONTROL FOR YOUR TELEVISION SET
Fits Any Make or Model
You Make ADDED PROFITS INSTALLING REMOTES FOR OTHERS
• WILL COMPLETELY TURN SET OFF & ON
• CONTROL VOLUME
• ADJUST FINE TUNING
• CHANGE STATIONS
• ADJUST CONTRAST
(All Electronic)

Simple & Complete Instructions
Schematics & Parts List $1.00.
FREE (with above order)
Catalog listing all parts, manufacturers and prices, or we can supply separate, in kit form, or assembled.
Satisfaction Guaranteed—Or Money Refunded

Television Remote Control Co., R-1
820 No. Fairfax Ave., Los Angeles 46, California
Gentlemen: Enclosed find $1.00 (no stamps) Please send postpaid your complete TV Remote Control Schematics & Parts Catalog.
NAME .....
ADDRESS .....
CITY ..... ZONE ..... STATE .....

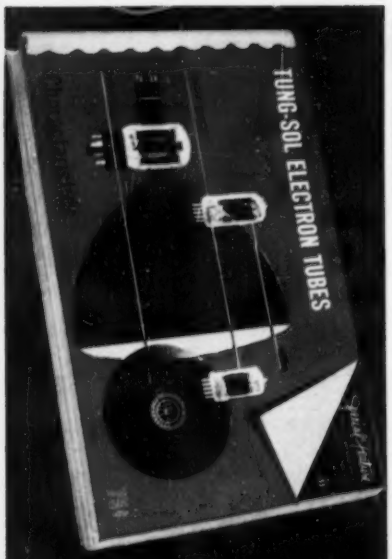

Better'n Ever!

18th Edition Tung-Sol Electron Tube Characteristics Manual

The newest, up-to-the-minute tube data is right here in this 152-page book. It lists 572 Types of Receiving Tubes—122 Cathode Ray Tubes—Dial Lamps—Color Codes and Ballast Tube Numbering Codes. There are news sections on Premium Type Tubes—Germanium and Silicon Crystal Diodes—115 Obsolete Tubes—and a 17-page Service Market and Selling Section. Bring your technical tube data up-to-date now. Get a copy of this new Tung-Sol manual. Servicemen can obtain it from their wholesalers. The name of a Tung-Sol wholesaler will be given upon request.

TUNG-SOL ELECTRIC INC.
Newark 4, N. J.

Sales Offices: Atlanta · Culver City (Los Angeles) Chicago · Dallas · Denver · Detroit · Newark · Seattle

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Germanium Products.

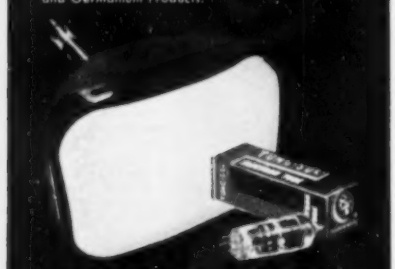

TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

want this business they as individual businessmen must carry out sales promotion programs to get it. Irrespective of how many excellent manufacturer and industry public relations programs are developed, they will lose their effectiveness if individual service businesses do not tie in with sales promotional campaigns of their own. It is the only way an individual shop can capture set owner interest and gain personal identification of its facilities and reliability as a source for electronics home instrument servicing.

New Booklets Available

Two new booklets recently announced provide TV service operators with more excellent public relations "ammunition" to build good-will for their activities and to identify themselves as sources of competent dependable service.

Tung-Sol Electric recently released an unusual 16-page booklet titled "Your Eyes and Television." Completely illustrated with the interest-impelling caricatures that add a special touch to *Tung-Sol's* sales promotional material, the book will be read with deep interest by every set owner who gets a copy.

Promotion-wise service operators will recognize the interest that eye specialists and optometrists will have in this booklet. A service operator who has a supply of these booklets imprinted with his own ad will find eye specialists happy to distribute them to patients which will make his service business known to many new, prospective service customers.

General Electric recently announced a pocket-sized eight-page booklet titled "Facts About Television Service" for service distribution to TV set owners. The text covers in simple, non-technical language the complexity of a television receiver, the implosion and high-voltage dangers involved when unskilled persons tamper with a set, and reasons for calling a skilled technician when repairs are necessary. One page is devoted to hints to the set owner on the care of his set.

The *G-E* booklets are suitable for distribution by service operators to set owners at the shop or on home service calls and they may also be used as direct mail pieces.

The *Tung-Sol* booklets are available from the company's tube distributors and the *General Electric* booklet (ETR-641) can be obtained from that firm's tube distributors.

Rebuilt Picture Tubes

RTMA recently obtained the views of the Bureau of Internal Revenue with respect to the application of radio-TV manufacturer's excise tax on the rebuilding of TV picture tubes. They reported it as follows:

1. *Q.* Under what circumstances is a rebuilt television picture tube "manufactured or produced?"

A. If a used tube is not opened or disassembled but is merely subjected to a reconditioning electrical treat-

INSURANCE against KICKBACKS because of NOISY CONTROLS

In 3 sizes
2 oz., 4 oz., 8 oz.

Your guarantee for quieting noisy television and radio controls, switches and other moving parts is QUIETROLE . . . the original, quality lubricant-cleaner. There is no substitute for "real insurance" to satisfy your customers.

Carried by recognized jobbers . . . everywhere.

manufactured by
QUIETROLE COMPANY
Spartanburg, South Carolina

AMPERITE
Studio Microphones at P.A. Prices

Ideal for
BROADCASTING
RECORDING
PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- Not affected by any climatic conditions.
- Guaranteed to withstand severe "knocking around."

Models
RBLG—200 ohms
RBHG—Hi-imp.
List $42.00

"Kontak" Mikes
Model SKH, list $12.00
Model KKH, list $18.00

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder

AMPERITE Company, Inc.
561 BROADWAY • NEW YORK 12, N. Y.
Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto

ment, there is no manufacturing process and no tax applies to the reconditioning. If used tube is opened, new or reconditioned parts installed in the used or reconditioned shell, and the tube re-exhausted and resealed, the process is a manufacturing operation and the rebuilt tube so produced is a taxable article under Section 3404 (b) of the Code.

2. *Q.* Who is the manufacturer or producer for excise tax purposes?

A. Where the tube remains identified as the property of the rebuilder's customer throughout the operation and the identical tube is returned to the customer after the replacement of defective parts, the rebuilder is only acting on behalf of the owner and and is not the manufacturer for excise tax purposes. In such a case the customer who has the tube rebuilt on his behalf is the producer of the rebuilt tube and liable for tax on his sale or use. An individual owner of a television set who had his kinescope rebuilt for his own use would not be liable for tax in accordance with Reg. 46, Sec. 316.7 which provides:

"However, the tax on the use of such taxable articles will not attach in cases where an individual incidentally manufactures, produces, or imports for his personal use, or causes to be manufactured, produced or imported for his personal use any taxable article."

A dealer who has tubes rebuilt for sale by him will be liable for tax on such sale.

It will be presumed that the rebuilder of the tube is the "manufacturer" unless the rebuilder establishes that by agreement with the customer, ownership remained in the customer and the customer understood that he, not the rebuilder, is the manufacturer of the rebuilt tube and therefore liable for the tax applicable to the sale or use by manufacturers of tubes. —30—

MEASURING CURRENT

By MONROE CORN

SOMETIMES it is necessary to measure the current drawn by an electrical appliance. Usually this involves "cutting in" on the line so that an ammeter may be connected. A simple method which avoids any "cutting in" is shown in the diagram. By using an ordinary a.c. extension line cord and making connection so that the plug is offset, the ammeter can readily be connected to complete the circuit. —30—

How to make current measurements on electrical appliances without cutting line.

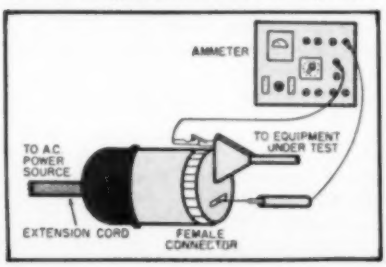

ORDER BY MAIL FROM
WHOLESALE RADIO
Low Prices • Complete Stocks • Fast Shipments

SUPER DIRECTRONIC
4 BAY ULTRA FRINGE TV AERIAL SYSTEM
ELECTRONICALLY ROTATES IN ALL DIRECTIONS

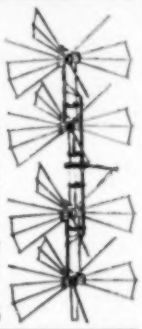

Specially designed to give the finest reception on all channels, in ultra-fringe areas where signals arrive from more than one direction. High gain superior to any broadband aerial. Greater gain on low-band channels. Special center attached reflectors for peak signal. Equal distribution of weight. No motors or electric power, clearest signal is obtained electronically. COMPLETE WITH 6 POSITION DIRECTRONIC BEAM SELECTOR, 150' OF TUBULAR TRI-X CABLE, UNIVERSAL "U" CLAMPS.
Order model AX-548 ..... $44.95

DUAL BAY DIRECTRONIC
FOR FRINGE AREA
Model TX-599 ($18.95)

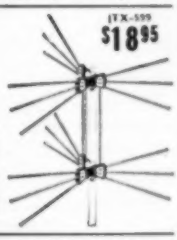

Operates same as Super Directronic above, except has two bays instead of four. Complete with three 31½ ft. masts, 75 ft. flat three cond. cable. Beam selector sw., guy ring and mtg. base.
AX-599 Same as TX-599, less masts, guy ring and mtg. base. $16.95

Three Models Cover All Channels
UHF YAGI TV ANTENNAS
Model 3A—Channels 14-28
Model 3B—Channels 27-62
Model 3C—Channels 49-83
$3.75 ea.

TV TUBE BRIGHTENER
Gives CRT's Longer Life!
No Soldering Needed!
$2.94
No connections to AC line. Extra long 18" leads. Install anywhere in set. Autoformer type with hi-lo sw. Choice of two degrees of brilliancy. Complete with bracket and screws for mounting. Stancor model P-8192.

"Standard Coil's" Latest Model
NEW! SUPER CASCODE TV TUNER
Improved Design
MODEL TV 2232 $24.50

More DX than ever before with the new Super Cascode. Has tube complement of 6J6 osc. & conv., and a 6BQ7 or 6BZ7 as RF amp. Designed for inter-carrier circuit and also adaptable for split sound I.F. circuits, such as "630" and similar types by use of part No. XM 752 trap assembly (available separately). I.F. set at 22.3 mc but is adj. 19-26 mc. Adaptable to UHF. Shaft length 5⅛" overall. Easily cut when shorter shaft is required.
XM-752 Trap Assembly $2.25
UHF STRIPS—Now available for Standard Coil tuners. To order specify channel No. and series designated by letter such as F, G, Q, etc., stamped on each strip of your present tuner. (Set consists of osc. & ant.) $9.40 SET

Don't Waste Time Waiting for Test Pattern
TV Bar Generator
$14.95
Makes Bar Patterns On Any TV Screen, Anytime
Make accurate on-the-spot linearity adjustments. Adj. number of vert. & horiz. bars. Complete unit; no other equipment required. RMS BAR-1.

Easily Installed! Custom Built!
AUTO RADIOS
All Models—6 tubes, 3 Gang Supers
ELECTRO-TOUCH TUNING
FE-153—'52, '53 Ford CE-633—'53 Chev.
CE-352—'51, '52 Chev. DE-532—'53 Dodge
$55.97

MANUAL TUNING
F-100—'49, '50 Ford
D-200—'49, '50 Dodge, Plymouth
F-151—'51 Ford
F-152—'52 Ford
D-251—'51, '52 Dodge
C-351—'51, '52 Chev.
B-451—'48, '49, '50, '51, '52 Hudson
S-531—'50, '51, '52 Studebaker
K-731—'51, '52 Henry J
$39.97
C-300—'49, '50 Chev.
P-651—'51, '52 Plym.
DM-132—'53 Dodge
PM-236—'53 Plymouth
CM-333—'53 Chev.
MM-430—'52, '53 Mercury
FM-731—'53 Ford
$41.97
UNIVERSAL UNDERDASH MOUNT
5 tube super for all cars and trucks. Model W-100 ..... $27.97

EXACT DUPLICATE G.E. & DUMONT TV REPLACEMENT PARTS IN STOCK
For Fast Service, Address Orders to Dept. RN-4
WRITE FOR FREE "F.Y.I." BULLETIN PACKED WITH VALUES
WHOLESALE RADIO PARTS CO., Inc.
311 W. BALTIMORE ST., BALTIMORE 1, MD.

PEN-OSCIL-LITE
Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps • Write for information.
GENERAL TEST EQUIPMENT
38 Argyle Buffalo 22, N. Y.

BARGAIN HUNTING?
RADIO SERVICEMEN!
Write for SENSATIONAL CATALOG
HENSHAW RADIO SUPPLY
3619 TROOST KANSAS CITY, MO.

GET INTO ELECTRONICS

You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin Jan., March, June, Sept. Campus life. Write for catalog.
VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana

SPINTITE

REG. U. S. PAT. OFFICE

120 STYLES and SIZES

THE ORIGINAL WRENCH WITH THE SCREWDRIVER ACTION

for

- ASSEMBLY WORK
- REPAIR WORK
- RADIO
- TELEVISION
- INDUSTRIAL
- AIRCRAFT

WALDEN WORCESTER

STEVENS WALDEN, Inc.
WORCESTER 4, MASS.

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL**	CHANNEL	FREQUENCY (mc.)	POWER (Video)*
Alabama	Decatur	WMSL-TV	23	524-530	21.5
Arizona	Mesa	KTYL-TV	12	204-210	13.5
California	Eureka	KIEM-TV	3	60-66	17.5
"	Monterey	.....	8	180-186	10
"	Salinas	.....	8	180-186	10
Georgia	Macon	WTWV	47	668-674	100
"	Rome	WROM-TV	9	186-192	2.9
"	Valdosta	WGOV-TV	37	608-614	88
Idaho	Pocatello	KWIK-TV	10	192-198	3.2
"	Pocatello	KJRL-TV	6	82-88	7.2
Illinois	Champaign	.....	3	60-66	100
"	Springfield	.....	20	506-512	18.2
Kansas	Pittsburg	KOAM-TV	7	174-180	105
"	Wichita	.....	16	482-488	200
Louisiana	New Orleans	WJMR-TV	61	752-758	200
Maine	Portland	WPMT	53	704-710	22.5
Massachusetts	North Adams	.....	74	830-836	1
Michigan	Lansing	WILS-TV	54	710-716	25.5
Mississippi	Gulfport	WGCM-TV	56	722-728	21.5
Missouri	Clayton (area of St. Louis)	KFUO-TV	30	566-572	175
"	Hannibal	KHMO-TV	7	174-180	10.5
"	St. Louis	WIL-TV	42	638-644	46
"	Sedalia	KDRO-TV	6	82-88	6.3
Montana	Billings	KOOK-TV	2	54-60	17.5
"	Butte	.....	6	82-88	2
New York	Elmira	.....	18	494-500	58.3
North Carolina	Winston-Salem	WTOB-TV	26	542-548	200
North Dakota	Minot	KCJB-TV	13	210-216	29.5
"	Minot	.....	10	192-198	58
Ohio	Ashtabula	WICA-TV	15	476-482	19
Oklahoma	Oklahoma City	.....	25	536-542	17.5
"	Oklahoma City	KLPR-TV	19	500-506	91
Oregon	Eugene	KSPF-TV	20	506-512	19.5
Pennsylvania	Scranton	WARM-TV	16	482-486	245
South Carolina	Columbia	WIS-TV	10	192-198	265
Texas	Dallas	KLIF-TV	29	560-566	50
"	Longview	KTVE	32	578-584	20
"	McAllen	KRIO-TV	20	506-512	86
"	Midland	KMID-TV	2	54-60	50
"	Texarkana	KCMC-TV	6	82-88	18.5
Virginia	Hampton (area Norfolk)	WVEC-TV	15	476-482	220
"	Newport News	WACH	33	584-590	20.5
West Virginia	Parkersburg	.....	15	476-482	19
"	Wheeling	.....	51	692-698	24
Wisconsin	Beloit	WGEZ-TV	57	728-734	21
"	Eau Claire	WEAU-TV	13	210-216	52.2
"	Milwaukee	WCAN-TV	25	536-542	105

*ERP = (effective radiated power). **Call letters without TV suffix from application files and subject to change; except where included in calls such as KKTV or WTVT. .. = Call letters to be announced

Loudspeaker Enclosures

(*Continued from page 47*)

gards the efficiency of the system, whereas the latter system takes into account the relative efficiencies of the two systems. The two schools of thought are not compatible.

In listening to a pair of loudspeaker enclosures, we cannot compare the two systems if one of these systems is working at a much higher level than the other. Ear sensitivity is not linear with loudness. If we were to listen to a speaker system which was running at a considerably higher output level than the other, our hearing characteristic, which follows the familiar Fletcher-Munson curves, would paint a different acoustic picture for this higher level system than for the one operating at a lower output level. We would experience a different balance of frequencies, audibly, from one system to the other. So it is perhaps necessary to consider the performance of the two systems when operating at the same *output* level rather than at the same input power.

In an effort to make this test as objective as possible, it was decided that the proper basis upon which to make this equal output comparison would be at a listening level one would expect to prevail in a normal living room. We wouldn't care to make this test at a level so high nor so low that it would in no way represent the normal listening level. With both systems operating at this equal output power of comfortable level, however, we could then compare the distortion products involved.

In addition to this requirement, for purposes of objective measurements, data should be taken on *one system at a time*, then that system should be removed, and the alternate system reintroduced into the same identical spot. Not only would this procedure give each system the same qualitative room conditions, but it would at the same time remove from the vicinity of the system under test, the mutual acoustic coupling of one system upon the other, especially when placed close to one another. Still again, the *same speaker should be used in both enclosures*, if it is enclosures that we are testing. Manufacturers of loudspeakers do their best to maintain standards of quality, however, commercial tolerances are a necessary prerequisite to successful commercial endeavor, and no matter how close those tolerances may be, there will be slight differences in two finished products albeit they bear the identical model number, and successive serial numbers. Especially must we be careful when measuring systems around resonances. Even though a shipping container may, in bold print, proclaim that the speaker has a resonance of 68 cps, there is the possibility of its resonance turning out to be five or ten cycles higher or lower. This variation may then throw

SEE LEO FIRST FOR . . . .

hallicrafters

I can SAVE you money . . . Liberal Trade-ins

LEO I. MEYERSON W9GFQ

JUST ARRIVED! THE NEW 100 WATT HT-20 XMTR—$449.50

$179.50

S-76 RECEIVER

Extra selectivity with double superheterodyne circuit. One RF, two conversion and 3 IF stages. Range 550-1550 Kc, 1.7-34 Mc in four bands. 8 tubes plus voltage regulator and rectifier. Complete with tubes, less speaker.

$224.50

SX-71 RECEIVER

Double Conversion sharp selectivity, plus built-in NBFM at moderate cost. 11 tubes plus voltage regulator and rectifier. Low down payment.

NAME YOUR TERMS • LOW DOWN PAYMENTS • PERSONALIZED SERVICE

HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT

S-81	$49.50	S-40B	$119.95	ST-83	$129.95
S-82	$49.50	S-53A	$ 89.95	S-78A	$ 89.50
A-84	$99.50	S-72L	$119.95	SX-62	$299.50
S-38C	$49.50	S-77A	$119.95	S-72 Portable	$109.95
R-46 Speaker	$19.95	SX-73	$975.00		

Famous WRL RADIO REFERENCE MAP 25c

CU on 10-20 & 75 Meters

NEW LOG BOOK 25c

For mobile or fixed station. Spiral binding. Full column log listing all FCC required info. Will accommodate 1,525 stations. "Q" signals, phonetic alphabet, amateur international prefixes.

PHONE 7795 — WRITE—WIRE

IT'S NEW! IT'S FREE!

WRL 1953 CATALOG

Send for your copy today. Contains everything new in radio and television. Jam-packed with bargains. Leo I. Meyerson, W9GFQ

Send For FREE Copy

World Radio LABORATORIES — EVERYTHING IN RADIO — INCORPORATED

COUNCIL BLUFFS, IOWA

WORLD RADIO LABORATORIES
744 West Broadway
Council Bluffs, Iowa
R-5

Please send me:

☐ Radio Map 25c ☐ SX-71 Info
☐ New Catalog ☐ S-76 Info
☐ Used Equipment List ☐ New Log Book 25c

Name .....
Address .....
City ..... State .....

MOSLEY 3-WAY TV ANTENNA SWITCH for Multiple UHF and VHF ANTENNA INSTALLATIONS

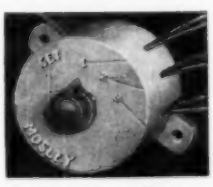

Cat. No. F-20 — MOSLEY 3-Way TV Antenna Switch
List Price $3.75

- Install anywhere. Extension rod supplied for back of set mounting.
- Constant impedance—Low loss—Solderless.
- Sturdy rotary switch making silver-to-silver contact.
- In brown or ivory polystyrene case.
- Also available in Flush Wall Plate style.

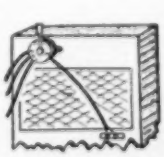

At Radio Parts Jobbers

MOSLEY Electronics 8622 St. Charles Rock Road St. Louis 14, Missouri

COMPLETE TRAINING
FOR BETTER RADIO-TV SERVICE JOBS

Radio-TV RECEIVER CIRCUITRY and OPERATION
Radio-TV TROUBLESHOOTING and REPAIR
ONLY $12 for the complete 2-volume course
3 MONTHS TO PAY

Let these two great new Ghirardi training books teach you to handle **all** types of AM, FM and TV service jobs by approved **professional** methods—**and watch your efficiency and earnings soar!**

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book is brand new. Each contains the latest data on the latest methods and equipment—NOT a re-hash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICING were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi
RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern troubleshooting and servicing.

1—Radio and Television Receiver
TROUBLESHOOTING AND REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price $6.75 separately.

2—Radio and Television Receiver
CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately $6.

New low price . . . . easy terms

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at $50 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably. Completely indexed so you can look up needed facts in a jiffy.

Under this new offer, you save 75c on the price of the two books—and have the privilege of paying in easy installments **while you use them!** No lessons to wait for. You learn fast—and you learn right!

10-DAY EXAMINATION PRIVILEGE

Dept. RN-53, Rinehart Books, Inc.
Technical Division,
232 Madison Ave., New York 16, N. Y.

Send me GHIRARDI'S NEW 2-VOL. SERVICE LIBRARY. I enclose $3 and will send you $3 a month for three months until the total price of only $12.00, plus a few cents postage, is paid. It is understood I may read the books for 10 days. Then, if not satisfactory, I will return them postage paid and you agree to refund my $3 and cancel the remaining installments. (Books shipped postpaid for full remittance with order—same return privilege.)

Name .....

Address .....

City, Zone, State .....

Employer's Name & Address .....

OUTSIDE U.S.A.—$13.00 cash only. Same 10-day return privilege with money refunded.

out of the window "A-B" comparison tests made around resonance systems *assumed* to be the same. Therefore it is essential that the same speaker be used in the various enclosure systems for the results to be truly useful.

Although it is our considered opinion that these measurements should be made on a basis of equal sound power output from the systems, in all fairness to the alternate method of measuring distortion (equal input method) a comparison was made, on this latter basis, of the Helmholtz resonator and the bass reflex enclosure of equivalent size. This comparison is given in Fig. 13, and was made on the basis of one-half watt input to the two systems. It will be observed that measurements below 50 cps were not made. This was not a premeditated condition, but one which befell the tests simply because distortion meters will not operate on incoming signals that have over one hundred per-cent distortion. Such instruments work on the principle of eliminating the fundamental from the input signal and making measurements of all the combined resulting harmonics. Where the harmonics are two to three times the amplitude of the fundamental, this fundamental cannot be tuned out by the meter. Consequently, distortions in the hundreds of percents may not be read by the distortion meter and we are limited to an analysis of the distortion products over an area where the measurement falls below one hundred per-cent. The interesting thing to note is that at the frequencies of 40 to 50 cycles which fall in the region of the lower resonant peak, the distortions for both systems was astronomically high, and not measurable by means of the distortion meter. As we go into the 50 cps region and higher, the distortion products fall below the 100% mark and become measurable.

It is worthy of note that there is very little to choose from as far as these figures are concerned. The "Helmholtz" resonator has a slight edge over the bass reflex system up to 70 cps, and then a reversal takes place, although the difference is quite slight.

Fig. 13. Total harmonic distortion for ½ watt input for 1¼ cu. ft. resonator and 1¼ cu. ft. bass reflex cabinet systems.

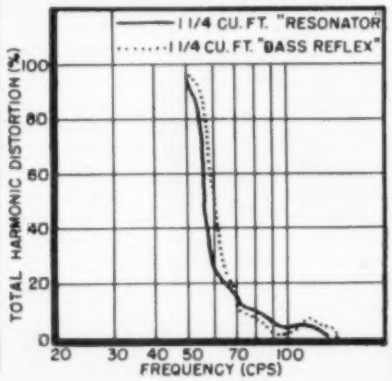

ELECTRONIC'S LATEST TROUBLE-SHOOTER

A compact—complete—circuit analyzer

ONLY $24.95

THE AMAZING TV SERVISET

Model E-C (Pat.) Pending

A precision engineered professional quality electronic test instrument. Ideal for field or bench servicing of Radio, Television, Radar, Communications gear, etc.

Now—Quickly—Conveniently—At Low Cost

CHECKS: sync, sweep, video, audio circuits, TV high voltage supplies (DC, RF, or Pulse), low voltage supplies, coils, condensers, resistors, tubes, transformers, speakers, etc. Will localize trouble to a particular stage, determine defective component and can actually be clamped in circuit to restore circuit operation temporarily in 80% of component or tube defects. Ideal for locating and confirming intermittents.

SPECIFICATIONS:

RF & AF Signal Tracer, RF & AF Signal Injector, AC & DC Voltage Indicator 0-60-550-20,000, DC Polarity Indicator 60-550-20,000 volts; Lo ohms 0-5, Hi ohms 0-500k-20 megohms, Tests Condensers .00025-12 mfd., Tests Resistors 2 ohms—20 megohms, 2 Capacitance Sub ranges .01-1 & 4-40 mfd., 3 Resistance Sub ranges 50-500 ohms, 5k-25k, 100k-1 meg.

Will complement your existing equipment and will outperform other testers costing many times more.

A MUST FOR THE MODERN TV AND ELECTRONICS SERVICE ENGINEER.

Comes in handy cloth pouch, complete with all accessories including **ALNICO** phone, TV high voltage adapter, phone extension cord, test lead, Klipzon adapter and complete detailed Instruction Manual, disclosing latest TV trouble-shooting techniques.

See Serviset at your distributor today. If he can't supply, order direct from factory. $24.95 postpaid.

LEE ELECTRONIC LABS., INC.
Dept. RN-5
233 Dudley Street Boston 19, Mass.

STAY ON THE AIR
WHEN POWER FAILS...with an ONAN Electric Plant

Model 10EL, 10KW A.C.

When storms, floods, or fires interrupt electricity and force you off the air, you lose listeners and income. Guard against loss, assure vital public service during emergencies by installing an Onan Electric Plant. Onan Standby Electric plants serve many network and private stations. Automatic models to 35,000 watts.

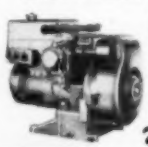

PORTABLE ELECTRIC PLANTS FOR MOBILE RADIO USES

Supply A.C. power for broadcasting at scene of events. Light in weight. Can be carried by hand or in trunk of car. A.C. models: 400 to 3,000 watts.

Write for **FREE** *Folder*

D. W. ONAN & SONS INC.
7896 University Avenue
Minneapolis 14, Minnesota

ENCLOSURE	DISTORTION
Horn (Fig. 3D)	76%
Resonator	32%
Horn (Fig. 3E)	31%
Resonator	32%
Bass Reflex (Fig. 3F)	27%
Resonator	31%

Table 1. Relative total harmonic distortion taken at 70 cps. Output of resonator is made equal to output of individual enclosure with which it was compared.

To return to our preferred method of making distortion measurements, namely, at equal output power, we must refer back to Figs. 10, 11, and 12, which compare the output of the "resonator" with the series of larger cabinets. It will be recalled that these larger enclosures produced considerably more output in the low frequency region than did the "resonator." Accordingly, to make the necessary measurements on an equal output basis, the input to the "resonator" had to be adjusted upwards to the point where its acoustic output was equal to that of the larger enclosure with which it was being compared. To make this adjustment point-by-point with frequency would not be entirely fair to the smaller system, inasmuch as there may be single areas of very high response on the part of the larger system which would be unattainable by the smaller system unless driven into regions of diaphragm excursion nonlinearities. Accordingly, merely to point out the trend, one frequency in the low frequency end was chosen as being close to the midpoint between the two resonant points of the system, specifically 70 cps. This would be the trough area between the two resonant peaks and would represent a point where the diaphragm excursion would be rather limited. The results of this last set of measurements are given in Table 1. From this table it will be noted that in two cases the "resonator" produced more distortion products, and in one case, less.

Distortion will generally increase when a system is driven harder. Several factors contribute to this increase. The diaphragm itself may be driven beyond its limits of linear excursion, the voice coil may travel out of regions of flux linearity, the diaphragm may "break up" acoustically, heating of the voice coil may cause poor load regulation, and the acoustic damping may not be sufficiently great to adequately control the diaphragm velocities. Therefore, it is necessary to conclude in this final analysis that the greater distortion of the "resonator" as compared to the larger enclosures, simply stems from the fact that the speaker has to be pushed harder to give the same output as the larger system. This would be the case for any frequency that might be chosen in this area. Even though a large number of points were chosen, who is to say that more distortion can be tolerated at 60 cps for one system than

Smaller than a desk pen — just as convenient

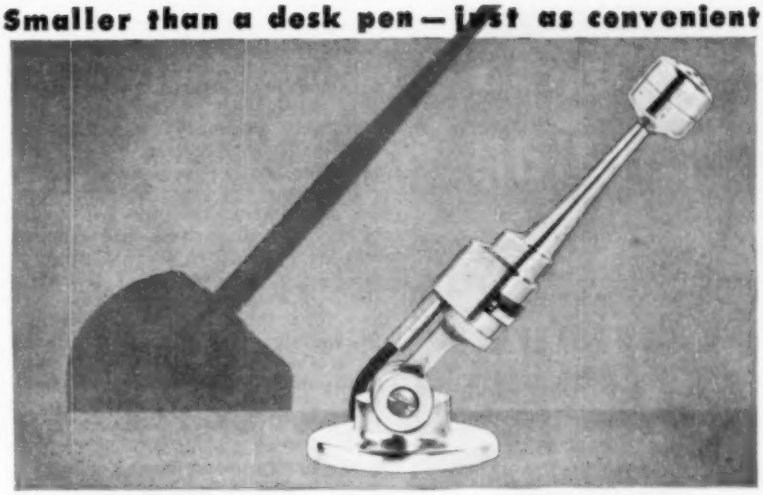

The NEW Turner C-4 Stand for Model 80 Microphone

The new C-4 stand gives complete maneuverability and convenience with the Model 80. It pivots the microphone in a 135° arc for any operational angle — swings parallel to base needing little more packing space than two packs of cigarettes.

The microphone is held firmly by the unique, positive-action hinge, yet moves smoothly and easily to any desired position without adjustment. Microphone quickly and easily removed.

This new, matching stand is solidly built of die-cast zinc overlaid with beautiful satin chrome plate. It is heavy enough to prevent tipping — it will not slide with the weight of the cord. The C-4 stand complements the graceful shape of the Model 80; the combined unit is an attractive but inconspicuous addition to a speakers' table. Ideal for use with wire recorders, public address systems, pulpits, office and factory call systems, amateur operators and other similar uses.

Model C-4 matching stand. ⅝"—27 thread. List Price.....$ 5.75

Model 80 Microphone. List Price.....$15.95

TURNER

THE TURNER COMPANY

900 17th St., N. E. Cedar Rapids, Iowa

In Canada: Canadian Marconi Company, Toronto, Ont., and Branches

Export: Ad Auriema, Inc., 89 Broad Street, New York 4, N. Y.

ATTENTION! LONG ISLAND

SERVICEMEN · HAMS · ENGINEERS · INDUSTRIALS
EXPERIMENTERS · HOBBYISTS · MODEL RAILROADERS
for your convenience

ARROW ELECTRONICS
opens a new, complete store at
215 FRONT STREET
Hempstead, Long Island, N.Y.

Featuring complete stocks of RCA, Dumont, G.E., Sylvania and all other national lines of everything in Radio, TV and Electronic parts, equipment and components.

You are cordially invited to make Arrow, Hempstead your headquarters for all your needs in electronics. Experienced, courteous, personnel—unbeatable prices—unequalled service.

ARROW ELECTRONICS, Inc. 82 Cortlandt St., New York 7, N.Y. 215 Front St., Hempstead, N.Y.

Sarkes Tarzian

"Centre-Kooled"

PATENTS NO. 2618692 & 2670384

SELENIUM RECTIFIERS

Power Type

Available over a range that includes a few volts and milliamperes of current to hundreds of volts and thousands of amperes. Fourteen cell sizes provide widest available range of selection.

Radio Type

Versatile low-cost rectifiers that have found application in all types of electronic equipment as well as radio and television receivers. A complete line is available.

Embedments

A recent "first" in the industry, Sarkes Tarzian embedments offer the advantages of hermetically sealed rectifiers at a fraction of the size, weight and cost.

Diodes

Currently available in two sizes, (1/8" and 5/16" housings) Sarkes Tarzian diodes are designed for use as limiters, bias voltage, low current relay voltage and many other very low current applications.

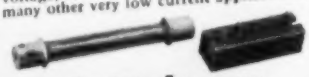

High Voltage

This popular line of tubular rectifiers offers the design engineer a compact—long lived high voltage—low current source of DC power.

Please write, wire or phone for complete information on all types of Sarkes Tarzian Selenium Rectifiers.

Sarkes Tarzian, Inc. RECTIFIER DIVISION

Dept. R-4, 415 N. College Ave., Bloomington, Ind.

at 50 cps for another system, or at 80 cps for still another system as against 65 cps for still a fourth system. One might bounce these distortion figures around without any logical answer other than to say that at one particular frequency, system A distorts more than system B, and *vice versa* for another frequency.

Now what general conclusion may we derive from this total analysis? It is obvious that the small enclosure may be designed in various ways. It may be of the type that utilizes a simple aperture, or a duct. But volume for volume, the speaker will give the same general response whether it be of the Helmholtz resonator type, as popularly known, or the bass reflex type. Next we must recognize that as the speaker enclosure size gets larger, more acoustic output may be expected in the low frequency area, for a given input. Also, in general, volume for volume there is a balance of distortion products between the two systems, but that as the volume increases, proportionately less distortion ensues for a given output. Finally, we may say that for optimum acoustic reproduction it is desirable to utilize as much space as possible, and that it must be utilized judiciously in an acoustically economical fashion. But we must also realize that under certain circumstances where space is not available, and where limitations in acoustic volume must be maintained, that very acceptable results can be obtained from the small enclosures.

—30—

FM IMPROVEMENT

By GEORGE R. ANGLADO

HERE is one way I have found for jacking up the gain of an FM set that has the lead-in coupled to the antenna coil through a condenser. The value of this condenser will range anywhere from 100 μμfd. to 250 μμfd.

Our set is a Western Auto Model D-2929 and upon inspecting this condenser it was found to have a value of 250 μμfd. We got to thinking about the losses developed in condensers in different parts of the circuit and decided to experiment with lower values.

We took out the 250 μμfd. unit and substituted a 100 μμfd. unit in its place, with the dial set on a weak station. This condenser value improved reception considerably and we wondered if lowering this value still further would provide additional improvement. The next step was to substitute a 50 μμfd. unit. The results were astonishing. The signal more than doubled its input. After this we figured that the next step was to hook the lead-in directly to the coil. The results were disappointing. The signal was OK but the noise was up.

A still lower value condenser did the job. The signal improved approximately five times. Noise dropped to a minimum and stability was improved. Although the coil was mounted in a can on top of the chassis, reception could have been further improved if the can was removed and about 5 or 6 turns of #18 or #20 wire wound over the coil. Readers can try this scheme on any FM set that has an antenna coupling condenser of more than 10 μfd. —30—

COMPARISON PROVES EICO OFFERS GREATEST V-O-M values!

GET the MOST for your money — *Before you buy*, see chart below!

World-renowned EICO VOLT-OHM-MILLIAMMETERS

*#536 KIT $12.90. Wired $14.90

#526 KIT (with 1% multipliers) only $13.90. Wired $16.90

VERIFY AT YOUR DEALER'S	EICO	Co. A	Co. B	Co. C	Co. D
	$12.90 up (KIT)	All Over $24.00			EICO price range
31 ranges?	YES	No	No	No	No
Full-size 3-inch meter?	YES	Yes	Yes	Yes	No
400 ua sensitivity?	YES	Yes	Yes	Yes	No
Zero to 1 v. range on both AC and DC?	YES	No	No	No	No
5000 v. range on both AC and DC?	YES	Yes	No	Yes	No
AC/DC sens: 1000 Ω /v.?	YES	Yes	Yes	Yes	No
DC and AC Current Ranges?	YES	No	No	No	No
In KIT and Wired Form?	YES	Wired Only	Wired Only	Wired Only	Wired Only
Lowest cost in the Industry?	YES *See Above	No	No	No	No:
		All over $24.00			EICO price range

Write for FREE Catalog MR-3 & name of local dealer

Prices 5% higher on West Coast

ELECTRONIC INSTRUMENT CO., Inc.

84 WITHERS STREET, BROOKLYN 11, N. Y.

Examine FREE

PULSE TECHNIQUES

by S. Moskowitz and J. Racker

Get this new self-training book for 10 days' free examination

Here is everything you need to know about pulse techniques—a subject of increasing importance in television, communications, and all electronic equipment. This book covers transient response of linear networks, design of pulse networks, pulse shaping and clamp circuits, pulse generation, measurement, and instruments, pulse communication systems, and aerial navigations aids.

PARTIAL CONTENTS: Fourier-transform method. Response of an ideal low-pass filter to a step voltage. Physical significance of response curves. Response to a pulse series. Determination of network response by Fourier transforms. Use of partial fractions in the solution of transform problems Laplacian transform and inverse Laplacian of a step voltage. Typical network problems using L transforms. High-pass RC filter. Pulse transformers. Step-voltage build-up time response of a step-down transformer. Delay-time response. Special coaxial delay lines. Design of lumped lines. Supersonic delay lines. Shunt-peaking amplifier. Four-terminal coupling networks. Transmission-line amplifiers. Cathode follower. Limited circuits. Clipping circuits. Peak-riding clipper. Integrating circuits. Positive-bias restorer. Electro-coupled pulse oscillators. Relaxation oscillators. Multi-vibrators. Sweep circuits. Time calibration. Pulse-counting systems. Commutation. Modulation. Synchronization. Commercial pulse communication system. Introduction to radar systems. Timing unit. Radar receiver. Navar set. Loran system. Get this authoritative handbook today! Coupon below brings you "Pulse Techniques" on FREE trial for 10 days. Mail it NOW!

MAIL COUPON TODAY

Prentice-Hall, Inc., Dept. M-RTN-553B
70 Fifth Avenue, New York 11, N. Y.

Please send me a copy of PULSE TECHNIQUES for FREE examination. Within 10 days I will either return the book and owe nothing, or keep it and remit $2.65 down (plus postage) and $2 monthly for 2 months.

Name .....

Address .....

City ..... Zone... State....

1953 Du Mont "Telesets"

(*Continued from page 70*)

action shown in Fig. 7 takes place at this grid. Note that the polarity of the noise pulses from the plate of V_{220B} is opposite to the polarity of the noise in the composite video signal. Because of this the noise pulses cancel and the resultant signal appears as shown at C in Fig. 7. In this way a large portion of the noise in the composite video signal is eliminated before application to the sync clipper.

Tube V_{220A} is biased well beyond cut-off, so that it conducts only on the horizontal sync pulse, and the video and blanking information does not appear in its output. In addition to eliminating the video and blanking information, V_{220A} removes most of the vertical sync signal.

The component values used in the cathode-bias network of V_{220A} are chosen so that the comparatively long duration, vertical sync pulses (27 microseconds) build up a charge across the cathode bypass condenser, C_{215}. This charge increases the bias on V_{220A} during the vertical sync interval and the vertical sync does not appear in the output of V_{220A}.

The comparatively short horizontal sync pulses (5 microseconds) do not increase the bias on the tube and thus appear in the output of the stage. V_{220A} operates as a cathode follower with output taken off across R_{220}.

The advantage of this type of sync clipper lies in the fact that short duration pulses do not increase the bias on the tube. In the usual grid-leak-biased clipper circuit the grid bias is determined by the peak amplitude of the input signal. As a result, high amplitude noise pulses increase the grid bias and compress or completely eliminate the sync signal.

The price paid for this advantage is the elimination of the vertical sync, therefore, a second sync clipper must be used to separate the vertical sync signal. This function is performed by V_{220B}. The composite signal at the grid of V_{220A} is applied to the grid of V_{220B} through R_{215}. V_{220B} is negatively biased beyond cut-off so that it does not pass the video signal. The grid circuit time constant (R_{215} and C_{220}) is

Fig. 7. Noise pulses from the video amplifier (A) and inverted noise pulses from the inverter (B) cancel each other to produce reduced noise amplitude shown in (C).

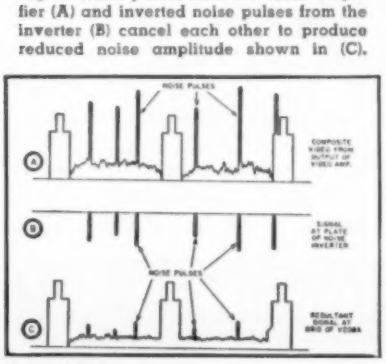

BROADCAST BAND & AERO

Ideal for Use in Boats, etc.

MN-26-C Remote Controlled Navigational Direction finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC. 24 V. Self contained dynamotor supply. Complete installation, including receiver, control box, loop, azimuth control, Left-Right Indicator, plugs, loop transmission line and flex. shafts.
BRAND NEW $89.50
LIKE NEW $69.50

MN-26-Y 150 to 325 KC, 325 to 695 KC, 3-4 to 7 megacycles, comp. installation $69.50
Receiver alone 35.95
MN-26-C alone, like new 39.50
MN-26-C or MN-26-Y as is less tubes 13.95
With tubes, Used good 24.95
MN-20-E Loop, Brand New 6.95
MN-52 Crank drive, New 2.90

MONTHLY SPECIAL!

TS10 TEST UNIT

Complete with attenuator, indicators and 350 feet of coaxial cable. Original cost $300.00. New Condition, ONLY **$14.95**

SCR-274N COMMAND and ARC-5 EQUIPMENT

	AS IS	EXC. USED (With tubes)	NEW
BC-450 Control Box (3 Receiver)	....	$1.95	$3.95
BC-456 Modulator	$2.95	4.95	....
BC-451 Control Box (Transmitter)	....	1.95	3.95
BC-442 Relay Unit ANT With Condenser	....	3.95	....
Without Condenser	....	1.29	2.95
Flexible Shafting with Gear to fit receivers	....	....	2.45
5 Receiver Rack	....	2.29	2.98
2 Transmitter Rack	....	2.39	3.97
Single Transmitter Rack	....	2.25	2.95
DM-32 Dynamotor for Command Set	....	3.25	9.95
DM-33 Dynamotor for Command Set	....	2.95	3.95
Shock Mts. for 3 Receiver Rack, 2 Trans. Rack, Modulator or Ant. Relay Unit	....	1.95	2.45

BC457 TRANSMITTER—4 to 5.3 mc and
BC458 TRANSMITTER—5.3 to 7 mc and
BC455 RECEIVER—6 to 9 mc (as is, less tubes and crystals) ..... ONLY **$4.95** each
Both units for **$8.95**

HAND SETS

TS9, excellent condition $4.95
TS13, excellent condition 5.95
TS Type, exc., less cord 2.95

WANTED!

All TS, APR, APS, ARC, ARN, ART, SCR, R89 and BC equipment . . . write today! Quote lowest prices in your first letter

RT 34 APS 13 Transceiver used as a tail warning radar on 415 MC. Contains(1) a 30MC IF strip and various other parts, these units have been stripped of RF sections and all tubes, but are an excellent buy if only for parts and IF Strip ..... used $ 4.95
BC 624 receiver (SCR 522), less tubes. 100-156MC ..... used 14.95

TRANSCEIVER—140-144 mc, 2 meter, used, excellent condition, less dynamotor, less tubes ..... only $17.95

SPECIAL BUYS!

BC-1206 Beacon Receiver . . . 200-400KC . $ 9.95
MN-26LB Receiver exc. 89.50
RCA Sound Powered Phones . . . brand new, 12.95
two for 24.95
RA-ARN7 Receiver (used, exc.) 149.50
TRS-AP . . . S-Band Power Frequency Meter 195.00
TS-184/AP Test Set 89.50
APR-3 Radar Search Receiver, 85-1000MC . . . 195.00
APR-4 Radar Search Receiver, 38-4000MC . . . 450.00
TS100 Oscilloscope 175.00
IE 19A-SCR522 Test Unit 295.00
MG-Inverter ..... Used 69.50

MIKES and HEADSETS

HS-33 Low Impedance Headset, ... exc. $2.95 new $8.95
HS-23 Headset ..... used $2.95 new $4.95
CD-307 Ext. cord for HS 23-33 ..... like new .79
Throat Mike—T 30 ..... New .98
Lip Mike—Navy Type ..... New .98
Extension Cord and Switch Assembly for lip and throat Mikes ..... New .98
CW 49505 High Impedance headset complete with leather headband and rubber cushions. Used **98¢**

HS-18 Headset ..... used $1.29 new $1.98
HS-38 ..... exc. 1.95 new 2.29
HS-30, miniature headset . . . used 1.49 new 2.49

DYNAMOTORS

The best dynamotor for conversion to 6v. Multiple windings! After conversion you get choice of 190 or 350 v. at 50 MA or 250 v. at 100 MA. Complete dope sheet furnished.
BRAND NEW (See "CQ" Aug. Issue) **$4.65**

WOBULATOR
BUILD TV-FM-AM SWEEP GENERATOR

You can build "Versatile Sweep Frequency Generator" with APN-1 magnetic units **$5.95**

RT7/APN1 TRANSCEIVER UNIT—Used as an altimeter, it may be converted for signaling control circuits, etc. Complete with 14 tubes and dynamotor they are in good used condition at the amazingly low price of **$29.95**
Used, less tubes, as is **4.95**

MISCELLANEOUS EQUIPMENT

FL 8 used, exc. . . . $1.19 BC 347 each . . . used **95¢**
BC 906 each 9.95

YE-4B

General Electric Delay Line Unit 1000 ohms + or − 10% fatal pass 0 − 2 mc, 4 micro-second delay time. Brand new **$1.98**

SELSYN TRANSMITTER

Autosyn Transmitter Assembly for matching to 1-82 Indicator. Used, excellent condition.
ONLY $5.95. Complete with Indicator . . . **$14.95**

RL-42 Reversible Motor with antenna reel and clutch, used ..... $ 2.95
BC-433 RADIO COMPASS RECEIVER, 200 to 1700 KC, used, excellent condition, with tubes 39.95
used, exc., less tubes 24.95
used, as is, less tubes and cover, exc. for parts 8.95

Shipments F.O.B. warehouse. 20% Deposit on orders. Minimum order $5.00. Illinois residents, add regular sales tax to remittance.
Prices subject to change without notice.

R W ELECTRONICS Dept. N, 1712-14 S. Michigan Ave., Chicago 16, Ill.
PHONE: HArrison 7-9374

THE NEW WONDER OF ELECTRONIC CONTROL CAN BE YOURS FOR PRACTICALLY NOTHING

You get the complete outfit, including cabinet, 3 tubes (12SL7GT, GL5662, GL5610) and wiring diagram.

Single each $5.99
Lots of 3 each **4.98**

Can easily and quickly be modified for Electronic Remote Control of: Transmitters; Turn Radio and TV on and off; Open and Close Garage Doors from your car; etc. Schematic diagram included at No Extra Cost.

RED HOT ELECTRIFYING BARGAIN!
THYRATRON REMOTE CONTROL

SERVICEMEN • HOBBYISTS • HAMS • EXPERIMENTERS • RADIO SCHOOLS

Here's the chance of a lifetime to own a genuine Thyratron Electronic Remote Control of your own at a fraction of its regular price! This mighty handful (only 5¼x5x3¼) of miracle control can be made to perform hundreds of practical, fascinating feats of remote control. A complete schematic showing the circuit is included with each unit.

IT'S A STEAL! Buy it just for the parts alone. Take it apart! Look what you get: Valuable parts and tubes galore that you can so easily use in any other radio, Amplifier, etc.—or for experimenting.

LOOK AT ALL THE PARTS YOU GET

- Filament Trans.
- Control Relay
- 125L7GT
- GL-5610
- GL-5662
- 16 Mfd @ 150 volts
- 1 Mfd @ 200 volts
- .02 Mfd @ 200 volts
- .25 Mfd @ 600 volts
- .25 Mfd @ 600 volts
- 125 Ohm Variable Cont.
- 600 Ohm Calibration Cont.
- 1 Megohm—½ Watt
- 3K-ohm—1 Watt Wirewound
- 525-ohm—1 Watt Wirewound
- 8K-ohm—10 Watt Wirewound
- 2600 ohm—1 Watt Wirewound
- 75K-ohm—½ Watt
- 1 Megohm—½ Watt Carbon
- 150K-ohm—½ Watt
- 1 Megohm—½ Watt Carbon
- 47K-ohm—½ Watt Carbon
- 2 Megohm—½ Watt Carbon
- 1 Megohm—½ Watt Carbon
- 1 Megohm—½ Watt Carbon
- 24 ohm—2 Watt Wirewound
- Switch—SPST
- Pilot Lamp, Type 44
- Neon Bulb—NE-2
- Control Housing
- Bottom Plate
- Escutcheon

HOW CAN YOU LOSE? These parts are certainly worth THREE TIMES this amazing low cost. The General Electric Thyratron Type GL-5662 tube alone costs $3.30 wholesale. Besides consider the plate sensitive relay, filament transformer, tubes, condensers, resistors (many of them 1% precision). No matter how you use it, here's a great, great red-hot bargain. Operates on 115V AC.

MANUEL KLEIN CO. • 94 Chambers St. • New York 7, N. Y. • REctor 2-6460

get Milton S. Kiver's IMPORTANT NEW BOOK ON

"UHF antennas, converters and tuners"

A "Must" for Every TV Service Technician

136 pages 5½ x 8½"

Fact-Packed To Give You All The Answers on These Vital UHF Subjects:

UHF Antennas: Full coverage of UHF TV antennas, including Fan Dipole, double-"V", rhombic, parabolic reflector, yagi, corner reflector, horn and helical types. Analysis of each array — design, operation, directional characteristics, input impedance, gain. Tells you type best suited for any given conditions.

Transmission Lines, Matching Networks: Tells how to select proper transmission line to deliver maximum signal to the receiver for best quality picture — a full discussion of this important subject.

UHF Installation Practices: Practical advice on proper antenna location and routing of transmission line to set. Describes accurate method of checking for antenna mismatch and determining whether system is properly installed.

UHF Converters: Detailed analysis of existing converters, ranging from UHF turret tuner strips to all-channel self-contained converters. Helps you understand converter design and operation.

UHF Tuners: Full analysis of tuner design and operation, ranging from parallel-wire to "butterfly" types. Absolutely essential data for the TV Service Technician.

This book keeps you ahead in TV, makes you a UHF expert, brings you extra business and profits. Get your copy today.

ORDER UHF-1. *Only* $1.50

HOWARD W. SAMS & CO., INC.

ORDER TODAY

Order from your Parts Jobber, or write direct to Howard W. Sams & Co., Inc. 2203 E. 46th St., Indianapolis 5, Ind.

Send.....copy (ies) of "UHF Antennas, Converters & Tuners", $1.50 per copy.

Name.....

Address.....

City.....State.....

27 microseconds. As a result, the short duration horizontal sync pulses (5 microseconds) and equalizing pulses (2.5 microseconds) do not produce sufficient amplitude at the grid to drive the tube out of cut-off. Thus only vertical sync information appears across cathode resistor, R_{205}.

Since R_{205} is common to V_{205A} and V_{205B}, both the vertical and horizontal sync signals appear across it.

The composite sync signal appearing across R_{205} is applied to the cathode of the third sync clipper, V_{205A}. The signal at this point is positive and, since it is applied to the cathode of the stage, it drives the tube into cut-off, clipping the upper portion of the sync pulses. This clipping removes all noise superimposed on the sync signals.

The output of V_{205A} is applied to the grid of a phase splitter circuit, V_{205B}. V_{205B} provides the out-of-phase horizontal sync signals required for operation of the horizontal phase detector, V_{206} (Fig. 2). The phase detector produces a correction voltage when the horizontal oscillator frequency does not correspond to the incoming horizontal sync signal.

The horizontal oscillator, V_{210}, is a conventional cathode-coupled multivibrator. The vertical sweep signal is also generated by a multivibrator circuit. This circuit performs the combined functions of vertical oscillator and vertical deflection amplifier.

Servicing Hints

Oscillator Tube Replacement: Due to normal variations in interelectrode capacitances among tubes of the same type, replacement of an oscillator tube may result in excessive frequency shift. Readjustment of the oscillator frequency can usually be avoided by trying several tubes and selecting the one which causes the least frequency shift.

Horizontal Pull: When servicing the chassis on the bench keep the CRT leads well clear of the high-voltage compartment. If the leads are run close to the compartment the video signal may enter the horizontal sweep circuits causing a misleading horizontal pull in the picture.

Loss of Picture and Sound: The "B+" voltage for several of the circuits in this receiver is obtained from the cathode of the audio output tube, V_{215}. As a result, failure of the output tube, or the audio-transformer primary, will cause loss of the picture as well as the sound. The same symptoms will result if the speaker plug is disconnected. When these symptoms occur check these components and when servicing the set be sure to connect the loudspeaker.

I.F. Alignment

The i.f. stages of a TV receiver rarely drift out of alignment. Consequently, realignment should not be attempted until all other possibilities have been checked. The following are a few points which are helpful in de-

the Engineered Product

extends useful life of older TV tubes!

manufactured by

Perma-Power COMPANY

Chicago 25, Illinois

Manufacturers of Electronic Equipment Since 1928

MERIT PLATE TRANSFORMERS

1100 VCT/150MA	$ 6.47
1320,1100VCT/250MA,40V Bias Tap	8.08
2160VCT/125MA;1000VCT/150MA	9.99
1800,1600VCT/225MA	9.70
2900,2350VCT/300MA	24.11
4200,3600 VCT/300MA	30.58
5800,4770VCT/300MA (Sq. Cse)	47.04

MERIT FILAMENT TRANSFORMERS

2.5VCT/10AMP/10KV INS	$ 3.67
5VCT/3AMP/2500V INS	2.50
5VCT/30AMP/2500V INS	6.47
6.3VCT/1AMP/2500V INS	1.65
6.3V/1.2AMP/5KV INS (TV REPL)	2.12
6.3VCT/3AMP;6.3VCT/3AMP/2500V INS	4.04
5VCT/3AMP;6.3VCT/3AMP/2500V INS	4.06
10VCT/10AMP/3KV INS	5.88
12.6VCT/2AMP/2500V INS	2.64
25.2VCT/1AMP/2500V INS	2.64
12.6V/7AMP or 25.2V/3.5AMP/2500V INS	5.88

MERIT FILTER CHOKES

15HY/85MA/1500V INS	$ 2.94
10HY/110MA/1500V INS	2.94
12HY/150MA/1500V INS	3.53
15HY/150MA/2KV INS	5.14
5HY/200MA/1500V INS	4.11
10HY/150MA, 10HY/200MA, 10HY/250MA, 8HY/300MA — 3KV INS	3.82, 4.70, 6.47, 6.76

MERIT UNIVERSAL MODULATION

PRI-2000-20000/50MA Per Side; SEC-2000-20000/50:100MA* 15 WATTS	$ 6.32
PRI-2000-20000/150MA Per Side; SEC-2000-20000/150:300MA* 60 WATTS	9.41
PRI-2000-20000/220MA Per Side; SEC-2000-20000/220:440* 125 WATTS	13.23

*SERIES—PARALLEL

STEEL BOXES—BLACK CRACKLE FINISH

4 x 4 x 2	$ .70	15 x 9 x 7	$2.38
4 x 5 x 3	.80	12 x 7¼ x 6½	2.40
6 x 6 x 4	1.10	15 x 7¼ x 6½	2.48
12 x 7 x 6	2.08		

SLOPING FRONT CABINETS

8 x 8 x 8	$3.53	8 x 14 x 8	$4.23
8 x 10 x 8	3.93	12 x 18 x 12	7.70
8 x 12 x 8	4.08		

All prices F.O.B. our warehouse New York

LEEDS RADIO CO.

75 Vesey St. Dept. A New York City 7

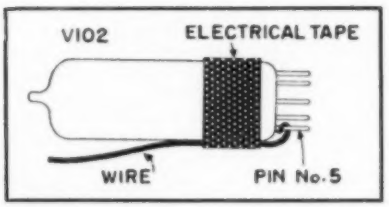

Fig. 8. A convenient method for applying alignment signal to mixer-oscillator.

termining whether or not a receiver requires realignment:

1. If the picture is weak (with or without snow), but the picture quality is satisfactory (good resolution, little smear, etc.), realignment is probably not required.

2. If the picture quality is unsatisfactory, and adjustment of the fine tuning has little effect, check the video amplifier stage before realigning.

3. If the picture quality is unsatisfactory, and adjustment of the fine tuning control has a marked effect on the picture quality, realignment is probably required.

Test Equipment Required: The following test equipment is required to align the i.f. stages of RA-166/167 and 170/171 chassis:

Sweep Generator: Frequency range—4 to 50 mc.
Deviation—10 mc. minimum.

Marker Generator: Frequency range—4 to 50 mc., with provisions for amplitude modulation of the signal, and crystal calibration.

Vacuum Tube Voltmeter

Crystal Detector Probe

Cathode-Ray Oscilloscope: The oscilloscope used should have good low-frequency response and a vertical deflection sensitivity of at least 0.1 r.m.s. volt-per-inch.

Procedure: The i.f. alignment procedure is shown in Table 2. Before beginning alignment place the station selector between channels to disable the oscillator, and remove fuse F_{201}, to disable the sweep circuits. A convenient method of connecting the signal generator to the mixer-oscillator tube, V_{102}, is shown in Fig. 8. Twist one end of a short length of wire around pin 5 of the tube and attach the wire to the tube envelope with electrical tape.

After completing the alignment procedure tune the receiver to the best signal available and examine the picture for traces of smear or trailing whites. If either condition is present adjust the top slug of Z_{201} to eliminate it. Do not adjust the slug more than one-half turn. —30—

RTG ELECTION

THE Radio Technicians Guild of Rochester, New York, has re-elected Harold Eskin to the presidency for a third term.

Serving with Mr. Eskin will be Don Lisow, vice-president; Francis Stoffel, secretary; and Alfred Best, treasurer.

The group has headquarters at 703 Temple Bldg. in Rochester.

—30—

The High Fidelity Record Changer for High Fidelity Record Reproduction

Collaro

7, 10, AND 12 INCH RECORDS Fully Automatic

3-SPEED RECORD CHANGERS

MODEL 3/522* Intermixes 10 and 12-inch records LIST PRICE $65.00 (less base)

MODEL 3/521* Non-Intermix Model LIST PRICE $54.50 (less base)

*Available in cream, brown or gray finish.

RECORD CHANGER BASE Wood, Mahogany Finish, heavy construction. LIST PRICE $9.50

On Sale at Leading Dealers. Write for Complete Literature.

ROCKBAR CORPORATION • 211 East 37th Street, New York 16, N. Y.

"Well, Mr. Thomas A. Edison . . . put the parts back. All it needs is a JENSEN NEEDLE."

WALDOM

TV Conversion Kit

Mask and Escutcheon Assemblies

For a professional conversion or custom installation

1 Metal Mask tailored for perfect fit. Green Sprayed Finish.

2 ¼" Tempered Safety Glass.

3 Beautiful Gold Finished Metal Escutcheon.

All popular sizes: 14", 16", 17", 20" and 21". Rectangular Tubes only. Easy to install instructions included.

See your distributor

Send for COMPLETE CATALOG

Waldom carries a complete line of Electronic Components and Croname Products.

WALDOM ELECTRONICS, INC.

911 N. Larrabee St. Chicago 10, Illinois

WORLD'S LARGEST MANUFACTURER OF CUSTOM BUILT TELEVISION

MATTISON

SILVER ROCKET 630 CHASSIS
• with TUNEABLE •
BUILT-IN BOOSTER
for Better DX Reception

Featuring NEW CASCODE TUNER made for UHF interchangeable tuning strips and 70° COSINE YOKE

Tube Complement:
28 tubes
3 rectifiers
1 CRT
32

All Channel Booster

• Broad band single knob control pre-amplifier built in to eliminate long leads which may cause regeneration and attenuation of signal.

• ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES. THE SILVER ROCKET WILL OUT-PERFORM ANY CHASSIS MADE AND IS PRICED RIGHT TO SELL FAST WITH AN EXTRAORDINARY MARGIN OF PROFIT FOR YOU. WRITE FOR CONFIDENTIAL PRICE SCHEDULE.

ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY!

ANNOUNCING the New AMBASSADOR for 1953

The only open face console made in every expensive decorator finish . . . on guaranteed genuine mahogany, walnut, oak and other rare woods!

The AMBASSADOR 17" and 21"
Best Looking . . . Best Value, Too!
Full size console for eye level television. Available in every expensive decorator finish. Featuring removable safety glass. Dimensions height 42 inches, width 26 inches, depth 23 inches.

DEALERS! SERVICE DEALERS! Here is your opportunity to become the "important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS. FREE!! Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and "$1,000,000 FLOOR PLAN."

When you buy from Mattison you need only one source of supply! You can buy a Mattison Chassis, a Mattison Cabinet or a complete Mattison TV Set!

Manufactured with integrity

Mattison Television & Radio Corp.
10 West 181st St., Dept.RN, N.Y.53, N.Y.

Technical BOOKS

"THE RADIO AMATEUR'S HANDBOOK" by the Headquarters Staff of ARRL. Published by *American Radio Relay League*, West Hartford, Conn. 900 pages including catalogue section and index. Price $3.00 in U.S. Thirtieth Edition (1953).

This latest edition of the "Handbook" has been revised to meet today's demand for an authoritative and up-to-date text.

The book is divided into 27 chapters, the first four of which comprise a background or introduction to the more technical chapters to follow. They include a history of amateur radio, electrical laws and circuits, vacuum tube principles, and data on high frequency communication.

The balance of the handbook deals with high frequency receivers and transmitters, power supplies, v.h.f. and u.h.f. apparatus and communications techniques, measurements, vacuum tube data, amateur station construction, etc.

The catalogue section includes the products of 89 companies and comprises 180 pages of data on commercial products. The book, as is customary, is lavishly illustrated and the text material is supplemented by some 95 charts and tables, 466 tube base diagrams, and 85 basic formulas.

It is scarcely necessary for a reviewer to evaluate this book since it is so widely known not only among the ham fraternity but others in the electronic field that to say that there is a new "Handbook" out is sufficient to send its "fans" storewards.

* * *

"VACUUM TUBE OSCILLATORS" by William A. Edson. Published by *John Wiley & Sons, Inc.*, New York. 464 pages. Price $7.50.

Since vacuum tube oscillators are to be encountered in practically every radio, television, or radar transmitter an understanding of their functions is of vital importance to the engineer.

It is this reviewer's belief that this is the first book dealing exclusively with this subject and as such merits the attention of the engineering profession.

The author has divided his subject matter into 18 chapters covering transient behaviour of linear systems, negative resistance oscillators, nonlinear oscillations, feedback systems and stability criteria, resonators, linear oscillators, conventional harmonic oscillators, crystal-controlled oscillators, intermittent behaviour, operation at high power levels, practical relaxation oscillators, locking and synchronization, frequency multiplication and division, tube and thermal noise, modulation of oscillators, a.f.c., and longline and multiple resonance effects.

The subject matter is presented at an engineering level and mathematical analyses are freely used. Prerequisite to an understanding of this work would be an engineering degree or work at a senior level in an engineering school. A fairly comprehensive bibliography has been appended for the benefit of those who wish to make further investigations on the subject.

* * *

"LINEAR SCALE NON-LOGARITHMIC SLIDE RULES" by Morris L. Groder. Published by *G & G Corporation*, 2003 E. 12th St., Brooklyn 29, N. Y. 64 pages. Price $2.98. Paper bound.

This little, pocket-size book tells how to construct a linear slide rule by using a straightedge, a pencil, a sheet of cross-section paper, and a compass.

According to the author, those who follow the instructions will be able to add, subtract, multiply, and divide on the same scales. Reciprocals, folded scales, and logarithms can be obtained by this technique too.

Complete instructions are included in the book and the author's easy-to-follow step-by-step instructions should cause no difficulty.

* * *

"MOST-OFTEN-NEEDED 1953 TELEVISION SERVICING INFORMATION" compiled by M. N. Beitman. Published by *Supreme Publications*, Chicago. 192 pages. Price $3.00. Paper bound.

This seventh volume in the *Supreme* TV series covers data on 1953 television models from 29 different manufacturers.

As with previous volumes, information on each receiver includes a circuit diagram, aligning data, response curves, special hints for adjusting various sections of the set, and other pertinent material for the rapid and accurate servicing of television receivers. —30—

SERVICING CRT's

By RICHARD BLITZER
Tele-Video Associates

WHEN the raster is gone or goes out intermittently, a common trouble is an open CRT heater. Very often we've found that the break apparently was in the soldered connections inside the pins. When your ohmmeter, or a lack of heater light, indicates an open heater, "sweat" the heater pins No. 1 and No. 12 with your iron, and apply additional solder. Try to get the solder to flow into the hollow pins. We have "saved" many a picture tube in this simple manner, and have had the customer swear by us instead of at us.

Another symptom of a bad CRT is the picture turning silvery when the brightness or contrast controls are turned up. This is usually necessary because the picture seems weak. We've tried the following trick with excellent results: Disconnect the CRT socket from the tube. Connect a wire from the cathode, pin No. 11, to the chassis. *Momentarily* touch a well insulated wire from the high voltage to the CRT grid, pin No. 2. A bright flash will be observed inside the neck of the tube. Shut off the power and reconnect the CRT as usual. You and the set owner will be pleasantly surprised to see the picture restored to its normal appearance. A momentary flash or two will not harm the CRT. —30—

SPRING SALE
PRICES SLASHED

T.V. TUBES—ROCK BOTTOM PRICES
In lots of 6 each No. only

6BG6 .....89c 6CB6 .....39c 6AQ5 .....38c
19BG6 .....89c 6AK5 .....69c 6CD6 ....$1.05
12AX7 .....47c 6BQ6 .....87c 6B4 .....49c

Tube Special—Broken Keys—Electrically Perfect
12SK7 .....6 for $2.00 12A6 ...20c; 4 for $1.00
6L6 ....69c; 4 for 2.25 12K8 ...49c; 7 for 3.00

Tube Sale—2A7-55-27-85-31-56-57, No Mixed Ass't, 6 of Any Type $2.25

Heavy Duty Shielded P.P. Input Trans.....$1.00
Signal Corps Transmitting Keys.....$3.00

Bat Handle S.P.S.T. or D.P.S.T. Toggle Switch. 25c

2 Gang Var. Cond. 456 K.C. with Osc. Section. 2¾ in. Pulley on ¼" Shaft..... 49c

2 Gang 5.W. Var. Cond. 50 MMFD per Sec. Double Spaced, 10-30 Meters with Tank Coil ¼ in. Shaft..... 39c

Westinghouse Ruprox Rectifier 0.64 Amp. 28 Volts. Reg. $11.00 ea. Special.....$1.98

BRAND NEW 10" PHONO RECORDS—Ass't. Jazz—Popular, Rhythm—Blues. Please specify. 12 for $1.79 or 24 for $3.00

Single Pole—10 Pos. 2 Gang Switch..... 39c

Grind your own Crystals. Pure Brazilian Quartz. Various sizes and thicknesses. ¼ lb. pkg.....$1.00

4 Tube Drilled Chassis, 4½"x6½"x1½". 29c each

Signal Corps Phones—2 M. Ohms (8 M. Ohms Imp.).....$1.25
2 Ft. Ext. Cord and Plug:..... 40c

TOBE TUBULAR ELECTROLYTICS
20-20 MFD. 150 V...49c 30-30 MFD. 150 V...57c
40-40 MFD. 150 V...59c

Low-Loss Short Wave Lock Type Air Trimmer Variable Condensers
5 Pl.—20Mmfd. 14c
7 Pl.—25-30 Mmfd..15c
8 Pl.—30-35 Mmfd..16c
14 Pl.—56 Mmfd 24c

3 GANG T.R.F. VARIABLE CONDENSERS .0003675 Cen. 65c

D.P.D.T. SLIDE TOGGLE SWITCH 18c

1,000 OHM WIRE WOUND POTENTIOMETER....15c
30 HY-FILTER CHOKE SHIELDED.....3 for $1.25
PIEZO CRYSTAL HOLDERS..12 for $1.00—$8.00 per C

RCA Band Switches—
3 gang, 3 pos. 3 band.30c 6 gang, 4 pos. 4-5 band 40c

Trimmer-Padder Asst.—all isolantite—singles, dual triples—100 Asst.....$2.28

ATTENTION: Prospectors, Explorers for Hidden Treasures! Construct a U.S. Army Type of Metallic Mine Detector Amplifier. Amplifier unit only (less tubes and batteries) with cables, headphone cord, and jack. Army wiring diagram. Type AN/PRS-1.....$1.95

Philco push button Rotary Switch Double Pole....35c

8 or 9 Gang Push Button Switch.....49c

DRILLED CHASSIS FOR 5-6 tubes 5"x10"x1½"..25c
PHONE JACKS—OPEN & CLOSED AUTO.....18c
156-1 RATIO VERNIER DIALS—4 in., ¾ in. Hub.35c
SALE—PHONO RECORD ALBUMS—12"—3 comp.—15c; 10"—3 comp.—15c; 4 comp.—20c; 12 comp.—69c

VULCAN HEAVY DUTY 100 WATT SOLDERING IRON. Built for U.S.N.—Brand New—Equiv. sells for $8.50.....OUR PRICE $2.99

MINIMUM ORDER $3.00—NO C.O.D.
SHIPMENTS—PLEASE INCLUDE POSTAGE
NEWARK SURPLUS MATERIALS CO.
324 Plane Street, Dept. M, NEWARK 1, N. J.

Please Allow at Least 60 Days for Change of Address.

Within the Industry
(*Continued from page 26*)

of the receiver sales division of *Allen B. Du Mont Laboratories, Inc.* . . . The appointment of **DONALD W. TAIT** as manager of sales promotion has been announced by the equipment sales division of *Raytheon Mfg. Co.* . . . **JOSEPH SCHLIG,** former manager of advertising and sales promotion for the *Westinghouse* electronic tube division, has been appointed assistant to the division's sales manager. . . . **J. H. (ROBBY) ROBINSON** has been named sales manager of *Aerolite Electronics Corp.* . . . **C. J. MOLTHOP** has been named to the newly-created post of manager of the new market development of the receiver division of *Allen B. Du Mont Laboratories, Inc.* . . . **MARION E. BOND,** chief engineer of the communications and electronics division of *Motorola Inc.*, died recently. He was known for his pioneering work in the mobile radio communications field . . . **C. CLINTON HONEYWELL** has been named chief engineer of *Servo-Tek Products Co.* of Hawthorne, N. J.

* * *

ROBERT T. CAVANAGH has been appointed assistant director of research of the *Du Mont* Research laboratories.

The promotion follows a leave of absence of 18 months from the division during which time Mr. Cavanagh served as chief engineer of the company's receiver division.

He joined the company as a research engineer in 1947. He holds an E.E. degree from the University of Toronto and is a registered engineer in the Association of Professional Engineers of the Province of Ontario.

RADIO Surplus Buys

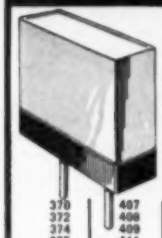

CRYSTALS
. . . in FT 241-A Holders—½" Pin SPC. Marked 54th OR 72nd Harmonic MC Freq. Listed below by fundamental frequency with fractions omitted.
500 KC Crystals $1.95
1000 KC Crystals
200 KC Crystals $3.95

370 372 374 375 376 377 379 380 381 383 384 385 386 387 388 390 391 392 393 394 395 396 397 398 400 401 402 403 404 405 406
407 408 409 411 412 413 414 415 416 418 419 420 422 423 424 425 426 427 428 430 431 433 434 435 436 437 438 440 441 442 443
444 445 446 447 448 450 451 452 453 454 455 456 457 458 459 461 462 463 464 465 466 468 469 470 472 473 474 475
476 477 478 480 481 483 484 485 486 487 488 490 491 492 493 494 495 496 497 498 501 502 503 504 505 506 507 508
509 511 512 513 514 515 516 518 519 520 522 523 525 526 527 529 530 531 533 534 536 537 538 540

$1.00 EACH
10 for $8.00. Postpaid

FOLLOWING CRYSTALS AVAILABLE IN FT 243 HOLDERS ½" PIN SPACING

4165 4240 4280 4310 4330 4335 4350 4370 4440 4445 4540 4635 4710 4880 4980 4995 5035
5127.5 5205 5285 5435 5485 5567 5660 5730 5852.5 5875 6073.3 6140 6350 6525 6550 6700 6825
6875 6975 7350 7450 7750 7875 7950 8273.3 8350 8450

$1.00 EACH
11 for $10.00. Postpaid

PLEASE ENCLOSE FULL AMOUNT WITH ORDER
QUANTITIES AVAILABLE
WRITE FOR YOUR REQUIREMENTS

C & H SALES CO.
BOX 356-MT EAST PASADENA STA. • PASADENA 8, CALIF.

Read RADIO & TELEVISION NEWS Every Month

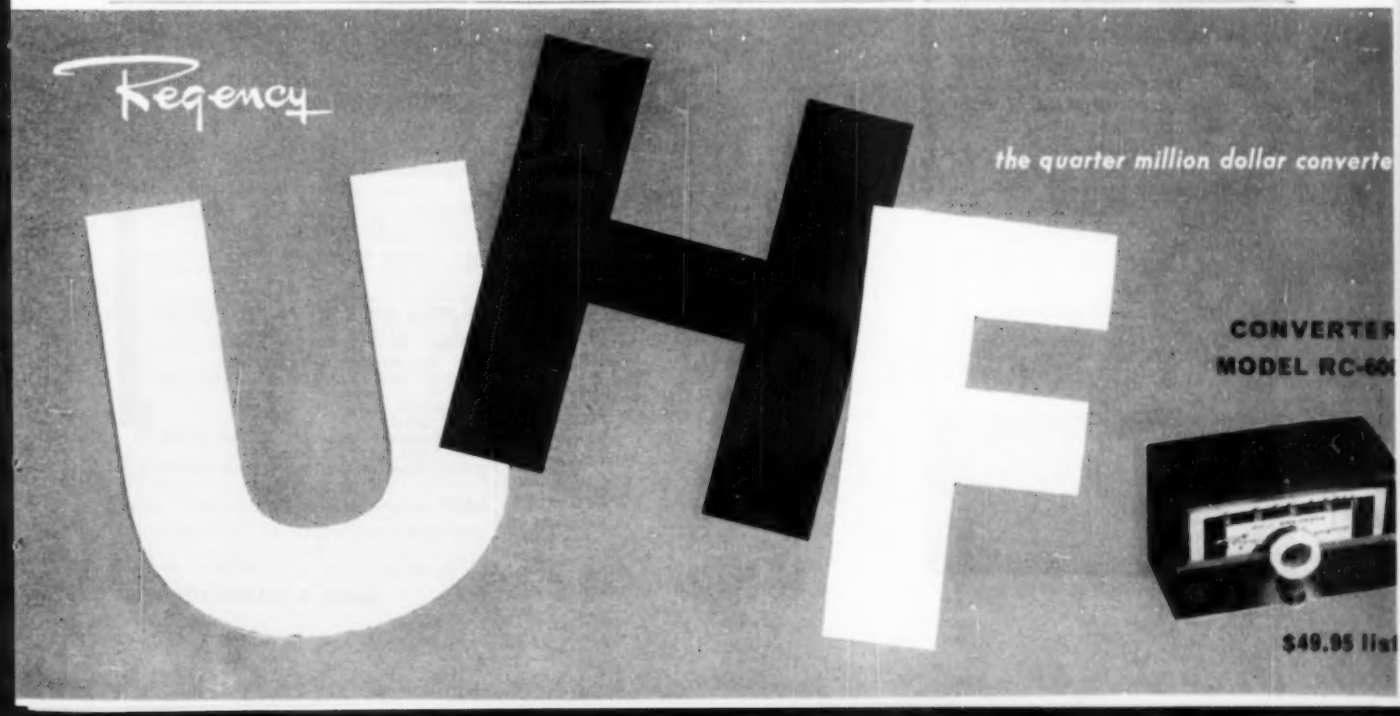

For Listeners in "Fringe" Areas

The two components below bring to music lovers in fringe areas (distances up to 80 miles) consistently clear, brilliant reception . . .

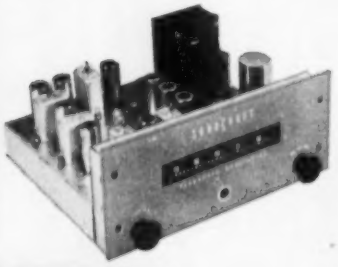

SONO CRAFT **FM TUNER**

Acclaimed for tonal quality and faithful reproduction. New blackout tuning indicator; 3 gang inductive tuning; dual limiter; all coils slug-tuned; 5 microvolt sensitivity for 20db quieting: 200KC bandwidth at 6db down; adjacent channel down 60db; 11 miniature tubes; AFC with disable switch; compact, 10" w., 4" h., 8" d.; easy installation . . . $89.95

REGENCY **DB98-FM SIGNAL BOOSTER**

Easy to operate; simple to install. Attractive steel hammertone finished case; polished aluminum dial; Internal impedance matching for 300 or 72 ohms. Push-pull triode design. Frequency range 88-108 MC. 20db gain on all FM channels. Automatically compensates for impedance mismatch. Uses one 6J6 tube as RF amplifier. Size 3-5/16" x 4⅛" x 5¼" $16.17

GIFT . . . from America's most advanced Hi-Fi studios . . . Come in for your copy of "Sound Advice" by Irving Greene, 124 pages of vital Hi-Fi data . . . It's FREE!

ASCO SOUND CORPORATION

175 WEST 45th STREET, 3rd FLOOR
NEW YORK 36, N. Y.

Wire Recorder

(*Continued from page 38*)

contactor) which is used to transfer the circuits from "record" to "playback." The jack assembly consists of a molded receptacle in which five spring contacts are secured. The crystal diaphragm-type microphone (which is standard equipment for the *"Minifon"*) employs a conventional phone plug of miniature dimensions. The length of the contact area of the sleeve plus the tip contact is such that when inserted into the special jack it will complete the circuit from the filament supply to negative ground. This insures that the filaments will be off when either microphone or headphone plugs are removed for erasing but will still permit operation of the drive motor. The tip of the microphone plug engages the third contact which feeds the output voltage from the microphone through a pre-equalizer resistance network to the grid of the input tube.

The "record-reproduce" head receives its signal voltage from the plate of the output tube with one side connected directly to the screen. The resulting plate current passing through the head provides the necessary d.c. bias component for recording.

A similar plug is provided for the stethoscope-type earphones with the exception that the sleeve length of this plug has been extended and, when inserted, picks up additional spring contacts. Two *Bakelite* rods are actuated when the long plug is inserted into the jack. These rods connect to the two changeover switches for playback.

The head, in the playback position, feeds its signal through a post-equalizer consisting of an 8 megohm resistor shunted by a 50 $\mu\mu$fd. condenser. The input grid is loaded with a 2 megohm resistor. The switching mechanism also transfers the plate of the output tube to the primary of the transformer, the secondary of which feeds the low impedance headset or an external amplifier. Care has been exercised in the design of the plate circuits because of the high gain afforded by the use of the three pentodes. Suitable decoupling networks provide the necessary isolation.

The "on-off" switch controls both the filaments to the amplifier tubes and the 9 volt d.c. motor. Motor hash and brush noise are effectively suppressed by two miniature r.f. chokes and suitable bypassing. A governor, in series with the battery supply, limits the motor speed to that required for proper operation.

EDITOR'S NOTE: The "Minifon" is distributed in the USA by Harvey Radio Co., New York City. The above discussion is from the paper, "A New Pocket Wire Recorder," by Oliver Read, presented at the Audio Engineering Society, October 29, 1952.

—30—

TV Receiver Sensitivity Measurements made Simple with

The New Portable "SensiMeter"*

. . . a "must" in fringe areas

Net **$129.50**
*Pat. Applied For

Approved by leading television manufacturers!

Consult your Jobber or write for further information

- Takes the guesswork out of TV service
- Checks receiver from antenna terminals to picture tube
- Microvolt scale is divided into 3 sections as a guide for the servicemen
- Sensitivity testing is accepted by servicemen as the best method of determining the cause of bad pictures

SI SERVICE INSTRUMENTS COMPANY
422 South Dearborn Street, Chicago 5, Illinois

LEARN

Television-Radio Electricity

REFRIGERATION-ELECTRONICS

IN THE GREAT SHOPS OF COYNE

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Come to the Great Shops of Coyne in Chicago. Get practical training in opportunity fields—TELEVISION-RADIO—ELECTRICITY—ELECTRONICS—vital in Defense Program. Prepare now for a better job in Industry or better service rating.

Approved for Veterans

Finance Plan—Enroll now, pay most of tuition later. If you need part-time work to help out with living expenses while at Coyne, we'll help you get it. **Special tuition plan for men of Draft Age.**

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. Cooke, President

COYNE SCHOOL

A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT
Established 1899
500 S. Paulina, Chicago

ELECTRICITY ★ TELEVISION
RADIO ★ REFRIGERATION ★ ELECTRONICS

B. W. COOKE, Pres.
COYNE School
500 S. Paulina St., Chicago 12, Ill. Dept. 53-85H
Send FREE BOOK and full details on:
☐ TELEVISION-RADIO ☐ ELECTRICITY

NAME .....

ADDRESS .....

CITY ..... STATE .....

Mac's Service Shop

(*Continued from page 66*)

"It should not now be too hard to picture what will happen when our lamp is swung rapidly back and forth in a small arc whose center is the original fixed position. This lateral movement of the light source produces an alternating voltage across the output of our combination photocell detector. The frequency of the alternating voltage will be exactly the same as the number of mechanical oscillations of our light source. If we could swing the lamp back and forth 400 complete oscillations per second, we could produce a 400 cycle audio voltage across our light-detector output.

"Furthermore, the amplitude of this audio voltage will depend, within limits, upon the length of the arc through which our lamp moves: if it is swung back and forth just a short distance either side of the normal position, the audio voltage will be small; but if the excursions of the lamp are made greater, the amplitude of the voltage across the photocell output will be increased.

"There is a very close analogy between this light-beam system and the FM transmitting-receiving system. The lamp is again the transmitter. Its *position* is similar to the *frequency* of the transmitter. Swinging the lamp back and forth is the same as moving the frequency of the transmitter back and forth across a center frequency. The shifting-position beam of light corresponds to the frequency-modulated carrier. The twin photocell arrangement that produces an audio voltage when actuated by the shifting beam of light is like an FM detector.

"As can be seen from this analogy, the big receiver difference between the AM system and the FM system is in the kind of detector used. We have to have a detector that will respond to frequency changes the way our twin photocells respond to position changes of the light source. This is not hard to accomplish—especially after Mr. Armstrong showed us how! For example, suppose we have two AM detectors tuned respectively to 455 and 445 kc. Suppose, too, that the response of each gradually falls to zero at precisely 10 kc. either side of the frequency to which it is tuned. Let us now present a 450 kc. carrier simultaneously to both detectors. They will respond with equal outputs since the carrier is exactly 5 kc. from the maximum response frequency of either, but since the outputs *are* equal, no voltage can be measured across the output circuits, just as was the case with our twin photocells.

"In the same way variations in amplitude of the 450 kc. carrier will not produce any voltage variations between the two outputs. But if we shift the frequency of the carrier one way or the other, immediately the output

RAD TEL ELECTRON TUBE

70% to 90% off list!

TOP TUBE BUYS

All Tubes Individually Boxed! Check this list for Rigidly-Tested, Full 1-Year Guaranteed Tubes.

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
1A5GT	.30	5U4G	.45	6BH6	.46	6W4GT	.44	19V8	.89
1A6G	.30	5V4	.73	6BJ6	.39	6W6GT	.44	24A	.63
1A7GT	.47	5W4	.50	6BK7	.59	6X4	.37	25AV5	.83
1AB5	.30	5X4	.40	6BQ6GT	.59	6X5GT	.37	25BQ6GT	.62
1B3	.65	5Y3G	.32	6BQ7	.95	6X8	.61	25L6GT	.39
1B5	.30	5Y3GT	.32	6BZ7	.95	6Y6G	.48	25W4	.56
1B7GT	.30	5Y4G	.35	6C4	.37	7A4	.47	25Z5	.40
1C5GT	.43	5Z3	.46	6C5GT	.39	7AF7	.53	25Z6GT	.37
1E7	.29	6A7	.59	6C6	.58	7B4	.44	26	.45
1G6	.30	6A8	.62	6C8G	.44	7C6	.40	27	.39
1H4G	.30	6AB4	.44	6CD6G	1.11	7E6	.30	32L7	.89
1H5GT	.40	6AG5	.43	6D6	.45	7N7	.52	35B5	.40
1L4	.46	6AJ5	.90	6E5	.48	7X7	.70	35C5	.39
1LC5	.51	6AK5	.75	6F5GT	.39	12A8	.61	35L6GT	.41
1N5	.46	6AL5	.38	6F6	.37	12AL5	.37	35W4	.37
1P5	.57	6AQ5	.39	6G6G	.52	12AT6	.37	35Z4	.39
1Q5	.58	6AQ6	.37	6H6GT	.41	12AT7	.56	35Z5GT	.37
1R5	.45	6AR5	.37	6J5GT	.37	12AU6	.38	36	.60
1S5	.39	6AS5	.50	6J6	.52	12AU7	.43	41	.42
1T4	.45	6AT6	.37	6J7G	.43	12AV6	.39	42	.42
1T5	.53	6AU6	.38	6J8	.30	12AV7	.59	43	.55
1U4	.45	6AV5	.83	6K5	.47	12AX4	.48	45	.55
1U5	.39	6AV6	.37	6K6GT	.37	12AX7	.48	45Z5	.49
1V	.60	6AX4	.53	6K7GT	.44	12AZ7	.69	50B5	.39
1X2	.63	6B4G	.64	6L6GA	.64	12BA6	.38	50C5	.39
2A3	.70	6BA6	.39	6Q7	.45	12BD6	.45	50C6	.59
2X2	1.50	6BA7	.57	6S4	.38	12BE6	.39	50L6GT	.41
3A4	.45	6BC5	.44	6S8	.53	12BF6	.39	50Y7	.90
3E5	.46	6BD5GT	.59	6SA7GT	.43	12BH7	.63	56	.50
3Q4	.48	6BD6	.45	6SD7GT	.41	12BY7	.65	57	.58
3Q5GT	.49	6BE6	.39	6SF5GT	.46	12J5GT	.42	58	.60
3S4	.46	6BF5	.41	6SG7GT	.41	12SA8	.70	70L7GT	1.09
3V4	.47	6BF6	.37	6SH7	.73	12SA7GT	.44	75	.41
		6BG6G	1.25	6SJ7GT	.41	12SF5	.50	76	.44
				6SK7GT	.41	12SG7GT	.52	77	.57
				6SL7GT	.48	12SJ7	.44	78	.47
				6SN7GT	.52	12SK7GT	.48	80	.35
				6SQ7GT	.37	12SL7GT	.47	83	.68
				6SR7GT	.45	12SN7GT	.52	85	.59
				6SS7	.42	12SQ7	.44	117L7	.99
				6T8	.56	12SR7	.49	117Z3	.37
				6U4	.60	14J7	.30	807	1.50
				6U5	.44	14W7	.30	1274	.99
				6U6	.63	19BG6G	.95	2050	1.85
				6U8	.61	19C8	.70	6113	1.00
				6V6GT	.39	19T8	.79		

Rad Tel TUBE CO.

"Integrity Is Our Chief Asset"

Phone: Essex 5-2947

TERMS: A 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse. Orders under $10—$1.00 Handling Charge. Subject to prior sale.

Don't Delay . . . Order Today!

115 COIT STREET

Dept. RN-553

IRVINGTON 11, N. J.

USED RECORDING TAPE (PLASTIC BASE)

$1.99 for 7"—1200 foot
1.09 for 5"— 600 foot
.69 for 4"— 300 foot
.29 for 3"— 150 foot
Plastic reels included with all above sizes.

Money cheerfully refunded if you do not find this tape cleanly erased and as good as new. (If you are skeptical and from Missouri send us 12c in stamps and we'll roll you a sample.)

New empty plastic reels in boxes for easy labeling: 3"-10c; 4"-22c; 5"-24c; 7"-30c ea. EMPTY BOXES: 3"-3c; 4"-5c; 5"-5c; 7"-10c ea.

We carry new recorders, recording blanks, tape recorders, etc. at large savings. PLEASE INCLUDE SUFFICIENT POSTAGE.

COMMISSIONED ELECTRONICS CO.
2503 Champlain St. N. W., Washington 9, D. C.

CODE SENDING RECEIVING SPEED

HIGH SPEED WITHOUT NERVOUS TENSION

REVEALING BOOK shows how "ragged" operators develop high speed and proficiency. Learn code for Amateur or Commercial Radiotelegraph License, or improve your sending and receiving with the Candler System which develops radio-telegraph experts and code champions.

CANDLER SYSTEM CO.
Box 928, Dept. Z.E. Denver, Colo.

FREE BOOK

TV HIGH VOLTAGE DETECTO PROBE

SAFE!! QUICK!!

TO INDICATE PRESENCE OR ABSENSE OF HIGH VOLTAGE: Place Lamp end of DETECTO PROBE near the plate (top cap) of rectifier tube. Failure of Lamp to light indicates lack of High Voltage. TO CHECK IF HIGH VOLTAGE SUPPLY IS OPERATING PROPERLY: Touch tip end of DETECTO PROBE to plate connection (top cap) of rectifier tube. If the High Voltage supply is operating properly, a hot spark at least long will be result.

ONLY 49¢

TO CHECK OPERATION OF HORIZONTAL AMPLIFIER: Place Lamp end of DETECTO PROBE near plate of horizontal output tube. If Lamp lights, the horizontal amplifier is operating properly. TO CHECK OPERATION OF HIGH VOLTAGE TRANSFORMER: Place Lamp end of DETECTO PROBE near plate of the horizontal output tube. Lamp should glow. Now place Lamp end of PROBE near the plate of rectifier tube. If High Voltage transformer is operating correctly, the Lamp will now glow more brightly.

ORDER DIRECT FROM YOUR RADIO PARTS JOBBER. If he cannot supply you, send 50c, coin or stamps, direct to: KAPNER HARDWARE, INC., Dept. RN-5, 2248 Second Ave., New York 29, N. Y.

RESCO

ULTRA-LINEAR
Williamson
AMPLIFIER KIT
Featuring the
ACRO TO-300

Build the finest amplifier ever developed. Complete with all components, punched chassis, and easy-to-follow instructions. Get the full benefits of Acrosound TO-300 performance as shown by specifications listed below.

ONLY AT RESCO . . . $74.50

ULTRA-LINEAR WILLIAMSON
ACRO TO-300

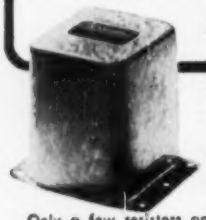

THE WORLD'S FINEST AUDIO OUTPUT TRANSFORMER

Only a few resistors and condensers are involved in converting to ultra-linear operation — layout remains the same. Get more out of your Williamson by giving it the specifications listed below.

SPECIFICATIONS
- Response — 1 db. 2 cps. to 200 kc.
- 30 watts of clean power within 1 db. 20 cps. to 30 kc.
- Less than 1% IM at 20 watts.
- Square wave transmission to 50 kc.

ACRO TO-300 ..... net $24.75
ACRO TO-310 ..... net $18.75
(TO-310 used to change over 6V6 amplifier to ultra-linear operation)

FREE Write for reprint of Ultra-Linear Operation of Williamson Amplifier and conversion information.

☐ TO-300 ☐ TO-310 (Shipping wt.—7 lbs.)
☐ Amplifier Kit (Shipping wt.—25 lbs.)
☐ Check or M.O. enclosed. Include postage.
Name .....
Address .....
City ..... Zone ..... State .....

Radio Electric
SERVICE CO. OF PENNA., INC.
7th & Arch Streets, Phila. 6, Pa.

of the detector toward whose frequency the carrier is moving begins to increase and the output of the other begins to decrease, just as happened with our photocells.

"I think you can take it from there," Mac broke off. "This detector responds to frequency change exactly the way our twin photocells responded to light change. The output of the double-barrelled detector produces an alternating voltage whose frequency is equal to the frequency with which the carrier moves back and forth across the center frequency. The amplitude of the audio voltage is directly proportional to how far the carrier frequency is shifted back and forth."

"Is that really the way an FM detector works?"

"It is how it works, but the actual methods used are different. There are several different types of FM detectors, but they all produce zero voltage when the carrier is at the center of the FM channel and increasing voltages of opposite polarity as it moves away from this center frequency in one direction or the other. The actual methods used to accomplish this end are not easy to explain without going into phase, vectors, etc.; but I doubt if your Mr. Smith is interested in these technical details. He doubtless will be satisfied if you can show him how a frequency modulation system *can* work."

"Lots of FM detectors have limiters ahead of them. How come?"

"It's pretty hard to design an FM detector—or anything else—that works perfectly," Mac explained. "Most of them tend to have *some* response to wide changes in amplitude, such as are produced by noise pulses. The best way to keep these amplitude surges from appearing in the detector output is to keep them from reaching its input. Limiter stages do just that. They are designed to pass only a certain amplitude of signal, no matter how large a signal is presented to them. As a result, the signal they deliver is uniform in amplitude, with all the surges pruned off. The important frequency deviation, of course, is unchanged; so our FM detector can do a good job of translating these frequency changes into audio voltages without having to contend with disturbing changes in amplitude, too."

Barney snapped shut the notebook in which he had been scribbling while Mac talked, and a gleeful grin spread across his freckled face. "Boy, am I going to give Mr. Smith the works tonight!" he exclaimed in happy anticipation. —30—

GERMAN EXHIBIT

THE postponed German Radio and Television Exhibition has now been rescheduled for August 29th through September 6th at the Dusseldorf Exhibition grounds.

The Exhibit was postponed last year when the industry was unable to complete the requisite television circuits to enable programming for demonstrating the TV receivers. —30—

!!WANTED!!

In order to supply government and industrial requirements, we are paying top dollar for all types of radio and electronic surplus. We specialize in test equipment and complete radios, such as:

APA, APN, APQ, APR, APS, APT, ARB, ARC, ARN, ART, ATC, BC, DY, I, IE, LM, MG, PE, PU, SCR, TCS, TN, TS, and many others.

WE ESPECIALLY NEED: APA10, APN9, APR4, APS4, ARC1, ARC3, ART13, ATC, BC221, BC342, BC348, BC611, BC721, DY12, DY17, 1100, LM10 to LM18, MG149F, MG149H, PU14, R5/ARN7, R5A/ARN7, SCR718C, TCS, TN16, TN17, TN18, TN19, TN54, TS3, TS13/AP, TS33, TS35, TS45, TS75, TS76, TS102, TS147/UP, TS148/UP, TS173, TS174, TS175, TS250, TS251, TS323, (1CT, 1F, 1G, 5CT, 5DG, 5F, 5G, 6DG, 6G 115V, 60 c.p.s. Selsyns), and all types of Hewlett Packard, General Radio Co., Measurements Corp., Boonton Radio, Ferris, Leeds & Northrup, and other test equipment.

Please state accurate description, condition, and your lowest price. Explain modifications, if any. We pay freight charges.

PURCHASING AGENTS, ENGINEERS, EXPORTERS, INDUSTRIAL BUYERS, DEALERS, AND INDIVIDUALS, Please send us your requirements.

WRITE FOR OUR LATEST SURPLUS CATALOG

PHOTOCON SALES

417 N. Foothill Blvd.
Pasadena 8, California

SYcamore 2-4131
RYan 1-6751

South River
★★NEWS★★

CHIMNEY
CORNER GUARD

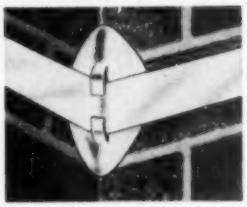

Box of Six . . . . 49¢

An exclusive South River device for protecting, strengthening, and safeguarding chimney and strapping. Prevents chipping of chimney. Permits uniform tightening of banding. Safeguards mounting equipment.

South River Antenna Mounting Accessories are carried by every leading TV Parts Jobber from coast to coast.

Write for your copy of our new 1953 catalog.

SOUTH RIVER METAL PRODUCTS CO., INC.
SOUTH RIVER, N. J.

PIONEER AND OUTSTANDING PRODUCER OF FINEST LINE OF ANTENNA MOUNTS

There's Cash Afloat

(*Continued from page* 37)

Gas tubes and audio type amplifiers are involved here, as well as Rochelle salts and magnetostrictive transducers. However, receiving type tubes, and spare vibrators and fuses are the most frequently required service items.

The depth finder is an example of the breathtaking growth of small-boat marine electronics. A surprising number of private pleasure craft are installing them, but one of their most outstanding applications is with fishing fleets. Schools of fish show up on a depth indicator, and there is no need to dwell on what this means to a commercial fisherman. The fishermen also find fog a condition of their work a large part of the time and their electronic instruments are worth their weight in gold if they get the catch to market promptly.

There is nothing to the installation or maintenance of the above that the able-bodied and conscientious worker cannot creditably handle. Instruction books furnished with all new equipment specify in sufficient detail any special requirements of that equipment. Perhaps the most important single requirement is that power feed wiring be heavy enough so the voltage drop in the line never goes above a few per-cent. This information is usually given tabularly in instruction books for different distances to the vessel's batteries. The heavy wire required (No. 6 and larger) can be obtained from auto supply houses.

Next to warrant careful treatment is the telephone antenna and ground system. Insulation must be very good, impervious to water and dirt, and the mechanical structure must be corrosion-proof and capable of riding out any weather the boat will float in. Most radiotelephone manufacturers also supply antennas designed for their gear. Lead-ins must get out in the open, fast; and not meander through the boat. Ground connections must be heavy and direct.

Engines will require standard treatment for radio noise suppression if reception is expected with the boat underway.

Then, the worker must cultivate neatness in routing wires, drilling holes, and making connections. The man who has just shelled out $49,000 for some gleaming ark will be very glum with anyone who chops up or scratches his treasure. Study the construction of every type of boat that comes along, so the most favorable placement of equipment and its wiring will come almost instinctively. And wear rubber soled shoes on varnished decks. The owner may feel more concern over that varnish than over his wife!

What is in it, for all of this effort? Expect a markup of from 25% to 35% on new equipment. This may not sound like much, but the price of just

Built for the BROADCASTER

Here at last is a magnetic tape recorder specifically designed to meet all the requirements of broadcast, recording and industrial engineers—the Concertone NWR-1.

The Concertone NWR-1 incorporates advances in engineering and performance found in no other tape recorder: Automatic brake system needs no adjustment. Direct drive from dual speed hysteresis synchronous motor • Accommodates up to 5 heads • Suitable for rack panel installation or portable cases • May be serviced during operation • Full pushbutton remote control • Accepts up to NAB size reels without adapters • Metering of input, output and bias levels.

Write for Bulletin 301

Manufactured by

Berlant Associates

4917 W. Jefferson Blvd., Los Angeles 16, Calif.

TRAIN *At Home* FOR OPPORTUNITIES IN

UHF-TV SERVICING

Set Your Own Pace with This Practical Program!

Get in on the ground floor of this fast-growing field. Train now to cash in on the opportunities that are yours in UHF-TV SERVICING with proven, practical T.C.I. training. Here is non-mathematical training that's complete . . . down-to-cases . . . up-to-the-minute. Here is training you take in your spare time, without leaving your present job! Think of it—in your own home you learn TV set conversion, master antenna installation, the latest in UHF-TV, money-making short cuts and much more. You learn to trouble-shoot, test and repair TV sets the only practical way—by actually doing this work yourself!

HERE'S HOW YOU LEARN BY DOING!

You get the experience you need by working on a large screen, modern TV receiver that's given to you with the course and is yours to keep. As an optional feature you get two weeks of field experience on service calls and on the repair bench with one of Chicago's largest independent TV servicing organizations. You profit from the experience and know-how of men in the field. Not through books alone but by actually doing the work yourself, you get the knowledge you need to qualify for opportunities in UHF-TV SERVICING! Age is no barrier. Many T.C.I. students are over 40! Mail Coupon for full facts, FREE Catalog and SAMPLE LESSON. Act NOW!

THESE MEN LIKE YOURSELF SAY T. C. I. TRAINS YOU BEST!

"I've almost completed your course now, but I have been servicing TV sets since almost the beginning of the course." E.R.M., Rhode Island.

"Thanks to your course, jobs that used to take me several hours now take but a few minutes to complete." W.L.K., Wash.

"I like the easy way your lessons are presented. I'm very pleased with your course and have recommended it to a friend." L.R.S., Texas.

VETERANS T.C.I. is approved for G.I. training under Public Law 550. Check Coupon.

TELEVISION
Communications Institute
205 W. Wacker Dr.,
Dept. 1-AK, Chicago 6, Ill.

MAIL NOW FOR FREE BOOKLET

TELEVISION COMMUNICATIONS INST.
205 W. Wacker Dr., Dept. 1-AK, Chicago 6, Ill.

YES! Rush full facts on UHF-TV training. Include FREE Catalog and Sample Lesson. I am not obligated. Salesman will not call.

Name ..... ☐ Veterans Check here

Address .....

City ..... Zone ..... State .....

☐ BEGINNERS: Check here for information on Pre-TV Radio Course.

a 10-watt radiotelephone and antenna will come to around $475 to which the installation fee (usually $50 or more) is added. Sales like these are worth spending a few days on! Service charges in general should run around $5 per hour, depending on locality; or about one dollar more than TV service since a higher degree of responsibility and government licensing are required.

The names of the more prominent marine radio manufacturers can be found in such periodicals as *"Yachting"* and *"Motorboating,"* and cooperation can be expected from the manufacturers in setting up any venture that holds promise of expanding their market. Some of them have even made a practice of shipping equipment on consignment.

The impetus given electronics by television and government needs has sent developments ahead at rocket speed. To keep up with most applications of the art, complex facilities and extremely specialized training are absolutely necessary. The amateur who would like to turn professional, or the small operator looking for a business opportunity is therefore often reluctant (and in some cases unable) to plunge into the maelstrom of general radio and TV servicing. But here is one field in radio, *and it may be the last*, where a profitable career can still be built without the backing of Fort Knox.

If the idea of attempting to start "cold" in the field is not too appealing, opportunity exists in several maritime centers—such as northern seacoast cities in the summer, and Florida and Gulf of Mexico ports in the winter—for you to break in on the job, working for somebody already established. The most popular man on many waterfronts is the radiotelephone specialist, and the clamor for him is such that it is not at all uncommon, when you step foot on the dock, to hear the call echoing through the fleet moored alongside: "Here comes the radioman!"

There's loot in those boats—and these days it doesn't take a Blackbeard to get it! —30—

This yachtswoman is familiarizing herself with a new direction finder by comparing the null line of radio bearings with the line of sight. Servicing such equipment involves no unique techniques. This unit covers the broadcast and short-wave bands as well as the radio beacon band.

20-20 PLUS!
S-256-Q Output Transformer

+1 db 10—100,000 cps
40 watts 30—40,000 cps

10 watts at 10 cps
20 watts at 15 cps

Insertion loss 0.4 db

Pri: 5,000ΩCT
Sec: 16, 12, 8, 4, 2Ω

May be operated between halved or doubled impedances

Now in Stock

Write today for the new 1953 Peerless Catalog

PEERLESS
Electrical Products
A DIVISION OF ALTEC

9356 Santa Monica Blvd., Beverly Hills, Calif.
161 Sixth Avenue, New York 13, New York

ALL-CHROME CRYSTAL BULLET MIKE (Astatic T-3). 30-10,000 cycle response. —52db. Swivel head (L.P. $27.35). YOUR PRICE . $ 8.95
TWISTED PAIR INTERCOM WIRE, plastic ±22 solid, tinned. Asstd. colors— 100 ft./$1.79; 1000 ft./ 15.00
MULTI-WIRE CABLE, ±22 sel. tinned, plastic, coded. 1½" O.D.—14 wire—15c ft./ 50 ft. 5.95. 22 wire—23c ft./ 50 ft.—$9.75; 32 wire 29c ft.
STEP-DOWN XFMR 115V. AC pri; Sec.: 50V. 75ma; 6.3V, 300 ma. 2¾" sq. x 2" . . . 1.49

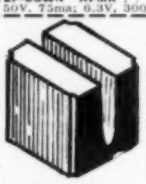

!!ALNICO MAGNET SPECIALS!!
"U" Type (¾"sq.x⅝"). 3/16" gap. Exc. for Wire or Tape Erase; spkr. or phone magnet—ea. 49c; 12/$5.00
BAR MAGNET (3½"x¾"x¼"). . . polished—ea. 39c; 12/$4.00
ROUND BAR (1¼"x⅝" O.D.). . . polished—ea. 69c; 6/$3.50
ALNICO MAGNET KIT powerful Bar, Block, "U", Rod, etc. Kit of 10 asstd. $1.98
(WRITE FOR LATEST "ALNICO" SUPPLEMENT)

RADIO HARDWARE TREASURE . . FULL LB. CAN of Nuts, Screws, Washers, Lugs, etc. 89c; 3 lbs /$2.49
SOUND POWER PHONE UNITS (Navy ANBH-1A). . Use as mike or rcvr. Sealed metal case. . . . . ea. $1.95; 2/ 3.49
DPDT BAT TOGGLES (AHH). 6A/125V . . . . . ea. 49c; 12/ 5.00
3PDT PUSH-PUSH SWITCH . . . . . ea. 39c; 12/ 4.00
5" DYNAM. TV SPEAKER . . 62 ohm field. 98
EXPERIMENTAL TUBES for Test, Research, etc. Fil. tested. Kit of 40 asstd. rcvg. types 1.98
1N21 CRYSTAL DIODES (silicon). . . ea. 69c; 10/ 6.50
HB-7 HEADBANDS . . leather, less plug . . . . . ea. 69c; 3/ 1.98
PL54/JK26 CONNECTORS . . . . . set 39c; 10/ 3.49
PL291/JK48 MIDGET CONNECTORS . . . . . set 49c; 10/ 4.49
JONES 33 CONTACT CONN. . Panel male; cable female. Off cable . . . . . set $1.29; 5 sets/ 5.00
DUAL 15mmf AIR TRIMMER, 8D shaft. 29
5" SCOPE VISOR . . moulded vinyl. 98
5" C.R. TUBE FRONT BEZEL 98
5" SCOPE GRID . . calib. 360° radially 39
8¼" CLEAR CONVEX LENS, round . ea. 39c; 10/ 3.50

!!SUPER $$$ SAVINGS!! . . with the new "JUMBO RADIO-ELECTRONICS PARTS KIT" . . a "Gold Mine" assortment of inventory odds & ends: Wire, Coils, Resistors, Condensers, Switches, Controls, Etc., Etc. (shpg. wt. 20 lbs.) $3.95

W-1108 ARMY FIELD WIRE . . perfect, ½ mile roll (shpg. wt. 60 lbs.) $7.95
On rolls 100-400 ft. . . . . 1c ft.
6" FLEXIBLE SHAFT EXTENDER . . ¼"x3/16". . . . . ea. 39c; 10/ 3.50
1/17 H.P. G-E MOTOR (Type SD). . 1725 RPM; 110V. DC. 7 amp. Dble. ¾" shaft. O.D. 4¾"x5½". Shpg. wt. 13 lbs. 2.95

"DIRECT FACTORY SPEAKER REPAIRS SINCE 1927"
SPECIALISTS ON ALL TYPES OF "HIGH FIDELITY" UNITS
Min. order $3.00. 20% deposit req. on all C.O.D.'s. Full remittance with foreign orders. Please add sufficient postage—excess refunded.
LEOTONE RADIO CORP.
67 Dey Street
New York 7, N. Y.

OSCILLOSCOPES ARE "GOLD MINES"!

. . . if you learn how to use them fully on all types of service jobs!

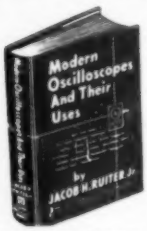

Learn to handle the oscilloscope fully on all types of AM, FM and TV service work—and watch your efficiency and earnings soar!

MODERN OSCILLOSCOPES AND THEIR USES, a fact-jammed 326 page book by Jacob H. Ruiter, Jr., of the Allen B. DuMont Laboratories contains exactly the help you need—written in a way you can clearly understand. It shows you how to use your scope for fast accurate work on all types of jobs from trouble-shooting to realigning; how to make connections; how to adjust circuit components; how to set controls and how to analyze patterns fast and accurately. 370 helpful illustrations including dozens of pattern photos make things doubly clear.

No other type of specific service training stands to mean so much to you in terms of being able to do better, faster and more profitable work!

✓ When, where, why and exactly how to use oscilloscopes
✓ How to interpret oscilloscope patterns
✓ How to handle tough jobs in less time

MAIL ORDER 10-DAY FREE EXAMINATION

Dept. RN-53, RINEHART BOOKS, Inc., Technical Division,
232 Madison Ave., New York 16, N. Y.

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-DAY EXAMINATION. If I decide to keep the book, I will then remit $6.00 plus a few cents postage in full payment. If not, I will return book postpaid and owe you nothing.

Name .....
Address .....
City, Zone, State .....
Employer's Name & Address .....
OUTSIDE U.S.A.—Price $6.50 cash only. Money back in 10 days if book is returned.

Sine-Wave Clipper

(*Continued from page* 51)

wave generator is connected to the input terminals of the instrument. The set-up used is shown in Fig. 6.

Turn on all the equipment, allow sufficient time for "warm-up" of the scope and generator, then adjust the scope controls until three or four cycles of the signal can be easily observed. The frequency is not too important, and the generator may be set to deliver a sine wave from 30 to 30,000 cps.

Gradually turn "up" the amplitude or output control of the sine-wave generator. The output signal should first appear as shown in Fig. 4D, then the pulse peak should flatten, as the signal level is increased, until a pattern similar to those shown in Figs. 4A, B, and C is obtained. The output of the sine-wave generator should be between 3 and 5 volts when the proper pattern is obtained.

If too much signal is applied, a pattern similar to the one shown in Fig. 4E will be obtained. Under these conditions there is some danger of damaging the transistor.

After the output signal level of the sine-wave generator has been set, the frequency of the generator should be varied and "spot checks" made at different frequencies over the audio range. The scope should be readjusted at each point as may be necessary to obtain a complete and steady pattern of two or three cycles.

In a few instances, it may be found that the output of the sine-wave generator varies sufficiently to require readjustment of its amplitude control to insure complete "clipping" at some frequencies. In such a case, an effort should be made to select a signal level that will insure a good rectangular output signal from the clipper at any frequency, but without distortion at any point (as shown in Fig. 4E). If such a setting of the amplitude control can be found, it will save considerable time when a series of tests is to be made at different frequencies.

Applications: There are three major applications of the output signal obtained from the sine-wave clipper. It may be used for gain measurements, for rapidly checking frequency and transient response characteristics of an amplifier, or as a source of pulse signals. Let us discuss each application separately.

Gain measurements: When proper clipping occurs, the output signal level of the sine-wave clipper remains constant, *irrespective of minor variations* in the input signal level. Because of this, the output signal is ideally suited for gain measurements at different frequencies.

The basic instrument set-up illustrated in Fig. 3 may be employed. The scope is first used to check the output from the sine-wave clipper so that the sine-wave generator can be ad-

NEW
IT'S TERRIFIC!
EICO
7 MODEL 470 -INCH PUSH-PULL SCOPE

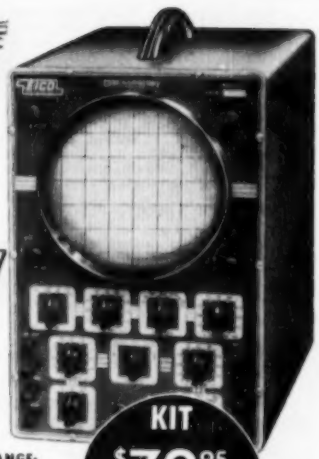

- BOOSTED VERT. SENSITIVITY: 10 mv rms/in.
- EXTENDED FLAT FREQ. RESPONSE: 10 cps—1 MC (± 2 db).
- 3-STEP FREQ.-COMPENSATED ATTENUATOR; cathode follower input.
- INTERNAL VOLTAGE CALIBRATOR; dir.-cal. screen.
- EXTENDED SWEEP RANGE: 15 cps—100 kc.
- INT. POS. OR NEG., EXT. & LINE SYNC.
- ON FRONT PANEL: sawtooth, 60 cps outputs; intensity mod. & ext. sync inputs.
- VAR. PHASING of int. 60 cps sweep.
- DIRECT CONNECTION TO CRT PLATES.

KIT $79.95
Factory Wired $129.50

ORDER NOW!
For full specifications on Model 470 and the complete EICO line, write for latest catalog.

Lafayette Radio
FAMOUS IN RADIO FOR 32 YEARS
NEW YORK 13, N. Y., 100 Sixth Avenue
BOSTON 10, MASS., 110 Federal Street
NEWARK 2, N. J., 24 Central Avenue
PLAINFIELD, N. J., 139 West 2nd Street
BRONX 58, N. Y., 542 East Fordham Road

MONEY MAKERS!

FOR MOBILE-RADIO SERVICE ENGINEERS!

Provide for future expansion in this profitable field, with Lampkin frequency- and modulation-measuring equipment.

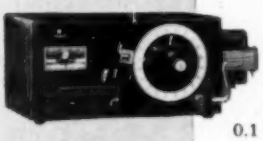

For Any Number of Frequencies, AM or FM. The Type 105-B MFM.

The Type 105-B Micrometer Frequency Meter, or MFM, measures center-frequency on any number of nearby transmitters, AM or FM, 0.1 MC. to 175 MC. Performs as signal generator for mobile receivers, 20 MC. up. Meets FCC requirements for mobile services, with accuracy guaranteed better than 0.0025%. Can be checked against WWV. Price $220.00 net.

The Type 205 FM Modulation Meter for Multiple Mobile Frequencies.

Instantly tunable anywhere, 25 MC. to 200 MC., the Type 205 measures maximum FM deviation due to modulation, as required by the FCC. Indicates 0-25 KC. deviation. Simple to use, easy to carry. No charts or tables. Price $240.00 net.

Send name and address for literature

Name .....
Address .....
City ..... State .....

LAMPKIN LABORATORIES, INC.
MFM DIVISION
BRADENTON, FLORIDA

SURPLUS SPECIALS

Sweep Generator Capacitor—Rotating split stator. Cylindrical silver plated rotor concentric to stator. High speed ball bearings. Capacity 5-10 mmfd. Build your o w n motor-driven television sweep frequency generator.

Stock No. R-95

Special $2.25 each

D-101 Dynamotor. 27 volt input at 1.5 amps. 220 volts dc output at 80 milliamperes. Large quantity available. New—original packing.

Stock No. R-60

Special $4.95 each

Redmond 6 Volt DC Motor—An ideal small dc motor for the experimenter. Operates from 6 volts dc at 3000 rpm. Requires 1.75 amperes for 1/100 horsepower.

Stock No. R-337

Special $2.95 each

CATHODE RAY TUBE REJUVENATOR

Don't throw away old picture tubes with low brilliance. Restore brightness 3 to 9 months. Install in 30 seconds—no tools. See page 62 RTN, October 1952. For parallel AC filament circuits.

Special, each **$2.95**

Dealer quantity prices on request. Regular List, $6.98.

RESISTOR KIT

Carbon deposited resistors on ceramic form. German manufacture. You get 99 resistors, 11 each of 9 values as follows in 9 compartment hinged cover type plastic box: 100 ohm ½ watt; 820 ohm 1 watt; 2200 ohm ½ watt; 4700 ohm 1 watt; 8200 ohm 1 watt; 10000 ohm 1 watt; 68000 ohm, ½ watt; 100000 ohm 1½ watt; 470000 ohm ½ watt. Only 1,000 kits available. Act now.

Special Price, $1.98 per kit.

AMPERE DEMAND METER

Stewart Warner-748A. Indicates up to 20 Amperes hour time average current drain. High time lag—follows heating effect of supply transformers. Use to check motor and line overload as well as peak average demand. Indicator average and average peak recorder pointers.

Stock No. R-119

Special @ $3.95 each

1 RPM MOTOR

115 volts, 60 cycles. Synchron model 600. Use for timing devices models, displays, gadgets, etc.

Stock No. R-5

Price $2.95 each

NEW TRIPLETT METERS

Model	Description	Price
341	0-500 ma. RF 3" rd.	$6.50
232	0-10 V. AC. 2" rd.	6.50
327A	0-1 ma. DC. 0-100 good-bad scale. 3" sq.	6.50
327A	0-60 micro-amps. DC. 0-1000 ohm scale. 3" sq.	8.50
327A	0-400 micro-amps. DC. 3" sq. 0-25-50-100 V. AC scale	8.50
221	0-8 ma. DC. 2" rd. 0-100 good-bad scale	4.50
242T	0-1.2 ma. DC. 2" rd. 0-100 ma. scale	4.50

Weston "S" Meter—Mod. 605. Type 234L. Tune for max. 2.5 ma. movement. **Price $3.50.**

Weston Volt-Ammeter—Mod. 604. Type 221-P. 0-60 Amps. DC and 0-30 volts DC. Normally reads current—depress switch for volts. Complete with shunt at **$9.50 each.**

Write for free catalogue of Electronic, Aircraft, Hydraulic and other equipment.

Minimum order $2.00. Prices F.O.B. Paterson, N. J.

Electro Devices
INCORPORATED
4 Godwin Ave. Paterson, N. J.

justed to supply sufficient signal for proper clipping. Once this is done, the *output control of the sine-wave clipper* (R_2, Fig. 2) is adjusted to deliver the desired input signal to the amplifier.

The input signal amplitude to the amplifier will now remain constant at the predetermined level, even if the frequency of the sine-wave generator is changed (provided, of course, that the signal supplied to the sine-wave clipper by the generator does not drop so low as to prevent proper clipping action. Should this occur, however, it is readily spotted as a change in the waveform of the signal observed on the scope).

Gain measurements now become merely a matter of determining the output signal level. Since the input signal is of known amplitude and unvarying, actual gain is a matter of simple calculation.

Frequency and transient response checks: The rectangular wave signal obtained from the sine-wave clipper may be used in a fashion similar to square waves for rapidly checking the over-all frequency response of an amplifier, attenuator, or filter network (see "Wide Frequency Range Square-Wave Clipper," March, 1950, RADIO & TELEVISION NEWS.)

The high frequency response of a circuit or network is determined by applying a high frequency rectangular wave to its input and observing the output signal waveshape on the screen of an oscilloscope. Poor high frequency response will cause excessive rounding at the peak of the "leading edge" of the sharper rectangular pulse (see Fig. 7). Poor transient response or "ringing" will cause a signal overshoot at this point.

A low frequency signal is used to check the low frequency response of the circuit, but, in this case, the broader "flat top" (again, refer to Fig. 7) is observed. Excessive "tilting" of the flat top indicates phase shift at lower frequencies.

When using the rectangular wave in checking a circuit's response, it must be remembered that the rectagular wave's narrow pulse is representative of a *square wave* of somewhat higher frequency than the actual repetition rate of the signal.

In a similar fashion, the wider portion of the signal is representative of a *square wave* of somewhat lower frequency.

Fig. 7. Poor high frequency response causes rounding at the peak of "leading edge."

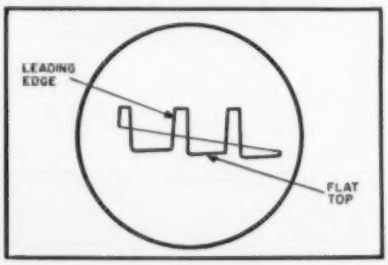

DON'T PASS THIS BUY

LINK & BOSCH MOBILE POLICE RECEIVERS, 5 tubes (RF stage) fixed tunable 2-3 mc. adj. squelch control, W/6 volt power supply, 250V/100 ma. IDEAL/Ham, C.D. MARS & MARINE services. Makes hot recvr w/HF converter, used operating cond. With new 5" PM spkr. ... **$12.95**

HERE'S YOUR ANSWER TO LOW ANGLE PROBLEM, radiates good DX sigs, everywhere. **VERTICAL WHIP ANTENNA ASSY.** for 10, 15, 20, 40, 80 M 9½ ft., **$1.45**; 24 ft., **$3.75**, 16 ft. **$2.45**; 32 ft. ... **$ 4.75**

NEW 6 & 12 VOLT DYNAMOTOR, 180 V/50 ma, 300 V/150 ma, higher ratings on 12 V ... **11.95**

COMPACT ELTRON VIBRATOR PACK, 6v in, 90V/ 30 ma output, will operate on 4 D cells, 2½" dia x 3½" H. Swell for portables ... **3.95**

JAEGER 6 V DC CLOCK made for Kaiser-Frazer; 2" face W/ 2 panel lamps, draws 3 ma will run on dry cells. L.P. $17.00 ... **5.95**

HAYDON SYNCHRONOUS MOTOR, 24 volts 60 cy will operate on 115V line with series capacitor, high torque geared shaft output, 5 RPHR with cam/dwr ... **1.25**

SENSITIVE RELAYS

SIGMA 5AH 3000 ohm/2ma, plugin	$4.95
SIGMA 5AH 10,000 ohm/1ma, plugin	6.95
SIGMA 5R2 5000 ohm/1.5ma, sealed	5.95
SIGMA 5R 150 ohm, operates 2-24 VDC	2.45
SIGMA 41F 10K ohm .04 watt AC/DC SPDT	1.75
KURMAN BK-3S 10,000 ohm/.5ma	4.95
G.E. COMPACT, 10,000 ohm/1.5ma SPNO	1.65

COMPACT GEAR BOX ASSY 800/1 ratio high torque suitable model controller, wt ½ lb. ... **1.95**

RACHET RELAY, 4 position, 6-12 VDC ... **3.95**

SPECIAL 90 VAC SYNCRO CAPACITORS

3x .6 mf	$2.75	3x .3 mf	$3.75
3x10 mf	5.95	3x50 mf	7.95
10 mf/600 VDC/220 VAC round met. case			1.95
20 mf/285 VAC/600 VDC rect. met. case			2.95
50 mf/600 VDC rect. metal case			6.95

EVEREADY #467, 67½ v. B. battery outdated but good as new, stock up at giveaway $ for **1.95**

ELECTRONIC SPECIALTY SUPPLY CO.
58 WALKER STREET, NYC 13, N. Y. WALKER 5-8187

The June Issue of

RADIO & TELEVISION NEWS

Will Be on Sale May 26

Reserve Your Copy Now!

AUDELS TV-RADIO SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO & TELEVISION REPAIRMEN, SERVICEMEN & STUDENTS

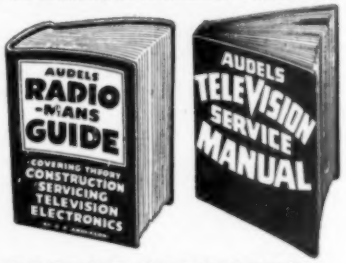

2 VOLS. $6 COMPLETE $1 A PAY ONLY MO.

IT PAYS TO KNOW!

AUDELS T.V.-RADIO SERVICE LIBRARY presents the important subjects of Modern Radio, Television, Industrial Electronics, F.M. Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc. Covers Basic Principles—Construction—Installation — Operation — Repairs — Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems & Methods of Conversion. 1001 Facts—Over 1260 Pages—625 Illustrations—Parts & Diagrams—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers T.V. & Radio Questions.

Get this information for Yourself.
7 DAY TEST—ASK TO SEE IT!

MAIL ORDER

AUDEL, Publishers, 49 W. 23 St., N.Y. 10
Mail AUDELS T.V. RADIO SERVICE LIBRARY 2 Vols. $6 on 7 days free trial. If O. K. I will remit $1 in 7 days and $1 monthly until $6 is paid. Otherwise I will return them.

Name _____

Address _____

Occupation _____ RN

Employed by _____

If an analysis of the signal waveshapes is qualified with these facts in mind, then the techniques of square-wave testing may be applied directly to the use of rectangular waves in circuit analysis.

Pulse signal source: Since a pulse is basically a rectangular waveform, the output of the sine-wave clipper may be used in the same fashion as the signal obtained from a pulse generator. If narrower pulses are desired, an *RC* or *RL* differentiation network may be used after the clipper.

Conclusion

The sine-wave clipper circuit described, although designed for a specific application, is basically nothing more than an overdriven transistor amplifier, operated without bias. Because of this, the basic circuit given should offer the experimenter ample opportunity to become familiar with the operation of the basic resistance-coupled transistor amplifier.

However, those experimenters who have not previously worked with transistor circuits should exercise reasonable care when experimenting with modifications of the basic circuit given. Be sure the maximum ratings of the transistor are not exceeded. Transistors are both relatively expensive and easily damaged.

—30—

Photocell Relay

(*Continued from page* 65)

source may be arranged to fall across a doorway so that anyone entering the room interrupts the light beam. This, in turn, may cause a chime, doorbell, or buzzer to sound. Such an arrangement is particularly useful for small stores, small offices, etc.

Door Opener: The photocell relay may be arranged in a garage so that light striking the unit from an auto's headlights acts to operate a door-opening motor. In this application, the long tube (see Fig. 3) should be used to prevent operation due to extraneous light from passing cars, street lamps, etc.

Counter: A light source may be arranged to fall across a hall or areaway so that anyone passing interrupts the light beam. An electromechanical counter can be used to keep a record of the number of persons passing a given spot in a day or for any other period of time.

Light Switch: The photocell relay may be arranged so that daylight falls on it, and connected so that when the light level falls, due to clouds or the approach of evening, room lights are automatically switched on.

Smoke Alarm: If the light source and photocell relay are arranged across the top of a room, smoke from a beginning fire will interrupt the beam and operate the unit. An alarm signal could be sounded if such an arrangement seems desirable.

—30—

The New Model 670-A

SUPER-METER

a combination

VOLT-OHM MILLIAMMETER plus CAPACITY REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS

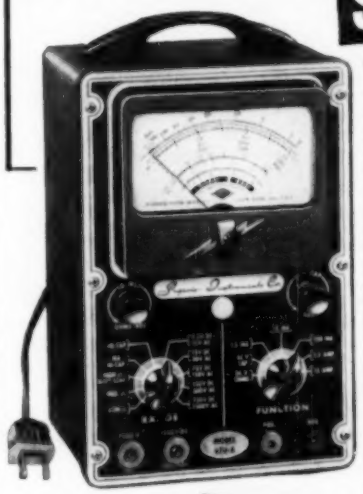

SPECIFICATIONS:
D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
DECIBELS: −6 to +18 +14 to +38 +34 to +58

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions. Size 6¼" x 9½" x 4½".

$28.40 NET

Write Dept. RN-5 for complete catalog

ADDED FEATURE
The Model 670-A includes a special GOOD - BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

AT YOUR RADIO PARTS JOBBER

Manufactured and Guaranteed by
SUPERIOR INSTRUMENTS CO.
227 Fulton Street • New York 7, N. Y.

BARGAINS • BARGAINS • BARGAINS

You can depend on STEVE-EL to come up with "terrific buys"! Our latest catalog is chock full of 'em. WRITE TODAY!

STEVE-EL BRAND
(House of BARGAINS)
HAS DONE IT AGAIN!

INTERCOM SPECIAL

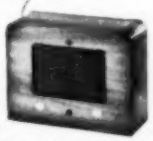

Now you can own an intercom that has a thousand uses at a price you would normally pay for a kit. This intercom comes housed in wooden cabinets complete y wired and ready to operate. Outfit consists of one master, one sub station and fifty feet of two wire cable. Ideal for home as baby sitter. Perfect for office or factory. Order now as quantities are limited.

YOUR COST COMPLETE only $15.95

Steve-El Brand
TUBES

Brand new, individually boxed. Many FAR BELOW WHOLESALE COST!

1A7	90.62	6SL7	.52
1B3	.61	6SN7	.54
1P5	.64	6SQ7	.42
1R5	.49	6T8	.74
1T4	.49	6U6	.57
1U4	.48	6U8	.78
1U5	.48	6V6	.46
5U4	.47	6V8	.83
5W4	.46	6W4	.45
5Y3	.29	6W6	.52
5Z4	.62	6X4	.34
6A8	.51	7C6	.43
6AQ5	.62	7X7	.62
6AR5	1.14	12AT6	.46
6AK6	.64	12AU6	.48
6AL5	.41	12AU7	.56
6AU6	.43	12AV6	.52
6AX4	.59	12AX4	.59
6BA6	.48	12AZ7	.94
6BC5	.58	12BA6	.47
6BC7	.86	12BE6	.47
6BE6	.48	12SA7	.52
6BG6	1.21	12SK7	.49
6BH6	.62	12SL7	.57
6BJ6	.53	12SN7	.54
6BK7	.86	12SQ7	.42
6BQ6	.76	14AF7	.59
6BQ7	.86	19T8	.78
6C8G	.48	25BQ6	.77
6CD6	1.79	25W4	.48
6F6	.49	25L6	.48
6J6	.79	25Z6	.42
6K6	.41	32L7	.91
6L6GA	.89	35Z5	.33
6L6G	.89	35L6	.48
6SA7	.52	50L6	.48
6SQ7	.49	80	.38
6SK7	.49		

SPECIAL DISCOUNTS
50 Asst. 5% 100 Asst. 10%

STEVE-EL ELECTRONICS CORP.
Dept. N-5 61 Reade St. New York 7, N. Y. COrtlandt 7-0086

BARGAINS • BARGAINS • BARGAINS

Here's how to SAVE MONEY ON INSTRUMENTS!

√ . . . how to do faster, better testing with fewer instruments

√ . . . how to increase the usefulness of your present instruments

√ . . . how to choose the right instrument for each job

√ . . . how to understand instrument operating principles

√ . . . how to evaluate instrument readings and put them to practical use

BASIC ELECTRONIC TEST INSTRUMENTS

By RUFUS P. TURNER

254 pages, 171 illus., Price $4.00

The Instrument Book Written Especially for • SERVICEMEN • AMATEURS • EXPERIMENTERS

★ HERE'S a brand new book that can save you money on instruments and help you use your present instruments lots more efficiently!

Over 60 instruments—from the most modern TV pattern generators to special-purpose bridges—are carefully described. Their uses are fully explained and valuable work-saving short cuts outlined.

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's; V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes (this material alone is worth the entire price of the book to busy servicemen!); r-f test oscillators and signal generators; audio test oscillators; radio frequency and audio frequency measuring devices; audio-amplifier testing devices; r-f signal tracers and tube testers.

Among other things, BASIC ELECTRIC TEST INSTRUMENTS is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators; TV linearity pattern generators, square-wave generators, distortion meters and others.

SEE WHAT IT CAN DO!

You are shown new uses for VOM's, 'scopes, signal generators and other old standbys. You learn how easy it is to extend the range of many old instruments; how power drain measurements can be used for fast TV trouble-shooting; how a useful and accurate bridge can be built from a combination of familiar general-purpose instruments; how to calculate shunts and multipliers; how to measure r-f impedance with a simple T-network; how to measure inductance and capacitance with a grid-dip oscillator and scores of other money-saving "tricks."

Just off the press! Read BASIC ELECTRONIC TEST INSTRUMENTS for 10 days at our risk!

10-DAY FREE EXAMINATION

Dept. RN-53, Rinehart Books, Inc.
Technical Division,
232 Madison Ave., New York 16, N. Y.

Send Turner's BASIC ELECTRONIC TEST INSTRUMENTS for 10-day FREE EXAMINATION. If I decide to keep book, I will then remit $4.00 plus postage. Otherwise I will return book postpaid promptly and owe you nothing.

Name .....

Address .....

City, Zone, State .....

Employer's Name and Address .....

OUTSIDE U.S.A.—Price $4.50, cash only. Money back if book is returned postpaid in 10 days.

Parts Show Exhibitors

(Continued from page 32)

Penn Television Products
Pentron Corporation
Perma-Power Co.
Permo, Inc.
Permoflux Corporation
Philmore Manufacturing Co., Inc.
Phoenix Electronics, Inc.
Pickering & Company, Inc.
Pilot Radio Corporation
Potter & Brumfield
Precise Development Corporation
Precision Apparatus Co., Inc.
Premier Metal Products Co.
Presto Recording Corporation
Pyramid Electric Co.

Quam-Nichols Co.

Racon Electric Company
Radelco Manufacturing Co.
Radiart Corporation
Radio City Products Co., Inc.
Radio Corporation of America
Radio Craftsmen, Inc.
*Radio-Electronics
Radio Merchandise Sales, Inc.
Radio Receptor Co., Inc.
*RADIO & TELEVISION NEWS
*RADIO-ELECTRONIC ENGINEERING
*Radio & Television Weekly
*Radio & TV Journal
Radion Corporation
Ram Electronics, Inc.
Rauland-Borg Corporation
Rauland Corporation
Raytheon Manufacturing Co.
Recoton Corporation
Reeves Soundcraft Corporation
Rego Insulated Wire Co.
Rek-O-Kut Co.
John F. Rider Publisher, Inc.
River Edge Industries
Rockbar Corporation
Rohn Manufacturing Co.
Rytel Electronics Manufacturing Co.

Howard W. Sams & Co., Inc.
San Fernando Electric Mfg. Co.
Sangamo Electric Co.
Walter L. Schott Co.
*Service Magazine
*Service Management
Shure Brothers
Simpson Electric Co.
Mark Simpson Manufacturing Co., Inc.
Herman H. Smith, Inc.
Snyder Manufacturing Co.
Sola Electric Co.
Sonar Radio Corp.
Sonic Industries
South River Metal Products Co., Inc.
Spirling Products Co., Inc.
Sprague Products Co.
Standard Coil Products Co., Inc.
Standard Electrical Products Co.
Standard Transformer Corporation
Stephens Manufacturing Corporation
Stevens Walden, Inc.
Stromberg-Carlson Co.
Sutton Electronic Company, Inc.
*Sutton Publishing Co.
Switchcraft, Inc.
Sylvania Electric Products Inc.

Talk-A-Phone Co.
Tech-Master Products Co.
Technical Appliance Corporation
Tele-Ex-Pand Prods. Sales Corp.
Tele-Matic Industries, Inc.
Telrex, Inc.
Tenna-Trailer Co.
Thomas Electronics, Inc.
Thordarson-Meissner Division
Triad Transformer Manufacturing Co.

WANTED!

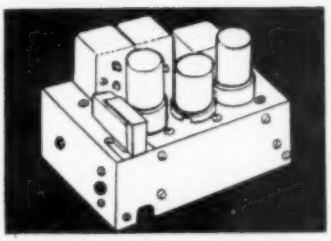

CASH REWARD

For ART-13 XTAL CALIBRATORS

Also need ART-13 Xmitters (or any parts or spares), BC-348 Q and R, BC-788C, I-152C, R5/ARN-7, APN-9, DY-17.

IF IN YOUR POSSESSION PLEASE NOTIFY US IMMEDIATELY!

V & H RADIO & ELECTRONICS

2033 W. Venice Blvd., Los Angeles 6, Calif.
Phone Collect: REpublic 3-1127

TRAIN FOR A SUPERVISORY POSITION IN

ELECTRONICS

Thorough 2-year course covers electrical circuits and machinery, basic electronics and industrial electronics. Franklin Technical Institute graduates are in demand as junior engineers for research and test work, sales engineering, supervisory work on production lines and drafting room design work. Other engineering and technical courses. Coed. Day, evening. 45th year. Write for catalog.

FRANKLIN TECHNICAL INSTITUTE
46 Berkeley Street Boston 16, Mass.

HI-FI WILLIAMSON TYPE AMPLIFIER KIT

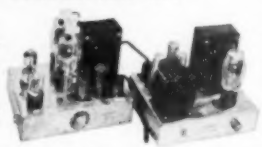

Using STANCOR transformers. Easy-to-assemble amplifier kit. Comes with schematic and instruction sheet based on famous Williamson circuit. Frequency response ±1 db. from 20-50,000 Kc. at 8 watts. Intermodulation distortion is only 3% at 8 watts output. Total harmonic distortion at 1000 cycles is non-existent below 10 watt power level.

SPECIAL
Price Per Kit $44.95
Less Tubes

WITH CBS HYTRON TUBES		TOTAL PRICE
	2—GL807	
	2—6SN7GT	
	1—5U4G	$52.75

IRISH PLASTIC RECORDING TAPE
BRAND NEW! NOT SURPLUS. This First Grade recording tape is ¼ in. wide. Frequency response: 50 to 8,000 cy. Plastic reel included with each.
600 FT. $1.35 1,200 FT. $2.10

For Your HI-Fidelity Requirements
Visit Our New Sound Studio

All orders F.O.B. Los Angeles. Minimum order $5.00. 25% deposit required with order.

OLYMPIC-KASSLER
Dept. O.E.S., 7636 Santa Monica Blvd.
Los Angeles 46, Calif.

Tricraft Products Co.
Trimm, Inc.
Trio Manufacturing Co.
Triplett Electrical Instrument Co.
Tung-Sol Electric, Inc.
Turner Co.
TV Products Co.

Ungar Electric Tools, Inc.
United Catalog Publishers, Inc.
United Transformer Co.
University Loudspeakers, Inc.
Utah Radio Products Co., Inc.

Vaco Products Co.
Van Cleef Bros., Inc.
Vidaire Electronics Mfg. Co.
Video Accessory Manufacturing Co.
V-M Corporation

Waldom Electronics, Inc.
P. Wall Co.
Ward Leonard Electric Co.
Ward Products Corporation
Webster-Chicago Corporation
Webster Electric Co.
Weller Electric Corporation
Wells & Winegard
Wen Products, Inc.
Westinghouse Electric Corporation
Weston Electrical Instrument Corporation
Wilcox-Gay Corporation
Wincharger Corporation

Xcelite, Incorporated

*Trade Papers

OREGON HAM MEET

THE 1953 Oregon Amateur Radio Association (O.A.R.A.) Convention will be held in Salem's Marion Hotel May 23 and 24.

A full program of entertainment is being planned for visiting amateurs, including lectures by eminent authorities, contests, equipment displays, swap and shop room, etc. The prize list is headed by a Johnson Viking II wired and ready to operate and includes dozens of useful items.

Registration fees are $7.00 for general and advanced class amateurs; $5.00 for Novice class hams; and $3.00 for non-licensed guests. Advanced registration is now underway.

Reservations and requests for additional information should be sent to James W. Simmons, W7KVV, 1790 N. 24th St., Salem, Oregon. —30—

PHOTO CREDITS

Page	Credit
38	Harvey Radio Co., Inc.
40 (top left & center), 54 (Fig. 1), 55 (Fig. 2)	Radio Corp. of America
40 (top right), 41	Polytechnic Research and Development Co.
57	Electro-Voice, Inc.
58	Irving Greene
63	JFD Manufacturing Co.
67, 68, 69 (Figs. 3 & 4), 70 (Fig. 6)	Allen B. Du Mont Laboratories, Inc.
74	Radio Tetuan
128	General Electric Company

IF YOU CANNOT ATTEND THE CHICAGO ELECTRONIC PARTS SHOW, PLEASE
Send for literature to Dept. R5, BRITISH INDUSTRIES CORP., 164 DUANE STREET, NEW YORK 13, N. Y.

Now available for Immediate Delivery

NEW AMAZING OSCILLOSCOPE by PRECISE

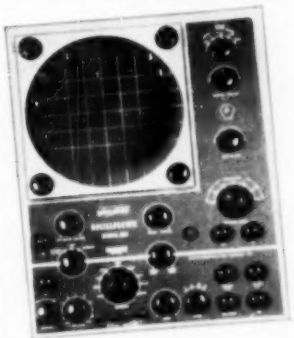

Accept no substitute for this latest PRECISE Original—No other "scope" can compare with this new test instrument because:—Precise uses No Surplus—only the finest components in our precision engineered products. Precise offers an iron clad guaranty with every purchase. Precise also offers you an instructively illustrated, 3 color, step-by-step construction book —the most comprehensive in the market today!

HERE ARE A FEW OF THE MANY PRECISE FEATURES IN THE NEW OSCILLOSCOPE

• True electronic sweep magnifier • Astigmatism control • Push-Pull vertical front input thru output; push-pull horizontal • Internal blanking and Z modulation with blanking amplifiers • Driven and non-driven sweep • Over 5MC flat response-DC amplifiers • Cathode follower input on vertical and horizontal • Internal calibrator • Horizontal and vertical stepping attenuator • New 7" tube to Precise specifications • Highest sensitivity available aside from finest laboratory scopes

THE PRECISE MODEL 300 SCOPE FEATURES:

Vertical sensitivity of 10 mv. r.m.s./in. • Phasing control • Intensity modulation

Selling price: **300 KIT $94.95**

PRECISE Model 630 RF-AF-TV Generator

Check All These Features

Factory assembled pre-tuned RF head.* Fundamentals through 110 mc. Audio: 20-20,000 cycles, variable percent modulation, cathode follower output stepping attenuator, external modulation, speech amplifier, crystal marker. Reaches 330 mc. on harmonics.

Kit Model 630K—Dir. Net . . . ea. $33.95
Kit Model 630KA*—Dir. Net . . . . . ea. $38.95
Factory wired Model 630—Dir. Net ea. 53.95

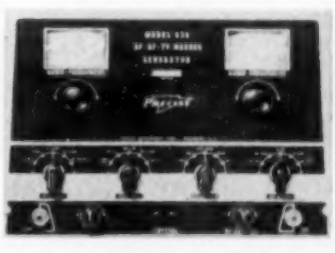

TEE·VEE Supply Co.

SEND FOR CATALOG LISTING 1953 PRECISE INSTRUMENTS
3211-13 Washington Street
Jamaica Plain 30, Mass.

Performance JUSTIFIES THE CLAIM . . .

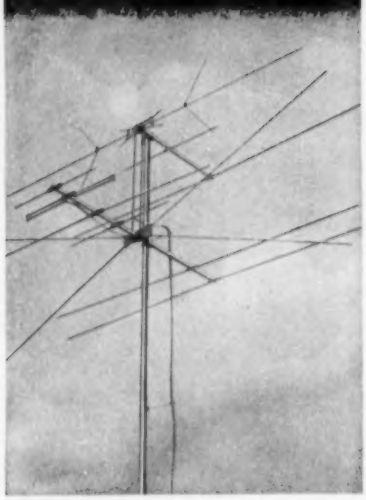

THE *Greatest* HIGH-GAIN VHF-UHF ANTENNA EVER BUILT!

The Far-Reaching Kay-Townes

BJU-1

Original, Revolutionary Design . . . FIXED IMPEDANCE Point System Provides All-Channel, High-Gain Reception With a Single Transmission Line!*

Ultimate High-Gain sharp picture reception throughout the entire television spectrum . . . ALL CHANNELS, 2 to 83!

No matching pads or isolation filters . . . no coils or condensers which tend to cut down signals and increase costs of installations. Simplified, but more effective engineering not only results in sharper reception, but reduces service call-backs to absolute minimum. VHF reception improved by addition of UHF system.

One lead-in wire only. Built to high standards of performance and workmanship. Sold in kits of 2, 3, 4 bay units . . . BJU-1, BJU-1X, BJU-2.

SOLD ONLY THROUGH SELECTED WHOLESALE OUTLETS . . .

Contact your jobber or write for name of nearest distributor.

*Patent Applied for

THE BEST SET IS ONLY AS GOOD AS ITS ANTENNA!

KAY-TOWNES ANTENNA CO.
ROME, GEORGIA

INDEX OF ADVERTISERS, MAY, 1953

Airex Radio Corporation . . . 117
Allied Radio Corporation . . . 9
Allied Radio . . . 118
Almo Radio Company . . . 94
Altec Lansing Corporation . . . 162
American Phenolic Corporation . . . 26
American Television & Radio Company . . . 101
Amperite Company, Inc. . . . 146
Amplifier Corporation of America . . . 24
Argos Products Company, Inc. . . . 134
Arkay Radio Kits, Inc. . . . 120
Arrow Electronics . . . 151
Arrow Sales . . . 131
Asco Sound Corporation . . . 158
Ashe Radio Co., Walter . . . 123
Atlas Sound Corporation . . . 120
Audak Company, Inc. . . . 138
Audel & Company, Theo. . . . 164
Barbey Company, Geo. . . . 84
Belden Mfg. Company . . . 87
Bell Telephone Labs., Inc. . . . 108
Bell Telephone Labs., Ind. . . . 93
Berlant Associates . . . 161
Brook Electronics, Inc. . . . 160
Buchan Company, R. J. . . . 124
Burroughs Radio . . . 133
C & H Sales Company . . . 157
Cameradio . . . 169
Candler System Company . . . 159
Cannon Electric Company . . . 32
Capitol Radio Engineering Inst. . . . 143
Centralab, Inc. . . . 77
Champion Bronze Powder . . . 138
Channel Master Corporation . . . 22-23
Clayton Radio . . . 102
Cleveland Institute of Radio Electronics . . . 119
Collins Audio Products . . . 29
Columbia Electronic Sales . . . 94
Commissioned Electronics Company . . . 159
Communication Equipment Company . . . 76
Concord Radio Corporation . . . 15, 108
Coyne Electrical School . . . 158
Crest Laboratories, Inc. . . . 143
DeForest's Training, Inc. . . . 5
Delco Radio Parts . . . 85
Editors & Engineers, Ltd. . . . 138
Eitel-McCullough, Inc. . . . 130
Electro Devices . . . 164
Electronics Institute, Inc. . . . 118
Electronic Instrument Company, Inc. . . . 34, 152
Electronic Measurements Corporation . . . 129
Electronic Specialty Supply Company . . . 164
Electro Products . . . 104
Electro-Voice, Inc. . . . 8
Erie Resistor Corporation . . . 126
Espey Manufacturing Company, Inc. . . . 129
Fair Radio Sales . . . 137
Federated Purchaser, Inc. . . . 112
Fisher Radio . . . 78
Franklin Technical Institute . . . 166
Fretco Television Company . . . 144
G & G Radio Supply Company . . . 110
G & H Wood Products . . . 84
G. L. Electronics . . . 100
Garrard Sales Corporation . . . 167
General Electric Company . . . 13
General Electric Company . . . 19
General Electric Company . . . 30, 31
General Test Equipment . . . 147
Goodheart, R. E. . . . 114
Greenlee Tool Company . . . 96
Green Tele Radio . . . 92
Hallicrafters Company . . . 7
Harjo Sales . . . 86
Harrison Radio . . . 142
Harvey Radio Company . . . 110
Heath Company . . . 79, 82
Henshaw Radio Supply . . . 147
Hughes Research . . . 121
Hytron Radio & Electronics Company . . . 97
Illinois Condenser Company . . . 140
Indiana Technical College . . . 124
Instructograph Company . . . 168
Insuline Corporation of America . . . 92
JFD Mfg. Company . . . 11
J. S. H. Sales Company . . . 136
Jensen Industries, Inc. . . . 155
Kapner Hardware, Inc. . . . 159
Kay-Townes Antenna Company . . . 168
Kirk, James . . . 118
Klein Company, Manuel . . . 153
L. A. Ham Shack . . . 120, 126
Lafayette Radio . . . 163
Lampkin Laboratories . . . 163
LaPointe Plascamold Corporation . . . 103
Leeds Radio Company . . . 154
Lee Electronic Labs., Inc. . . . 150
Littelfuse, Incorporated . . . 17
Leotone Radio Company . . . 162
MacInnes, Norman R. . . . 139
MacMillen Company . . . 90
McGee Radio Company . . . 88, 89
McGraw-Hill Book Company . . . 128
McIntosh Engineering Labs., Inc. . . . 105
Mallory & Company, P. R. . . . 20, 4th cover
Mattison Television & Radio Corp. . . . 156
Metropolitan Supply . . . 108
Michel Mfg. Company . . . 84
Miles Reproducer Company . . . 133
Milwaukee School of Engineering . . . 106
Mosley Electronic . . . 149
Moss Electronics . . . 99
National Electric Products . . . 72, 73
National Electronics of Cleveland . . . 96
National Radio Institute . . . 3
National Schools . . . 109
National Telecolorvision Screen Company . . . 108
Newark Electric Company . . . 84
Newark Surplus Materials . . . 157
Newcomb Audio Products Company . . . 141
Ohmite Mfg. Company . . . 16
Olson Radio Warehouse . . . 107
Olympic-Kassler . . . 166
Onan & Sons, D. W. . . . 150
Oxford Electronics . . . 130
Peak Electronics . . . 140
Penn Boiler & Burner Mfg. Company . . . 102
Perma Power . . . 154
Pfanstiehl Chemical Company . . . 140
Philco Corporation . . . 27
Phillips Tube Company . . . 144
Photocon Sales . . . 160
Pickering & Company, Inc. . . . 6
Platt Electronics . . . 135
Poly-Tech Company . . . 92
Premax Products . . . 136
Premier Radio Tube Company . . . 127
Prentice Hall, Inc. . . . 136, 152
Progressive Electronics Company . . . 122
Pyramid Electric Company . . . 12
Quietrole Company . . . 146
RCA Institutes, Inc. . . . 75, 169
R. W. Electronics . . . 153
Radiart Corporation . . . 10
Radio City Products Inc. . . . 139
Radio Craftsmen, Inc. . . . 14
Radio Electric Service Company . . . 160
Radio Products Sales . . . 144
Radio-Television Training Ass'n . . . 25
Rad-Tel Tube Company . . . 159
Rauland Corporation . . . 28
Raytheon Mfg. Company . . . 18
Regency . . . 132, 157
Relay Sales . . . 116
Rider Pub. Inc., John F. . . . 124
Rinehart Books . . . 130, 150, 162, 166
Rock Bar . . . 155
Sams & Company, Inc., Howard W. . . . 83, 154
Sangamo Electric Company . . . 133
Sarkes-Tarzian, Inc. . . . 152
Schott Company, Walter L. . . . 24
Scott, H. H. . . . 134
Service Instruments Company . . . 158
South River Metal Products Company . . . 160
Sprayberry Academy of Radio . . . 71
Stan Burn Radio & Electronics . . . 132
Standard Surplus . . . 125
Standard Transformer . . . 145
Steve-El Electronics . . . 165
Stephan Sales Corporation . . . 169
Stevens Walden Inc. . . . 148
Sun Radio & Washington, D. C. . . . 134
Superior Instrument . . . 165
Tab . . . 170
Tech-Master Products Company . . . 94, 95
Technograph Printed Electronics . . . 114
Tee-Vee Supply . . . 167
Telematic Industries . . . 98
Television Communications Institute . . . 161
Television Materials Corporation . . . 118
Television Remote Control Company . . . 145
Telrex, Inc. . . . 33
Terado Company . . . 120
Transvision Inc. . . . 96, 115
Trio Manufacturing Company . . . 91
Tri-State College . . . 168
Tung-Sol Electric Company . . . 146
Turner Company . . . 151
United Catalogue Publishers, Inc. . . . 143
Utah Mfg. Company . . . 114
V & H Radio & Electronics . . . 166
Valparaiso Technical Institute . . . 147
Van Sickle Radio Supply Company . . . 102, 145
Waldom Electronics Inc. . . . 155
Wall Mfg. Company . . . 111
Western Electronics . . . 133
Western Radio Television Institute . . . 92
Wholesale Radio Parts . . . 147
Windsor Electronic . . . 102
World Radio Laboratories, Inc. . . . 149
YMCA Trade & Technical School . . . 145

Unlimited Opportunities in

RADIO ENGINEERING

DEGREE IN 27 MONTHS

Complete Radio Engineering course, including Telev., U.H.F. and F.M. Bachelor of Science Degree also in Mech., Civil, Elect., Chem., and Aero. Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep courses. Personalized, practical instruction. Founded 1884. Placement service. Growing shortage of engineers. Prepare now for unlimited opportunities ahead. Approved for Korean vets. **Enter June, September, January, March. Write for catalog.**

TRI-STATE COLLEGE
1653 College Avenue, ANGOLA, INDIANA

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY
4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

Classified

Rate 50c per word. Minimum 10 words

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice: television; broadcasting; servicing; aviation, marine, police radio. 12 or 18 months. Catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

FOR SALE

SELENIUM Rectifiers, 150 ma, 115 volt, 70c. Radio Surplus, 41 West Main, Branford, Connecticut.

TAPE Recorders, Tapes, Accessories. Unusual Values. Dressner, 624-R East 20th St., N.Y.C. 9.

ALL types of Antennas for Amateur and TV. Aluminum Tubing. Willard Radcliff, Fostoria, Ohio.

TUBES and equipment bought, sold, and exchanged. For action and a fair deal, write B. N. Gensler, W2LNI, 136 Liberty, N. Y. 6, N. Y.

TELEVISION towers from 10 to 90 feet use "Tuffy", "America's favorite tower". Write Youngstown Steel Towers Co., Box 2825, Youngstown 8, Ohio.

NEW RCA 3AP1A original cartons, $8.75 each. Tubes, surplus—bought, sold. Free list. Write, Mark, Box 14, New York City 72.

DIAGRAMS Radio, Record Changers, Recorders, 75c; Television with Service Data, $1.25 up. State manufacturer and model number. Kramer's Radio Service, Dept. F53, 36 Columbus Ave., New York 23, N. Y.

ISOLATION transformer 35w 117v sec 117 or 135 plus 6.3v.45a 2¼x2½x3. $2.45 includes postage 3 lbs. Bulletin available. Empire Electronics Company, 409a Avenue L, Brooklyn 30, N. Y.

BOOSTERS Standard Coil B-51 in original factory sealed cartons $7.95—UHF Diamond Back antenna min. 12 D.B. gain $8.95. Pacific Television Enterprises, 915 Dairy Ave., Corcoran, Calif.

TWO complete Radio Shops will sell, one or both in part or complete. Write for particulars. Zanes Radio & TV Service, Box 11, Coldwater, Kansas.

TV-FM antennas. All types including UHF. Mounts, accessories. Lowest prices. Wholesale Supply Co., Dept. H, Lunenburg, Mass.

WANTED

WANTED—Top Prices Paid—Navy Selsyns 1DG, 1F, 1CT, 1G, 5DG, 5D, 5CT, 5G, 6G, 7G, etc. and BC-348, BC-221, AN/ART-13, AN/ARC-1, AN/ARC-3, RTA-1B, AN/APR-4. Lectronic Research, 719 Arch St., Philadelphia.

AN/APR-4, other "APR-," "ARR-," "TS-," "IE-," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. For Sale: Reconditioned Watthour Meters, four for $10.00. Engineering Associates, 434 Patterson Rd., Dayton 9, Ohio.

WILL buy all Art-13/type T-47A, $200.00, Art-13/type T-47, $150.00, BC-348 unmodified, $75.00, BC-348 modified, $55.00, APN-9, $200.00, ARC-3 complete, $750.00, R77 Receivers, $400.00, ARC-1, $600.00, BC-312, $65.00, BC-342, $60.00. Ship via Express C.O.D., subject to inspection to: H. Finnegan, 49 Washington Ave., Little Ferry, N. J.

MISCELLANEOUS

TEST Equipment Repaired and Calibrated by Factory Staff. All makes. Ship Instruments Parcel Post Insured. Immediate service. Douglas Instrument Laboratory, 176 Norfolk Ave., Boston 19, Mass.

SPEAKERS repaired, wholesale prices, guaranteed workmanship. Amprite Speaker Service, 70 Vesey St., New York City 7.

BUSINESS Cards $2.50 1,000. Samples free. Signal, Box 927A, Los Altos, Calif.

TAPE Recording Exchange for education, amusement. Foreign members. World Tape Pals, Box 9211, Dallas, Texas.

RICHES—Security—Happiness, Yours to Achieve. For booklet, send $1.00, care of W. A. Horn, P.O.B. 763, San Francisco, Calif.

Introducing THE *Self-Powered* BROOK

HIGH QUALITY AUDIO PRE-AMPLIFIER... MODEL 7

OTHER STANDARD BROOK AMPLIFIERS
MODEL 10C4 30-WATT REMOTE CONTROL
MODEL 12A4 10-WATT REMOTE CONTROL
MODEL 4 PRE-AMPLIFIER

. . . BROOK know-how in transformer design paved the way to incorporate a power transformer in one chassis; yet, **HUM LEVEL IS MINIMIZED TO VANISHING POINT.**

. . . Ideally suited to any quality basic amplifier

. . . Famous BROOK 10-position stepped bass and treble controls; plus separate 9-position record playback control, equalized for virtually all records, offer the music and audio connoisseur an exceptionally wide range of flexibility in tone control.

. . . Five input channels for radio, TV or recorders; including one channel to accommodate any type pickup; or microphone.

. . . In performance, the MODEL 7 offers the NATURAL, IMMEASURABLE TONAL QUALITY which built the BROOK reputation.

Write today for technical data on the complete line of Brook High Quality Audio Amplifiers; also name of nearest dealer. Dept. RF-3

BROOK ELECTRONICS, INC.

First in the High Quality Audio Field Since 1934

34 DeHART PLACE, ELIZABETH 2, N.J.

RCA INSTITUTES, INC.
A service of Radio Corporation of America
350 West 4th St., New York 14, N. Y.
OFFERS COURSES IN ALL TECHNICAL PHASES OF RADIO, TELEVISION, ELECTRONICS
Approved for Veterans
Write Dept. RN-53 for Catalog

ANOTHER OUTSTANDING JOBBER
CAMERADIO CO.
1121 Penn Ave
Pittsburgh 22, Pa
HAS THE SENSATIONAL NEW EICO 470-K 7" SCOPE KIT IN STOCK!

$79.95

Nationally Famous **T.V. SETS**

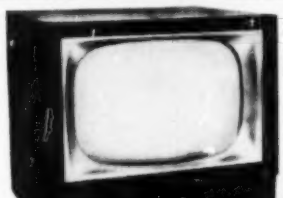

Here is true quality comparable to models selling for as much as $200 more. Check these luxury features; Ultra sensitivity; Dynamic Range control; UHF adaptability; Duo Power supply; Acousticlear sound system. . . All in a beautiful mahogany finish cabinet.

17" Table **$122.68** Plus $12.27 Fed. Excise Tax
20" Table **$134.50** Plus $13.45 Fed. Excise Tax
20" Consolette **$150.00** Plus $15.00 Fed. Excise Tax

Full 1 yr. factory picture tube warranty and standard 90 day RTMA parts warranty on both cabinet sets and Chassis.

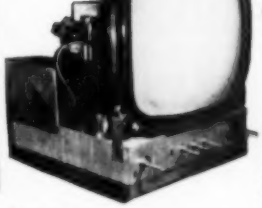

T. V. CHASSIS *Also Available*

Ready to Operate, Complete with Picture Tube and Speaker
17" SET **$99.95** pl. $9.99 Fed. Excise Tax
20" SET **$112.50** pl. $11.25 Fed. Excise Tax

Featuring all the outstanding qualities listed above. Ideal for custom-built wall installations, shelves, cabinets . . . den, playroom, bedroom, etc. Great for commercial use in taverns, clubs, restaurants, etc.

Dealer Inquiries Invited

Mail and phone orders filled. Enclose $25 deposit, balance C.O.D. Shipping charges additional.

STEPHEN Sales Corp. 45 CROSBY ST., N. Y. 12, N. Y. WORTH 4-8233

T2FD ANTENNA RESISTOR

For T2FD Antenna. CQ Feb. 53 Globar Non-Inductive "RF," 400 Ohm Antenna Resistors & Mtg Clips.....$2.49

STORAGE BATTERIES

36 Volt WILLARD Mini-BRAND 5 oz. DSGN...98c; 4 /$3.00
(4) 36V Batt/acid.....3.35
2V/20AH Battery with 3 Volt Vibrator.....2.98
2V/20AM w/vib & acid..3.59
6V/6AH Willd NT6/BB214U.....2.98
6V/6AH Battery w/acid.....3.25
6V/40AH Battery.....6.98
6V/40AH Battery w/acid.....9.25
Hydrometer 1.00 to 1.24 Sp Grav.....1.98
We ship acid in bottles, K'exp only.

CHROME VANADIUM SPEED DRILLS

29PCS CHROME VANADIUM SPEED STEEL. Top Quality for Machinists or all purpose use. Standard Full Length 1/16" to 1/2" by 64ths. With Hi-gh Drill Index.....$9.69
12 PCS SET 1/16" to 1/2" Less 1/64ths. Index.....$3.49
60 PCS DRILLS #1 to 60. With Drill Index.....$7.98
13 PCS 1/16" to 1/4" w/Index....$2.69
1/4 SPEED ELECTRIC DRILL w/Jacobs Wormgear Chuck & 60 Pcs Drills & Index. "TAB" SPECIAL.....$22.00
1/2" SPEED ELECTRIC DRILL w/Jacobs Wormgear Chuck & 29 Pcs Drills & Index. "TAB" SPECIAL.....$39.00

VARIAC

Made by General Radio. Model 200CU. Rated 0-135 Volts at 7.5A. Reconditioned. Tested and ★Set★ Guaranteed.....$15.95
"GR" 100R/0-230V/2KW/9A.....30.00
"GR" 50B/0-270V/7KW/28A.....110.00
BRUSHES 200CU & 110,/116U...49c; 5/$2

STEP UP TRANSFORMER

Primary 7.5KW, W/110V Input. Two Secondaries DLVR 220V at 7.5 Amp Each, or One 440V at 7.5A. Same but 220V Pri. Will Deliver 2X440 at 7.5A Each, or 880V at 7.5A. "TAB" SPECIAL.....$110.00

CONTACTOR

G. E. CR 2811 C 22 AO. Heavy Duty Electric Starter Transmitter or Motor Starter Switch. For Single or 2 or 3 Phase Appl. Rated 1 Phase 3HP/110V, 7½HP/220V 10 HP/600V. Rated 2 or 3 Phase 7½ HP/110V, 15HP/220V - 25HP/600V. Control★Inpt. 220V/1PH/60 Cy. Enclosed 45Amp Open 50 Amp...$19.00; 2/$36.00

SOLDERING IRONS & GUNS

"WELLER" Cun 115VAC 100 Watt..$8.69
"WEN" Gun 115VAC 250 Watt.....9.49
"P-IMAX" Gun 115VAC Soldering Tip 7.69

ESICO IRONS 230V AC /DC

55Watt/3/8Tip/11½Lng/3Lbs.....$1.25
60Watt/1/4Tip/12"Lng/.8Lbs.....1.91
100Watt/3/8Tip/12"Lng/.75Lbs.....2.59
150Watt/1/2Tip/12"Lng/.75Lbs.....3.17

ESICO INDUSTRIAL CONST. USE IRONS 120VAC /DC--Similar to American Beauty types as shown

61A60/60W 1/8Tip 7"Lng 2.5oz.....$3.20
=38/AM Beauty3138/100W 3/8Tip.....5.29
Element=38/AM Beauty3138/100W.....2.00
=58/Am Beauty3158/200W 5/8Tip.....6.30
Element=58/Am Beauty3158/200W.....2.75
=78/Am Beauty3178/300W 3/4Tip.....3.16
Element=78/Am Beauty3178/300W.....3.65
=98/Am Beauty3198/550W 1¼Tip.....10.08
Element=98/Am Beauty 3198/550W.....4.80
Eaton Temp Regulating Stand.....4.20
Kester Solder, 1 lb. 062 Roll.....$1.29 or With any soldering iron. Special.....90c

WRITE FOR QUANTITY PRICES

TOOL KIT

High Quality Forged, Tempered Tool Steel, 6¼" Adj Wrench, 5½" Long Nose Pliers, 5¼" Cutters. With Carry Case.....$2.25
8 Screw Drivers, Assorted Hitch Quality Magnetized, Tool Steel, Hammer-Proof.
Unbreakable Plastic Handles, 12" & smaller, Incld Phillips Type.....$1.25
6 Screw Drivers, Above.....1.10

RHEOSTATS

15 ohm 25 W w/knob.....1.98; 3 for $5.00
20 ohm 50 W Model J.....2.35; 6 for 12.00
60 ohm 50 W w/knob.....2.49; 3 for 7.00
100 ohm 50 W Model K.....2.75; 3 for 6.00
250 ohm 25 W.....ea 1.39; 4 for 5.00
300 ohm 225W Model P.....3.98; 2 for 7.00
350, 500, 2000 ohm Slotted shaft, 25 watt.....79c; 3 for 2.00
1000 ohm 25W Model J.....2.10; 5 for 10.00

SOCKET ASSEMBLY

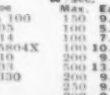

For 10 slide lamps. Excellent on-off Indicator for control panel. As illustrated with lamps SPECIAL.....$2.98
SLIDE LAMP, type T-2 24V.....10c; 10 for.....$1.50
SLIDE LAMP, type T-2, 12V.....18c; 10 for $1.50
PILOT LIGHT SOCKET 1" Bezel High Polish Finish.....75c; 10 for $6.40
1" LIGHT SOCKET, w/115VoWattBulb..85c

LO-VOLT PHOTOFLASH KIT

Includes DX Flash Lamp Rated 150 Watt Sec. Flash Lamp Holder & 8" Reflector & Cable. Power Transformer & CD Flash Capacitors. 15/ 200 Mfd Each W/Output of 100 Watt Sec. All Resistors, Capacitors, Rectifiers & Sockets.....$29.98
Extra Flash Lamp Holders W/8" Reflector & Cord $3.98; W/Lamp DX.....$12.98

TAB "SUN-FLASH" LAMPS

"Tab" No.	Replaces	W/Sec. Max.	Each
DX	SPHG FA 100	100	9.00
USW	GE FT 105	100	5.98
U10	GE FT 114	100	7.25
No. 1	AMGLO 5804X	100	10.98
23SC	GE FT 210	200	9.98
53GT	GE FT 403	500	13.50
VA	SYLV 4330	200	9.98
22MT	FT 214	250	9.98
22ST	FT 110	200	9.98
V4X4	X400	200	10.98

PHOTOFLASH CAPACITORS

180MFD 500WVDC.....$1.98
200MFD 450WVDC.....2.89
300MFD 450WVDC.....3.98
16MFD 600VAC 2800VDC Intmit't.....6.95
32MFD 1.2KVDC 23W. Sec.....7.49
27MFD/460VAC/2KV Int. 84W. Sec.....8.95

"TAB"

THAT'S A BUY

FILTER CHOKES

Dual 30 Hy/60ma Cnd.....$ .98
15Hy/40ma AC DC sets.....3 for .98
12Hy/80ma H'Snd/3KVins.....2.25
10Hy/125ma UTC Cnd H'Snd/1KVins. 1.69
50Hy/125ma Cnd H'Snd.....2.89
20Hy/300ma or 15Hy/400ma/12KVins 8.95
13.5 HY 1 Amp./17KVins/Raytheon..39.95
12HY/300ma, Hmsld 5KVins.....4.95
10HY 100 MA Freed.....1.49
6HY/175ma 250ohm..$1.49; 2 for 2.49

POWER TRANSFORMERS

2500V for Cnt 6.3V/6A. 2.5 V/1.75A cnd Hvins 4/BC412 equivint $7.98; 2 for $14.98
1000VCT /45MA. Sec. 60 ma. 360vct.55ma. 3x5V/3A. 6.3vct/1A. 6.3vct/3A end Hvins can be used as rating Hypersil core..$4.98
950VCT /100MA. 5V/5A. 5V/2.5A. 6.3V/3A. 45V/3A. 10V/1.5A.....$5.49
900V 35MA. 2x2.5V/2A. xcint 1800-volt w/two 2x2 ll windes hsld.....3.49
900V 340MA.6.3V/2A. 5V/3A.....2.98
840VCT 110MA. 350vct 21ma. 2x5V/3A. 6.3vct 1A. 6.3vct 3A.....4.98
780VCT /250MA. 5V/6A. 12.6V/5.5A 4.98
770VCT /200MA. 5V/6A. 12.6V/5.5A 6.95
760VCT /120MA. 2.3vct/10A. 6.3vct/2A. 5V/3A. 10V/3.25A.....6.98
700VCT 120MA. 5V/3A. 6.3V/3A. 6.3V/3A.....$3.98; 2 for 7.25
550VCT 150MADC. 5V/3A. 6.3V/5A. 3.49
500VCT /60MA. 6.3V/4A Hsld.....2.98
420VCT /90MA. 6.3V/1.9A. w t t b INPTS 6, 12, 24, 115VDC & 115/230VAC Vibrator Trans.....1.98

FILAMENT TRANS.

2.5V /2A @ 79c; 2 for $1.49; 10 for $6.49
2.5VCT /10A 5KVINS.....3.59
2.5VCT 10A /12KV INSUL G.E.....8.25
5V /115A CSD KENYON HVINS.....16.95
7.5VCT /12A CSD KENYON 15 KVINS 10.95
12.6VCT /1.25A CSD HMSLD.....1.98
24V /1.25A CSD @.....$1.98; 2 for 3.49
2X12V /2A or 24V /2A @ $3.89; 2 for 6.98
42.5V /2A SEL RECT TRANS.....4.85

TABOGRAM

WRITE FOR IT

WE STOCK LARGE VARIETY OF COMPONENTS. TELL US YOUR NEEDS. SELL US YOUR TUBES & EQUIPMENT

"HO" RAILPACK

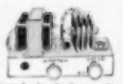

0 to 12 VDC/2 Amp. Variable DC supply, uncased & all completely built-inpt 115v/60 cy. Usable LAB supply, filament D.C. plating, battery charging, model railroad. Includes voltage or speed control and center off reversing sw. Ideal for two ★Model Transmitters★. "TAB" SPECIAL.....$10.95; 2 for $20.00

SELENIUM RECTIFIERS

We specialize in Rectifiers and Power supplies to your spec's. Immediate delivery. Current 18/14 36/28 54/40 130/100

cent.	Volts	Volts	Volts	Volts
1AMP	1.38	2.15	3.70	7.50
2AMP	2.20	3.60	7.40	10.50
4AMP	4.25	7.95	12.95	25.25
6AMP	4.75	9.00	13.50	33.00
10AMP	6.75	12.75	20.00	40.00
12AMP	8.50	16.25	25.50	45.00
20AMP	13.25	25.50	39.00	79.50
24AMP	16.25	32.50	49.00	90.00
30AMP	20.00	38.50		
36AMP	25.00	48.50		

Full-Wave Selen. Rect & Trans. in Kit Form. All 115V/60 cy inputs up to 14VDC at 12 amps.....$ 23.98
up to 28VDC at 12 amps.....31.98
up to 28VDC at 48 amps.....117.00

RECTIFIER XFMRS

18-12-9-CT-9-12-18V/12 Amp.....$ 8.75
18-12-9-CT-9-12-18V/12 Amp.....16.75
18.8-19.2-20.4-21.4 Volts/12A.....12.25
31-32-34-36 Volts/12A.....21.98
18 Volts/12 Amps.....$15.95; 2 for 29.50

CIRCUIT BREAKER FUSES

PUSH TO RESET
Amps 3—5—7—10—15—20
Each 27c 4 for.....$1.00
25 for $5.00; 100 for $18
Circuit Breaker Fuse W/2 Mtng Clips 39c
3 for $1.00; 20 for $5.98; 100 for.....$25
Fuse is 3AG Size. Operates up to 24 Volts
Please specify current (amps) desired.
Heinemann Mega Buss. Amps: 0.22, .5, .7, 9, 12, 15, 20, 30, 35, 40, 80, 100.
Each $1.69; 10 for $15.98

BATTERY CHARGER RECTIFIER

10-0-10V (CT) 120 Amp., fan cooled. Replace your old inefficient sulfide rectifier w/new selenium type. SPECIAL....$11.98

RELAY SPECIALS

SPST min. size 115V/60CY 3A CTS 98c; 3 for.....$2.75
SPDT min. sizes 115V/60CY 3A CTS $1.39; 3 for.....$3.75
SPDT 24V DC, 5A CTS 98c;
SPNO 115VAC 15A CTS 2.98
DPDT & SPNO 12VDC 10A CTS.....$2.98; 4 for $10
DPDT Clare SK5010. Octal Base 18-28V, 2Amp Cts. Nitrogen Sld. $1.49; 4 for $5.00

FEDERAL RECTIFIER KIT

"FEDERALS"—All Purpose Selenium Rectifier Kit. You can make 24 different Rectifiers ½ Wave/FW/CT/or Bridge. 8 Plate Rated 18V 12Amp each. All Hardware & Lugs. "TAB" SPECIAL.....$19.50

AUDIO AMPLIFIERS READY TO GO

Model 30SMP 5 Watt Ampl. as Pictured Above Features Mike & Phono Inpts. W/Sep. Gain Cntrls. Latest Compensated Tone Cntrl. Design. Complete with Tubes. "TAB" SPECIAL $14.98

Model 200MO Mike OSC. Broadcasts Through Your Radio with No Direct Connection. W/Tubes.....$6.98
Model 100PO Phono OSC. Phonograph Broadcasts Through Your Radio. No Direct Hookup. W/Tube.....$4.98
Model 362PA 3 Tube Phono Ampl. Ideal for Custom Building Your Phonograph. W/Tubes. SPECIAL.....$4.98

AUDIO COMPONENTS

GE RPX041 Phono Cart..$ 4.49
GE RPX050 Triple Play.....5.69
Electrovoice Triple Play.....2.69
Pickup Arm&Xtal Hi-Output.....2.39
PM 12"GE 8120ID Speaker.....19.00
PM 8" Blue 8T18-1 Permflux.....13.00
PM 10"Hi-Fi Woofer & Separate Horn Tweeter, 10watt 40-20KC.....19.98
Crystal Mike & Cable.....3.98
Crystal Mike Cartridge (Lapel type).....2.98
Crystal Mike Cart. Ceramic Wetgrnf.....3.98

OIL CAPACITORS

Mfd	Each	Mfd	Each	Mfd	Each
50wvdc		1000wvdc		12500wvdc	
4	$0.40	1	$0.79	2	95.00
150wvdc		2	.89	15000wvdc	
1-1-3-3	.98	5	2.98	.0016	9.98
300wvdc		15	4.98	25000wvdc	
1.3	.29	1400wvdc		.00025	7.49
400 wvdc		.25	1.29	1	95.00
.1	.39	.5	1.39	AC RATED	
.5	.45	1500wvdc		220vac/ 600vdc	
1	.69	.5	1.49	1	.69
2	.79	.75	1.69	2	.89
6	1.09	1	2.49	4	.89
10	1.39	2000wvdc		5	1.29
2x.1	.79	.1	1.49	225vac/ 630dc	
2x.5	.94	2x.1	1.69	3.3	.79
3x.1	.91	1	1.75	230vac 630dc	
3x.25	.99	2	3.98	3	1.29
600wvdc		3	3.69	5	1.29
.034	.30	8	9.49	330vac 1000dc	
.1	.35	2500wvdc		1.25	.63
.2	.37	.25	2.29	1.5	.70
.5	.42	3000wvdc		2	.98
1	.53	.1	2.49	3	1.75
2	.65	.5	4.45	4	.33
4	1.69	4	7.89	2.5	.90
5	2.25	4000wvdc		3	.98
6	2.59	2	8.98	5	1.00
7	2.89	5000wvdc		10	1.29
10	3.10	.2	4.49	15	3.98
2x.1	.99	4	19.98	25	6.49
2x.25	.78	6000wvdc		405vac/ 1200dc	
2x.5	.89	1	7.49	.15	1.29
2x1	1.05	7000wvdc		600vac/ 1800dc	
2x2	1.25	.002	1.69	16	6.98
2x8	3.25	.0075	1.98	660vac/ 2000dc	
3x.05	.75	7500wvdc		4	1.50
3x.22	.85	.03	2.98	800wvdc	
3x.25	.98	.05	3.49	10	9.98
400wvdc		10000wvdc		1	.69
4	1.50	.03	3.49	600wvdc	
800wvdc		12000wvdc		1	1.98
1	.69	.002	4.98	16	7.98

866A KIT AND XFORMER

2 Tubes, Sckts, xfmr 115v 60cy Inpt, output 2.5vct. 10A Hvinsul. SPECIAL.....$5.49

Diode Probe Tube

Unexcelled for No-Loss VHF testing. Ultra-sensitive subminiature-envelope. New w/ data VR92.....25c; 5 for $1.00

INFRARED SNOOPERSCOPE

SEE-IN-DARK TUBE

Image-Converter Tube HiSensitivity simplified design 2" dia. Willemite screen-Resolution up to 350 line/in. Complete data & tube ea.....$4.98; 2 for $9.49

SNOOPERSCOPE PWR SUPPLY

1800VDC 35MA. Using Doubler CKT. Transformer, Rectifiers, Socket, Resistors, Capacitors and Diagram.....$6.98

TELEVISION ANTENNA

DELTA BEAM Adjustable Indoor Antenna, uses best principles of specialized antennas. Dsgn for fringe areas.....$4.95

TV CONICAL ANTENNA All Channel Sturdy Perfan 8 elements & 100 ft. Copper Twinex Cross Bar & Hdware.....$5.98

DOUBLE-V Ant. All Channel. Sturdy Const. w/ Mtg. & 100 ft. Twinex.....$4.49

WINDOW CONICAL ANT. mounts outside window. All Channel Reception.....$3.95

10 Foot Interlocking Mast Sections, heavy duty, rust proof.....85c

300 Ohm Television Twinex all copper, for dipole 100ft $8.98; 1% Ft $12.49

RG59U Coax 100Ft. $8.00; 500Ft.....22.00

METER SPECIALS

0-5MADC Tuning Meter "AN" Aircraft Mtg.....$1.29
0-30VDC "AN" $1.98; 4 for 7.00
0-60 ADC "AN".....$3.25; 3 for 9.00
0-15VAC GE 215 RND 80Ieye.....1.29
0-150VAC WSTGH 2½ RND 60 eye.....3.49
0-150VAC 3" 125-250 Scale RA35.....5.98
0-1 MADC GE 3" RND Brkt CSD.....5.39
0-1MADC WSTGH 3½" Sq.....6.49
0-50 Microamps Westcraft 3½"Sq.....15.98
0-500MADC 2½" RND Triplett 221T.....4.98
VU-20+3 Weston 301 3" Sq.....14.98
0-120 MA RF 3½" RND Weston 301.....14.98

ONE YEAR GTD PICTURE TUBES

10 RP4	$13.98
10 RP4	14.49
12" Glass	17.95
12" Metal	21.98
16" Rectangular	20.95
16" Glass	22.95
16" Metal	23.98
19" Rectangular	23.49
19" Round	27.98
20" Rectangular	29.95
21" Rectangular	30.98

Your old picture tube is worth money, write for trade-in allowance toward RMA coded and dated tubes with one year guarantee. Ship your defective picture tube prepaid.

Guarantee Money Back Guarantee (Cost of Mdse. Only) $5 Min. Order F.O.B. N.Y.C. Add Shpg. Charges & 25% Dep. Tubes Gtd. via R-Exp. only. Prices subject to Change Without Notice. Rector 2-6245

TUBES

"TAB" TESTED & GUARANTEED

PRICES SUBJECT TO CHANGE
WRITE FOR COMPLETE TUBE LISTING

0A2	$0.95	3D6/1299	.69	6SD7GT	.80	FG105	17.64
0A3 /VR75	1.04	3D21A	4.98	6SF5	.77	117L7GT/ MTGT	1.59
0B2	1.37	3D22	15.95	6SG7	.73	117N7GT	1.59
0B3 /VR90	1.09	3D23	4.90	6SG7	.72	117P7GT	1.39
0C3 /VR105	1.15	3E29	14.95	6SH7	.61	117Z6GT	1.19
0D3 /VR150	.98	4-125A	29.00	6SJ7	.70	117Z7GT	1.39
1B3 8016	.81	4-250A	40.00	6SK7GT	.69	F123A	7.90
1B21 /471A	2.85	4-1000A	108.50	6SL7GT	.69	F127A	19.98
1B22	2.20	4E27	22.25	6SN7GT	.70	F250TA	3.90
1B23	9.90	EL5BHD	16.98	6SN7WGT	2.25	CV148	4.98
1B24	9.45	5C21 /C6J	5.95	6SQ7GT	.63	FG166	49.00
1B26	9.45	5D21	42.05	6SR7	.65	FG172	49.00
1B27	12.75	5C30 /C5B	16.98	6SS7	.75	250TH	22.25
1B32 /532A	3.90	5D21	19.50	6ST7	.98	250TL	17.75
1B35	9.15	5D22		6SU7GTY	2.60	250TH	22.90
1B37	16.98	RK65	36.50	6V6	1.39	304TL	8.90
1B38	29.95	5J29	12.40	6V6GT	.57	388A	1.49
1B40	9.45	5R4GY	1.55	6W4GT	.57	GL417A	8.95
1B41	49.95	5R4GYW	1.75	12AH7GT	1.45	417A	
1B42	18.00	6AG5	.79	12AR5	1.98	5842	18.50
1B43	1.75	6AH3	1.39	12AX5W	2.98	GL434A	12.69
1B53	49.95	6AH5G	1.49	12AL5	.75	446A	1.05
1B56	38.50	6AH6	1.22	12AT6	.52	446B	3.69
1B57	175.00	6AJ5	1.40	12AT7	.81	450TH	52.00
1B60	69.75	6AK5	.72	12AU6	.72	450TL	52.00
1B63	50.00	6AK5W	2.98	12AU7	.63	460 HF200	
1B63A	75.00	6AK6	1.05	12AV6	.49		15.95
2C36	27.00	6AL5	.54	12AV7	.98	GL471A	2.69
2C39	21.00	6AL7GT	1.29	12AW6	1.79	CK501X	1.26
2C39A	29.50	6AQ5	2.90	12AX4GT	1.20	CK501AX	2.10
2C40	7.25	6AQ5	.55	12AX7	.79	GL502A	.79
2C43	14.75	6AQ5W	3.98	12AY7	2.95	CK502AX	1.49
2C43 /464A	9.49	6AQ7GT	.81	12AZ7	1.95	CK505AX	1.49
2C44	5.49	6AQ7GT	1.29	12BA6	.59	CK505AX	1.79
2C51	5.49	6AR5	.79	12BA7	.79	CK506AX	1.49
2D21	1.26	6AS5	2.98	12BD6	1.23	GL508A	9.98
2E35	1.49	6AS6	.79	12BE6	.59	CK509AX	1.79
2E36	1.49	6AS6	2.43	12BF6	.85	CK512AX	1.45
2E41	1.54	6AT6	4.65	12BH7	1.25	GL521B	2.98
2E43	1.49	6AT6	.63	12BY7	1.35	CK525AX	1.29
2G21	1.49	6AU6GT	1.10	12BZ7	1.25	CK526AX	1.49
2J31	27.00	6AU6	.59	12SF5	.69	GL530	7.90
2J31A	79.50	6AV5GT	1.25	12SC7	.80	CK529AX	1.79
2J32	37.00	6AV6	.49	12SF5GT	.72	GL530	22.00
2J33	27.0C	6BA6	1.89	12SF7GT	.49	GL531DX	2.98
2J33	27.00	6BE6	1.21	12SG7	.63	531	6.98
2J36	108.00	6BA6	.63	12SH7	.63	CK532DX	1.89
2J37	12.70	6BC5	1.27	12SJ7GT	.59	WL532	1.49
2J38	11.75	6BC5	.61	12SK7	.72	CK533AX	1.20
2J39	44.00	6BC7	1.23	12SL7GT	.65	CK534AX	.99
2J42	187.00	6BD6	.83	12SN7GT	.75	CK536AX	.99
2J48	24.25	6BE6	.59	12SQ7GT	.63	CK537AX	3.04
2J49	67.25	6BE6	.59	12SR7	.63	CK538DX	.98
2J50	21.25	6BF6	.65	19T8	.99	CK540DX	1.99
2J55	249.50	6BF7	2.55	19V8	1.62	CK542DX	.99
2J56	85.00	6BF7	1.39	RK20A	8.95	CK543DX	.99
2J56	149.00	6BG7	1.98	24G 3C24	1.98	CK544DX	.99
2J61	49.95	6BH6	.63	258G6GT	1.99	CK546DX	1.99
2J62	39.45	6BK5	.69	25L6GT	.69	CK547DX	1.98
2K22	39.45	6BK7	2.15	25Z5	.79	CK571AX	
2K23	39.45	6BL7GT	1.45	25Z6GT	.99	5886	2.49
2K25	28.50	6BN6	1.49	FG27A	8.70	CK5773AX	
2K25/ 723AB	24.90	6BN7	1.69	RK28A	4.89	6029	3.49
2K26	29.00	6BQ6GT	1.20	28D7	1.95	WL579	10.49
2K33	259.00	6BY5G	1.45	FG32		5558	13.95
2K35	389.95	6C21	29.45	35Z5GT	.59	WL653	65.00
2K41	125.00	6C6	.69	RK39	2.95	WL654	117.00
2K44	130.0C	6CD6G	1.69	RK48	6.85	WL686	65.00
2K45	110.00	6D4	2.70	RK49	7.50	703A	4.75
2K48	120.00	C6J /5C21	1.69	50L6GT	.69	705A	1.98
2K52	.69	6J4	6.66	RK63	.74	707A	7.90
1822	2.70	6J5GT	.47	RO	.69	707B	13.50
1823 /RK22	4.95	6J6	.81	R1	1.69	715A	6.00
1824	5.50	6K4A	6.45	R2	1.69	715B	11.50
1825	4.50	6L6	2.09	R4	1.39	715C	24.00
1826	3.70	6L6G	1.35	R5	1.45	717A	.90
1828	3.35	6L6GA	1.35	R3V	1.79	718EV	48.45
3C22	89.00	6L6GAY	2.29	R4 6Z4	.99	718CY	48.45
3C23	9.90	6SA7GT	.63	FG95			
3C31 /C1B	3.49	6SA7GTY	3.37	FG98	24.85	719A	28.50
3C33	14.98	6SA7GTY	1.19	100TH	19.95	721A	2.49
3C34 /HK24	5.49	6SB6GT	.90	FG104	7.83	722A /287	2.45
3C45	12.89	6SC7			37.98	723A	31.95

THAT'S A BUY "TAB" THAT'S A BUY

DEPT. 5RN. 111 LIBERTY STREET NEW YORK 6, N. Y., U. S. A.

12 Reasons why Television Engineers should specify

SYLVANIA PICTURE TUBES

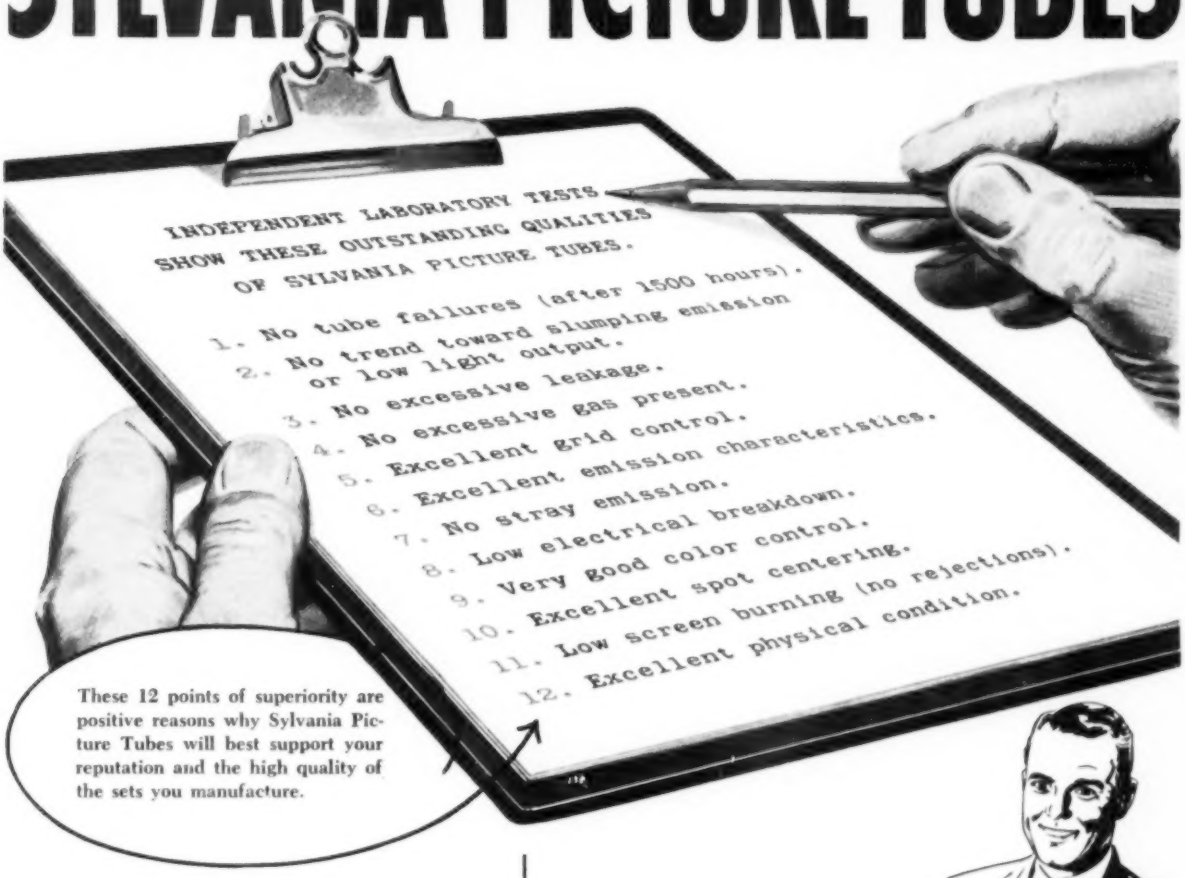
INDEPENDENT LABORATORY TESTS
SHOW THESE OUTSTANDING QUALITIES
OF SYLVANIA PICTURE TUBES.
1. No tube failures (after 1500 hours).
2. No trend toward slumping emission or low light output.
3. No excessive leakage.
4. No excessive gas present.
5. Excellent grid control.
6. Excellent emission characteristics.
7. No stray emission.
8. Low electrical breakdown.
9. Very good color control.
10. Excellent spot centering.
11. Low screen burning (no rejections).
12. Excellent physical condition.

These 12 points of superiority are positive reasons why Sylvania Picture Tubes will best support your reputation and the high quality of the sets you manufacture.

To definitely establish the superiority of Sylvania Picture Tubes, in comparison with other brands, Sylvania called an outside research organization . . . the United States Testing Company.

Eight picture tubes of nine different manufacturers were selected and submitted to identical electrical and mechanical tests.

Shown above is Sylvania's outstanding record. The test results showed that Sylvania Picture Tubes outlasted and outperformed all others tested. For the detailed report of these significant tests, write to: Sylvania Electric Products Inc., Dept. 3R-2105, 1740 Broadway, New York 19, N. Y.

Send for this Report

"SYLVANIA'S SUPERIOR QUALITY IS BASED ON PROVED PERFORMANCE!"

SYLVANIA

RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS

Depend on Mallory
for
Approved Precision Quality

Make the Most of the New UHF Market... With the Mallory UHF Converter

THE Mallory UHF Converter is ready to add to your profits in a big way when UHF television comes to your area. And now is the time to start laying the ground work.

The Mallory Converter adds *all* UHF channels to *any* TV set . . . in *any* UHF broadcast area . . . without sacrificing reception of VHF channels.

It can be installed in a matter of minutes . . . no internal changes in any set.

Mallory precision quality insures high quality picture definition and easy tuning.

The small attractive cabinet is styled in deep maroon plastic. It blends tastefully with either modern or period furniture.

There is no better way to serve your customers than by selling them the Mallory UHF Converter. Because it tunes in *all* channels in *any* area, they have nothing more to buy . . . no adjustments to make . . . even if they move to another city.

ASK YOUR MALLORY DISTRIBUTOR about the Converter's success where UHF is already on the air. It has been a "Best-Seller" for others . . . as it can be for you.

Installation is fast and easy. The Mallory Converter is installed right in your customers' homes. You need no special tools . . . just connect the antenna lead and power lines from the Converter to set. That's all.

MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • VIBRAPACK® POWER SUPPLIES • FILTERS

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA